

# Circuit Variables and Circuit Elements

## Drill Exercises

DE 1.1  $q = \int_0^{\infty} 20e^{-5000t} dt = 4000 \mu\text{C}$

DE 1.2  $i = \frac{dq}{dt} = te^{-\alpha t}$ ,  $\frac{di}{dt} = (1 - \alpha t)e^{-\alpha t}$ ,  $\frac{di}{dt} = 0$  when  $t = \frac{1}{\alpha}$ ;

Therefore  $i_{\max} = \frac{1}{\alpha e} = \frac{1}{0.03679e} \cong 10 \text{ A}$

DE 1.3 [a]



(a)



(b)



(c)



(d)

Therefore

(a)  $v = -20 \text{ V}$ ,  $i = -4 \text{ A}$ ; (b)  $v = -20 \text{ V}$ ,  $i = 4 \text{ A}$

(c)  $v = 20 \text{ V}$ ,  $i = -4 \text{ A}$ ; (d)  $v = 20 \text{ V}$ ,  $i = 4 \text{ A}$

[b] Using the reference system in Fig. 1.3(a),  $p = vi = (-20)(-4) = 80 \text{ W}$ , so the box is absorbing power.


[c] The box is absorbing 80 W.

$$\text{DE 1.4} \quad p = vi = 20 \times 10^4 e^{-10,000t} \text{ W}; \quad w = \int_0^\infty 20 \times 10^4 e^{-10,000t} dt = 20 \text{ J}$$

$$\text{DE 1.5} \quad p = 800 \times 10^3 \times 1.8 \times 10^3 = 1440 \times 10^6 = 1440 \text{ MW}$$

from Oregon to California

DE 1.6

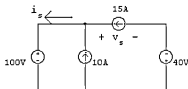

The interconnection is valid:

$$i_s = 10 + 15 = 25 \text{ A}$$

$$p_{100\text{V}} = 100i_s = 2500 \text{ W (absorbing)}$$

$$p_{10\text{A}} = -100(10) = -1000 \text{ W (generating)}$$

$$-100 + v_s - 40 = 0 \quad \text{so } v_s = 140 \text{ V}$$

$$p_{15\text{A}} = -15(140) = -2100 \text{ W (generating)}$$

$$p_{40\text{V}} = 15(40) = 600 \text{ W (absorbing)}$$

$$\sum p_{\text{dev}} = p_{10\text{A}} + p_{15\text{A}} = 3100 \text{ W}$$

$$\sum p_{\text{abs}} = p_{100\text{V}} + p_{40\text{V}} = 3100 \text{ W}$$

$$\sum p_{\text{dev}} = \sum p_{\text{abs}} = 3100 \text{ W}$$

$$\text{DE 1.7} \quad [\text{a}] \quad v_l - v_c + v_1 - v_s = 0, \quad i_l R_l - i_c R_c + i_1 R_1 - v_s = 0$$

$$i_s R_l + i_s R_c + i_s R_1 - v_s = 0$$

$$[\text{b}] \quad i_s = v_s / (R_l + R_c + R_1)$$

$$\text{DE 1.8} \quad [\text{a}] \quad 24 = v_2 + v_5 - v_1 = 3i_5 + 7i_5 - (-2i_5) = 12i_5$$

$$\text{Therefore } i_5 = 24/12 = 2 \text{ A}$$


$$[\text{b}] \quad v_1 = -2i_5 = -4 \text{ V}$$

$$[\text{c}] \quad v_2 = 3i_5 = 6 \text{ V}$$

$$[\text{d}] \quad v_5 = 7i_5 = 14 \text{ V}$$

[e]  $p_{24} = -(24)(2) = -48 \text{ W}$ ; therefore 24 V source is delivering 48 W.

DE 1.9

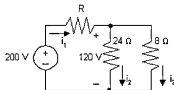

$$i_2 = 120/24 = 5 \text{ A}$$


$$i_3 = 120/8 = 15 \text{ A}$$

$$i_1 = i_2 + i_3 = 20 \text{ A}$$

$$-200 + 20R + 120 = 0$$


$$R = 80/20 = 4 \Omega$$

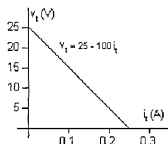DE 1.10 [a] Plotting a graph of  $v_t$  versus  $i_t$  gives




Note that when  $i_t = 0$ ,  $v_t = 25 \text{ V}$ ; therefore the voltage source must be 25 V. When  $v_t$  is zero,  $i_t = 0.25 \text{ A}$ , hence the resistor must be  $25/0.25$  or  $100\Omega$ .

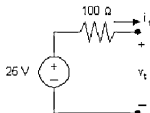A circuit model having the same  $v - i$  characteristic is a 25 V source in series with a  $100\Omega$  resistor.




[b]

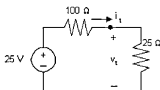

$$i_t = \frac{25}{125} = 0.2 \text{ A}; \quad p = (0.2)^2(25) = 1 \text{ W}.$$

DE 1.11 [a] Since we are constructing the model from two elements, we have two choices on interconnecting them—series or parallel. From the  $v-i$  characteristic we require  $v_t = 25 \text{ V}$  when  $i_t = 0$ . The only way we can satisfy this requirement is with a parallel connection. The constraint that  $v_t = 0$  when  $i_t = 0.25 \text{ A}$  tells us the ideal current source must produce  $0.25 \text{ A}$ . Therefore the parallel resistor must be  $25/0.25$  or  $100\Omega$ .

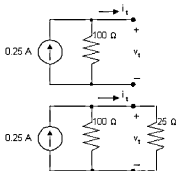

[b]

$$-0.25 + \frac{v_t}{100} + \frac{v_t}{25} = 0, \quad 5v_t = 25, \quad v_t = 5 \text{ V}$$

$$p = \frac{v_t^2}{25} = 1 \text{ W}.$$

## Problems

P 1.1  $i = \frac{dq}{dt} = 24 \cos 4000t$

Therefore,  $dq = 24 \cos 4000t \, dt$

$$\int_{q(0)}^{q(t)} dx = 24 \int_0^t \cos 4000y \, dy$$

$$q(t) - q(0) = 24 \frac{\sin 4000y}{4000} \bigg|_0^t$$

But  $q(0) = 0$  by hypothesis, i.e., the current passes through its maximum value at  $t = 0$ , so  $q(t) = 6 \times 10^{-3} \sin 4000t \text{ C} = 6 \sin 4000t \text{ mC}$

P 1.2  $p = (6)(100) \times 10^{-3} = 0.6 \text{ W}; \quad w = (0.6)(3)(60)(60) = 6480 \text{ J}$

P 1.3 Assume we are standing at box A looking toward box B, then  $p = vi$ .

[a]  $p = (120)(5) = 600 \text{ W}$  from A to B

[b]  $p = (250)(-8) = -2000 \text{ W}$  from B to A

[c]  $p = (-150)(16) = -2400 \text{ W}$  from B to A

[d]  $p = (-480)(-10) = 4800 \text{ W}$  from A to B

P 1.4 [a]



$$p = vi = (40)(-10) = -400 \text{ W}$$

Power is being delivered by the box.

[b] Entering

[c] Gain

P 1.5 [a]  $p = vi = (-60)(-10) = 600 \text{ W}$ , so power is being absorbed by the box.

[b] Entering

[c] Lose



P 1.6 [a] Looking from A to B the current  $i$  is in the direction of the voltage rise across the 12 V battery, therefore  $p = vi = -12(30) = -360 \text{ W}$ .


Thus the power flow is from B to A, and Car A has the "dead" battery.

[b]  $w = \int_0^t p \, dx = \int_0^t 360 \, dx$

$$w = 360t = 360(1 \times 60) = 21.6 \text{ kJ}$$

P 1.7  $p = vi$ ;  $w = \int_0^t p \, dx$

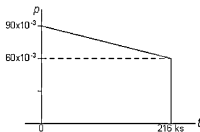Since the energy is the area under the power vs. time plot, let us plot  $p$  vs.  $t$ .



$$p(0) = (6)(15 \times 10^{-3}) = 90 \times 10^{-3} \text{ W}$$

$$p(216 \text{ ks}) = (4)(15 \times 10^{-3}) = 60 \times 10^{-3} \text{ W}$$

$$w = (60 \times 10^{-3})(216 \times 10^3) + \frac{1}{2}(216)(30) = 16.2 \text{ kJ}$$

Note:  $60 \text{ hr} \equiv 216,000 \text{ s} = 216 \text{ ks}$

P 1.8 [a]  $p = vi = 30e^{-500t} - 30e^{-1500t} - 40e^{-1000t} + 50e^{-2000t} - 10e^{-3000t}$   
 $p(1 \text{ ms}) = 3.1 \text{ mW}$

$$\begin{aligned} \text{[b]} \quad w(t) &= \int_0^t (30e^{-500x} - 30e^{-1500x} - 40e^{-1000x} + \\ &\quad 50e^{-2000x} - 10e^{-3000x}) dx \\ &= 21.67 - 60e^{-500t} + 20e^{-1500t} + 40e^{-1000t} - \\ &\quad 25e^{-2000t} + 3.33e^{-3000t} \mu\text{J} \end{aligned}$$

$$w(1 \text{ ms}) = 1.24 \mu\text{J}$$

[c]  $w_{\text{total}} = 21.67 \mu\text{J}$

P 1.9 [a]  $v(20 \text{ ms}) = 100e^{-1} \sin 3 = 5.19 \text{ V}$   
 $i(20 \text{ ms}) = 20e^{-1} \sin 3 = 1.04 \text{ A}$   
 $p(20 \text{ ms}) = vi = 5.39 \text{ W}$

[b]

$$\begin{aligned}
p &= vi = 2000e^{-100t} \sin^2 150t \\
&= 2000e^{-100t} \left[ \frac{1}{2} - \frac{1}{2} \cos 300t \right] \\
&= 1000e^{-100t} - 1000e^{-100t} \cos 300t \\
w &= \int_0^\infty 1000e^{-100t} dt - \int_0^\infty 1000e^{-100t} \cos 300t dt \\
&= 1000 \left. \frac{e^{-100t}}{-100} \right|_0^\infty - 1000 \left\{ \frac{e^{-100t}}{(100)^2 + (300)^2} [-100 \cos 300t + 300 \sin 300t] \right\} \bigg|_0^\infty \\
&= 10 - 1000 \left[ \frac{100}{1 \times 10^4 + 9 \times 10^4} \right] = 10 - 1 \\
w &= 9 \text{ J}
\end{aligned}$$

P 1.10 [a]  $0 \leq t \leq 10 \text{ ms}$ :

$$v = 1000t \text{ V}; \quad i = 0.6 \text{ mA}; \quad p = 0.6t \text{ mW}$$

 $10 \leq t \leq 25 \text{ ms}$ :

$$v = 10 \text{ V}; \quad i = 0.6 \text{ mA}; \quad p = 6 \text{ mW}$$

 $25 \leq t \leq 35 \text{ ms}$ :

$$v = 75 - 2500t \text{ V}; \quad i = 0 \text{ mA}; \quad p = 0 \text{ mW}$$

 $35 \leq t \leq 60 \text{ ms}$ :

$$v = -50 + 1000t \text{ V}; \quad i = -0.4 \text{ mA}; \quad p = 20 - 400t \text{ mW}$$

 $60 \leq t \leq 70 \text{ ms}$ :

$$v = -50 + 1000t \text{ V}; \quad i = 0 \text{ mA}; \quad p = 0 \text{ mW}$$

 $70 \leq t \leq 80 \text{ ms}$ :

$$v = 20 \text{ V}; \quad i = -0.5 \text{ mA}; \quad p = -10 \text{ mW}$$

 $80 \leq t \leq 90 \text{ ms}$ :

$$v = 180 - 2000t \text{ V}; \quad i = 0 \text{ mA}; \quad p = 0 \text{ mW}$$


 $90 \leq t \leq 95 \text{ ms}$ :

$$v = 180 - 2000t \text{ V}; \quad i = 0.9 \text{ mA}; \quad p = 162 - 1800t \text{ mW}$$

 $95 \leq t \leq 100 \text{ ms}$ :

$$v = -200 + 2000t \text{ V}; \quad i = 0.9 \text{ mA}; \quad p = -180 + 1800t \text{ mW}$$
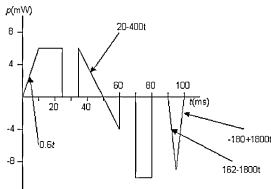
$$\begin{aligned}
 \text{[b]} \quad w(25) &= \frac{1}{2}(6)(10) + (6)(15) = 120 \mu\text{J} \\
 w(60) &= 120 + \frac{1}{2}(15)(6) - \frac{1}{2}(10)(4) = 145 \mu\text{J} \\
 w(90) &= 145 - (10)(10) = 45 \mu\text{J} \\
 w(100) &= 45 - \frac{1}{2}(10)(9) = 0 \mu\text{J}
 \end{aligned}$$



P 1.11 [a]  $p = vi = (2e^{-500t} - 2e^{-1000t}) \text{ W}$

$$\frac{dp}{dt} = -1000e^{-500t} + 2000e^{-1000t} = 0 \text{ at } t = 1.4 \text{ ms}$$

$$p_{\max} = p(1.4 \text{ ms}) = 0.5 \text{ W}$$

$$\begin{aligned}
 \text{[b]} \quad w &= \int_0^{\infty} [2e^{-500t} - 2e^{-1000t}] dt = \left[ \frac{2}{-500}e^{-500t} - \frac{2}{-1000}e^{-1000t} \right]_0^{\infty} \\
 &= 2 \text{ mJ}
 \end{aligned}$$

P 1.12 [a]  $p = vi = 900 \sin(200\pi t) \cos(200\pi t) = 450 \sin(400\pi t) \text{ W}$

Therefore,  $p_{\max} = 450 \text{ W}$

[b]  $p_{\max}(\text{extracting}) = 450 \text{ W}$

$$\begin{aligned}
 \text{[c]} \quad p_{\text{avg}} &= 200 \int_0^{5 \times 10^{-3}} 450 \sin(400\pi t) dt \\
 &= 9 \times 10^4 \left[ \frac{-\cos 400\pi t}{400\pi} \right]_0^{2.5 \times 10^{-3}} = \frac{225}{\pi} [1 - \cos 2\pi] = 0
 \end{aligned}$$

$$\text{[d]} \quad p_{\text{avg}} = \frac{180}{\pi} [1 - \cos 2.5\pi] = \frac{180}{\pi} = 57.3 \text{ W}$$

P 1.13 [a]  $q = \text{area under } i \text{ vs. } t \text{ plot}$

$$\begin{aligned}
 &= \left[ \frac{1}{2}(5)(4) + (10)(4) + \frac{1}{2}(8)(4) + (8)(6) + \frac{1}{2}(3)(6) \right] \times 10^3 \\
 &= [10 + 40 + 16 + 48 + 9]10^3 = 123,000 \text{ C}
 \end{aligned}$$



$$\begin{aligned}
\text{[b]} \quad w &= \int p dt = \int v i dt \\
v &= 0.2 \times 10^{-3} t + 9 \quad 0 \leq t \leq 15 \text{ ks} \\
0 \leq t &\leq 4000 \text{ s} \\
i &= 15 - 1.25 \times 10^{-3} t \\
p &= 135 - 8.25 \times 10^{-3} t - 0.25 \times 10^{-6} t^2 \\
w_1 &= \int_0^{4000} (135 - 8.25 \times 10^{-3} t - 0.25 \times 10^{-6} t^2) dt \\
&= (540 - 66 - 5.3333)10^3 = 468.667 \text{ kJ} \\
4000 \leq t &\leq 12,000 \\
i &= 12 - 0.5 \times 10^{-3} t \\
p &= 108 - 2.1 \times 10^{-3} t - 0.1 \times 10^{-6} t^2 \\
w_2 &= \int_{4000}^{12,000} (108 - 2.1 \times 10^{-3} t - 0.1 \times 10^{-6} t^2) dt \\
&= (864 - 134.4 - 55.467)10^3 = 674.133 \text{ kJ} \\
12,000 \leq t &\leq 15,000 \\
i &= 30 - 2 \times 10^{-3} t \\
p &= 270 - 12 \times 10^{-3} t - 0.4 \times 10^{-6} t^2 \\
w_3 &= \int_{12,000}^{15,000} (270 - 12 \times 10^{-3} t - 0.4 \times 10^{-6} t^2) dt \\
&= (810 - 486 - 219.6)10^3 = 104.4 \text{ kJ} \\
w_T &= w_1 + w_2 + w_3 = 468.667 + 674.133 + 104.4 = 1247.2 \text{ kJ}
\end{aligned}$$

$$\begin{aligned}
\text{P 1.14 [a]} \quad p &= v i \\
&= 400 \times 10^3 t^2 e^{-800t} + 700t e^{-800t} + 0.25 e^{-800t} \\
&= e^{-800t} [400,000 t^2 + 700t + 0.25] \\
\frac{dp}{dt} &= \{e^{-800t} [800 \times 10^3 t + 700] - 800 e^{-800t} [400,000 t^2 + 700t + 0.25]\} \\
&= [-3,200,000 t^2 + 2400t + 5] 100 e^{-800t} \\
\text{Therefore, } \frac{dp}{dt} &= 0 \text{ when } 3,200,000 t^2 - 2400t - 5 = 0
\end{aligned}$$

so  $p_{\max}$  occurs at  $t = 1.68 \text{ ms}$ .

$$\begin{aligned}
\text{[b]} \quad p_{\max} &= [400,000(.00168)^2 + 700(.00168) + 0.25] e^{-800(.00168)} \\
&= 666 \text{ mW}
\end{aligned}$$

$$\begin{aligned}
\text{[c]} \quad w &= \int_0^t p dx \\
w &= \int_0^t 400,000x^2 e^{-800x} dx + \int_0^t 700x e^{-800x} dx + \int_0^t 0.25 e^{-800x} dx \\
&= \frac{400,000 e^{-800x}}{-512 \times 10^6} [64 \times 10^4 x^2 + 1600x + 2] \Big|_0^t + \\
&\quad \frac{700 e^{-800x}}{64 \times 10^4} (-800x - 1) \Big|_0^t + 0.25 \frac{e^{-800x}}{-800} \Big|_0^t
\end{aligned}$$

When  $t = \infty$  all the upper limits evaluate to zero, hence

$$w = \frac{(400,000)(2)}{512 \times 10^6} + \frac{700}{64 \times 10^4} + \frac{0.25}{800} = 2.97 \text{ mJ.}$$

P 1.15 [a]  $p = 0 \quad t < 0, \quad p = 0 \quad t > 3 \text{ s}$

$$\begin{aligned}
p &= vi = t(3-t)(6-4t) = 18t - 18t^2 + 4t^3 \text{ mW} \quad 0 \leq t \leq 3 \text{ s} \\
\frac{dp}{dt} &= 18 - 36t + 12t^2 = 12(t^2 - 3t + 1.5) \\
\frac{dp}{dt} &= 0 \quad \text{when } t^2 - 3t + 1.5 = 0 \\
t &= \frac{3 \pm \sqrt{9-6}}{2} = \frac{3 \pm \sqrt{3}}{2} \\
t_1 &= 3/2 - \sqrt{3}/2 = 0.634 \text{ s}; \quad t_2 = 3/2 + \sqrt{3}/2 = 2.366 \text{ s} \\
p(t_1) &= 18(0.634) - 18(0.634)^2 + 4(0.634)^3 = 5.196 \text{ mW} \\
p(t_2) &= 18(2.366) - 18(2.366)^2 + 4(2.366)^3 = -5.196 \text{ mW}
\end{aligned}$$

Therefore, maximum power is being delivered at  $t = 0.634 \text{ s}$ .

[b]  $p_{\max} = 5.196 \text{ mW}$  (delivered)





[c] Maximum power is being extracted at  $t = 2.366 \text{ s}$ .

[d]  $p_{\max} = 5.196 \text{ mW}$  (extracted)

[e]  $w = \int_0^t p dx = \int_0^t (18x - 18x^2 + 4x^3) dx = 9t^2 - 6t^3 + t^4$

$$w(0) = 0 \text{ mJ} \quad w(2) = 4 \text{ mJ}$$
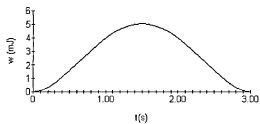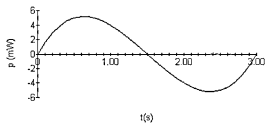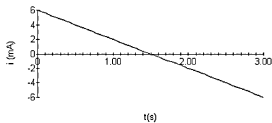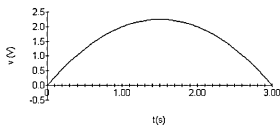
$$w(1) = 4 \text{ mJ} \quad w(3) = 0 \text{ mJ}$$



$$\begin{aligned}
 \text{P 1.16 [a]} \quad p &= vi = 12 \times 10^5 t^2 e^{-1000t} \text{ W} \\
 \frac{dp}{dt} &= 12 \times 10^5 [t^2(-1000)e^{-1000t} + e^{-1000t}(2t)] \\
 &= 12 \times 10^5 t e^{-1000t} [t(2 - 1000t)] \\
 \frac{dp}{dt} &= 0 \text{ at } t = 0, \quad t = 2 \text{ ms}
 \end{aligned}$$

We know  $p$  is a minimum at  $t = 0$  since  $v$  and  $i$  are zero at  $t = 0$ .

$$[\text{b}] \quad p_{\max} = 12 \times 10^5 (2 \times 10^{-3})^2 e^{-2} = 649.61 \text{ mW}$$

$$\begin{aligned}
 [c] \quad w &= 12 \times 10^5 \int_0^\infty t^2 e^{-1000t} dt \\
 &= 12 \times 10^5 \left\{ \frac{e^{-1000t}}{(-1000)^3} [10^6 t^2 + 2,000t + 2] \right\}_0^\infty = 2.4 \text{ mJ}
 \end{aligned}$$

P 1.17 [a] From the diagram and the table we have

$$p_a = -v_a i_a = -(46.16)(6) = -276.96 \text{ W} \quad (\text{del})$$

$$p_b = v_b i_b = (14.16)(4.72) = 66.8352 \text{ W} \quad (\text{abs})$$

$$p_c = v_c i_c = (-32)(-6.4) = 204.80 \text{ W} \quad (\text{abs})$$

$$p_d = -v_d i_d = -(22)(1.28) = -28.16 \text{ W} \quad (\text{del})$$

$$p_e = -v_e i_e = -(33.60)(1.68) = -56.448 \text{ W} \quad (\text{del})$$

$$p_f = v_f i_f = (66)(-0.4) = -26.40 \text{ W} \quad (\text{del})$$

$$p_g = v_g i_g = (2.56)(1.28) = 3.2768 \text{ W} \quad (\text{abs})$$

$$p_h = -v_h i_h = -(-0.4)(0.4) = 0.16 \text{ W} \quad (\text{abs})$$

$$\sum P_{\text{del}} = 276.96 + 28.16 + 56.448 + 26.40 = 387.9680 \text{ W}$$

$$\sum P_{\text{abs}} = 66.8352 + 204.80 + 3.2768 + 0.16 = 275.072 \text{ W}$$

Therefore,  $\sum P_{\text{del}} \neq \sum P_{\text{abs}}$  and the subordinate engineer is correct.

[b] We can also check the data using Kirchhoff's laws.

From Fig. P1.17 the following equations should be satisfied:

$$i_a - i_b - i_d = 0 \quad (\text{ok})$$

$$i_b + i_c - i_e = 0 \quad (\text{no})$$

$$i_f - i_a - i_c = 0 \quad (\text{ok})$$

$$i_d = i_g \quad (\text{ok})$$

$$i_g + i_e + i_h = 0 \quad (\text{no})$$

$$i_h = -i_f \quad (\text{ok})$$

Using Kirchhoff's current law, it appears  $i_e$  is in error.

From Kirchhoff's voltage law we have

$$v_b - v_a - v_c = 0 \quad (\text{ok})$$

$$-v_d - v_b + v_e + v_g = 0 \quad (\text{ok})$$

$$-v_e + v_c + v_f + v_h = 0 \quad (\text{ok})$$

Therefore all the voltages are consistent with Kirchhoff's voltage law.

Assume  $i_e$  is in error. Therefore,

$$i_e = i_b + i_c = -i_g - i_h = 4.72 - 6.40 = -1.68 \text{ A}$$

So the error is in the sign of  $i_e$ ;  $i_e$  equals minus 1.68 A.

Correcting  $i_e$  leads to

$$\sum P_{\text{del}} = \sum P_{\text{abs}} = 331.52 \text{ W}$$

P 1.18

$$\begin{aligned}
 p_a &= v_a i_a = (48)(12) = 576 \text{ W} && (\text{abs}) \\
 p_b &= v_b i_b = (18)(-4) = -72 \text{ W} && (\text{del}) \\
 p_c &= -v_c i_c = -(30)(-10) = 300 \text{ W} && (\text{abs}) \\
 p_d &= v_d i_d = (36)(16) = 576 \text{ W} && (\text{abs}) \\
 p_e &= -v_e i_e = -(36)(8) = -288 \text{ W} && (\text{del}) \\
 p_f &= -v_f i_f = -(-54)(14) = 756 \text{ W} && (\text{abs}) \\
 p_g &= -v_g i_g = -(84)(22) = -1848 \text{ W} && (\text{del}) \\
 \sum P_{\text{del}} &= 72 + 288 + 1848 = 2208 \text{ W} \\
 \sum P_{\text{abs}} &= 576 + 300 + 576 + 756 = 2208 \text{ W} \\
 \text{Therefore, } \sum P_{\text{del}} &= \sum P_{\text{abs}} = 2208 \text{ W}
 \end{aligned}$$

- P 1.19 [a] From an examination of reference polarities, the following elements employ the passive convention:  $a$ ,  $c$ ,  $e$ , and  $f$ .

[b]


$$\begin{aligned}
 p_a &= -56 \text{ W} && (\text{del}) \\
 p_b &= -14 \text{ W} && (\text{del}) \\
 p_c &= 150 \text{ W} && (\text{abs}) \\
 p_d &= -50 \text{ W} && (\text{del}) \\
 p_e &= -18 \text{ W} && (\text{del}) \\
 p_f &= -12 \text{ W} && (\text{del}) \\
 \sum P_{\text{abs}} &= 150 \text{ W}; && \sum P_{\text{del}} = 56 + 14 + 50 + 18 + 12 = 150 \text{ W}.
 \end{aligned}$$

- P 1.20 (a) 9 (b) 7 (c) 4 (d)  $v_a - R_a$ ,  $v_b - R_b$ ,  $v_c - R_c$  (e) 6

(f)

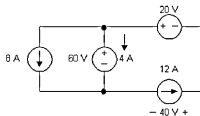- (1)  $v_a - R_a - R_d - R_b - v_b$
- (2)  $R_d - R_f - R_e$
- (3)  $v_b - R_b - R_d - R_f - R_c - v_c$
- (4)  $v_c - R_c - R_f - R_a - v_a$
- (5)  $v_a - R_a - R_f - R_e - R_b - v_b$
- (6)  $v_a - R_a - R_d - R_c - R_c - v_c$
- (7)  $v_b - R_b - R_c - R_c - v_c$

P 1.21 The interconnect is valid since it does not violate Kirchhoff's laws.



$$-60 + 20 + 40 = 0 \quad (\text{KVL})$$

$$8 + 4 - 12 = 0 \quad (\text{KCL})$$


$$\sum P_{\text{dev}} = 4(60) + 8(60) = 720 \text{ W}$$

$$\sum P_{\text{abs}} = 12(20) + 12(40) = 720 \text{ W}$$

$$\sum P_{\text{dev}} = \sum P_{\text{abs}} = 720 \text{ W}$$

P 1.22 [a] Yes, Kirchhoff's laws are not violated.

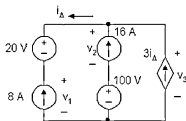[b] No, because the voltages across the independent and dependent current sources are indeterminate. For example, define  $v_1$ ,  $v_2$ , and  $v_3$  as shown:



Kirchhoff's voltage law requires

$$v_1 + 20 = v_3$$

$$v_2 + 100 = v_3$$

Conservation of energy requires

$$8(20) + 8v_1 + 16v_2 + 1600 - 24v_3 = 0$$

or

$$v_1 + 2v_2 - 3v_3 = -220$$

Now arbitrarily select a value of  $v_3$  and show the conservation of energy will be satisfied. Examples:

If  $v_3 = 200$  V then  $v_1 = 180$  V and  $v_2 = 100$  V. Then

$$180 + 200 - 600 = -220 \text{ (CHECKS)}$$

If  $v_3 = -100$  V, then  $v_1 = -120$  V and  $v_2 = -200$  V. Then

$$-120 - 400 + 300 = -220 \text{ (CHECKS)}$$

- P 1.23 [a] Yes, independent voltage sources can carry whatever current is required by the connection; independent current source can support any voltage required by the connection.

[b] 30 V source: absorbing

10 V source: delivering

8 A source: delivering

[c]  $P_{30V} = (30)(8) = 240 \text{ W (abs)}$

$$P_{10V} = -10(8) = -80 \text{ W (del)}$$

$$P_{8A} = -20(8) = -160 \text{ W (del)}$$

$$\sum P_{\text{abs}} = \sum P_{\text{del}} = 240 \text{ W}$$

- [d] Yes, 30 V source is delivering, the 10 V source is delivering, and the 8 A source is absorbing

$$P_{30V} = -30(8) = -240 \text{ W (del)}$$

$$P_{10V} = -10(8) = -80 \text{ W (del)}$$

$$P_{8A} = +40(8) = 320 \text{ W (abs)}$$

- P 1.24 The interconnection is valid because it does not violate Kirchhoff's laws.

$$i_{\Delta} = -25 \text{ A}; \quad 6i_{\Delta} = -150 \text{ V}$$


$$-200 + 50 - (-150) = 0$$

But the power developed in the circuit cannot be determined, as the currents in the 200 V, 50 V, and  $6i_{\Delta}$  sources are unspecified.

- P 1.25 The interconnection is not valid because it violates Kirchhoff's current law:

$$3 \text{ A} + (-5 \text{ A}) \neq 8 \text{ A}.$$

P 1.26

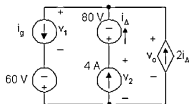

$$i_{\Delta} = 4 \text{ A so } i_g = 12 \text{ A}$$

$$v_o = 100 \text{ V}$$

$$-60 + v_1 = 100, \text{ so } v_1 = 160 \text{ V}$$

$$v_2 - 80 = 100, \text{ so } v_2 = 180 \text{ V}$$

$$\sum P_{\text{dev}} = 180(4) + 100(8) + 60(12) = 2240 \text{ W}$$

$$\begin{aligned} \text{CHECK: } \sum P_{\text{diss}} &= 160(12) + 80(4) = 1920 + 320 \\ &= 2240 \text{ W} \text{ — CHECKS} \end{aligned}$$

P 1.27 The interconnection is valid because it does not violate Kirchhoff's laws:

$$p_{V\text{-sources}} = -(100 - 60)(5) = -200 \text{ W.}$$

P 1.28 First there is no violation of Kirchhoff's laws, hence the interconnection is valid.

Kirchhoff's voltage law requires

$$v_1 + v_2 = 150 - 50 = 100 \text{ V}$$

The conservation of energy law requires

$$20v_1 - 10v_1 + 10v_2 + 500 - 1500 = 0$$

or

$$v_1 + v_2 = 100$$

Hence any combination of  $v_1$  and  $v_2$  that adds to 100 is a valid solution. For example if  $v_1 = 80 \text{ V}$  and  $v_2 = 20 \text{ V}$ 

$$P_{\text{abs}} = 80(20) + 10(20) + 50(10) = 2300 \text{ W}$$



$$P_{\text{dev}} = 1500 + 80(10) = 2300 \text{ W}$$

$$\text{If } v_1 = 60 \text{ V and } v_2 = 40 \text{ V}$$

$$P_{\text{abs}} = 60(20) + 10(40) + 500 = 2100 \text{ W}$$

$$P_{\text{dev}} = 60(10) + 1500 = 2100 \text{ W}$$

$$\text{If } v_1 = -100 \text{ V and } v_2 = 200 \text{ V}$$


$$P_{\text{abs}} = 10(100) + 10(200) + 10(50) = 3500 \text{ W}$$

$$P_{\text{dev}} = 20(100) + 10(150) = 3500 \text{ W}$$

P 1.29 [a]  $1.6 = i_g - i_a$   
 $80i_a = 1.6(30 + 90) = 192$  therefore,  $i_a = 2.4 \text{ A}$   
 $i_g = i_a + 1.6 = 2.4 + 1.6 = 4 \text{ A}$   
 [b]  $v_g = 90(1.6) = 144 \text{ V}$   
 [c]  $\sum P_{\text{dis}} = 2.4^2(80) + 1.6^2(120) = 768 \text{ W}$   
 $\sum P_{\text{dev}} = (4)(192) = 768 \text{ W}$   
 Therefore,  $\sum P_{\text{dis}} = \sum P_{\text{dev}} = 768 \text{ W}$

P 1.30 [a]  $v_o = 8i_a + 14i_a + 18i_a = 40(20) = 800 \text{ V}$   
 $800 = 10i_o$   
 $i_o = 800/10 = 80 \text{ A}$   
 [b]  $i_g = i_a + i_o = 20 + 80 = 100 \text{ A}$   
 [c]  $p_g(\text{delivered}) = (100)(800) = 80,000 \text{ W} = 80 \text{ kW}$

P 1.31 [a]

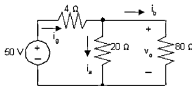

$$20i_a = 80i_b \quad i_g = i_a + i_b = 5i_b$$

$$i_a = 4i_b$$


$$50 = 4i_g + 80i_b = 20i_b + 80i_b = 100i_b$$

$$i_b = 0.5 \text{ A, therefore, } i_a = 2 \text{ A} \quad \text{and} \quad i_g = 2.5 \text{ A}$$





P 1.34 [a]

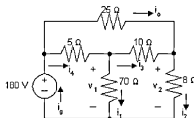

$$v_2 = 180 - 100 = 80 \text{ V}$$

$$i_2 = \frac{v_2}{8} = 10 \text{ A}$$

$$i_3 + 4 = i_2, \quad i_3 = 10 - 4 = 6 \text{ A}$$

$$v_1 = v_2 + v_3 = 80 + 6(10) = 140 \text{ V}$$

$$i_1 = \frac{v_1}{70} = \frac{140}{70} = 2 \text{ A}$$

$$[b] \quad p_{5\Omega} = 8^2(5) = 320 \text{ W}$$

$$p_{25\Omega} = (4)^2(25) = 400 \text{ W}$$

$$p_{70\Omega} = 2^2(70) = 280 \text{ W}$$


$$p_{10\Omega} = 6^2(10) = 360 \text{ W}$$

$$p_{8\Omega} = 10^2(8) = 800 \text{ W}$$


$$[c] \quad \sum P_{\text{dis}} = 320 + 400 + 280 + 360 + 800 = 2160 \text{ W}$$

$$P_{\text{dev}} = 180i_g = 180(12) = 2160 \text{ W}$$

P 1.35 [a]

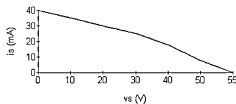


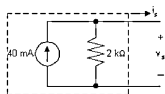[b]  $\Delta v = 20 \text{ V}; \quad \Delta i = 10 \text{ mA}; \quad R = \frac{\Delta v}{\Delta i} = 2 \text{ k}\Omega$



[c]  $2i_1 = 3i_s, \quad i_1 = 1.5i_s$

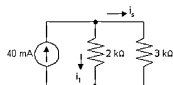$40 = i_1 + i_s = 2.5i_s, \quad i_s = 16 \text{ mA}$




[d]  $v_s(\text{open circuit}) = (40 \times 10^{-3})(2 \times 10^3) = 80 \text{ V}$

[e]  $v_s(\text{open circuit}) = 55 \text{ V}$

[f] Linear model cannot predict the nonlinear behavior of the practical current source.

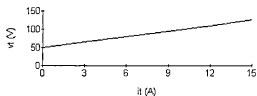
P 1.36 [a] Plot the  $v - i$  characteristic




From the plot:

$$R = \frac{\Delta v}{\Delta i} = \frac{(125 - 50)}{(15 - 0)} = 5 \Omega$$

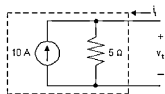When  $i_t = 0$ ,  $v_t = 50 \text{ V}$ ; therefore the ideal current source has a current of 10 A




[b]

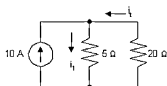


$$10 + i_t = i_1 \quad \text{and} \quad 5i_1 = -20i_t$$

Therefore,  $10 + i_t = -4i_t$  so  $i_t = -2$  A

P 1.37 [a]

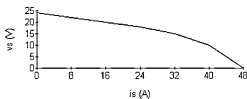
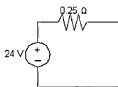
$$[b] \quad R = \frac{24 - 18}{24 - 0} = \frac{6}{24} = 0.25 \, \Omega$$




$$[c] \quad i = \frac{24}{1.25} = 19.2 \, \text{A}, \quad v = 24 - 19.2(0.25) = 19.2 \, \text{V}$$

$$[d] \quad i_{sc} = \frac{24}{0.25} = 96 \, \text{A}$$

$$[e] \quad i_{sc} = 48 \, \text{A} \quad (\text{from graph})$$

[f] Linear model cannot predict nonlinear behavior of voltage source.

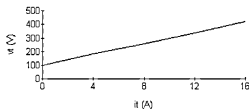
P 1.38 [a] Plot the  $v-i$  characteristic:




From the plot:

$$R = \frac{\Delta v}{\Delta i} = \frac{(420 - 100)}{(16 - 0)} = 20 \, \Omega$$

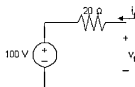When  $i_t = 0$ ,  $v_t = 100$  V; therefore the ideal voltage source has a voltage of 100 V




[b]

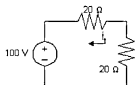

$$i_t = -100/(20 + 20) = -2.5 \text{ A; Therefore, } p_{20\Omega} = (-2.5)^2(20) = 125 \text{ W}$$

P 1.39 [a]

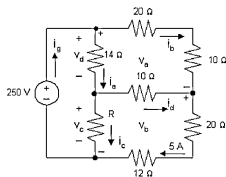

$$v_b = 5(20 + 12) = 160 \text{ V}$$

$$v_b + v_a = 250 \text{ V, so } v_a = 90 \text{ V}$$

$$i_b = 90/(20 + 10) = 3 \text{ A}$$

$$i_d = 5 - i_b = 2 \text{ A}$$

$$v_c = v_b + 10(i_d) = 180 \text{ V}$$

$$v_d = 250 - v_c = 70 \text{ V} = 14(i_a); \text{ therefore, } i_a = 5 \text{ A}$$


$$i_c = i_a - i_d = 5 - 2 = 3 \text{ A}$$

$$R = v_c/i_c = 180/3 = 60 \Omega$$

[b]  $i_g = 5 + 3 = 8 \text{ A}$

$$p_g (\text{supplied}) = (250)(8) = 2000 \text{ W}$$

P 1.40

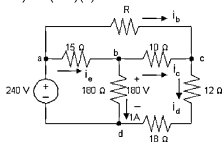

$$v_{ab} = 240 - 180 = 60 \text{ V}; \quad \text{therefore, } i_e = 60/15 = 4 \text{ A}$$

$$i_c = i_e - 1 = 4 - 1 = 3 \text{ A}; \quad \text{therefore, } v_{bc} = 10i_c = 30 \text{ V}$$

$$v_{cd} = 180 - v_{bc} = 180 - 30 = 150 \text{ V};$$

$$\text{therefore, } i_d = v_{cd}/(12 + 18) = 150/30 = 5 \text{ A}$$

$$i_b = i_d - i_c = 5 - 3 = 2 \text{ A}$$

$$v_{ac} = v_{ab} + v_{bc} = 60 + 30 = 90 \text{ V}$$

$$R = v_{ac}/i_b = 90/2 = 45 \Omega$$

$$\text{CHECK: } i_g = i_b + i_e = 2 + 4 = 6 \text{ A}$$

$$p_{\text{dev}} = (240)(6) = 1440 \text{ W}$$

$$\begin{aligned} \sum P_{\text{dis}} &= 1(180) + 4(45) + 9(10) + 25(12) \\ &\quad + 25(18) + 16(15) = 1440 \text{ W (CHECKS)} \end{aligned}$$



P 1.41 [a]  $15.2 = 10,000i_\beta - 0.80 + (200)30i_\beta$

$$16 = (16,000)i_\beta$$

$$i_\beta = 1 \text{ mA}$$

$$200(30i_\beta) + v_y + 500(29i_\beta) - 25 = 0$$

$$v_y = 25 - 6000i_\beta - 14,500i_\beta$$


$$\text{Therefore, } v_y = 4.5 \text{ V}$$

[b]  $\sum P_{\text{gen}} = 15.2i_\beta + 25(29)i_\beta + 0.8i_\beta = 741i_\beta = 741 \text{ mW}$

$$\begin{aligned}\sum P_{\text{dis}} &= 10^4(i_\beta)^2 + 200(30i_\beta)^2 + 29i_\beta(4.5) + 500(29i_\beta)^2 \\ &= 741 \text{ mW.}\end{aligned}$$

P 1.42 [a]  $i_2 = 0$  because no current can exist in a single conductor connecting two parts of a circuit.

[b]

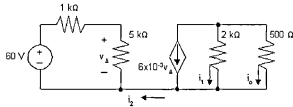


$$60 = 6000i_g \quad i_g = 10 \text{ mA}$$

$$v_\Delta = 5000i_g = 50 \text{ V} \quad 6 \times 10^{-3}v_\Delta = 300 \text{ mA}$$


$$2000i_1 = 500i_o, \text{ so } i_1 + 4i_1 = -300 \text{ mA; therefore, } i_1 = -60 \text{ mA}$$

[c]  $300 - 60 + i_2 = 0$ , so  $i_o = -240 \text{ mA}$ .

P 1.43 [a]

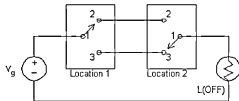

[b]

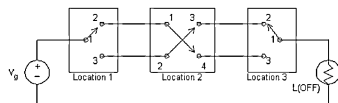


# 2

## Some Circuit Simplification Techniques

### Drill Exercises

DE 2.1

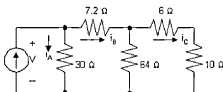

$$16 \parallel 64 = 12.8 \, \Omega, \quad 12.8 + 7.2 = 20 \, \Omega, \quad 20 \parallel 30 = 12 \, \Omega$$

[a]  $v = 5(12) = 60 \, \text{V}$

[b]  $p_{5A(\text{dc})} = (5)(60) = 300 \, \text{W}$

[c]  $i_A = 60/30 = 2 \, \text{A} \quad i_C = 3(64)/(80) = 2.4 \, \text{A}$   
 $i_B = 5 - 2 = 3 \, \text{A} \quad p_{10\Omega} = (2.4)^2 10 = 57.6 \, \text{W}$

DE 2.2 [a]  $v_o(\text{no load}) = 200(75)/100 = 150 \, \text{V}$


[b]  $75 \parallel 150 = 50 \, \text{k}\Omega$ , therefore  $v_o = 200(50)/75 = 133.3 \, \text{V}$

[c]  $i = 200/25,000 = 8 \, \text{mA}$ ,  $p_{25k} = (8 \times 10^{-3})^2 (25,000) = 1.6 \, \text{W}$

[d] Maximum dissipation at no load since  $v_o$  is maximum

$$p = \frac{v_o^2}{75,000} = 0.3 \, \text{W}$$

DE 2.3

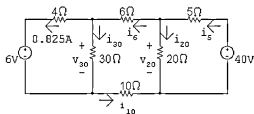

$$v_{30} = 6 + 4(0.825) = 9.3 \text{ V}; \quad i_{30} = \frac{v_{30}}{30} = 0.31 \text{ A}$$

$$i_6 = i_{30} + 0.825 = 1.135 \text{ A}; \quad i_{10} = 0.825 + 0.31 = 1.135 \text{ A}$$

$$-v_{30} - 6i_6 + v_{20} - 10i_{10} = 0$$


$$\therefore v_{20} = 9.3 + 16(1.135) = 27.46 \text{ V}$$


$$i_{20} = \frac{27.46}{20} = 1.373 \text{ A}; \quad i_5 = i_6 + i_{20} = 2.508 \text{ A}$$

$$i_{30} = 0.31 \text{ A}; \quad i_6 = 1.135 \text{ A}; \quad i_{10} = 1.135 \text{ A};$$

$$i_{20} = 1.373 \text{ A}; \quad \text{and} \quad i_5 = 2.508 \text{ A}$$

DE 2.4

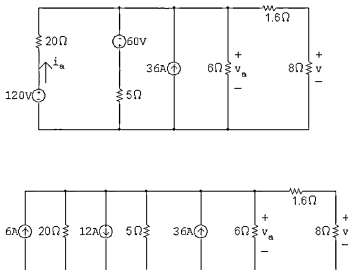

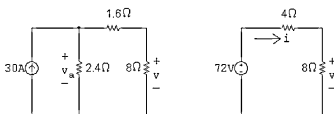


$$i = \frac{72}{12} = 6 \text{ A}$$

$$[\text{a}] \quad v = \frac{72}{12}(8) = 48 \text{ V}, \quad i_{120\text{V}} = \frac{120 - 57.6}{20} = 3.12 \text{ A}$$

$$[\text{b}] \quad v_a = 6(9.6) = 57.6 \text{ V}, \quad p_{120\text{V}}(\text{del}) = 120i_a = 374.40 \text{ W}$$

DE 2.5 [a] 110 V source acting alone:

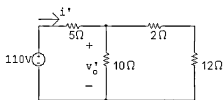


$$R_o = \frac{10(14)}{24} = \frac{35}{6} \Omega$$

$$i' = \frac{110}{5 + 35/6} = \frac{132}{13} \text{ A}$$

$$v_o' = \left(\frac{35}{6}\right) \left(\frac{132}{13}\right) = \frac{770}{13} \text{ V}$$

4 A source acting alone:

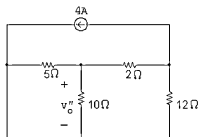

$$5 \Omega \parallel 10 \Omega = 50/15 = 10/3 \Omega$$

$$10/3 + 2 = 16/3 \Omega$$

$$16/3 \parallel 12 = 48/13 \Omega$$

Hence our circuit reduces to:



It follows that

$$v_a'' = 4(48/13) = (192/13) \text{ V}$$


and

$$v_o'' = \frac{-v_a''}{(16/3)}(10/3) = -\frac{5}{8}v_a'' = -(120/13) \text{ V}$$

$$\therefore v_o = v_o' + v_o'' = \frac{770}{13} - \frac{120}{13} = 50 \text{ V}$$

$$[\text{b}] \quad p = \frac{v_o^2}{10} = 250 \text{ W}$$

DE 2.6 70-V source acting alone:

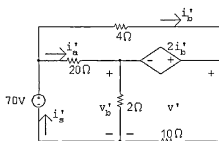

$$v' = 70 - 4i_b'$$

$$i_s' = \frac{v_b'}{2} + \frac{v'}{10} = i_a' + i_b'$$

$$70 = 20i_a' + v_b'$$

$$i_a' = \frac{70 - v_b'}{20}$$

$$\therefore i'_b = \frac{v'_b}{2} + \frac{v'}{10} - \frac{70 - v'_b}{20} = \frac{11}{20}v'_b + \frac{v'}{10} - 3.5$$


$$v' = v'_b + 2i'_b$$

$$\therefore v'_b = v' - 2i'_b$$

$$\therefore i'_b = \frac{11}{20}(v' - 2i'_b) + \frac{v'}{10} - 3.5 \quad \text{or} \quad i'_b = \frac{13}{42}v' - \frac{70}{42}$$

$$\therefore v' = 70 - 4\left(\frac{13}{42}v' - \frac{70}{42}\right) \quad \text{or} \quad v' = \frac{3220}{94} = \frac{1610}{47} \text{ V}$$

50-V source acting alone:

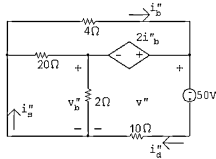

$$v'' = -4i''_b$$

$$v'' = v''_b + 2i''_b$$

$$v'' = -50 + 10i''_d$$

$$\therefore i''_d = \frac{v'' + 50}{10}$$

$$i''_s = \frac{v''_b}{2} + \frac{v'' + 50}{10}$$

$$i''_b = \frac{v''_b}{20} + i''_s = \frac{v''_b}{20} + \frac{v''_b}{2} + \frac{v'' + 50}{10} = \frac{11}{20}v''_b + \frac{v'' + 50}{10}$$

$$v''_b = v'' - 2i''_b$$

$$\therefore i''_b = \frac{11}{20}(v'' - 2i''_b) + \frac{v'' + 50}{10} \quad \text{or} \quad i''_b = \frac{13}{42}v'' + \frac{100}{42}$$

$$\text{Thus, } v'' = -4\left(\frac{13}{42}v'' + \frac{100}{42}\right) \quad \text{or} \quad v'' = -\frac{200}{47} \text{ V}$$

$$\text{Hence, } v = v' + v'' = \frac{1610}{47} - \frac{200}{47} = \frac{1410}{47} = 30 \text{ V}$$

## Problems


P 2.1 [a]  $p_{4\Omega} = i_s^2 4 = (12)^2 4 = 576 \text{ W}$        $p_{18\Omega} = (4)^2 18 = 288 \text{ W}$

$p_{3\Omega} = (8)^2 3 = 192 \text{ W}$        $p_{6\Omega} = (8)^2 6 = 384 \text{ W}$

[b]  $p_{120\text{V}}(\text{delivered}) = 120i_s = 120(12) = 1440 \text{ W}$

[c]  $p_{\text{diss}} = 576 + 288 + 192 + 384 = 1440 \text{ W}$

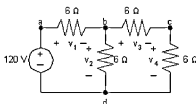P 2.2 [a] From Ex. 3-1:  $i_1 = 4 \text{ A}$ ,  $i_2 = 8 \text{ A}$ ,  $i_s = 12 \text{ A}$   
 at node x:  $-12 + 4 + 8 = 0$ , at node y:  $12 - 4 - 8 = 0$



[b]  $v_1 = 4i_s = 48 \text{ V}$        $v_3 = 3i_2 = 24 \text{ V}$

$v_2 = 18i_1 = 72 \text{ V}$        $v_4 = 6i_2 = 48 \text{ V}$

loop abda:  $-120 + 48 + 72 = 0$ ,

loop bcd:  $-72 + 24 + 48 = 0$ ,


loop abcd:  $-120 + 48 + 24 + 48 = 0$

P 2.3  $\frac{1}{R_{\text{eq}}} = \frac{1}{6} + \frac{1}{10} + \frac{1}{15} = \frac{10}{30} = \frac{1}{3}$ ;       $R_{\text{eq}} = 3 \Omega$

$v_{(2+8+5)\Omega} = (20)(3) = 60 \text{ V}$ ,       $i_{(2+8+5)\Omega} = 60/15 = 4 \text{ A}$

$P_{5\Omega} = (4)^2(5) = 80 \text{ W}$

P 2.4 [a]

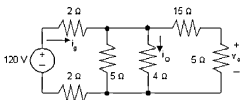

$R_{\text{eq}} = 2 + 2 + (1/4 + 1/5 + 1/20)^{-1} = 6 \Omega$

$i_g = 120/6 = 20 \text{ A}$

$v_{4\Omega} = 120 - (2 + 2)20 = 40 \text{ V}$

$i_o = 40/4 = 10 \text{ A}$



$$i_{(15+5)\Omega} = 40/(15+5) = 2 \text{ A}$$

$$v_o = (5)(2) = 10 \text{ V}$$

$$[\text{b}] \quad i_{15\Omega} = 2 \text{ A}; \quad P_{15\Omega} = (2)^2(15) = 60 \text{ W}$$


$$[\text{c}] \quad P_{120\text{V}} = (120)(20) = 2.4 \text{ kW}$$

$$\text{P 2.5 } [\text{a}] \quad R_{\text{eq}} = R \parallel R = \frac{R^2}{2R} = \frac{R}{2}$$

$$\begin{aligned} [\text{b}] \quad R_{\text{eq}} &= R \parallel R \parallel R \parallel \cdots \parallel R \quad (n \text{ R's}) \\ &= R \parallel \frac{R}{n-1} \\ &= \frac{R^2/(n-1)}{R + R/(n-1)} = \frac{R^2}{nR} = \frac{R}{n} \end{aligned}$$


[\text{c}] One solution:
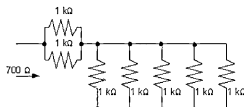
$$\begin{aligned} 700 \Omega &= 200 \Omega + 500 \Omega \\ &= 1000/5 + 1000/2 \\ &= 1 \text{ k}\Omega \parallel 1 \text{ k}\Omega \parallel 1 \text{ k}\Omega \parallel 1 \text{ k}\Omega \parallel 1 \text{ k}\Omega + 1 \text{ k}\Omega \parallel 1 \text{ k}\Omega \end{aligned}$$



[\text{d}] One solution:

$$\begin{aligned} 5.5 \text{ k}\Omega &= 5 \text{ k}\Omega + 0.5 \text{ k}\Omega \\ &= 2 \text{ k}\Omega + 2 \text{ k}\Omega + 1 \text{ k}\Omega + 0.5 \text{ k}\Omega \\ &= 2 \text{ k}\Omega + 2 \text{ k}\Omega + \frac{2 \text{ k}\Omega}{2} + \frac{2 \text{ k}\Omega}{4} \\ &= 2 \text{ k}\Omega + 2 \text{ k}\Omega + 2 \text{ k}\Omega \parallel 2 \text{ k}\Omega + 2 \text{ k}\Omega \parallel 2 \text{ k}\Omega \parallel 2 \text{ k}\Omega \end{aligned}$$

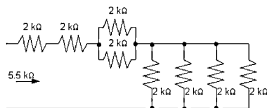

P 2.6 [a]  $12\Omega\|24\Omega = 8\Omega$       Therefore,  $R_{ab} = 8 + 2 + 6 = 16\Omega$

$$[b] \frac{1}{R_{eq}} = \frac{1}{24\text{ k}\Omega} + \frac{1}{30\text{ k}\Omega} + \frac{1}{20\text{ k}\Omega} = \frac{15}{120\text{ k}\Omega} = \frac{1}{8\text{ k}\Omega}$$

$$R_{eq} = 8\text{ k}\Omega; \quad R_{eq} + 7 = 15\text{ k}\Omega$$

$$\frac{1}{R_{ab}} = \frac{1}{15\text{ k}\Omega} + \frac{1}{30\text{ k}\Omega} + \frac{1}{15\text{ k}\Omega} = \frac{5}{30\text{ k}\Omega} = \frac{1}{6\text{ k}\Omega}$$

$$R_{ab} = 6\text{ k}\Omega$$

P 2.7 [a] For circuit (a)

$$R_{ab} = 15\|(18 + 48\|16) = 10\Omega$$

For circuit (b)

$$\frac{1}{R_e} = \frac{1}{20} + \frac{1}{15} + \frac{1}{20} + \frac{1}{4} + \frac{1}{12} = \frac{30}{60} = \frac{1}{2}$$

$$R_e = 2\Omega$$

$$R_e + 16 = 18\Omega$$

$$18\|18 = 9\Omega$$

$$R_{ab} = 10 + 8 + 9 = 27\Omega$$

For circuit (c)

$$48\|16 = 12\Omega$$

$$12 + 8 = 20\Omega$$

$$20\|30 = 12\Omega$$

$$12 + 18 = 30\Omega$$

$$30\|15 = 10\Omega$$

$$10 + 10 + 20 = 40\Omega$$

$$R_{ab} = 40\|60 = 24\Omega$$

$$[b] P_a = \frac{20^2}{10} = 40\text{ W}$$

$$P_b = \frac{144^2}{27} = 768\text{ W}$$

$$P_c = 6^2(24) = 864\text{ W}$$

- P 2.8 [a]  $5\|20 = 100/25 = 4\ \Omega$   $5\|20 + 9\|18 + 10 = 20\ \Omega$   
 $9\|18 = 162/27 = 6\ \Omega$   $20\|30 = 600/50 = 12\ \Omega$   
 $R_{ab} = 5 + 12 + 3 = 20\ \Omega$
- [b]  $5 + 15 = 20\ \Omega$   $30\|20 = 600/50 = 12\ \Omega$   
 $20\|60 = 1200/80 = 15\ \Omega$   $3\|6 = 18/9 = 2\ \Omega$   
 $15 + 10 = 25\ \Omega$   $3\|6 + 30\|20 = 2 + 12 = 14\ \Omega$   
 $25\|75 = 1875/100 = 18.75\ \Omega$   $26\|14 = 364/40 = 9.1\ \Omega$   
 $18.75 + 11.25 = 30\ \Omega$   $R_{ab} = 2.5 + 9.1 + 3.4 = 15\ \Omega$
- [c]  $3 + 5 = 8\ \Omega$   $60\|40 = 2400/100 = 24\ \Omega$   
 $8\|12 = 96/20 = 4.8\ \Omega$   $24 + 6 = 30\ \Omega$   
 $4.8 + 5.2 = 10\ \Omega$   $30\|10 = 300/40 = 7.5\ \Omega$   
 $45 + 15 = 60\ \Omega$   $R_{ab} = 1.5 + 7.5 + 1.0 = 10\ \Omega$
- P 2.9 [a]  $R_{\text{cond}} = 845(0.0397) = 33.5465\ \Omega$   
 $R_{\text{total}} = 2(1/2)R_{\text{cond}} = 33.5465\ \Omega$   
 $P_{\text{loss}} = (2000)^2(33.5465) = 134.186\ \text{MW}$   
 $P_{\text{calif}} = 800(2) - 134.186 = 1465.814\ \text{MW}$   
 $\text{Efficiency} = (1465.814/1600) \times 100 = 91.61\%$
- [b]  $P_{\text{calif}} = 2000 - 134.86 = 1865.814\ \text{MW}$   
 $\text{Efficiency} = 93.29\%$
- [c]  $P_{\text{loss}} = (3000)^2 \cdot 2 \cdot (1/3) \cdot 845 \cdot (0.0397) = 201.279\ \text{MW}$   
 $P_{\text{oregon}} = 3000\ \text{MW}, \quad P_{\text{calif}} = 3000 - 201.279 = 2798.7\ \text{MW}$   
 $\text{Efficiency} = (2798.70/3000) \times 100 = 93.29\%$
- P 2.10  $i_{10k} = \frac{(18)(15)}{40} = 6.75\ \text{mA}$   
 $v_{15k} = -(6.75)(15) = -101.25\ \text{V}$   
 $i_{3k} = 18 - 6.75 = 11.25\ \text{mA}$   
 $v_{12k} = -(12)(11.25) = -135\ \text{V}$   
 $v_o = -101.25 - (-135) = 33.75\ \text{V}$

$$\text{P 2.11 [a]} \quad v_{1k} = \frac{1}{1+5}(30) = 5 \text{ V}$$

$$v_{15k} = \frac{15}{15+60}(30) = 6 \text{ V}$$

$$v_x = v_{15k} - v_{1k} = 6 - 5 = 1 \text{ V}$$

$$[\text{b}] \quad v_{1k} = \frac{v_s}{6}(1) = v_s/6$$

$$v_{15k} = \frac{v_s}{75}(15) = v_s/5$$

$$v_x = (v_s/5) - (v_s/6) = v_s/30$$

$$\text{P 2.12} \quad 60 \parallel 30 = 20 \Omega$$

$$i_{30\Omega} = \frac{(25)(75)}{125} = 15 \text{ A}$$

$$v_o = (15)(20) = 300 \text{ V}$$

$$v_o + 30i_{30} = 750 \text{ V}$$

$$v_g - 12(25) = 750$$

$$v_g = 1050 \text{ V}$$

$$\text{P 2.13} \quad 5 \Omega \parallel 20 \Omega = 4 \Omega; \quad 4 \Omega + 6 \Omega = 10 \Omega; \quad 10 \parallel 40 = 8 \Omega;$$

$$\text{Therefore, } i_g = \frac{125}{8+2} = 12.5 \text{ A}$$

$$i_{6\Omega} = \frac{(40)(12.5)}{50} = 10 \text{ A}; \quad i_o = \frac{(5)(10)}{25} = 2 \text{ A}$$

$$\text{P 2.14 [a]} \quad 40 \parallel 10 = 8 \Omega \quad i_{75V} = \frac{75}{10} = 7.5 \text{ A}$$

$$8 + 7 = 15 \Omega \quad i_{4+3\Omega} = 7.5 \left( \frac{30}{45} \right) = 5 \text{ A}$$

$$15 \parallel 30 = 10 \Omega \quad i_o = -5 \left( \frac{10}{50} \right) = -1 \text{ A}$$

$$[\text{b}] \quad i_{10\Omega} = i_{4+3\Omega} + i_o = 5 - 1 = 4 \text{ A}$$

$$P_{10\Omega} = (4)^2(10) = 160 \text{ W}$$

P 2.15 [a]  $v_{9\Omega} = (1)(9) = 9 \text{ V}$

$$i_{2\Omega} = 9/(2 + 1) = 3 \text{ A}$$

$$i_{4\Omega} = 1 + 3 = 4 \text{ A};$$

$$v_{25\Omega} = (4)(4) + 9 = 25 \text{ V}$$

$$i_{25\Omega} = 25/25 = 1 \text{ A};$$

$$i_{3\Omega} = i_{25\Omega} + i_{9\Omega} + i_{2\Omega} = 1 + 1 + 3 = 5 \text{ A};$$

$$v_{40\Omega} = v_{25\Omega} - v_{3\Omega} = 25 - (-5)(3) = 40 \text{ V}$$

$$i_{40\Omega} = 40/40 = 1 \text{ A}$$

$$i_{5\parallel 20\Omega} = i_{40\Omega} + i_{25\Omega} + i_{4\Omega} = 1 + 1 + 4 = 6 \text{ A}$$

$$v_{5\parallel 20\Omega} = (4)(6) = 24 \text{ V}$$

$$v_{32\Omega} = v_{40\Omega} + v_{5\parallel 20\Omega} = 40 + 24 = 64 \text{ V}$$

$$i_{32\Omega} = 64/32 = 2 \text{ A};$$

$$i_{10\Omega} = i_{32\Omega} + i_{5\parallel 20\Omega} = 2 + 6 = 8 \text{ A}$$

$$v_g = 10(8) + v_{32\Omega} = 80 + 64 = 144 \text{ V}.$$

[b]  $P_{20\Omega} = \frac{(v_{5\parallel 20\Omega})^2}{20} = \frac{24^2}{20} = 28.8 \text{ W}$

P 2.16 [a] Let  $i_s$  be the current oriented down through the resistors. Then,

$$i_s = \frac{V_s}{R_1 + R_2 + \cdots + R_k + \cdots + R_n}$$

and

$$v_k = R_k i_s = \frac{R_k}{R_1 + R_2 + \cdots + R_k + \cdots + R_n} V_s$$

[b]  $i_s = \frac{200}{5 + 15 + 30 + 10 + 40} = 2 \text{ A}$

$$v_1 = 2(5) = 10 \text{ V}$$

$$v_2 = 2(15) = 30 \text{ V}$$

$$v_3 = 2(30) = 60 \text{ V}$$

$$v_4 = 2(10) = 20 \text{ V}$$

$$v_5 = 2(40) = 80 \text{ V}$$

P 2.17 [a]  $v_o = \frac{25}{25}(20) = 20 \text{ V}$

[b]  $v_o = \frac{25}{5 + R_e} R_e$


$$R_e = \frac{(20)(12)}{32} = 7.5 \text{ k}\Omega$$

$$v_o = \frac{25}{12.5}(7.5) = 15 \text{ V}$$

[c]  $\frac{v_o}{25} = \frac{20}{25} = 0.80$

[d]  $\frac{v_o}{25} = \frac{15}{25} = 0.60$

P 2.18 [a]

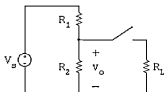

No load:

$$v_o = \frac{R_2}{R_1 + R_2} V_s = \sigma V_s$$

$$\therefore \sigma = \frac{R_2}{R_1 + R_2}$$

Load:

$$v_o = \frac{R_e}{R_1 + R_e} V_s = \beta V_s$$

$$\therefore \beta = \frac{R_e}{R_1 + R_1} \quad R_e = \frac{R_2 R_L}{R_2 + R_L}$$

$$\therefore \beta = \frac{R_2 R_L}{R_1 R_2 + R_L (R_1 + R_2)}$$

$$\text{But } R_1 + R_2 = \frac{R_2}{\sigma} \quad \therefore R_1 = \frac{R_2}{\sigma} - R_2$$

$$\therefore \beta = \frac{R_2 R_L}{R_2 \left( \frac{R_2}{\sigma} - R_2 \right) + \frac{R_L R_2}{\sigma}}$$

$$\beta = \frac{R_L}{R_2 \left( \frac{1}{\sigma} - 1 \right) + \frac{R_L}{\sigma}}$$

or

$$\beta R_2 \left( \frac{1}{\sigma} - 1 \right) + \frac{\beta R_L}{\sigma} = R_L$$

$$\beta R_2 \left( \frac{1}{\sigma} - 1 \right) = R_L \left( 1 - \frac{\beta}{\sigma} \right)$$

$$\therefore R_2 = \frac{(\sigma - \beta)}{\beta(1 - \sigma)} R_L$$

$$R_1 = \frac{(1 - \sigma)}{\sigma} R_2 = \left( \frac{\sigma - \beta}{\sigma \beta} \right) R_L$$

$$[\text{b}] \quad R_1 = \frac{(0.9 - 0.7)}{0.63} (126) \text{ k}\Omega = 40 \text{ k}\Omega$$

$$R_2 = \frac{(0.9 - 0.7)}{(0.7)(0.1)} (126) \text{ k}\Omega = 360 \text{ k}\Omega$$

P 2.19 [a] Let  $v_o$  be the voltage across the parallel branches, positive at the upper terminal, then

$$i_g = v_o G_1 + v_o G_2 + \cdots + v_o G_N = v_o (G_1 + G_2 + \cdots + G_N)$$

$$\text{It follows that} \quad v_o = \frac{i_g}{(G_1 + G_2 + \cdots + G_N)}$$

The current in the  $k^{\text{th}}$  branch is  $i_k = v_o G_k$ ; Thus,

$$i_k = \frac{i_g G_k}{[G_1 + G_2 + \cdots + G_N]}$$

$$[\text{b}] \quad i_{6.25} = \frac{1142(0.16)}{[4 + 0.4 + 1 + 0.16 + 0.1 + 0.05]} = 32 \text{ mA}$$

$$\text{P 2.20} \quad R_e = \frac{4}{8} \times 10^3 = 500 \Omega$$

$$\therefore \sum G = \frac{1}{500} = 2 \text{ mS}$$

$$i_1 = 2i_2 = 2(10i_3) = 20i_4$$

$$i_2 = 10i_3 = 10i_4$$

$$i_3 = i_4$$

$$8 = 20i_4 + 10i_4 + i_4 + i_4 = 32i_4$$

$$\therefore i_4 = \frac{8}{32} = 0.25 \text{ mA}$$

$$R_4 = \frac{v_g}{i_4} = \frac{4}{0.25 \times 10^{-3}} = 16 \text{ k}\Omega$$

$$i_3 = i_4 = 0.25 \text{ mA}$$


$$\therefore R_3 = 16 \text{ k}\Omega$$

$$i_2 = 10i_4 = 2.5 \text{ mA}$$


$$R_2 = \frac{v_g}{i_2} = \frac{4}{2.5 \times 10^{-3}} = 1.6 \text{ k}\Omega$$

$$i_1 = 20i_4 = 5 \text{ mA}$$



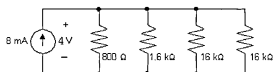
$$R_1 = \frac{v_g}{i_1} = \frac{4}{5 \times 10^{-3}} = 800 \Omega$$



P 2.21 [a]

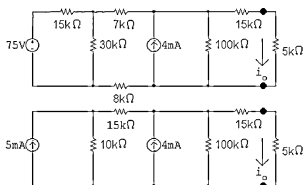




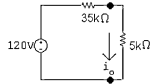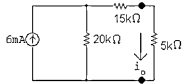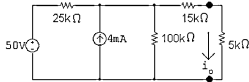

$$i_o = 120/40 \text{ k}\Omega = 3 \text{ mA}$$

[b]

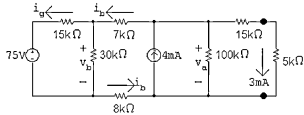

$$v_a = (3)(20) = 60 \text{ V}$$

$$i_a = \frac{v_a}{100} = 0.6 \text{ mA}$$

$$i_b = 4 - 3.6 = 0.4 \text{ mA}$$

$$v_b = 60 - (0.4)(15) = 54 \text{ V}$$

$$i_g = 0.4 - 54/30 = -1.4 \text{ mA}$$

$$p_{75V} \text{ (developed)} = (75)(1.4) = 105 \text{ mW}$$


Check:

$$p_{4mA} \text{ (developed)} = (60)(4) = 240 \text{ mW}$$

$$\sum P_{dev} = 105 + 240 = 345 \text{ mW}$$




$$\begin{aligned} \sum P_{dis} &= (-1.4)^2(15) + (1.8)^2(30) + (0.4)^2(15) + (0.6)^2(100) + \\ &\quad (3)^2(20) \\ &= 345 \text{ mW} \end{aligned}$$

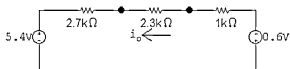P 2.22 Apply source transformations to both current sources to get




$$i_o = \frac{-6}{6} = -1 \text{ mA}$$

P 2.23 [a]

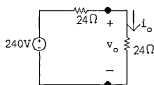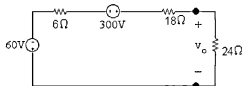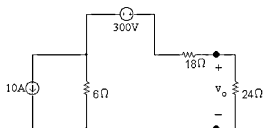

$$\therefore v_o = \frac{1}{2}(240) = 120 \text{ V}; \quad i_o = 120/24 = 5 \text{ A}$$

[b]

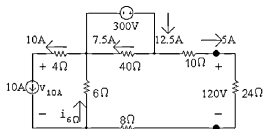

$$p_{300V} = -12.5(300) = -3750 \text{ W}$$

Therefore, the 300 V source is developing 3.75 kW.

$$[c] -10 + i_{6\Omega} + 7.5 - 12.5 = 0; \quad \therefore i_{6\Omega} = 15 \text{ A}$$

$$v_{10A} + 4(10) + 6(15) = 0; \quad \therefore v_{10A} = -130 \text{ V}$$

$$p_{10A} = 10v_{10A} = -1300 \text{ W}$$

Therefore the 10 A source is developing 1300 W.

$$[d] \sum p_{dev} = 3750 + 1300 = 5050 \text{ W}$$

$$p_{4\Omega} = 100(4) = 400 \text{ W}$$


$$p_{40\Omega} = (7.5)^2(40) = 2250 \text{ W}$$

$$p_{6\Omega} = (15)^2(6) = 1350 \text{ W}$$


$$p_{42\Omega} = (5)^2(42) = 1050 \text{ W}$$

$$\sum p_{diss} = 400 + 1350 + 2250 + 1050 = 5050 \text{ W (CHECKS)}$$

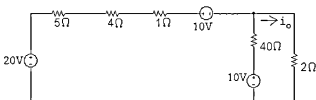
P 2.24 Applying a source transformation to each current source yields



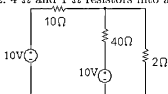
Now combine the 20 V and 10 V sources into a single voltage source and the 5 Ω, 4 Ω and 1 Ω resistors into a single resistor to get



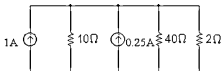Now use a source transformation on each voltage source, thus






which can be reduced to

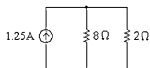


$$\therefore i_o = \frac{(1.25)(8)}{10} = 1 \text{ A}$$

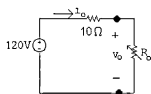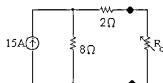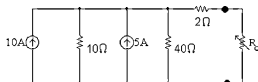P 2.25 First, find the Thévenin equivalent with respect to  $R_o$ .




$R_o$	$i_o$	$v_o$	$R_o$	$i_o$	$v_o$
0	12	0	20	4	80
2	10	20	30	3	90
6	7.5	45	40	2.4	96
10	6	60	50	2	100
15	4.8	72	70	1.5	105

P 2.26

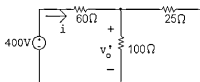

$$100 \Omega \parallel 25 \Omega = 20 \Omega \quad \therefore i = \frac{400}{60 + 20} = 5 \text{ A}$$

$$v'_o = 20i = 100 \text{ V}$$

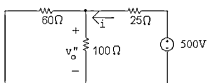




$$100\Omega \parallel 60\Omega = 37.5\Omega$$


$$i = \frac{500}{25 + 37.5} = 8 \text{ A}$$

$$v''_o = 37.5i = 300 \text{ V}$$


$$v_o = v'_o + v''_o = 100 + 300 = 400 \text{ V}$$

P 2.27

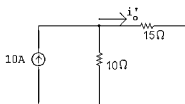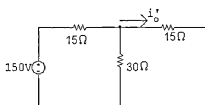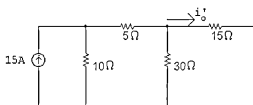


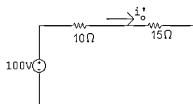

$$i'_o = \frac{100}{25} = 4 \text{ A}$$

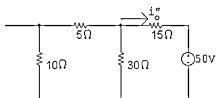

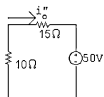
$$15\Omega \parallel 30\Omega = 10\Omega$$



$$i''_o = \frac{-50}{25} = -2 \text{ A}$$

$$\therefore i_o = i'_o + i''_o = 4 - 2 = 2 \text{ A}$$

P 2.28

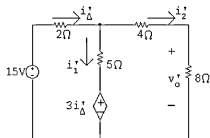


$$15 = 2i'_\Delta + 5i_1 + 3i'_\Delta$$

$$15 = 2i'_{\Delta} + 12i'_2$$

$$i'_{\Delta} = i'_1 + i'_2, \quad i'_1 = 27/26 \text{ A}; \quad i'_{\Delta} = 51/26 \text{ A}$$
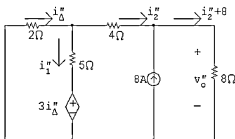
$$\therefore i'_2 = \frac{12}{13} \text{ A}; \quad v'_o = \frac{96}{13} \text{ V}$$



$$-2i''_{\Delta} = 5i''_1 + 3i''_{\Delta} \quad \therefore i''_{\Delta} = -i''_1$$

$$i''_2 = i''_{\Delta} - i''_1 = 2i''_{\Delta}$$

$$4i''_2 + (8 + i''_2)8 = -2i''_{\Delta}$$


$$\therefore i''_2 = -\frac{64}{13} \text{ A}; \quad i''_1 = \frac{32}{13} \text{ A}; \quad i''_{\Delta} = -\frac{32}{13} \text{ A}$$

$$\therefore 8 + i''_2 = \frac{40}{13} \text{ A}$$


$$\therefore v''_o = 8 \left( \frac{40}{13} \right) = \frac{320}{13} \text{ V}$$

$$\therefore v_o = v'_o + v''_o = \frac{96}{13} + \frac{320}{13} = 32 \text{ V}$$

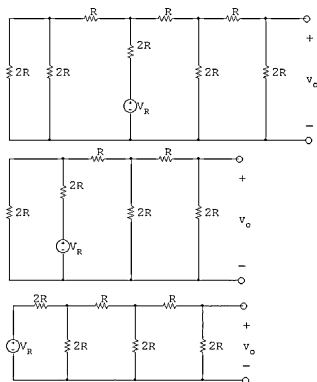
P 2.29 [a] The evolution of the circuit shown in Fig. P2.29 is illustrated in the following steps:



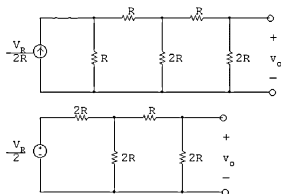[b] Starting at the left end of the circuit and working toward the right end, a series of source transformations yields:






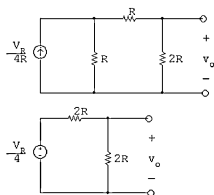







$$\frac{V_R/4}{4R}(2R) = \frac{V_R}{8}$$

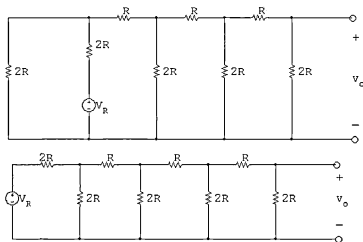P 2.30 [a] The evolution of the circuit in Fig. P2.30 can be shown in two steps, thus:



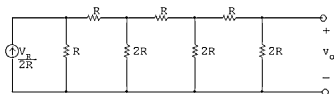[b] Moving from left to right, a series of source transformations yields:



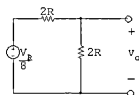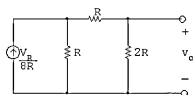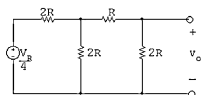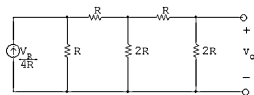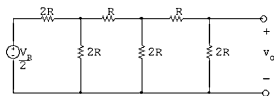

$$v_o = \frac{V_R/8}{4R}(2R) = \frac{V_R}{16}$$

P 2.31

$$\text{Eq.(2.34)} \quad v_o = \frac{1}{2}V_R \quad (\text{Switch 1})$$

$$\text{Eq.(2.35)} \quad v_o = \frac{1}{4}V_R \quad (\text{Switch 2})$$

$$\text{Eq.(2.36)} \quad v_o = \frac{1}{8}V_R \quad (\text{Switch 3})$$

$$\text{Eq.(2.37)} \quad v_o = \frac{1}{16}V_R \quad (\text{Switch 4})$$

Given  $V_R = 16$  V:

Switch Position				$v_o$
1	2	3	4	
0	0	0	0	$v_o = 0$ V
0	0	0	$V_R$	$v_o = \frac{1}{16}V_R = 1$ V
0	0	$V_R$	0	$v_o = \frac{1}{8}V_R = 2$ V
0	0	$V_R$	$V_R$	$v_o = \frac{1}{16}V_R + \frac{1}{8}V_R = 3$ V
0	$V_R$	0	0	$v_o = \frac{1}{4}V_R = 4$ V
0	$V_R$	0	$V_R$	$v_o = \frac{1}{4}V_R + \frac{1}{16}V_R = 5$ V
0	$V_R$	$V_R$	0	$v_o = \frac{1}{4}V_R + \frac{1}{8}V_R = 6$ V
0	$V_R$	$V_R$	$V_R$	$v_o = \frac{1}{4}V_R + \frac{1}{8}V_R + \frac{1}{16}V_R = 7$ V
$V_R$	0	0	0	$v_o = \frac{1}{2}V_R = 8$ V
$V_R$	0	0	$V_R$	$v_o = \frac{1}{2}V_R + \frac{1}{16}V_R = 9$ V
$V_R$	0	$V_R$	0	$v_o = \frac{1}{2}V_R + \frac{1}{8}V_R = 10$ V
$V_R$	0	$V_R$	$V_R$	$v_o = \frac{1}{2}V_R + \frac{1}{8}V_R + \frac{1}{16}V_R = 11$ V
$V_R$	$V_R$	0	0	$v_o = \frac{1}{2}V_R + \frac{1}{4}V_R = 12$ V
$V_R$	$V_R$	0	$V_R$	$v_o = \frac{1}{2}V_R + \frac{1}{4}V_R + \frac{1}{16}V_R = 13$ V
$V_R$	$V_R$	$V_R$	0	$v_o = \frac{1}{2}V_R + \frac{1}{4}V_R + \frac{1}{8}V_R = 14$ V
$V_R$	$V_R$	$V_R$	$V_R$	$v_o = \frac{1}{2}V_R + \frac{1}{4}V_R + \frac{1}{8}V_R + \frac{1}{16}V_R = 15$ V

*This page intentionally left blank*

---

## Techniques of Circuit Analysis

---

### Drill Exercises

DE 3.1 [a] 11, 8 resistors, 2 independent sources, 1 dependent source

[b] 9

[c] 9,  $R_4 - R_5$  forms an essential branch as does  $R_8 - 10\text{ V}$ . The remaining seven branches contain a single element.

[d] 7

[e] 6

[f] 4

[g] 6

DE 3.2 Solution given in text.

DE 3.3 Solution given in text.

DE 3.4 Solution given in text.

DE 3.5 [a] The two node voltage equations are

$$-15 + \frac{v_1}{60} + \frac{v_1}{15} + \frac{v_1 - v_2}{5} = 0$$

$$5 + \frac{v_2}{2} + \frac{v_2 - v_1}{5} = 0$$

Solving,  $v_1 = 60\text{ V}$  and  $v_2 = 10\text{ V}$ ;

Therefore,  $i_1 = (v_1 - v_2)/5 = 10\text{ A}$

[b]  $p_{15\text{A}}(\text{del}) = (15)(60) = 900\text{ W}$

[c]  $p_{5\text{A}} = -5(10) = -50\text{ W}$

DE 3.6 Use the lower node as the reference node. Let  $v_1 =$  node voltage across  $1\ \Omega$  resistor and  $v_2 =$  node voltage across  $12\ \Omega$  resistor. Then

$$\frac{v_1}{1} + \frac{v_1 - v_2}{8} = 4.5$$

$$\frac{v_2}{12} + \frac{v_2 - v_1}{8} + \frac{v_2 - 30}{4} = 0$$

Solving,  $v_1 = 6$  V       $v_2 = 18$  V Thus,  $i = (v_1 - v_2)/8 = -1.5$  A  
 $v = v_2 + 2i = 15$  V

DE 3.7 Use the lower node as the reference node. Let  $v_1 =$  node voltage across the 8  $\Omega$  resistor, let  $v_2 =$  node voltage across the 4  $\Omega$  resistor. Then

$$\frac{v_1 - 50}{6} + \frac{v_1}{8} + \frac{v_1 - v_2}{2} - 3i_1 = 0$$

$$-5 + \frac{v_2}{4} + \frac{v_2 - v_1}{2} + 3i_1 = 0$$

$$i_1 = \frac{50 - v_1}{6}$$

Solving,  $v_1 = 32$  V;       $v_2 = 16$  V;       $i_1 = 3$  A  $p_{50V} = -50i_1 = -150$  W (delivering)

$p_{5A} = -5(v_2) = -80$  W (delivering)

$p_{3i_1} = 3i_1(v_2 - v_1) = -144$  W (delivering)

DE 3.8 Use the lower node as the reference node. Let  $v_1 =$  node voltage across the 7.5  $\Omega$  resistor and  $v_2 =$  node voltage across the 2.5  $\Omega$  resistor. Place the dependent voltage source inside a supernode between the node voltages  $v$  and  $v_2$ . The node voltage equations are

$$\text{node 1: } \frac{v_1}{7.5} + \frac{v_1 - v}{2.5} = 4.8$$

$$\text{supernode: } \frac{v - v_1}{2.5} + \frac{v}{10} + \frac{v_2}{2.5} + \frac{v_2 - 12}{1} = 0$$

We also have:  $v + i_x = v_2$  and  $i_x = v_1/7.5$ . Solving this set of equations for  $v$  gives  $v = 8$  V

$$\text{DE 3.9 } \frac{v_1 - 60}{2} + \frac{v_1}{24} + \frac{v_1 - (60 + 6i_\phi)}{3} = 0, \quad i_\phi = \frac{60 + 6i_\phi - v_1}{3}$$

Therefore  $v_1 = 48$  V

DE 3.10

$$\frac{v_o}{40} + \frac{v_o - 10}{10} + \frac{v_o + 20i_\Delta}{20} = 0, \quad i_\Delta = \frac{10 - v_o}{10} + \frac{10 + 20i_\Delta}{30}$$

Therefore  $v_o = 24$  V

DE 3.11 Define three clockwise mesh currents  $i_1$ ,  $i_2$ , and  $i_3$  in the lower left, upper, and lower right windows. The three mesh-current equations are

$$80 = 31i_1 - 5i_2 - 26i_3$$

$$0 = -5i_1 + 125i_2 - 90i_3$$

$$0 = -26i_1 - 90i_2 + 124i_3$$

[a] Solving,  $i_1 = 5$  A; therefore the 80 V source is delivering 400 W to the circuit.

[b] Solving,  $i_3 = 2.5$  A; therefore  $p_{8\Omega} = (6.25)(8) = 50$  W

DE 3.12 [a]  $b = 8$ ,  $n = 6$ ,  $b - n + 1 = 3$

[b] Define three clockwise mesh currents  $i_1$ ,  $i_2$ , and  $i_3$  in the upper, lower left, and lower right windows. The three mesh-current equations are

$$-(-3v_\phi) + 19i_1 - 2i_2 - 3i_3 = 0$$

$$25 - 10 = -2i_1 + 7i_2 - 5i_3$$

$$10 = -3i_1 - 5i_2 + 9i_3$$

$$\text{We also have } v_\phi = 3(i_3 - i_1)$$

Solving for  $i_1$  and  $i_3$  gives  $i_1 = -1$  A,  $i_3 = 3$  A Therefore  $v_\phi = 12$  V and  $p_{3v_\phi} = -(-3v_\phi)i_1 = -36$  W

DE 3.13 Let  $i_a$  = lower left mesh current cw, let  $i_b$  = upper mesh current cw, and  $i_c$  = lower right mesh current cw. Then

$$25 = 14i_a - 6i_b - 8i_c$$


$$0 = -6i_a + 16i_b - 8i_c$$

$$0 = -8i_a - 8i_b + 16i_c + 5i_\phi$$

$$i_\phi = i_a, \quad i_a = 4 \text{ A}, \quad i_c = 2 \text{ A}$$

$$v_o = 8(i_a - i_c) = 16 \text{ V}$$

DE 3.14

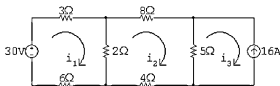

$$\text{Mesh 1: } 30 = 11i_1 - 2i_2$$

$$\text{Mesh 2: } 0 = -2i_1 + 19i_2 - 5i_3$$


Current source:  $i_3 = -16$  A

Solution gives  $i_1 = 2$  A,  $i_2 = -4$  A,  $i_3 = -16$  A

The current in the  $2\Omega$  resistor is  $i_1 - i_2 = 6$  A

$$\therefore P_{2\Omega} = (6)^2(2) = 72 \text{ W}$$

DE 3.15

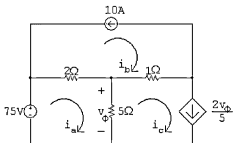


$$\text{Mesh a: } 7i_a - 2i_b - 5i_c = 75$$

$$\text{Current sources: } i_b = -10 \text{ A; } i_c = \frac{2v_\phi}{5}$$

$$\text{Dependent variable: } v_\phi = 5(i_a - i_c)$$

$$\text{Solution: } i_a = 15 \text{ A; } i_b = -10 \text{ A; } i_c = 10 \text{ A; } v_\phi = 25 \text{ V}$$

DE 3.16

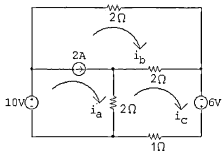

$$\text{Supermesh a,b: } 2i_a + 4i_b - 4i_c = 10$$

$$\text{Mesh c: } -2i_a - 2i_b + 5i_c = 6$$

$$\text{Current source: } i_a - i_b = 2 \text{ A}$$

$$\text{Solution: } i_a = 7 \text{ A; } i_b = 5 \text{ A; } i_c = 6 \text{ A}$$

$$\therefore p_{1\Omega} = i_c^2(1) = (6)^2(1) = 36 \text{ W}$$




DE 3.17 Let  $v_1$  denote the voltage across the 2 A source. Let  $v_1$  be a voltage rise in the direction of the 2 A current.

$$\frac{v_1 - 20}{15} - 2 + \frac{v_1 - 25}{10} = 0, \quad v_1 = 35 \text{ V}$$

$$p_{2A} = -35(2) = -70 \text{ W} \quad p_{2A}(\text{del}) = 70 \text{ W}$$

DE 3.18

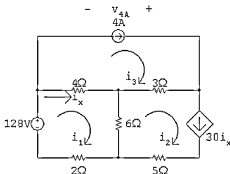

$$\text{Mesh 1: } 12i_1 - 6i_2 - 4i_3 = 128$$

$$\text{Mesh 2: } -6i_1 + 14i_2 - 3i_3 + 30i_x = 0$$

$$\text{Current source: } i_3 = 4 \text{ A}$$

$$\text{Dependent variable: } i_x = i_1 - i_3$$


$$\text{Solution: } i_1 = 9 \text{ A; } i_2 = -6 \text{ A; } i_3 = 4 \text{ A; } i_x = 5 \text{ A}$$

$$\therefore v_{4A} = 3(i_3 - i_2) - 4i_x = 10 \text{ V}$$

$$\text{The power delivered by the 4A source is } p_{4A} = (10)(4) = 40 \text{ W}$$

DE 3.19 To find the Thévenin resistance, deactivate the independent voltage source and note that  $R_{Th} = [5 \parallel 20 + 8] \parallel 12 = 6 \Omega$ . With the terminals a, b open, the current delivered by the 72 V source is  $72/24$  or 3 A. The current (left-to-right) in the  $5 \Omega$  resistor is  $(20/25)(3) = 2.4 \text{ A}$ , and the current (left-to-right) in the  $12 \Omega$  resistor is  $(5/25)3$  or 0.6 A. The Thévenin voltage  $v_{Th} = v_{ab}$  is the drop across the  $8 \Omega$  resistor plus the drop across the  $20 \Omega$  resistor. Thus  $v_{Th} = (8)(0.6) + (20)(3) = 64.8 \text{ V}$ .

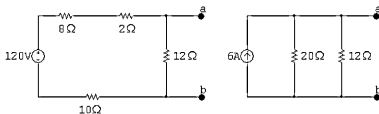DE 3.20 After one source transformation, the circuit becomes



Therefore  $I_N = 6 \text{ A}$ ,  $R_N = 20 \parallel 12 = 7.5 \Omega$

DE 3.21 Find the Thévenin equivalent with respect to A, B.

$$\frac{V_{Th} + 36}{12,000} + \frac{V_{Th}}{60,000} - 0.018 = 0, \quad V_{Th} = 150 \text{ V}$$


$$R_{Th} = 15,000 + \frac{(60,000)(12,000)}{72,000} = 25 \text{ k}\Omega;$$

Therefore,  $v_{meas} = 150 \left( \frac{100,000}{125,000} \right) = 120 \text{ V}$

DE 3.22 Summing the currents away from node a, where  $v_{Th} = v_{ab}$ . We have

$$\frac{v_{Th}}{8} + 4 + 3i_x + \frac{v_{Th} - 24}{2} = 0, \quad i_x = \frac{v_{Th}}{8}$$

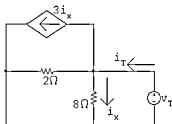Solving for  $v_{Th}$  yields  $v_{Th} = 8 \text{ V}$



$$i_T = 4i_x + v_T/2, \quad i_x = v_T/8$$

Therefore  $i_T = v_T$  and  $R_{Th} = v_T/i_T = 1 \Omega$

DE 3.23 Use the bottom node as the reference. Let  $v_1$  be the node voltage across the  $60\ \Omega$  resistor. Then

$$\frac{v_1}{60} + \frac{v_1 - (v_{Th} + 160i_\Delta)}{20} - 4 = 0,$$

$$\frac{v_{Th}}{40} + \frac{v_{Th}}{80} + \frac{v_{Th} + 160i_\Delta - v_1}{20} = 0$$

$$i_\Delta = \frac{v_{Th}}{40}, \quad \text{therefore} \quad v_{Th} = 30\text{ V}$$

Let  $i_T$  be the test current into terminal a:

$$i_T = \frac{v_T}{80} + \frac{v_T}{40} + \frac{v_T + 160(v_T/40)}{80}, \quad \frac{i_T}{v_T} = \frac{1}{10}$$

Therefore,  $R_{Th} = 10\ \Omega$

DE 3.24 First find the Thévenin equivalent circuit. To find  $v_{Th}$ , use the bottom node as the reference. Let  $v_{Th} = v_{ab}$  and  $v_1$  be node voltage across the  $20\text{ V} - 4\ \Omega$  branch. The two node Voltage equations are

$$\frac{v_{Th} - 100 - v_\phi}{4} + \frac{v_{Th} - v_1}{4} = 0, \quad (v_\phi = v_1 - 20)$$

$$\frac{v_1 - 100}{4} + \frac{v_1 - 20}{4} + \frac{v_1 - v_{Th}}{4} = 0$$

Solving for  $v_{Th}$  gives  $v_{Th} = 120\text{ V}$ . To find  $R_{Th}$ , deactivate the two independent sources and apply a test voltage source across a, b. Let  $v_T$  be positive at a and  $i_T$  directed into a. Then the two node Voltage equations are

$$\frac{v_T - v_\phi}{4} + \frac{v_{Th} - v_\phi}{4} = i_T, \quad \frac{v_\phi}{4} + \frac{v_\phi}{4} + \frac{v_\phi - v_T}{4} = 0$$

Therefore  $v_\phi = v_T/3$  and  $12i_T = 4v_T$

So  $R_{Th} = v_T/i_T = 3\ \Omega$

[a] For maximum power transfer,  $R_L = R_{Th} = 3\ \Omega$

[b]  $p_{\max} = (120/6)^2(3) = 1200\text{ W}$

DE 3.25 When  $R_L = 3\ \Omega$ , the voltage across  $R_L$  is 60 V. As before, let  $v_1$  be the node voltage across the 20 V—4  $\Omega$  branch, then  $v_\phi = v_1 - 20$  and

$$\frac{60}{3} + \frac{60 - v_1}{4} + \frac{60 - 100 - v_\phi}{4} = 0$$

Therefore  $v_1 = 60$  V and  $v_\phi = 40$  V. The current out of the plus terminal of the 100 V source is

$$i_1 = \frac{100 - 60}{4} + \frac{100 + 40 - 60}{4} = 10 + 20 = 30\text{ A}$$

[a] Therefore 100 V is delivering 3000 W to the circuit.

[b] The current out of the plus terminal of the dependent source is 20 A.  
Therefore the dependent source is delivering 800 W to the circuit.


[c] The load power is  $(1200/3800)100$  or 31.58% of this generated power.

## Problems

P 3.1 [a] Five

[b] Three

[c]

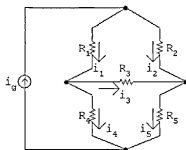

Sum the currents at any three of the four essential nodes a, b, c, and d. Using nodes a, b, and c we get

$$-i_g + i_1 + i_2 = 0$$

$$-i_1 + i_4 + i_3 = 0$$

$$i_5 - i_2 - i_3 = 0$$


[d] Two.

[e] Sum the voltages around two independent closed paths, avoiding a path that contains the independent current source since the voltage across the current source is not known. Using the upper and lower meshes formed by the five resistors gives

$$R_1 i_1 + R_3 i_3 - R_2 i_2 = 0$$

$$R_3 i_3 + R_5 i_5 - R_4 i_4 = 0$$

P 3.2

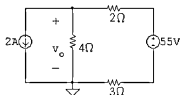

$$2 + \frac{v_o}{4} + \frac{v_o - 55}{5} = 0$$

$$v_o = 20 \text{ V}$$

$$p_{2A} = (20)(2) = 40 \text{ W (absorbing)}$$

P 3.3 Let  $v_2$  be the node voltage across the  $80 \Omega$  resistor, positive at the upper terminal.

$$\text{Then } -4 + \frac{v_1}{20} + \frac{v_2}{80} + \frac{v_2}{40} = 0$$

(Note we have created a super node in writing this expression.)

$$v_1 + 60 = v_2$$

$$\therefore v_1 = 20 \text{ V}$$


$$\therefore v_2 = 80 \text{ V}$$

$p_{\text{del}} = 60i_g$  where  $i_g$  is the current out of the positive terminal

$$4 = i_g + \frac{v_1}{20}; \quad i_g = 3 \text{ A}$$

$$\therefore p_{\text{del}} = 60(3) = 180 \text{ W}$$

P 3.4 [a]

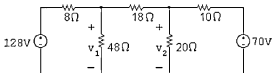

$$\frac{v_1}{48} + \frac{v_1 - 128}{8} + \frac{v_1 - v_2}{18} = 0$$

$$\frac{v_2}{20} + \frac{v_2 - v_1}{18} + \frac{v_2 - 70}{10} = 0$$

$$\text{Solving, } v_1 = 96 \text{ V; } v_2 = 60 \text{ V}$$

$$i_a = \frac{128 - 96}{8} = 4 \text{ A}$$

$$i_b = \frac{96}{48} = 2 \text{ A}$$

$$i_c = \frac{96 - 60}{18} = 2 \text{ A}$$

$$i_d = \frac{60}{20} = 3 \text{ A}$$

$$i_e = \frac{60 - 70}{10} = -1 \text{ A}$$


$$[b] \ p_{dev} = 128(4) + 70(1) = 582 \text{ W}$$

P 3.5 Use the lower terminal of the  $5 \Omega$  resistor as the reference node.

$$\frac{v_o - 60}{10} + \frac{v_o}{5} + 3 = 0$$

$$\text{Solving, } v_o = 10 \text{ V}$$

P 3.6 [a]

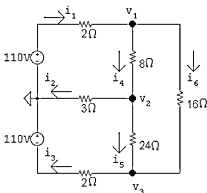

$$\frac{v_1 - 110}{2} + \frac{v_1 - v_2}{8} + \frac{v_1 - v_3}{16} = 0$$

$$\frac{v_2 - v_1}{8} + \frac{v_2}{3} + \frac{v_2 - v_3}{24} = 0$$

$$\frac{v_3 + 110}{2} + \frac{v_3 - v_2}{24} + \frac{v_3 - v_1}{16} = 0$$

$$\text{Solving, } v_1 = 74.64 \text{ V; } v_2 = 11.79 \text{ V; } v_3 = -82.5 \text{ V}$$

$$\text{Thus, } i_1 = \frac{110 - v_1}{2} = 17.68 \text{ A} \quad i_4 = \frac{v_1 - v_2}{8} = 7.86 \text{ A}$$

$$i_2 = \frac{v_2}{3} = 3.93 \text{ A} \quad i_5 = \frac{v_2 - v_3}{24} = 3.93 \text{ A}$$

$$i_3 = \frac{v_3 + 110}{2} = 13.75 \text{ A} \quad i_6 = \frac{v_1 - v_3}{16} = 9.82 \text{ A}$$

$$[\text{b}] \sum P_{\text{dev}} = 110i_1 + 110i_3 = 3457.14 \text{ W}$$

$$\sum P_{\text{dis}} = i_1^2(2) + i_2^2(3) + i_3^2(2) + i_4^2(8) + i_5^2(24) + i_6^2(16) = 3457.14 \text{ W}$$

$$\text{P 3.7 } 2.4 + \frac{v_1}{125} + \frac{v_1 - v_2}{25} = 0$$

$$\frac{v_2 - v_1}{25} + \frac{v_2}{250} + \frac{v_2}{375} - 3.2 = 0$$

$$\text{Solving, } v_1 = 25 \text{ V; } v_2 = 90 \text{ V}$$

CHECK:

$$p_{125\Omega} = \frac{(25)^2}{125} = 5 \text{ W}$$

$$p_{25\Omega} = \frac{(90 - 25)^2}{25} = 169 \text{ W}$$

$$p_{250\Omega} = \frac{(90)^2}{250} = 32.4 \text{ W}$$


$$p_{375\Omega} = \frac{(90)^2}{375} = 21.6 \text{ W}$$

$$p_{2.4\text{A}} = (25)(2.4) = 60 \text{ W}$$

$$\sum p_{\text{abs}} = 5 + 169 + 32.4 + 21.6 + 60 = 288 \text{ W}$$

$$\sum p_{\text{dev}} = (90)(3.2) = 288 \text{ W} \quad (\text{CHECKS})$$

P 3.8 [a]

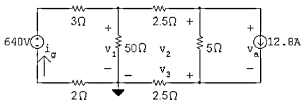

$$\frac{v_1}{50} + \frac{v_1 - 640}{5} + \frac{v_1 - v_2}{2.5} = 0$$

$$\frac{v_2 - v_1}{2.5} + \frac{v_2 - v_3}{5} + 12.8 = 0$$


$$\frac{v_3}{2.5} + \frac{v_3 - v_2}{5} - 12.8 = 0$$

Solving,  $v_1 = 380$  V;  $v_2 = 269$  V;  $v_3 = 111$  V,

$$[b] i_g = \frac{640 - 380}{5} = 52 \text{ A}$$

$$p_g(\text{del}) = (640)(52) = 33,280 \text{ W}$$

P 3.9

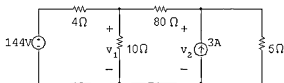


$$\frac{v_1 - 144}{4} + \frac{v_1}{10} + \frac{v_1 - v_2}{80} = 0 \quad \text{so} \quad 29v_1 - v_2 = 2880$$

$$-3 + \frac{v_2 - v_1}{80} + \frac{v_2}{5} = 0 \quad \text{so} \quad -v_1 + 17v_2 = 240$$

Solving,  $v_1 = 100$  V;  $v_2 = 20$  V

P 3.10

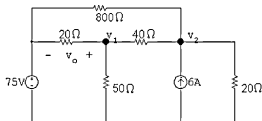

$$\frac{v_1 - 75}{20} + \frac{v_1}{50} + \frac{v_1 - v_2}{40} = 0$$




$$\frac{v_2 - v_1}{40} + \frac{v_2 - 75}{800} - 6 + \frac{v_2}{200} = 0$$

$$\text{Solving, } v_1 = 115 \text{ V; } v_2 = 287 \text{ V}$$

$$\therefore v_o = 115 - 75 = 40 \text{ V}$$

P 3.11

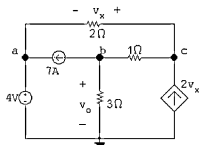

$$v_a = 4 \text{ V}$$


$$7 + \frac{v_b}{3} + \frac{v_b - v_c}{1} = 0$$

$$-2v_x + \frac{v_c - v_b}{1} + \frac{v_c - v_a}{2} = 0$$

$$v_x = v_c - v_a = v_c - 4$$

$$\text{Solving, } v_o = v_b = 1.5 \text{ V}$$

P 3.12

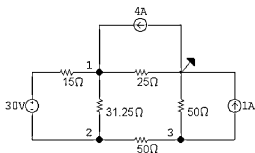

$$\frac{v_1 - (v_2 + 30)}{15} + \frac{v_1 - v_2}{31.25} + \frac{v_1}{25} - 4 = 0$$

$$-\left[\frac{v_1 - (v_2 + 30)}{15}\right] + \frac{v_2 - v_3}{50} + \frac{v_2 - v_1}{31.25} = 0$$

$$\frac{v_3 - v_2}{50} + \frac{v_3}{50} + 1 = 0$$

$$\text{Solving, } v_1 = 76 \text{ V; } v_2 = 46 \text{ V; } v_3 = -2 \text{ V; } i_{30V} = 0 \text{ A}$$

$$p_{4A} = -4v_1 = -4(76) = -304 \text{ W (del)}$$

$$p_{1A} = (1)(-2) = -2 \text{ W (del)}$$

$$p_{30V} = (30)(0) = 0 \text{ W}$$

$$p_{15\Omega} = (0)^2(15) = 0 \text{ W}$$

$$p_{25\Omega} = \frac{v_1^2}{25} = \frac{76^2}{25} = 231.04 \text{ W}$$

$$p_{31.25\Omega} = \frac{(v_1 - v_2)^2}{31.25} = \frac{30^2}{31.25} = 28.8 \text{ W}$$


$$p_{50\Omega(\text{lower})} = \frac{(v_2 - v_3)^2}{50} = \frac{48^2}{50} = 46.08 \text{ W}$$

$$p_{50\Omega(\text{right})} = \frac{v_3^2}{50} = \frac{4}{50} = 0.08 \text{ W}$$

$$\sum p_{\text{diss}} = 0 + 231.04 + 28.8 + 46.8 + 0.08 = 306 \text{ W}$$

$$\sum p_{\text{dev}} = 304 + 2 = 306 \text{ W (CHECKS)}$$

P 3.13

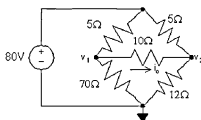


$$\frac{v_1}{70} + \frac{v_1 - v_2}{10} + \frac{v_1 - 80}{5} = 0$$

$$\frac{v_2}{12} + \frac{v_2 - v_1}{10} + \frac{v_2 - 80}{5} = 0$$

$$\text{Solving, } v_1 = 70 \text{ V; } v_2 = 60 \text{ V}$$

$$\text{Thus, } i_o = \frac{v_1 - v_2}{10} = 1 \text{ A}$$

- P 3.14 [a]  $\frac{v_o - 60}{10} + \frac{v_o}{5} + 3 = 0; \quad v_o = 10 \text{ V}$
- [b] Let  $v_x =$  voltage drop across 3 A source  
 $v_x = v_o - (100)(3) = -290 \text{ V}$   
 $p_{3A} \text{ (developed)} = (3)(290) = 870 \text{ W}$
- [c] Let  $i_g =$  current into positive terminal of 60 V source  
 $i_g = (10 - 60)/10 = -5 \text{ A}$   
 $p_{60V} \text{ (developed)} = (5)(60) = 300 \text{ W}$
- [d]  $\sum p_{\text{dis}} = (5)^2(10) + (3)^2(100) + (10)^2/5 = 1170 \text{ W}$   
 $\sum p_{\text{dis}} = 300 + 870 = 1170 \text{ W}$
- [e]  $v_o$  is independent of any finite resistance connected in series with the 3 A current source
- P 3.15 [a] From the solution to Problem 3.5 we know  $v_o = 10 \text{ V}$ , therefore  
 $p_{3A} = 3v_o = 30 \text{ W}$   
 $\therefore p_{3A} \text{ (developed)} = -30 \text{ W}$
- [b] The current into the negative terminal of the 60 V source is  
 $i_g = \frac{60 - 10}{10} = 5 \text{ A}$   
 $p_{60V} = -60(5) = -300 \text{ W}$   
 $\therefore p_{60V} \text{ (developed)} = 300 \text{ W}$
- [c]  $p_{10\Omega} = (5)^2(10) = 250 \text{ W}$   
 $p_{5\Omega} = (10)^2/5 = 20 \text{ W}$   
 $\sum p_{\text{dev}} = 300 \text{ W}$   
 $\sum p_{\text{dis}} = 250 + 20 + 30 = 300 \text{ W}$
- P 3.16 [a]

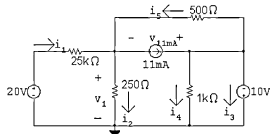

$$\frac{v_1 - 20}{25 \times 10^3} + \frac{v_1}{0.25 \times 10^3} + 11 \times 10^{-3} + \frac{v_1 + 10}{0.5 \times 10^3} = 0$$

$$v_1 = -5 \text{ V}$$

$$i_1 = \frac{20 + 5}{25,000} = 1 \text{ mA}$$

$$i_2 = \frac{v_1}{250} = \frac{-5}{250} = -20 \text{ mA}$$

$$i_5 = \frac{-10 + 5}{500} = -10 \text{ mA}$$

$$i_4 = \frac{-10}{1000} = -10 \text{ mA}$$

$$i_4 + i_3 - 11 + i_5 = 0$$

$$\therefore i_3 = 11 - i_4 - i_5 = 11 + 10 + 10 = 31 \text{ mA}$$

$$[\text{b}] \quad p_{20\text{V}} = 20i_1 = 20(1 \times 10^{-3}) = 20 \text{ mW}$$

$$p_{10\text{V}} = 10i_3 = 10(31 \times 10^{-3}) = 310 \text{ mW}$$

$$v_{11\text{mA}} + v_1 = -10, \quad v_{11\text{mA}} = -10 + 5 = -5 \text{ V}$$

$$p_{11\text{mA}} = -11v_{11\text{mA}} = -55 \text{ mW} \quad (\text{del})$$

$$\sum p_{\text{dev}} = 20 + 310 = 330 \text{ mW}$$

$$p_{25\text{k}} = 25 \times 10^3 i_1^2 = 25 \text{ mW}$$

$$p_{0.25\text{k}} = 0.25 \times 10^3 i_2^2 = 100 \text{ mW}$$


$$p_{0.5\text{k}} = 0.5 \times 10^3 i_5^2 = 50 \text{ mW}$$

$$p_{1\text{k}} = 1 \times 10^3 i_4^2 = 100 \text{ mW}$$

$$\sum p_{\text{diss}} = 25 + 100 + 50 + 100 + 55 = 330 \text{ mW}$$

$$\sum p_{\text{diss}} = \sum p_{\text{dev}} = 330 \text{ mW}$$

P 3.17 [a]

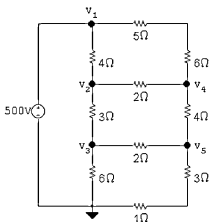

$$\frac{v_2 - 500}{4} + \frac{v_2 - v_4}{2} + \frac{v_2 - v_3}{3} = 0$$

$$\frac{v_3 - v_2}{3} + \frac{v_3}{6} + \frac{v_3 - v_5}{2} = 0$$

$$\frac{v_4 - v_2}{2} + \frac{v_4 - 500}{11} + \frac{v_4 - v_5}{4} = 0$$

$$\frac{v_5 - v_3}{2} + \frac{v_5}{4} + \frac{v_5 - v_4}{4} = 0$$

Solving,  $v_2 = 300$  V;  $v_3 = 180$  V;  $v_4 = 280$  V;  $v_5 = 160$  V


$$i_{5\Omega} = \frac{500 - v_4}{11} = \frac{500 - 280}{11} = 20 \text{ A}$$

$$p_{5\Omega} = (20)^2(5) = 2000 \text{ W}$$

$$\begin{aligned} \text{[b]} \quad i_{500\text{V}} &= \frac{v_1 - v_2}{4} + \frac{v_1 - v_4}{11} \\ &= \frac{500 - 300}{4} + \frac{500 - 280}{11} = 50 + 20 = 70 \text{ A} \end{aligned}$$

$$p_{500\text{V}} = 35,000 \text{ W}$$

Check:

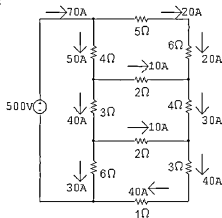

$$\begin{aligned} \sum P_{\text{dis}} &= (50)^2(4) + (40)^2(3) + (30)^2(6) + (20)^2(11) + (10)^2(2) \\ &\quad + (30)^2(4) + (10)^2(2) + (40)^2(4) = 35,000 \text{ W} \end{aligned}$$

$$\text{P 3.18 [a]} \quad \frac{v_o - v_1}{R} + \frac{v_o - v_2}{R} + \frac{v_o - v_3}{R} + \cdots + \frac{v_o - v_n}{R} = 0$$

$$\therefore n v_o = v_1 + v_2 + v_3 + \cdots + v_n$$

$$\therefore v_o = \frac{1}{n} [v_1 + v_2 + v_3 + \cdots + v_n] = \frac{1}{n} \sum_{k=1}^n v_k$$

$$\text{[b]} \quad v_o = \frac{1}{3} (150 + 200 - 50) = 100 \text{ V}$$


P 3.19 Place  $v_{\Delta}/5$  inside a supernode and use the lower node as a reference. Then

$$\frac{v_1 - 50}{10} + \frac{v_1}{30} + \frac{v_1 - v_{\Delta}/5}{39} + \frac{v_1 - v_{\Delta}/5}{78} = 0$$

$$134v_1 - 6v_{\Delta} = 3900; \quad v_{\Delta} = 50 - v_1$$

$$\text{Solving, } v_1 = 30 \text{ V}; \quad v_{\Delta} = 20 \text{ V}; \quad v_o = 30 - v_{\Delta}/5 = 30 - 4 = 26 \text{ V}$$

P 3.20

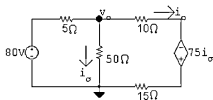

$$\frac{v_o - 80}{5} + \frac{v_o}{50} + \frac{v_o + 75i_o}{25} = 0; \quad i_o = \frac{v_o}{50}$$

$$\text{Solving, } v_o = 50 \text{ V}; \quad i_o = 1 \text{ A}$$

$$i_o = \frac{50 - (-75)(1)}{25} = 5 \text{ A}$$

$$p_{75i_o} = 75i_o i_o = -375 \text{ W}$$

$\therefore$  The dependent voltage source delivers 375 W to the circuit.

$$\text{P 3.21 } -3 + \frac{v_o}{200} + \frac{v_o + 5i_{\Delta}}{10} + \frac{v_o - 80}{20} = 0; \quad i_{\Delta} = \frac{v_o - 80}{20}$$

$$[\text{a}] \text{ Solving, } v_o = 50 \text{ V}$$

$$[\text{b}] i_{ds} = \frac{v_o + 5i_{\Delta}}{10}$$

$$i_{\Delta} = (50 - 80)/20 = -1.5 \text{ A}$$

$$\therefore i_{ds} = 4.25 \text{ A}; \quad 5i_{\Delta} = -7.5 \text{ V}; \quad p_{ds} = (-5i_{\Delta})(i_{ds}) = 31.875 \text{ W}$$

$$[\text{c}] p_{3A} = -3v_o = -3(50) = -150 \text{ W} \quad (\text{del})$$

$$p_{80V} = 80i_{\Delta} = 80(-1.5) = -120 \text{ W} \quad (\text{del})$$

$$\sum p_{\text{del}} = 150 + 120 = 270 \text{ W}$$

CHECK:


$$p_{200\Omega} = 2500/200 = 12.5 \text{ W}$$

$$p_{20\Omega} = (80 - 50)^2 / 20 = 900 / 20 = 45 \text{ W}$$

$$p_{10\Omega} = (4.25)^2 / 10 = 180.625 \text{ W}$$

$$\sum p_{\text{diss}} = 31.875 + 180.625 + 12.5 + 45 = 270 \text{ W}$$

P 3.22 [a]

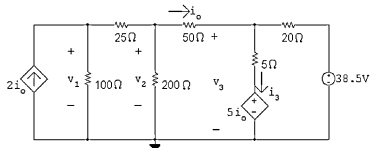

$$i_o = \frac{v_2 - v_3}{50}$$

$$-2i_o + \frac{v_1}{100} + \frac{v_1 - v_2}{25} = 0$$

$$\frac{v_2 - v_1}{25} + \frac{v_2}{200} + \frac{v_2 - v_3}{50}$$

$$\frac{v_3 - v_2}{50} + \frac{v_3 - 5i_o}{5} + \frac{v_3 - 38.5}{20} = 0$$

Solving,  $v_1 = -50 \text{ V}$ ;  $v_2 = -30 \text{ V}$ ;  $v_3 = 2.5 \text{ V}$ 

$$\text{[b]} \quad i_o = \frac{v_2 - v_3}{50} = \frac{-30 - 2.5}{50} = -0.65 \text{ A}$$

$$i_3 = \frac{v_3 - 5i_o}{5} = \frac{2.5 - 5(-0.65)}{5} = 1.15 \text{ A}$$

$$i_g = \frac{38.5 - 2.5}{20} = 1.8 \text{ A}$$

$$\sum p_{\text{dis}} = \sum p_{\text{dev}}$$

Calculate  $\sum p_{\text{dev}}$  because we don't know if the dependent sources are developing or absorbing power. Likewise for the independent source.

$$p_{2i_o} = -2i_o v_1 = -2(-0.65)(-50) = -65 \text{ W(dev)}$$

$$p_{5i_o} = 5i_o i_3 = 5(-0.65)(1.15) = -3.7375 \text{ W(dev)}$$

$$p_g = -38.5(1.8) = -69.30 \text{ W(dev)}$$

$$\sum p_{\text{dev}} = 69.3 + 65 + 3.7375 = 138.0375 \text{ W}$$

$$\begin{aligned}\text{CHECK} \\ \sum p_{\text{dis}} &= \frac{2500}{100} + \frac{900}{200} + \frac{400}{25} + (0.65)^2(50) + (1.15)^2 5 + (1.8)^2(20) \\ &= 138.0375 \text{ W}\end{aligned}$$

$$\therefore \sum p_{\text{dev}} = \sum p_{\text{dis}} = 138.0375 \text{ W}$$

$$\text{P 3.23 [a]} \quad -5 + \frac{v_1}{15} + \frac{v_1 - v_2}{5} = 0$$

$$\frac{v_2 - v_1}{5} + \frac{v_2}{30} + \frac{v_2}{10} + \frac{v_2 + 5i_{\Delta}}{30} = 0$$

$$i_{\Delta} = \frac{v_1 - v_2}{5}$$

$$\text{Solving, } v_1 = 30 \text{ V; } v_2 = 15 \text{ V; } i_{\Delta} = 3 \text{ A; } i_o = \frac{15 + 15}{30} = 1 \text{ A}$$

$$p_{5i_{\Delta}} = (-15)(1) = -15 \text{ W (del)}$$

$$p_{5A} = -5(30) = -150 \text{ W (del)}$$

$$\therefore p_{\text{dev}} = 165 \text{ W}$$

$$[\text{b}] \quad \sum p_{\text{abs}} = \frac{(30)^2}{15} + \frac{(15)^2}{30} + \frac{(15)^2}{10} + (3)^2(5) + (1)^2(30) = 165 \text{ W}$$

$$\therefore \sum p_{\text{dev}} = \sum p_{\text{abs}} = 165 \text{ W}$$

$$\text{P 3.24 } i_{\phi} = \frac{v_3 - v_4}{4} = \frac{235 - 222}{4} = 3.25 \text{ A}$$

$$30i_{\phi} = 30(3.25) = 97.5 \text{ V}$$

$$v_1 + 30i_{\phi} = v_4$$

$$v_1 = v_4 - 30i_{\phi} = 222 - 97.5 = 124.5 \text{ V}$$

$$v_3 + v_{\Delta} = 250$$

$$\therefore v_{\Delta} = 250 - 235 = 15 \text{ V}$$

$$3.2v_{\Delta} = (3.2)(15) = 48 \text{ A}$$

$$i_g = \frac{250 - 124.5}{2} + \frac{250 - 235}{1} = 77.75 \text{ A}$$



$$p_{250V} = -250i_g = -250(77.75) = -19,437.5 \text{ W(del)}$$

$$i_{30i_\phi} - i_\phi + v_4/40 + 48 = 0$$

$$i_{30i_\phi} = i_\phi - 222/40 - 48 = 3.25 - 5.55 - 48 = -50.3 \text{ A}$$

$$p_{30i_\phi} = (30i_\phi)i_{30i_\phi} = (97.5)(-50.3) = -4904.25 \text{ W(dev)}$$

$$p_{3.2v_\Delta} = (3.2v_\Delta)(v_4) = (48)(22) = 10,656 \text{ W(abs)}$$

$$\therefore \sum p_{\text{dev}} = 19,437.5 + 4904.25 = 24,341.75 \text{ W}$$

$$p_{10\Omega} = \frac{v_1^2}{10} = \frac{(124.5)^2}{10} = 1550.025 \text{ W}$$

$$p_{2\Omega} = \frac{(250 - 124.5)^2}{2} = 7875.125 \text{ W}$$

$$p_{1\Omega} = \frac{(250 - 235)^2}{1} = 225 \text{ W}$$

$$p_{20\Omega} = \frac{(235)^2}{20} = 2761.25 \text{ W}$$


$$p_{4\Omega} = (3.25)^2(4) = 42.25 \text{ W}$$

$$p_{40\Omega} = \frac{(222)^2}{40} = 1232.10 \text{ W}$$

$$\therefore \sum p_{\text{diss}} = 10,656 + 1550.025 + 7875.125 + 225 + 2761.250 + 42.25 + 1232.1 = 24,341.75 \text{ W}$$

Thus,  $\sum p_{\text{dev}} = \sum p_{\text{diss}}$ ; Agree with analyst

P 3.25

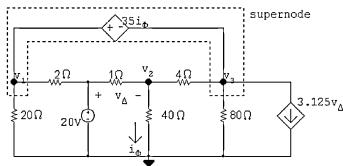

Node equations:

$$\frac{v_1}{20} + \frac{v_1 - 20}{2} + \frac{v_3 - v_2}{4} + \frac{v_3}{80} + 3.125v_\Delta = 0$$

$$\frac{v_2}{40} + \frac{v_2 - v_3}{4} + \frac{v_2 - 20}{1} = 0$$

Constraint equations:

$$v_\Delta = 20 - v_2$$

$$v_1 - 35i_\phi = v_3$$

$$i_\phi = v_2/40$$


Solving,  $v_1 = -20.25$  V;  $v_2 = 10$  V;  $v_3 = -29$  V

Let  $i_g$  be the current delivered by the 20 V source, then

$$i_g = \frac{20 - (20.25)}{2} + \frac{20 - 10}{1} = 30.125 \text{ A}$$

$$p_g (\text{delivered}) = 20(30.125) = 602.5 \text{ W}$$

P 3.26

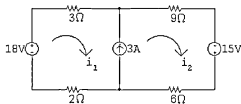

$$-18 + 3i_1 + 9i_2 - 15 + 6i_2 + 2i_1 = 0; \quad i_2 - i_1 = 3$$

Solving,  $i_1 = -0.6$  A;  $i_2 = 2.4$  A

$$p_{18V} = -18i_1 = 10.8 \text{ W (diss)}$$

$$p_{3\Omega} = (-0.6)^2(3) = 1.08 \text{ W}$$

$$p_{2\Omega} = (-0.6)^2(2) = 0.72 \text{ W}$$

$$p_{9\Omega} = (2.4)^2(9) = 51.84 \text{ W}$$

$$p_{6\Omega} = (2.4)^2(6) = 34.56 \text{ W}$$

$$\sum p_{\text{diss}} = 99 \text{ W}$$


$$v_o = 15i_2 - 15 = 36 - 15 = 21 \text{ V}$$

$$p_{3A} = -3v_o = -63 \text{ W (dev)}$$

$$p_{15V} = -15i_2 = -36 \text{ W (dev)}$$

$$\sum p_{\text{dev}} = 99 \text{ W} = \sum p_{\text{diss}}$$

P 3.27

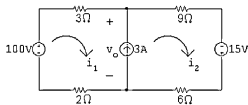

$$-100 + 5i_1 + 15i_2 - 15 = 0$$

$$5i_1 + 15i_2 = 115$$

$$i_2 - i_1 = 3; \quad i_2 = i_1 + 3; \quad 15i_2 = 15i_1 + 45$$

$$\therefore 20i_1 = 70$$

$$i_1 = 3.5 \text{ A}; \quad i_2 = 6.5 \text{ A}$$

$$v_o = 15i_2 - 15 = 97.5 - 15 = 82.5 \text{ V}$$

$$p_{100V} = -100i_1 = -350 \text{ W (dev)}$$

$$p_{3A} = -3v_o = -247.5 \text{ W (dev)}$$

$$p_{15V} = -15i_2 = -97.5 \text{ W (dev)}$$

$$\sum p_{\text{dev}} = \sum p_{\text{dis}} = 695 \text{ W}$$

$$\sum p_{\text{dis}} = (3.5)^2(5) + (6.5)^2(15) = 695 \text{ W}$$

P 3.28 [a] Summing around the supermesh used in the solution to Problem 3.27 gives

$$-(-10) + 5i_1 + 15i_2 - 15 = 0$$

$$i_2 = i_1 + 3$$

$$\therefore i_1 = -2 \text{ A}; \quad i_2 = 1 \text{ A}$$

$$p_{10\text{V}} = 10(-2) = -20 \text{ W (del)}$$

$$v_o = 15i_2 - 15 = 0 \text{ V}$$

$$p_{3\text{A}} = 3v_o = 0 \text{ W}$$

$$p_{15\text{V}} = -15i_2 = -15 \text{ W (del)}$$

$$\sum p_{\text{diss}} = (-2)^2(5) + (1)^2(15) = 35 \text{ W}$$

$$\sum p_{\text{dev}} = 35 \text{ W} = \sum p_{\text{diss}}$$


[b] With 3 A current source replaced with a short circuit

$$i_1 = -2 \text{ A}, \quad i_2 = 1 \text{ A}$$

$$\therefore \sum p_{\text{diss}} = (-2)^2(5) + (1)^2(15) = 35 \text{ W}$$

[c] A 3 A source with zero terminal voltage is equivalent to a short circuit carrying 3 A

P 3.29 [a]

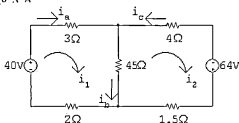

$$40 = 50i_1 - 45i_2$$

$$64 = -45i_1 + 50.5i_2$$

$$\text{Solving, } i_1 = 9.8 \text{ A}; \quad i_2 = 10 \text{ A}$$

$$i_a = i_1 = 9.8 \text{ A}; \quad i_b = i_1 - i_2 = -0.2 \text{ A}; \quad i_c = -i_2 = -10 \text{ A}$$

[b] If the polarity of the 64 V source is reversed, we have


$$40 = 50i_1 - 45i_2$$

$$-64 = -45i_1 + 50.5i_2$$

$$i_1 = -1.72 \text{ A} \quad \text{and} \quad i_2 = -2.8 \text{ A}$$

$$i_a = i_1 = -1.72 \text{ A}; \quad i_b = i_1 - i_2 = 1.08 \text{ A}; \quad i_c = -i_2 = 2.8 \text{ A}$$

P 3.30

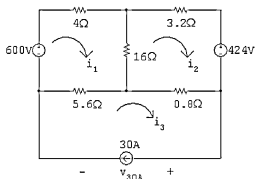

$$600 = 25.6i_1 - 16i_2 - 5.6i_3$$

$$-424 = -16i_1 + 20i_2 - 0.8i_3$$

$$30 = i_3$$

Solving,  $i_1 = 35$  A;  $i_2 = 8$  A;  $i_3 = 30$  A

$$[a] \ v_{30A} = 0.8(i_2 - i_3) + 5.6(i_1 - i_3) = 0.8(8 - 30) + 5.6(35 - 30) = 10.4 \text{ V}$$

$$p_{30A} = 30v_{30A} = 30(10.4) = 312 \text{ W (abs)}$$

Therefore, the 30 A source delivers  $-312$  W.

$$[b] \ p_{600V} = -600(35) = -21,000 \text{ W (del)}$$

$$p_{424V} = 424(8) = 3392 \text{ W (abs)}$$

Therefore, the total power delivered is 21,000 W

$$[c] \ p_{4\Omega} = (35)^2(4) = 4900 \text{ W}$$

$$p_{3.2\Omega} = (8)^2(3.2) = 204.8 \text{ W}$$

$$p_{16\Omega} = (35 - 8)^2(16) = 11,664 \text{ W}$$


$$p_{5.6\Omega} = (35 - 30)^2(5.6) = 140 \text{ W}$$

$$p_{0.8\Omega} = (-30 + 8)^2(0.8) = 387.2 \text{ W}$$

$$\sum p_{\text{resistors}} = 17,296 \text{ W}$$

$$\sum p_{\text{abs}} = 17,296 + 312 + 3392 = 21,000 \text{ W (CHECKS)}$$

P 3.31 [a]

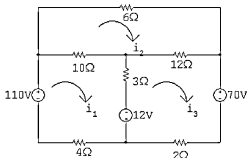

$$110 + 12 = 17i_1 - 10i_2 - 3i_3$$

$$0 = -10i_1 + 28i_2 - 12i_3$$

$$-12 - 70 = -3i_1 - 12i_2 + 17i_3$$

$$\text{Solving, } i_1 = 8 \text{ A; } i_2 = 2 \text{ A; } i_3 = -2 \text{ A}$$

$$p_{110} = -110i_1 = -880 \text{ W (del)}$$

$$p_{12} = -12(i_1 - i_3) = -120 \text{ W (del)}$$

$$p_{70} = 70i_3 = -140 \text{ W (del)}$$

$$\therefore \sum p_{\text{dev}} = 1140 \text{ W}$$

$$\text{[b] } p_{4\Omega} = (8)^2(4) = 256 \text{ W}$$

$$p_{10\Omega} = (6)^2(10) = 360 \text{ W}$$

$$p_{12\Omega} = (-4)^2(12) = 192 \text{ W}$$


$$p_{2\Omega} = (-2)^2(2) = 8 \text{ W}$$

$$p_{6\Omega} = (2)^2(6) = 24 \text{ W}$$

$$p_{3\Omega} = (10)^2(3) = 300 \text{ W}$$

$$\therefore \sum p_{\text{abs}} = 1140 \text{ W}$$

P 3.32 [a]

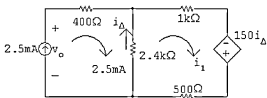

$$2400(i_1 - 0.0025) + 1500i_1 - 150(i_1 - 0.0025) = 0$$

$$\therefore i_1 = 1.5 \text{ mA}$$

$$i_{\Delta} = i_1 - 2.5 = -1.0 \text{ mA}$$

$$[b] v_o = (0.0025)(400) + (0.001)(2400) = 3.4 \text{ V}$$

$$p_{2.5\text{mA}} = -3.4(2.5) = -8.5 \text{ mW}$$


$$\therefore p_{2.5\text{mA}} (\text{deliver}) = 8.5 \text{ mW}$$

$$[c] 150i_{\Delta} = 150(-1.0 \times 10^{-3}) = -0.15 \text{ V}$$

$$p_{\text{dep source}} = 150i_{\Delta}i_1 = (-0.15)(0.0015) = -0.225 \text{ mW}$$

$$p_{\text{dep source}} (\text{absorbed}) = 0.225 \text{ mW}$$

P 3.33

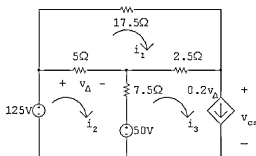

Mesh equations:

$$25i_1 - 5i_2 - 2.5i_3 = 0$$

$$75 = -5i_1 + 12.5i_2 - 7.5i_3$$

Constraint equations:

$$i_3 = 0.2v_{\Delta}$$

$$v_{\Delta} = 5(i_2 - i_1)$$

$$\text{Solving, } i_1 = 3.6 \text{ A; } i_2 = 13.2 \text{ A; } i_3 = 9.6 \text{ A; } v_{\Delta} = 48 \text{ V}$$

$$v_{cs} = 125 - v_{\Delta} - 2.5(i_3 - i_1) = 125 - 48 - 2.5(9.6 - 3.6) = 62 \text{ V}$$

$$p_{vc} = (62)(9.6) = 595.2 \text{ W (abs)}$$

$$p_{50V} = 50(i_2 - i_3) = 50(13.2 - 9.6) = 180 \text{ W (abs)}$$

$$p_{125V} = -125i_2 = -125(13.2) = -1650 \text{ W (del)}$$

Thus, the total power developed is 1650 W.

CHECK:

$$p_{17.5\Omega} = (3.6)^2(17.5) = 226.8 \text{ W}$$


$$p_{5\Omega} = (13.2 - 3.6)^2(5) = 460.8 \text{ W}$$

$$p_{2.5\Omega} = (9.6 - 3.6)^2(2.5) = 90 \text{ W}$$

$$p_{7.5\Omega} = (13.2 - 9.6)^2(7.5) = 97.2 \text{ W}$$

$$\therefore \sum p_{\text{abs}} = 226.8 + 460.8 + 90 + 97.2 + 180 + 595.2 = 1650 \text{ W}$$

P 3.34

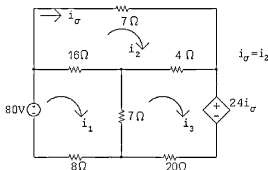

$$-80 + 31i_1 - 16i_2 - 7i_3 = 0$$

$$-16i_1 + 27i_2 - 4i_3 = 0$$


$$-7i_1 - 4i_2 + 31i_3 + 24i_2 = 0$$

Solving,  $i_1 = 3.5 \text{ A}$

$$p_{8\Omega} = (3.5)^2(8) = 98 \text{ W}$$



P 3.35 [a]

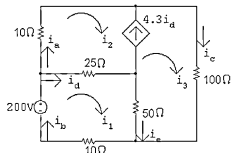

$$200 = 85i_1 - 25i_2 - 50i_3$$

$$0 = -75i_1 + 35i_2 + 150i_3 \quad (\text{super mesh})$$

$$i_3 - i_2 = 4.3(i_1 - i_2)$$

$$\text{Solving, } i_1 = 4.6 \text{ A; } i_2 = 5.7 \text{ A; } i_3 = 0.97 \text{ A}$$

$$i_a = i_2 = 5.7 \text{ A; } i_b = i_1 = 4.6 \text{ A}$$

$$i_c = i_3 = 0.97 \text{ A; } i_d = i_1 - i_2 = -1.1 \text{ A}$$

$$i_e = i_1 - i_3 = 3.63 \text{ A}$$

$$\text{[b] } 10i_2 + v_o + 25(i_2 - i_1) = 0$$

$$\therefore v_o = -57 - 27.5 = -84.5 \text{ V}$$

$$p_{4.3i_d} = -v_o(4.3i_d) = -(-84.5)(4.3)(-1.1) = -399.685 \text{ W(dev)}$$


$$p_{200V} = -200(4.6) = -920 \text{ W(dev)}$$

$$\sum P_{\text{dev}} = 1319.685 \text{ W}$$

$$\begin{aligned} \sum P_{\text{dis}} &= (5.7)^2 10 + (1.1)^2 (25) + (0.97)^2 100 + (4.6)^2 (10) + \\ &\quad (3.63)^2 (50) \\ &= 1319.685 \text{ W} \end{aligned}$$

$$\therefore \sum P_{\text{dev}} = \sum P_{\text{dis}} = 1319.685 \text{ W}$$

P 3.36

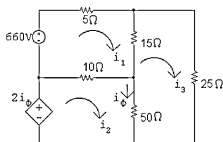

$$660 = 30i_1 - 10i_2 - 15i_3$$

$$20i_\phi = -10i_1 + 60i_2 - 50i_3$$

$$0 = -15i_1 - 50i_2 + 90i_3$$

$$i_\phi = i_2 - i_3$$

$$\text{Solving, } i_1 = 42 \text{ A; } i_2 = 27 \text{ A; } i_3 = 22 \text{ A; } i_\phi = 5 \text{ A}$$

$$20i_\phi = 100 \text{ V}$$

$$p_{20i_\phi} = -100i_2 = -100(27) = -2700 \text{ W}$$

$$\therefore p_{20i_\phi} (\text{developed}) = 2700 \text{ W}$$


CHECK:

$$p_{660\text{V}} = -660(42) = -27,720 \text{ W (dev)}$$

$$\therefore \sum P_{\text{dev}} = 27,720 + 2700 = 30,420 \text{ W}$$

$$\begin{aligned} \sum P_{\text{dis}} &= (42)^2(5) + (22)^2(25) + (20)^2(15) + (5)^2(50) + \\ &\quad (15)^2(10) \\ &= 30,420 \text{ W} \end{aligned}$$

P 3.37

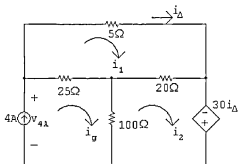

Mesh equations:

$$50i_1 - 20i_2 - 25i_3 = 0$$

$$-20i_1 + 120i_2 - 30i_\Delta - 100i_3 = 0$$

Constraint equations:

$$i_3 = 4; \quad i_\Delta = i_1$$

$$\text{Solving, } i_1 = 4 \text{ A; } i_2 = 5 \text{ A}$$

$$i_{25\Omega} = 4 - i_1 = 0 \text{ A}$$

$$i_{20\Omega} = i_2 - i_1 = 1 \text{ A}$$

$$i_{100\Omega} = 4 - i_2 = -1 \text{ A}$$

$$i_{5\Omega} = i_1 = 4 \text{ A}$$

$$v_{4A} = 100(4 - i_2) = -100 \text{ V}$$

$$p_{4A} = -v_{4A}i_g = -(-100)(4) = 400 \text{ W (abs)}$$

$$v_{30i_\Delta} = 30i_\Delta = 30i_1 = 120 \text{ V}$$

$$p_{30i_\Delta} = -30i_\Delta i_2 = -120(5) = -600 \text{ W}$$

Therefore, the dependent source is developing 600 W, all other elements are absorbing power, and the total power developed is thus 600 W.

CHECK:

$$p_{5\Omega} = 16(5) = 80 \text{ W}$$

$$p_{25\Omega} = 0 \text{ W}$$


$$p_{20\Omega} = 1(20) = 20 \text{ W}$$

$$p_{100\Omega} = 1(100) = 100 \text{ W}$$

$$p_{4A} = 400 \text{ W}$$

$$\sum p_{\text{abs}} = 80 + 0 + 20 + 100 + 400 = 600 \text{ W (CHECKS)}$$

P 3.38 [a]

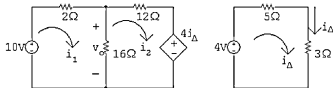

$$10 = 18i_1 - 16i_2$$

$$0 = -16i_1 + 28i_2 + 4i_\Delta$$

$$4 = 8i_\Delta$$


$$\text{Solving, } i_1 = 1 \text{ A; } i_2 = 0.5 \text{ A; } i_\Delta = 0.5 \text{ A}$$

$$v_0 = 16(i_1 - i_2) = 16(0.5) = 8 \text{ V}$$

$$[b] \quad p_{4i_{\Delta}} = 4i_{\Delta}i_2 = (4)(0.5)(0.5) = 1 \text{ W (abs)}$$

$$\therefore p_{4i_{\Delta}} (\text{deliver}) = -1 \text{ W}$$

P 3.39

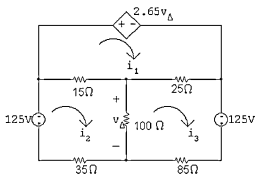

Mesh equations:

$$2.65v_{\Delta} + 40i_1 - 15i_2 - 25i_3 = 0$$

$$-15i_1 + 150i_2 - 100i_3 = -125$$

$$-25i_1 - 100i_2 - 210i_3 = 125$$

Constraint equations:

$$v_{\Delta} = 100(i_2 - i_3)$$

$$\text{Solving, } i_1 = 7 \text{ A; } \quad i_2 = 1.2 \text{ A; } \quad i_3 = 2 \text{ A}$$

$$v_{\Delta} = 100(i_2 - i_3) = 100(1.2 - 2) = -80 \text{ V}$$

$$p_{2.65v_{\Delta}} = 2.65v_{\Delta}i_1 = -1484 \text{ W}$$

Therefore, the dependent source is developing 1484 W.

CHECK:

$$p_{125V} = 125i_2 = 150 \text{ W (left source)}$$

$$p_{125V} = -125i_3 = -250 \text{ W (right source)}$$

$$\sum p_{\text{dev}} = 1484 + 250 = 1734 \text{ W}$$

$$p_{35\Omega} = (1.2)^2(35) = 50.4 \text{ W}$$

$$p_{85\Omega} = (2)^2(85) = 340 \text{ W}$$


$$p_{15\Omega} = (7 - 1.2)^2(15) = 504.6 \text{ W}$$

$$p_{25\Omega} = (7 - 2)^2(25) = 625 \text{ W}$$

$$p_{100\Omega} = (1.2 - 2)^2(100) = 64 \text{ W}$$

$$\sum p_{\text{diss}} = 50.4 + 340 + 504.6 + 625 + 64 + 150 = 1734 \text{ W}$$

P 3.40 [a]

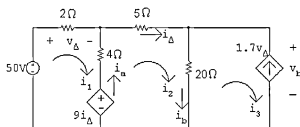

Mesh equations:

$$-50 + 6i_1 - 4i_2 + 9i_\Delta = 0$$

$$-9i_\Delta - 4i_1 + 29i_2 - 20i_3 = 0$$

Constraint equations:

$$i_\Delta = i_2; \quad i_3 = -1.7v_\Delta; \quad v_\Delta = 2i_1$$

$$\text{Solving, } i_1 = -5 \text{ A; } i_2 = 16 \text{ A; } i_3 = 17 \text{ A; } v_\Delta = -10 \text{ V}$$

$$9i_\Delta = 9(16) = 144 \text{ V}$$

$$i_a = i_2 - i_1 = 21 \text{ A}$$

$$i_b = i_2 - i_3 = -1 \text{ A}$$

$$v_b = 20i_b = -20 \text{ V}$$

$$p_{50\text{V}} = -50i_1 = 250 \text{ W (absorbing)}$$


$$p_{9i_\Delta} = -i_a(9i_\Delta) = -(21)(144) = -3024 \text{ W (delivering)}$$

$$p_{1.7\text{V}} = -1.7v_\Delta v_b = i_3 v_b = (17)(-20) = -340 \text{ W (delivering)}$$

[b]  $\sum P_{\text{dev}} = 3024 + 340 = 3364 \text{ W}$

$$\sum P_{\text{dis}} = 250 + (-5)^2(2) + (21)^2(4) + (16)^2(5) + (-1)^2(20) = 3364 \text{ W}$$

P 3.41 [a]

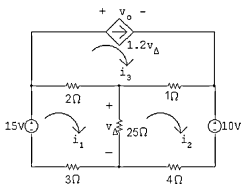

Mesh equations:

$$15 = 30i_1 - 25i_2 - 2i_3$$

$$-10 = -25i_1 + 30i_2 - i_3$$

Constraint equations:

$$i_3 = 1.2v_\Delta; \quad v_\Delta = 25(i_1 - i_2)$$

$$\text{Solving, } i_1 = 10 \text{ A}; \quad i_2 = 9 \text{ A}; \quad i_3 = 30 \text{ A}; \quad v_\Delta = 25 \text{ V}$$

$$i_{2\Omega} = i_1 - i_3 = 9 - 30 = -20 \text{ A}$$

$$p_{2\Omega} = (-20)^2(2) = 800 \text{ W}$$

$$[b] \quad p_{15V} = -15(10) = -150 \text{ W (dev)}$$

$$p_{10V} = 10i_2 = 10(9) = 90 \text{ W (abs)}$$


$$v_o = (i_1 - i_3)2 + (i_2 - i_3)1 = -40 - 21 = -61 \text{ V}$$

$$p_{1.2v_\Delta} = i_3 v_o = (30)(-61) = -1830 \text{ W (dev)}$$

$$\sum P_{\text{dev}} = 1830 + 150 = 1980 \text{ W}$$

$$\% \text{ delivered to } 2\Omega = \frac{800}{1980} \times 100 = 40.4\%$$

P 3.42 [a]

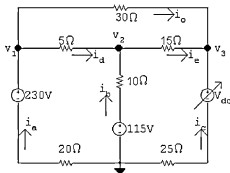

If  $i_o = 0$  then  $v_1 = v_3$ ; therefore,

$$\frac{v_1 - v_2}{5} + \frac{v_1 - 230}{20} = 0$$

$$\frac{v_2 - v_1}{5} + \frac{v_2 - v_3}{15} + \frac{v_2 - 115}{10} = 0$$

Solving,  $v_1 = 170 \text{ V} = v_3$ ;  $v_2 = 155 \text{ V}$

$$\therefore \frac{170 - 155}{15} + \frac{170 - v_{dc}}{25} = 0$$

Solving,  $v_{dc} = 195 \text{ V}$

$$[\text{b}] \quad i_a = \frac{230 - 170}{20} = 3 \text{ A}$$

$$i_b = \frac{115 - 155}{10} = -4 \text{ A}$$

$$i_c = \frac{195 - 170}{25} = 1 \text{ A}$$

$$i_d = \frac{170 - 155}{5} = 3 \text{ A}$$

$$i_e = \frac{155 - 170}{15} = -1 \text{ A}$$

$$p_{230\text{V}} = -230i_a = -690 \text{ W (dev)}$$

$$p_{115\text{V}} = -115i_b = 460 \text{ W (abs)}$$

$$p_{v_{dc}} = -v_{dc}i_c = -195 \text{ W (dev)}$$

$$p_{20\Omega} = i_a^2(20) = 180 \text{ W}$$

$$p_{5\Omega} = i_d^2(5) = 45 \text{ W}$$

$$p_{10\Omega} = i_b^2(10) = 160 \text{ W}$$


$$p_{15\Omega} = i_e^2(15) = 15 \text{ W}$$

$$p_{25\Omega} = i_c^2(25) = 25 \text{ W}$$

$$\sum p_{\text{diss}} = 460 + 180 + 45 + 160 + 15 + 25 = 885 \text{ W}$$

$$\sum p_{\text{dev}} = 690 + 195 = 885 \text{ W (CHECKS)}$$

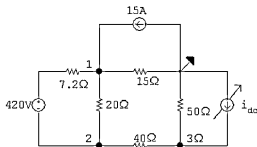P 3.43 Choose the reference node so that a node voltage is identical to the voltage across the 15 A source; thus:



Since the 15 A source is developing 3750 W,  $v_1$  must be 250 V.

Since  $v_1$  is known, we can sum the currents away from node 1 to find  $v_2$ ; thus:

$$\frac{250 - (420 + v_2)}{7.2} + \frac{250 - v_2}{20} + \frac{250}{15} - 15 = 0$$

$$\therefore v_2 = -50 \text{ V}$$

Now that we know  $v_2$  we sum the currents away from node 2 to find  $v_3$ ; thus:

$$\frac{v_2 + 420 - 250}{7.2} + \frac{v_2 - 250}{20} + \frac{v_2 - v_3}{40} = 0$$


$$\therefore v_3 = 50/3 \text{ V}$$

Now that we know  $v_3$  we sum the currents away from node 3 to find  $i_{dc}$ ; thus:

$$\frac{v_3}{50} + \frac{v_3 + 50}{40} = i_{dc}$$

$$\therefore i_{dc} = 2 \text{ A}$$

P 3.44 [a]

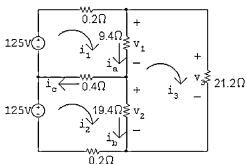

$$125 = 10i_1 - 0.4i_2 - 9.4i_3$$



$$125 = -0.4i_1 + 20i_2 - 19.4i_3$$

$$0 = -9.4i_1 - 19.4i_2 + 50i_3$$

$$\text{Solving, } i_1 = 23.93 \text{ A; } i_2 = 17.79 \text{ A; } i_3 = 11.40 \text{ A}$$

$$v_1 = 9.4(i_1 - i_3) = 117.76 \text{ V}$$

$$v_2 = 19.4(i_2 - i_3) = 123.90 \text{ V}$$

$$v_3 = 21.2i_3 = 241.66 \text{ V}$$

$$[b] P_{R1} = (i_1 - i_3)^2(9.4) = 1475.22 \text{ W}$$

$$P_{R2} = (i_2 - i_3)^2(19.4) = 791.29 \text{ W}$$


$$P_{R3} = i_3^2(21.2) = 2754.64 \text{ W}$$

$$[c] \sum p_{\text{dev}} = 125(i_1 + i_2) = 5213.99 \text{ W}$$

$$\sum p_{\text{load}} = 5021.15 \text{ W}$$

$$\% \text{ delivered} = \frac{5021.15}{5213.99} \times 100 = 96.3\%$$

[d]

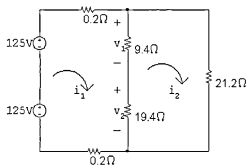

$$250 = 29.2i_1 - 28.8i_2$$

$$0 = -28.8i_1 + 50i_2$$

$$\text{Solving, } i_1 = 19.82 \text{ A; } i_2 = 11.42 \text{ A}$$


$$i_1 - i_2 = 8.41 \text{ A}$$

$$v_1 = (8.41)(9.4) = 79.01 \text{ V}$$

$$v_2 = 8.41(19.4) = 163.06 \text{ V}$$

Note  $v_1$  is low and  $v_2$  is high. Therefore, loads designed for 125 V would not function properly, and could be damaged.

P 3.45

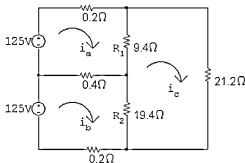

$$125 = (R_1 + 0.6)i_a - 0.4i_b - R_1i_c$$

$$125 = -0.4i_a + (R_2 + 0.6)i_b - R_2i_c$$

$$0 = -R_1i_a - R_2i_b + (R_1 + R_2 + 21.2)i_c$$

$$\Delta = \begin{vmatrix} (R_1 + 0.6) & -0.4 & -R_1 \\ -0.4 & (R_2 + 0.6) & -R_2 \\ -R_1 & -R_2 & (R_1 + R_2 + 21.2) \end{vmatrix}$$

When  $R_1 = R_2$ ,  $\Delta$  reduces to

$$\Delta = 21.6R_1^2 + 25.84R_1 + 4.24.$$

$$\begin{aligned} N_a &= \begin{vmatrix} 125 & -0.4 & -R_1 \\ 125 & (R_2 + 0.6) & -R_2 \\ 0 & -R_2 & (R_1 + R_2 + 21.2) \end{vmatrix} \\ &= 125[2R_1R_2 + R_1 + 22.2R_2 + 21.2] \end{aligned}$$

$$\begin{aligned} N_b &= \begin{vmatrix} (R_1 + 0.6) & 125 & -R_1 \\ -0.4 & 125 & -R_2 \\ -R_1 & 0 & (R_1 + R_2 + 21.2) \end{vmatrix} \\ &= 125[2R_1R_2 + 22.2R_1 + R_2 + 21.2] \end{aligned}$$


$$i_a = \frac{N_a}{\Delta}, \quad i_b = \frac{N_b}{\Delta}$$

$$i_{\text{neutral}} = i_a - i_b = \frac{N_a - N_b}{\Delta} = \frac{125[(R_1 - R_2) + 22.2(R_2 - R_1)]}{\Delta}$$

Now note that when  $R_1 = R_2$ ,  $i_{\text{neutral}}$  reduces to

$$i_{\text{neutral}} = \frac{0}{\Delta} = 0$$

P 3.46 [a]

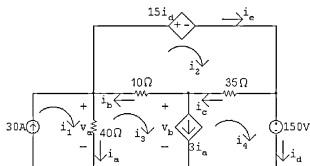

$$40(i_3 - i_1) + 10(i_3 - i_2) + 35(i_4 - i_2) + 150 = 0$$

$$35(i_2 - i_4) + 10(i_2 - i_3) + 15i_d = 0$$

$$i_d = i_4; \quad i_1 = 30 \text{ A}$$

$$\text{Solving, } i_1 = 30 \text{ A; } i_2 = 8 \text{ A; } i_3 = 24 \text{ A; } i_4 = 6 \text{ A}$$

$$i_a = 30 - 24 = 6 \text{ A; } i_b = 8 - 24 = -16 \text{ A; } i_c = 8 - 6 = 2 \text{ A;}$$

$$i_d = 6 \text{ A; } i_e = i_c + i_d = 6 + 2 = 8 \text{ A}$$

$$\text{[b] } v_a = 40i_a = 240 \text{ V; } v_b = 150 - 35i_c = 80 \text{ V}$$

$$p_{30\text{A}} = -30v_a = -30(240) = -7200 \text{ W (gen)}$$

$$p_{15i_d} = 15i_d i_e = 15(6)(8) = 720 \text{ W (diss)}$$

$$p_{3i_a} = 3i_a v_b = 3(6)(80) = 1440 \text{ W (diss)}$$

$$p_{150\text{V}} = 150i_d = 150(6) = 900 \text{ W (diss)}$$

$$p_{40\Omega} = (6)^2(40) = 1440 \text{ W (diss)}$$

$$p_{10\Omega} = (-16)^2(10) = 2560 \text{ W (diss)}$$

$$p_{35\Omega} = (2)^2(35) = 140 \text{ W (diss)}$$

$$\sum P_{\text{gen}} = 7200 \text{ W}$$

$$\sum P_{\text{diss}} = 720 + 1440 + 900 + 1440 + 2560 + 140 = 7200 \text{ W}$$


P 3.47 [a] The node voltage method requires summing the currents at two supernodes in terms of four node voltages and using two constraint equations to reduce the system of equations to two unknowns. If the connection at the bottom of the circuit is used as the reference node, then the voltages controlling the dependent sources are node voltages. This makes it easy to formulate the constraint equations. The current in

the 20 V source is obtained by summing the currents at either terminal of the source.

The mesh current method requires summing the voltages around the two meshes not containing current sources in terms of four mesh currents. In addition the voltages controlling the dependent sources must be expressed in terms of the mesh currents. Thus the constraint equations are more complicated, and the reduction to two equations and two unknowns involves more algebraic manipulation. The current in the 20 V source is found by subtracting two mesh currents.

Because the constraint equations are easier to formulate in the node voltage method, it is the preferred approach.

[b]

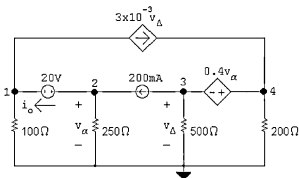

Node voltage equations:

$$\frac{v_1}{100} + \frac{v_2}{250} - 0.2 + 3 \times 10^{-3} v_3 = 0$$

$$\frac{v_3}{500} + \frac{v_4}{200} - 3 \times 10^{-3} v_3 + 0.2 = 0$$

Constraints:

$$v_2 - v_1 = 20; \quad v_4 - v_3 = 0.4v_\Delta; \quad v_\Delta = v_2$$


Solving,  $v_2 = 44$  V

$$i_o = 0.2 - 44/250 = 24 \text{ mA}$$

$$p_{20V} = 20i_o = 480 \text{ mW (abs)}$$

P 3.48 [a] There are three unknown node voltages and only two unknown mesh currents. Use the mesh current method to minimize the number of simultaneous equations.

[b]

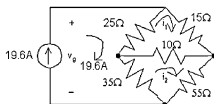

$$25(i_1 - 19.6) + 15i_1 + 10(i_1 - i_2) = 0$$

$$35(i_2 - 19.6) + 10(i_2 - i_1) + 55i_2 = 0$$

$$\text{Solving, } i_1 = 11.4 \text{ A; } i_2 = 8 \text{ A}$$

$$i_{10\Omega} = i_1 - i_2 = 3.4 \text{ A}$$

$$p_{10\Omega} = (3.4)^2(10) = 115.6 \text{ W}$$


[c] No, the voltage across the 19.6 A current source is readily available from the mesh currents, and solving two simultaneous mesh-current equations is less work than solving three node voltage equations.

[d]  $v_g = (19.6 - 11.4)(25) + (19.6 - 8)(35) = 611 \text{ V}$

$$p_{19.6\text{A}} (\text{developed}) = 19.6(611) = 11,975.6 \text{ W}$$

P 3.49 [a] There are three unknown node voltages and three unknown mesh currents, so the number of simultaneous equations required are the same for both methods. The node voltage method has the advantage of having to solve the three simultaneous equations for one unknown voltage provided the connection at either the top or bottom of the circuit is used as the reference node. Therefore recommend the node voltage method.

[b]

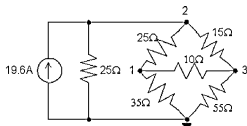

$$\frac{v_1}{35} + \frac{v_1 - v_2}{25} + \frac{v_1 - v_3}{10} = 0$$

$$\frac{v_2}{25} - 19.6 + \frac{v_2 - v_1}{25} + \frac{v_2 - v_3}{15} = 0$$


$$\frac{v_3 - v_1}{10} + \frac{v_3 - v_2}{15} + \frac{v_3}{55} = 0$$

$$\text{Solving, } v_2 = 271.9255 \text{ V}$$


$$p_{19.6\text{A}} = -(19.6)(271.9255) = -5329.74 \text{ W (dev)}$$

$\therefore$  The 19.6 A source is developing 5329.74 W
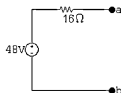
$$\text{P 3.50 } v_{\text{Th}} = \frac{60}{50}(40) = 48 \text{ V} \quad R_{\text{Th}} = 8 + \frac{(40)(10)}{50} = 16 \Omega$$



P 3.51 [a] Open circuit:

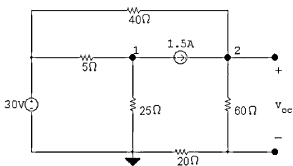


$$\frac{v_2}{80} + \frac{v_2 - 30}{40} - 1.5 = 0$$

$$\therefore v_2 = 60 \text{ V}$$

$$v_{\text{oc}} = \frac{60}{80}v_2 = 45 \text{ V} = v_{\text{Th}}$$


Short circuit:

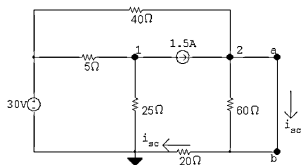


$$\frac{v_2 - 30}{40} - 1.5 + \frac{v_2}{20} = 0$$

$$\therefore v_2 = 30 \text{ V}$$

$$i_{sc} = \frac{v_2}{20} = 1.5 \text{ A}$$

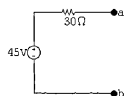
Therefore,  $R_{Th} = 45/1.5 = 30 \Omega$ 

[b]

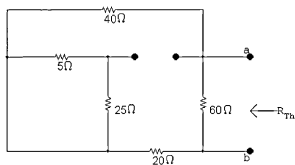

$$R_{Th} = 60 \parallel (40 + 20) = 30 \Omega \text{ (CHECKS)}$$

P 3.52

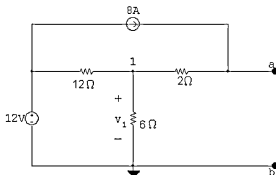


$$\frac{v_1 - 12}{12} + \frac{v_1}{6} - 8 = 0$$


$$v_1 = 36 \text{ V}$$

$$v_{Th} = v_1 + (2)(8) = 52 \text{ V}$$
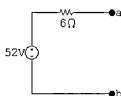
$$R_{Th} = 2 + \frac{(12)(6)}{18} = 6 \Omega$$



P 3.53

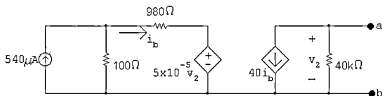

OPEN CIRCUIT

$$v_2 = -40i_b \quad 40 \times 10^3 = -16 \times 10^5 i_b$$

$$5 \times 10^{-5} v_2 = -80i_b$$

$$980i_b + 5 \times 10^{-5} v_2 = 900i_b$$

$$100(540 \times 10^{-6}) = 54 \text{ mV}$$



$$\therefore i_b = \frac{54 \times 10^{-3}}{1000} = 54 \mu\text{A}$$

$$v_{\text{Th}} = -16 \times 10^5 (54 \times 10^{-6}) = -86.40 \text{ V}$$


SHORT CIRCUIT

$$v_2 = 0; \quad i_{\text{sc}} = -40i_b$$


$$i_b = \frac{54 \times 10^{-3}}{1080} = \frac{54}{1.08} \times 10^{-6} = 50 \mu\text{A}$$

$$i_{\text{sc}} = -40(50) = -2000 \mu\text{A} = -2 \text{ mA}$$
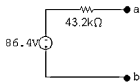
$$R_{\text{Th}} = \frac{-86.4}{-2} \times 10^3 = 43.2 \text{ k}\Omega$$



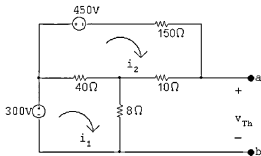P 3.54 After making a source transformation the circuit becomes




$$300 = 48i_1 - 40i_2$$

$$-450 = -40i_1 + 200i_2$$


$$\therefore i_1 = 5.25 \text{ A and } i_2 = -1.2 \text{ A}$$

$$v_{\text{Th}} = 8i_1 + 10i_2 = 30 \text{ V}$$

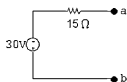
$$R_{Th} = (40 \parallel 8 + 10) \parallel 50 = 15 \Omega$$



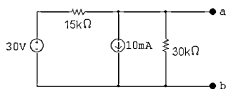
P 3.55 First we make the observation that the 8-mA current source and the 20 kΩ resistor will have no influence on the behavior of the circuit with respect to the terminals a,b. This follows because they are in parallel with an ideal voltage source. Hence our circuit can be simplified to




or

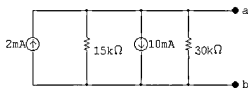

Therefore the Norton equivalent is

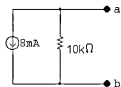

P 3.56 Open circuit voltage:

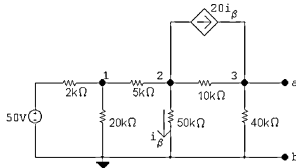


$$\frac{v_1 - 50}{2} + \frac{v_1}{20} + \frac{v_1 - v_2}{5} = 0$$

$$\frac{v_2 - v_1}{5} + \frac{v_2}{50} + \frac{v_2 - v_3}{10} + 20 \frac{v_2}{50} = 0$$

$$\frac{v_3}{40} + \frac{v_3 - v_2}{10} - 20 \frac{v_2}{50} = 0$$

Solving,  $v_3 = 100 \text{ V} = v_{Th}$

Short circuit current:

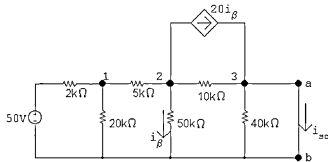


$$\frac{v_1}{20} + \frac{v_1 - 50}{2} + \frac{v_1 - v_2}{5} = 0$$

$$\frac{v_2 - v_1}{5} + \frac{v_2}{50} + \frac{v_2}{10} + 20 \frac{v_2}{50} = 0$$


Solving,  $v_1 = 36 \text{ V}$ ;  $v_2 = 10 \text{ V}$

$$i_{sc} = \frac{20(10)}{50,000} + \frac{10}{10,000} = 0.004 + 0.001 = 5 \text{ mA}$$
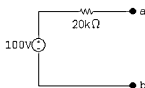
$$\therefore R_{Th} = \frac{v_{Th}}{i_{sc}} = 100/0.005 = 20 \text{ k}\Omega$$




P 3.57

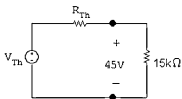

$$i_1 = 45/15,000 = 3 \text{ mA}$$
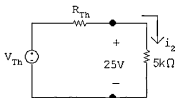
$$45 = v_{Th} - 0.003R_{Th}, \quad v_{Th} = 45 + 0.003R_{Th}$$




$$i_2 = 25/5000 = 5 \text{ mA}$$


$$25 = v_{Th} - 0.005R_{Th}, \quad v_{Th} = 25 + 0.005R_{Th}$$

$$\therefore 45 + 0.003R_{Th} = 25 + 0.005R_{Th} \quad \text{so} \quad R_{Th} = 10 \text{ k}\Omega$$

$$v_{Th} = 45 + 30 = 75 \text{ V}$$

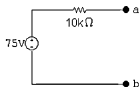

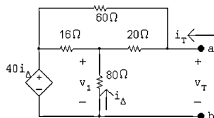P 3.58  $V_{Th} = 0$ , since circuit contains no independent sources.



$$i_T = \frac{v_T - v_1}{20} + \frac{v_T - 40i_\Delta}{60}$$

$$\frac{v_1 - 40i_\Delta}{16} + \frac{v_1}{80} + \frac{v_1 - v_T}{20} = 0$$


$$\therefore 10v_1 - 200i_\Delta = 4v_T \quad i_\Delta = \frac{-v_1}{80}, \quad 200i_\Delta = -2.5v_1$$

$$\therefore 12.5v_1 = 4v_T; \quad v_1 = 0.32v_T$$


$$60i_T = 4v_T - 2.5v_1 = 3.2v_T$$

$$\therefore \frac{v_T}{i_T} = \frac{60}{3.2} = 18.75 \Omega$$

$$R_{Th} = 18.75 \Omega$$

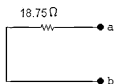

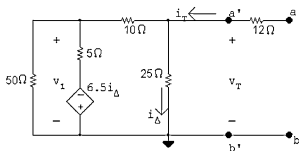P 3.59  $V_{Th} = 0$  since there are no independent sources in the circuit. To find  $R_{Th}$  we first find  $R_{a'b'}$ .



$$i_T = \frac{v_T}{25} + \frac{v_T - v_1}{10}$$

$$\frac{v_1}{50} + \frac{v_1 + 6.5i_\Delta}{5} + \frac{v_1 - v_T}{10} = 0 \text{ so } 16v_1 + 65i_\Delta = 5v_T$$

$$i_\Delta = \frac{v_T}{25}, \quad 65i_\Delta = 2.6v_T$$


$$16v_1 + 2.6v_T = 5v_T$$

$$\therefore v_1 = 0.15v_T$$

$$i_T = \frac{v_T}{25} + \frac{v_T - 0.15v_T}{10} = \frac{6.25}{50} v_T$$

$$\frac{v_T}{i_T} = 50/6.25 = 8 \Omega = R_{a'b'}$$
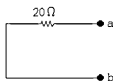
$$\therefore R_{Th} = 12 + 8 = 20 \Omega$$



P 3.60 [a] Since  $0 \leq R_o \leq \infty$  maximum power will be delivered to the  $6 \Omega$  resistor when  $R_o = 0$ .


$$[b] P = \frac{30^2}{6} = 150 \text{ W}$$

P 3.61 [a] From the solution of Problem 3.56 we have  $R_{Th} = 20 \text{ k}\Omega$  and  $v_{Th} = 100 \text{ V}$ .  
Therefore

$$R_o = R_{Th} = 20 \text{ k}\Omega$$

$$\text{[b]} \quad p = \frac{(50)^2}{20,000} = 125 \text{ mW}$$

[c]

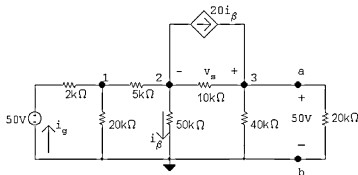

$$\frac{v_1}{20,000} + \frac{v_1 - 50}{2000} + \frac{v_1 - v_2}{5000} = 0$$

$$\frac{v_2}{50,000} + \frac{v_2 - v_1}{5000} + \frac{v_2 - 50}{10,000} + 20 \left( \frac{v_2}{50,000} \right) = 0$$

$$\text{Solving, } v_1 = 38 \text{ V; } v_2 = 17.5 \text{ V}$$

$$i_g = \frac{50 - 38}{2000} = 6 \text{ mA}$$

$$p_{50V} (\text{delivered}) = (50)(0.006) = 300 \text{ mW}$$

$$v_2 + v_s = 50 \text{ V}$$

$$v_s = 50 - (17.5) = 32.5 \text{ V}$$

$$i_\beta = \frac{v_2}{50,000} = 0.35 \text{ mA}$$

$$20i_\beta = 7 \text{ mA}$$

$$p_{20i_\beta} (\text{delivered}) = (32.5)(0.007) = 227.5 \text{ mW}$$


$$\sum p_{\text{dev}} = 300 + 227.5 = 527.5 \text{ mW}$$

$$\% \text{ delivered} = \frac{125}{527.5} \times 100 = 23.7\%$$

P 3.62 [a] From the solution to Problem 2.25 we have


$R_o(\Omega)$	$P_o(\text{W})$	$R_o(\Omega)$	$P_o(\text{W})$
0	0	20	320.00
2	200.00	30	270.00
6	337.50	40	230.40
10	360.00	50	200.00
15	345.60	70	157.50

[b]

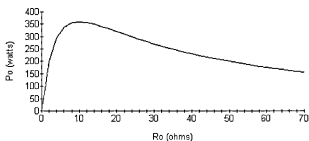

[c]  $R_o = 10 \Omega$ ,  $P_o(\text{max}) = 360 \text{ W}$

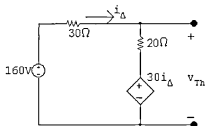P 3.63 We begin by finding the Thévenin equivalent with respect to  $R_o$ . After making a couple of source transformations the circuit simplifies to




$$i_{\Delta} = \frac{160 - 30i_{\Delta}}{50}; \quad i_{\Delta} = 2 \text{ A}$$

$$v_{\text{Th}} = 20i_{\Delta} + 30i_{\Delta} = 50i_{\Delta} = 100 \text{ V}$$

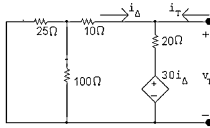Using the test-source method to find the Thévenin resistance gives






$$i_T = \frac{v_T}{30} + \frac{v_T - 30(-v_T/30)}{20}$$

$$\frac{i_T}{v_T} = \frac{1}{30} + \frac{1}{10} = \frac{4}{30} = \frac{2}{15}$$

$$R_{Th} = \frac{v_T}{i_T} = \frac{15}{2} = 7.5 \Omega$$

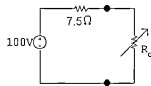Thus our problem is reduced to analyzing the circuit shown below.



$$p = \left( \frac{100}{7.5 + R_o} \right)^2 R_o = 250$$

$$\frac{10^4}{R_o^2 + 15R_o + 56.25} R_o = 250$$

$$\frac{10^4 R_o}{250} = R_o^2 + 15R_o + 56.25$$

$$40R_o = R_o^2 + 15R_o + 56.25$$


$$R_o^2 - 25R_o + 56.25 = 0$$

$$R_o = 12.5 \pm \sqrt{156.25 - 56.25} = 12.5 \pm 10$$

$$R_o = 22.5 \Omega$$


$$R_o = 2.5 \Omega$$

P 3.64 [a]

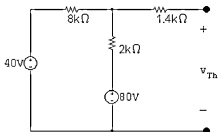

$$\frac{v_{Th} - 40}{8000} + \frac{v_{Th} - 80}{2000} = 0$$


$$\therefore v_{Th} = 72 \text{ V}$$

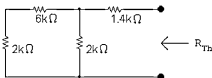

$$R_{Th} = 1400 + (2000)(8000)/1000 = 3 \text{ k}\Omega$$


$$R_o = R_{Th} = 3 \text{ k}\Omega$$

[b]

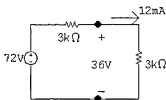

$$p_{\max} = \frac{(36)^2}{3} \times 10^{-3} = 432 \text{ mW}$$

P 3.65

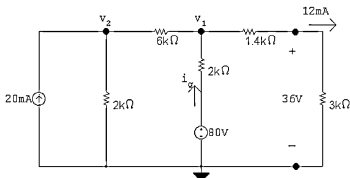

$$v_1 = (12 \times 10^{-3})(1.4 + 3) \times 10^3 = 12(4.4) = 52.8 \text{ V}$$

$$i_g = \frac{80 - 52.8}{2000} = 13.6 \text{ mA}$$

$$p_{80\text{V}} (\text{dev}) = (80)(0.0136) = 1088 \text{ mW}$$

$$-0.02 + \frac{v_2}{2000} + \frac{v_2 - 52.8}{6000} = 0$$

$$\therefore v_2 = 43.2 \text{ V}$$


$$p_{20\text{mA}} (\text{dev}) = (0.02)(43.2) = 864 \text{ mW}$$

$$\sum p_{\text{dev}} = 1088 + 864 = 1952 \text{ mW}$$

$$\% \text{ delivered to } R_o = \frac{432}{1952} \times 100 = 22.13\%$$

P 3.66 [a] We begin by finding the Thévenin equivalent with respect to the terminals of  $R_o$ .

Open circuit voltage

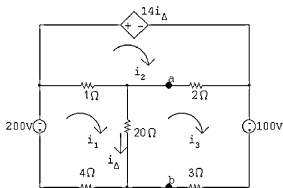

$$-200 = 25i_1 - 1i_2 - 20i_3$$

$$0 = -i_1 + 3i_2 - 2i_3 + 14i_\Delta$$


$$100 = -20i_1 - 2i_2 + 25i_3$$

$$i_\Delta = i_1 - i_3$$

$$\text{Solving, } i_1 = -2.5 \text{ A; } i_2 = 37.5 \text{ A; } i_3 = 5 \text{ A; } i_\Delta = -7.5 \text{ A}$$

$$v_{Th} = 20(i_1 - i_3) = 20(-7.5) = -150 \text{ V}$$

Now find the short-circuit current.

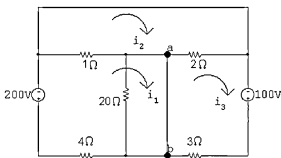

Note with the short circuit from *a* to *b* that  $i_\Delta$  is zero, hence  $14i_\Delta$  is also zero.

$$-200 = 5i_1 - 1i_2 + 0i_3$$


$$0 = -1i_1 + 3i_2 - 2i_3$$

$$100 = 0i_1 - 2i_2 + 5i_3$$

$$\text{Solving, } i_1 = -40 \text{ A; } i_2 = 0 \text{ A; } i_3 = 20 \text{ A}$$

$$i_{sc} = i_1 - i_3 = -60 \text{ A}$$


$$R_{Th} = (-150)/(-60) = 2.5 \Omega$$

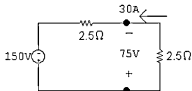

For maximum power transfer  $R_o = R_{Th} = 2.5 \Omega$

$$[b] \quad p_{max} = \frac{75^2}{2.5} = 2250 \text{ W}$$

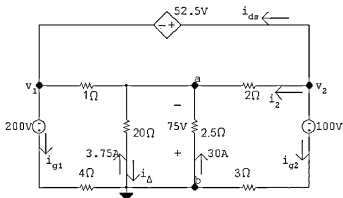P 3.67 From the solution of Problem 3.66 we know that when  $R_o$  is  $2.5\ \Omega$ , the voltage across  $R_o$  is  $75\text{ V}$ , positive at the lower terminal. Therefore our problem reduces to the analysis of the following circuit. In constructing the circuit we have used the fact that  $i_\Delta$  is  $-3.75\text{ A}$ , and hence  $14i_\Delta$  is  $-52.5\text{ V}$ .



Using the node Voltage method to find  $v_1$  and  $v_2$  yields

$$-33.75 + \frac{-75 - v_1}{1} + \frac{-75 - v_2}{2} = 0$$

$$v_1 + 52.5 = v_2$$

Solving,  $v_1 = -115\text{ V}$ ;  $v_2 = -62.5\text{ V}$ . It follows that

$$i_{g1} = \frac{-115 + 200}{4} = 21.25\text{ A}$$

$$i_{g2} = \frac{-62.5 + 100}{3} = 12.5\text{ A}$$

$$i_2 = \frac{-62.5 + 75}{2} = 6.25\text{ A}$$

$$i_{ds} = -6.25 - 12.5 = -18.75\text{ A}$$

$$p_{200V} = -200i_{g1} = -4250\text{ W(dev)}$$

$$p_{100V} = -100i_{g2} = -1250\text{ W(dev)}$$


$$p_{ds} = 52.5i_{ds} = -984.375\text{ W(dev)}$$

$$\therefore \sum p_{dev} = 4250 + 1250 + 984.375 = 6484.375\text{ W}$$

$$\therefore \% \text{ delivered} = \frac{2250}{6484.375}(100) = 34.7\%$$

$\therefore$  34.7% of developed power is delivered to load

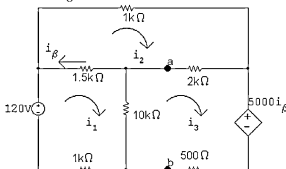- P 3.68 [a] Find the Thévenin equivalent with respect to the terminals of  $R_L$ .  
Open circuit voltage:



$$120 = 12,500i_1 - 1500i_2 - 10,000i_3$$

$$0 = -1500i_1 + 4500i_2 - 2000i_3$$

$$0 = -10,000i_1 - 2000i_2 + 12,500i_3 + 5000i_\beta$$


$$i_\beta = i_2 - i_1$$

Solving,

$$i_1 = 99.6 \text{ mA}; \quad i_2 = 78 \text{ mA}; \quad i_3 = 100.8 \text{ mA}; \quad i_\beta = -21.6 \text{ mA}$$

$$v_{\text{Th}} = v_{ab} = 10 \times 10^3(i_1 - i_3) = -12 \text{ V}$$

Short-circuit current:

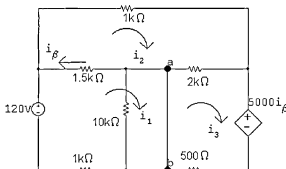

$$120 = 2500i_1 - 1500i_2 + 0i_3$$

$$0 = -1500i_1 + 4500i_2 - 2000i_3$$


$$0 = 0i_1 - 2000i_2 + 2500i_3 + 5000i_\beta$$

$$i_\beta = i_2 - i_1$$

Solving,

$$i_1 = 92 \text{ mA}; \quad i_2 = 73.33 \text{ mA}; \quad i_3 = 96 \text{ mA}; \quad i_\beta = -18.67 \text{ mA}$$

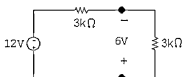
$$i_{sc} = i_1 - i_3 = -4 \text{ mA}; \quad R_{Th} = \frac{v_{Th}}{i_{sc}} = \frac{-12}{-4 \times 10^{-3}} = 3 \text{ k}\Omega$$



$$R_L = R_{Th} = 3 \text{ k}\Omega$$

$$[b] \quad p_{max} = \frac{6^2}{3 \times 10^3} = 12 \text{ mW}$$

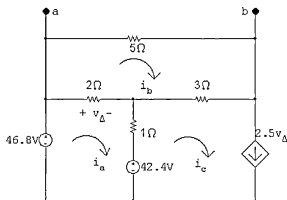P 3.69 Find the Thévenin equivalent with respect to the terminals of  $R_o$ . Open circuit voltage:



$$(46.8 - 42.4) = 3i_a - 2i_b - i_c$$


$$0 = -2i_a + 10i_b - 3i_c$$

$$i_c = 2.5v_\Delta; \quad v_\Delta = 2(i_a - i_b)$$

Solving,  $i_b = 74.8 \text{ A}$

$$\therefore v_{Th} = 5i_b = 374 \text{ V}$$

Short circuit current:

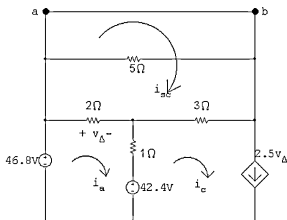

$$46.8 - 42.4 = 3i_a - 2i_{sc} - i_c$$

$$0 = -2i_a + 5i_{sc} - 3i_c$$

$$i_c = 2.5v_{\Delta}; \quad v_{\Delta} = 2(i_a - i_{sc})$$


Solving,

$$i_{sc} = 6.8 \text{ A}; \quad i_a = 8 \text{ A}; \quad i_c = 6 \text{ A}; \quad v_{\Delta} = 2.4 \text{ V}$$

$$R_{Th} = v_{Th}/i_{sc} = 374/6.8 = 55 \Omega$$

$$R_o = 55 \Omega$$

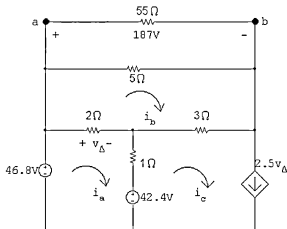with  $R_o$  equal to  $55 \Omega$  the circuit becomes



$$46.8 - 42.4 = 3i_a - 2i_b - 2.5(2)(i_a - i_b)$$



$$i_c = 2.5v_\Delta$$

$$v_\Delta = 2(i_a - i_b)$$


$$187 + 3i_b - 3(2.5)(2)(i_a - i_b) + 2i_b - 2i_a = 0$$

$$\text{Solving, } i_a = 59 \text{ A; } i_b = 40.8 \text{ A}$$

$$v_\Delta = 2(59 - 40.80) = 36.4 \text{ V}$$

$$i_c = 91 \text{ A}$$

Thus we have

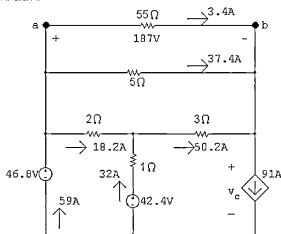

$$v_c = 42.4 - 32 - 150.6 = -140.20 \text{ V}$$


$$\sum P_{\text{dev}} = 46.8(59) + 42.4(32) + 140.20(91) = 16,876.20 \text{ W}$$

CHECK:

$$\begin{aligned} \sum P_{\text{dis}} &= (18.2)^2(2) + (50.2)^2(3) + (32)^2(1) + 187(3.4) + 187(37.4) \\ &= 16,876.20 \text{ W} \end{aligned}$$

$$\% \text{ delivered} = \frac{(55)(3.4)^2(100)}{16,876.2} = 3.77\%$$

P 3.70 [a] Open circuit voltage

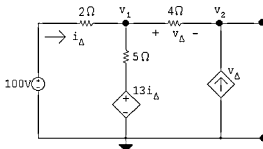

Node voltage equation:


$$\frac{v_1 - 100}{2} + \frac{v_1 - 13i_\Delta}{5} + \frac{v_1 - v_2}{4} = 0$$

Constraint equations:

$$i_\Delta = \frac{100 - v_1}{2}; \quad \frac{v_2 - v_1}{4} - v_\Delta = 0; \quad v_\Delta = v_1 - v_2$$

$$\text{Solving, } v_2 = 90 \text{ V} = v_{Th}; \quad v_1 = 0 \text{ V}; \quad v_\Delta = 0 \text{ V}; \quad i_\Delta = 5 \text{ A}$$

Short circuit current:

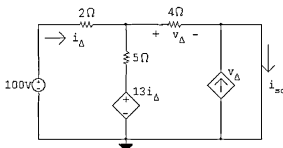

$$\frac{v_1 - 100}{2} + \frac{v_1 - 13i_\Delta}{5} + \frac{v_1}{4} = 0$$

$$i_\Delta = \frac{100 - v_1}{2}$$


$$\text{Solving, } v_1 = 80 \text{ V} = v_\Delta; \quad i_\Delta = 10 \text{ A}$$

$$i_{sc} = \frac{v_1}{4} + v_\Delta = 20 + 80 = 100 \text{ A}$$

$$R_{Th} = \frac{v_{Th}}{i_{sc}} = \frac{90}{100} = 0.9 \Omega$$


$$\therefore R_o = R_{Th} = 0.9 \Omega$$

[b]

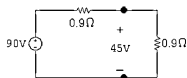

$$p_{\max} = \frac{(45)^2}{0.9} = 2250 \text{ W}$$

[c]

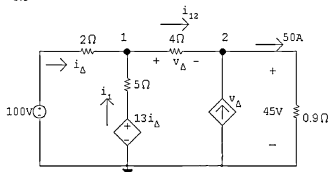

$$\frac{v_1 - 100}{2} + \frac{v_1 - 13i_{\Delta}}{5} + \frac{v_1 - 45}{4} = 0$$

$$i_{\Delta} = \frac{100 - v_1}{2}$$

$$\text{Solving, } v_1 = 85 \text{ V; } i_{\Delta} = 7.5 \text{ A; } v_{\Delta} = v_1 - v_2 = 85 - 45 = 40 \text{ V}$$

$$i_{100V} = i_{\Delta} = 7.5 \text{ A}$$

$$p_{100V} (\text{dev}) = 100(7.5) = 750 \text{ W}$$

$$i_{12} = v_{\Delta}/4 = 40/4 = 10 \text{ A}$$

$$i_1 = i_{12} - i_{\Delta} = 10 - 7.5 = 2.5 \text{ A}$$

$$p_{13i_{\Delta}} (\text{dev}) = (97.5)(2.5) = 243.75 \text{ W}$$


$$p_{v_{\Delta}} (\text{dev}) = (45)(40) = 1800 \text{ W}$$

$$\sum p_{\text{dev}} = 750 + 243.75 + 1800 = 2793.75 \text{ W}$$

$$\% \text{ delivered} = \frac{2250}{2793.75} \times 100 = 80.54\%$$

P 3.71 [a] First find the Thévenin equivalent with respect to  $R_o$ .

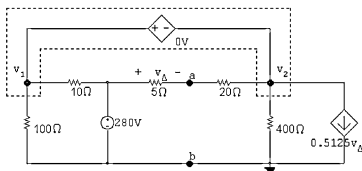Open circuit voltage:  $i_\phi = 0$ ;  $50i_\phi = 0$




$$\frac{v_1}{100} + \frac{v_1 - 280}{10} + \frac{v_1 - 280}{25} + \frac{v_1}{400} + 0.5125v_\Delta = 0$$

$$v_\Delta = \frac{(280 - v_1)}{25} \cdot 5 = 56 - 0.2v_1$$

$$v_1 = 210 \text{ V}; \quad v_\Delta = 14 \text{ V}$$

$$v_{Th} = 280 - v_\Delta = 280 - 56 + 0.2(210) = 266 \text{ V}$$

Short circuit current

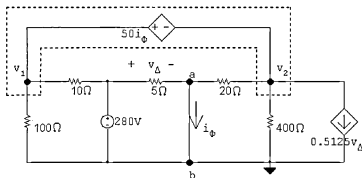

$$\frac{v_1}{100} + \frac{v_1 - 280}{10} + \frac{v_2}{20} + \frac{v_2}{400} + 0.5125(280) = 0$$

$$v_\Delta = 280 \text{ V}$$

$$v_2 + 50i_\phi = v_1$$

$$i_\phi = \frac{280}{5} + \frac{v_2}{20} = 56 + 0.05v_2$$


$$v_2 = -968 \text{ V}; \quad v_1 = -588 \text{ V}$$

$$i_\phi = i_{sc} = 56 + 0.05(-968) = 7.6 \text{ A}$$

$$R_{Th} = v_{Th}/i_{sc} = 266/7.6 = 35 \Omega$$


$$\therefore R_\phi = 35 \Omega$$

[b]

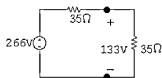

$$p_{\max} = (133)^2/35 = 505.4 \text{ W}$$

[c]

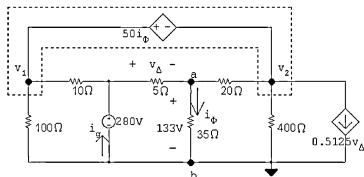

$$\frac{v_1}{100} + \frac{v_1 - 280}{10} + \frac{v_2 - 133}{20} + \frac{v_2}{400} + 0.5125(280 - 133) = 0$$


$$v_2 + 50i_\phi = v_1; \quad i_\phi = 133/35 = 3.8 \text{ A}$$

Therefore,  $v_1 = -189 \text{ V}$  and  $v_2 = -379 \text{ V}$ ; thus,

$$i_g = \frac{280 - 133}{5} + \frac{280 + 189}{10} = 76.30 \text{ A}$$

$$p_{280\text{V}} (\text{dev}) = (280)(76.3) = 21,364 \text{ W}$$

P 3.72 [a]

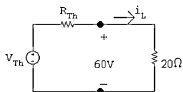


$$v_{oc} = V_{Th} = 75 \text{ V}; \quad i_L = \frac{60}{20} = 3 \text{ A}; \quad i_L = \frac{75 - 60}{R_{Th}} = \frac{15}{R_{Th}}$$

Therefore  $R_{Th} = \frac{15}{3} = 5 \Omega$

[b]  $i_L = \frac{v_o}{R_L} = \frac{V_{Th} - v_o}{R_{Th}}$

Therefore  $R_{Th} = \frac{V_{Th} - v_o}{v_o/R_L} = \left( \frac{V_{Th}}{v_o} - 1 \right) R_L$

P 3.73 [a]

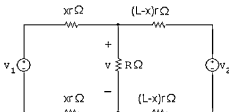

$$\frac{v - v_1}{2xr} + \frac{v}{R} + \frac{v - v_2}{2r(\ell - x)} = 0$$

$$v \left[ \frac{1}{2xr} + \frac{1}{R} + \frac{1}{2r(\ell - x)} \right] = \frac{v_1}{2xr} + \frac{v_2}{2r(\ell - x)}$$

$$v = \frac{v_1 R L + x R (v_2 - v_1)}{R L + 2r L x - 2r x^2}$$

[b] Let  $D = R L + 2r L x - 2r x^2$

$$\frac{dv}{dx} = \frac{(R L + 2r L x - 2r x^2) R (v_2 - v_1) - [v_1 R L + x R (v_2 - v_1)] 2r L - 2x}{D^2}$$

$$\frac{dv}{dx} = 0 \quad \text{when numerator is zero.}$$

The numerator simplifies to

$$x^2 + \frac{2L - v_1}{(v_2 - v_1)} x + \frac{R L (v_2 - v_1) - 2r v_1 L^2}{2r (v_2 - v_1)} = 0$$

Solving for the roots of the quadratic yields

$$x = \frac{L}{v_2 - v_1} \left\{ -v_1 \pm \sqrt{v_1 v_2 - \frac{R}{2r L} (v_2 - v_1)^2} \right\}$$

[c]  $x = \frac{L}{v_2 - v_1} \left\{ -v_1 \pm \sqrt{v_1 v_2 - \frac{R}{2r L} (v_1 - v_2)^2} \right\}$

$$v_2 = 1200 \text{ V}, \quad v_1 = 1000 \text{ V}, \quad L = 16 \text{ km}$$

$$r = 5 \times 10^{-5} \Omega/m; \quad R = 3.9 \Omega$$

$$\frac{L}{v_2 - v_1} = \frac{16,000}{1200 - 1000} = 80; \quad v_1 v_2 = 1.2 \times 10^6$$

$$\frac{R}{2rL} (v_1 - v_2)^2 = \frac{3.9(-200)^2}{(10 \times 10^{-5})(16 \times 10^3)} = 0.975 \times 10^5$$

$$\begin{aligned} x &= 80\{-1000 \pm \sqrt{1.2 \times 10^6 - 0.0975 \times 10^6}\} \\ &= 80\{-1000 \pm 1050\} = 80(50) = 4000 \text{ m} \end{aligned}$$

[d]

$$\begin{aligned} v_{\min} &= \frac{v_1 RL + R(v_2 - v_1)x}{RL + 2rLx - 2rx^2} \\ &= \frac{(1000)(3.9)(16 \times 10^3) + 3.9(200)(4000)}{(3.9)(16,000) + 10 \times 10^{-5}(16,000)(4000) - 10 \times 10^{-5}(16 \times 10^6)} \\ &= 975 \text{ V} \end{aligned}$$

$$\text{P 3.74} \quad \frac{dv_1}{dI_{g1}} = \frac{-R_1[R_2(R_3 + R_4) + R_3 R_4]}{(R_1 + R_2)(R_3 + R_4) + R_3 R_4}$$

$$\frac{dv_1}{dI_{g2}} = \frac{R_1 R_3 R_4}{(R_1 + R_2)(R_3 + R_4) + R_3 R_4}$$

$$\frac{dv_2}{dI_{g1}} + \frac{-R_1 R_3 R_4}{(R_1 + R_2)(R_3 + R_4) + R_3 R_4}$$

$$\frac{dv_2}{dI_{g2}} = \frac{R_3 R_4 (R_1 + R_2)}{(R_1 + R_2)(R_3 + R_4) + R_3 R_4}$$

P 3.75 From the solution to Problem 3.74 we have

$$\frac{dv_1}{dI_{g1}} = \frac{-25[5(125) + 3750]}{30(125) + 3750} = -\frac{175}{12} \text{ V/A}$$

and

$$\frac{dv_2}{dI_{g1}} = \frac{-(25)(50)(75)}{30(125) + 3750} = -12.5 \text{ V/A}$$

By hypothesis,  $\Delta I_{g1} = 11 - 12 = -1 \text{ A}$

$$\therefore \Delta v_1 = \left(-\frac{175}{12}\right)(-1) = \frac{175}{12} = 14.5833 \text{ V}$$

Thus,  $v_1 = 25 + 14.5833 = 39.5833 \text{ V}$

Also,

$$\Delta v_2 = (-12.5)(-1) = 12.5 \text{ V}$$

Thus,  $v_2 = 90 + 12.5 = 102.5 \text{ V}$

The PSpice solution is

$$v_1 = 39.5830 \text{ V}$$

and

$$v_2 = 102.5000 \text{ V}$$

These values are in agreement with our predicted values.

P 3.76 From the solution to Problem 3.74 we have

$$\frac{dv_1}{dI_{g2}} = \frac{(25)(50)(75)}{30(125) + 3750} = 12.5 \text{ V/A}$$

and

$$\frac{dv_2}{dI_{g2}} = \frac{(50)(75)(30)}{30(125) + 3750} = 15 \text{ V/A}$$

By hypothesis,  $\Delta I_{g2} = 17 - 16 = 1 \text{ A}$

$$\therefore \Delta v_1 = (12.5)(1) = 12.5 \text{ V}$$

Thus,  $v_1 = 25 + 12.5 = 37.5 \text{ V}$

Also,

$$\Delta v_2 = (15)(1) = 15 \text{ V}$$

Thus,  $v_2 = 90 + 15 = 105 \text{ V}$

The PSpice solution is

$$v_1 = 37.5 \text{ V}$$

and

$$v_2 = 105 \text{ V}$$

These values are in agreement with our predicted values.



P 3.77 From the solutions to Problems 3.74 — 3.76 we have

$$\frac{dv_1}{dI_{g1}} = -\frac{175}{12} \text{ V/A}; \quad \frac{dv_1}{dI_{g2}} = 12.5 \text{ V/A}$$

$$\frac{dv_2}{dI_{g1}} = -12.5 \text{ V/A}; \quad \frac{dv_2}{dI_{g2}} = 15 \text{ V/A}$$

By hypothesis,

$$\Delta I_{g1} = 11 - 12 = -1 \text{ A}$$

$$\Delta I_{g2} = 17 - 16 = 1 \text{ A}$$

Therefore,

$$\Delta v_1 = \frac{175}{12} + 12.5 = 27.0833 \text{ V}$$

$$\Delta v_2 = 12.5 + 15 = 27.5 \text{ V}$$

Hence

$$v_1 = 25 + 27.0833 = 52.0833 \text{ V}$$

$$v_2 = 90 + 27.5 = 117.5 \text{ V}$$

The PSpice solution is

$$v_1 = 52.0830 \text{ V}$$

and

$$v_2 = 117.5 \text{ V}$$

These values are in agreement with our predicted values.

P 3.78 By hypothesis,

$$\Delta R_1 = 27.5 - 25 = 2.5 \Omega$$

$$\Delta R_2 = 4.5 - 5 = -0.5 \Omega$$

$$\Delta R_3 = 55 - 50 = 5 \Omega$$

$$\Delta R_4 = 67.5 - 75 = -7.5 \Omega$$

So

$$\Delta v_1 = 0.5833(2.5) - 5.417(-0.5) + 0.45(5) + 0.2(-7.5) = 4.9168 \text{ V}$$

$$\therefore v_1 = 25 + 4.9168 = 29.9168 \text{ V}$$

$$\Delta v_2 = 0.5(2.5) + 6.5(-0.5) + 0.54(5) + 0.24(-7.5) = -1.1 \text{ V}$$

$$\therefore v_2 = 90 - 1.1 = 88.9 \text{ V}$$

The PSpice solution is

$$v_1 = 29.6710 \text{ V}$$

and

$$v_2 = 88.5260 \text{ V}$$

Note our predicted values are within a fraction of a volt of the actual values.

# The Operational Amplifier

## Drill Exercises

DE 4.1 [a]  $v_o = (-80/16)v_s$ ,  $v_o = -5v_s$

$$v_s(\text{ V}) \quad 0.4 \quad 2.0 \quad 3.5 \quad -0.6 \quad -1.6 \quad -2.4$$

$$v_o(\text{ V}) \quad -2.0 \quad -10.0 \quad -15.0 \quad 3.0 \quad 8.0 \quad 10.0$$

[b]  $-15 = -5v_s$ ,  $v_s = 3 \text{ V}$ ;  $10 = -5v_s$ ,  $v_s = -2 \text{ V}$

Therefore  $-2 \leq v_s \leq 3 \text{ V}$

DE 4.2  $v_o = (-R_x/16)v_s = (0.64R_x/16) = 10 \text{ V}$

Therefore  $R_x = \frac{160}{0.64} = 250 \text{ k}\Omega$ ,  $0 \leq R_x \leq 250 \text{ k}\Omega$

DE 4.3 [a]  $v_o = -\frac{250}{5}v_a - \frac{250}{25}v_b = -50(0.1) - 10(0.25) = -5 - 2.5 = -7.5 \text{ V}$

[b]  $v_o = -50v_a - 2.5 = -10 \text{ V}$ ; therefore  $50v_a = 7.5$ ,  $v_a = 0.15 \text{ V}$

[c]  $v_o = -5 - 10v_b = -10 \text{ V}$ ;  $10v_b = 5$ ,  $v_b = 0.5 \text{ V}$

[d]  $v_o = -50v_a + 10v_b = -5 + 2.5 = -2.5 \text{ V}$

$$v_o = -50v_a + 2.5 = -10 \text{ V};$$

$$50v_a = 12.5, \quad v_a = 0.25 \text{ V}$$

$$v_o = -5 + 10v_b = 15 \text{ V}; \quad 10v_b = 20; \quad v_b = 2.0 \text{ V}$$

DE 4.4 [a]  $\frac{v_n}{4500} + \frac{v_n - v_o}{63,000} = 0$ , therefore  $v_o = 15v_n$ ,  $v_n = v_p$

Thus  $v_o = 15v_p$ ,  $v_p = \frac{0.4R_x}{15,000 + R_x}$

So when  $R_x = 60 \text{ k}\Omega$ ,  $v_p = 0.32 \text{ V}$ ,  $v_o = 4.8 \text{ V}$

$$[b] \quad \frac{15(0.4R_x)}{15,000 + R_x} = 5, \quad R_x = 75 \text{ k}\Omega$$

DE 4.5 [a] Assume  $v_a$  is acting alone. Replacing  $v_b$  with a short circuit yields  $v_p = 0$ , therefore  $v_n = 0$  and we have

$$\frac{0 - v_a}{R_a} + \frac{0 - v'_o}{R_b} + i_n = 0, \quad i_n = 0$$

Therefore

$$\frac{v'_o}{R_b} = -\frac{v_a}{R_a}, \quad v'_o = -\frac{R_b}{R_a}v_a$$

Assume  $v_b$  is acting alone. Replace  $v_a$  with a short circuit. Now

$$v_p = v_n = \frac{v_b R_d}{R_c + R_d}$$

$$\frac{v_n}{R_a} + \frac{v_n - v''_o}{R_b} + i_n = 0, \quad i_n = 0$$

$$\left(\frac{1}{R_a} + \frac{1}{R_b}\right) \left(\frac{R_d}{R_c + R_d}\right) v_b - \frac{v''_o}{R_b} = 0$$

$$v''_o = \left(\frac{R_b}{R_a} + 1\right) \left(\frac{R_d}{R_c + R_d}\right) v_b = \frac{R_d}{R_a} \left(\frac{R_a + R_b}{R_c + R_d}\right) v_b$$

$$v_o = v'_o + v''_o = \frac{R_d}{R_a} \left(\frac{R_a + R_b}{R_c + R_d}\right) v_b - \frac{R_b}{R_a} v_a$$

$$[b] \quad \frac{R_d}{R_a} \left(\frac{R_a + R_b}{R_c + R_d}\right) = \frac{R_b}{R_a}, \quad \text{therefore} \quad R_d(R_a + R_b) = R_b(R_c + R_d)$$

$$R_d R_a = R_b R_c, \quad \text{therefore} \quad \frac{R_a}{R_b} = \frac{R_c}{R_d}$$

$$\text{When } \frac{R_d}{R_a} \left(\frac{R_a + R_b}{R_c + R_d}\right) = \frac{R_b}{R_a}$$

$$\text{Eq. (4.22) reduces to } v_o = \frac{R_b}{R_a} v_b - \frac{R_b}{R_a} v_a = \frac{R_b}{R_a} (v_b - v_a).$$

$$\text{DE 4.6 [a] } v_o = \frac{20(60)}{10(24)} v_b - \frac{50}{10} v_a = 5(v_b - v_a) = 20 - 5v_a$$

$$20 - 5v_a = \pm 10 \text{ V}$$

$$5v_a = 20 \mp 10, \quad v_a = 2 \text{ V}, \quad v_a = 6 \text{ V}$$

$$\text{Therefore } 2 \leq v_a \leq 6 \text{ V}$$

$$[b] \quad v_o = \frac{8(60)}{10(12)} v_b - 5v_a = 4v_b - 5v_a$$

$$4v_b - 5v_a = 16 - 5v_a = \pm 10 \text{ V}$$

$$16 \mp 10 = 5v_a, \quad v_a = 1.2 \text{ V}, \quad v_a = 5.2 \text{ V}$$

$$\text{Therefore } 1.2 \leq v_a \leq 5.2 \text{ V}$$

$$\text{DE 4.7 [a]} \quad A_{dm} = \frac{(24)(26) + (25)(25)}{(2)(1)(25)} = 24.98$$

$$[b] \quad A_{cm} = \frac{(1)(24) - 25(1)}{1(25)} = -0.04$$

$$[c] \quad \text{CMRR} = \left| \frac{24.98}{0.04} \right| = 624.50$$

$$\text{DE 4.8} \quad A_{cm} = \frac{(20)(50) - (50)R_x}{20(50 + R_x)}$$

$$A_{dm} = \frac{50(20 + 50) + 50(50 + R_x)}{2(20)(50 + R_x)}$$

$$\frac{A_{dm}}{A_{cm}} = \frac{R_x + 120}{2(20 - R_x)}$$

$$\therefore \frac{R_x + 120}{2(20 - R_x)} = \pm 1000$$

$$\text{If we use } +1000 \quad R_x = 19.93 \text{ k}\Omega$$

$$\text{If we use } -1000 \quad R_x = 20.07 \text{ k}\Omega$$

## Problems

- P 4.1 Since the current into the inverting input terminal of an ideal op-amp is zero, the voltage across the  $3.3\text{ M}\Omega$  resistor is  $(2.5)(3.3)$  or  $8.25\text{ V}$ . Therefore the voltmeter reads  $8.25\text{ V}$ .

P 4.2  $v_p = \frac{18}{24}(12) = 9\text{ V} = v_n$

$$\frac{v_n - 24}{30} + \frac{v_n - v_o}{20} = 0$$

$$v_o = (45 - 48)/3 = -1.0\text{ V}$$

$$i_L = \frac{v_o}{5} \times 10^{-3} = -\frac{1}{5} \times 10^{-3} = -200 \times 10^{-6}$$

$$i_L = -200\text{ }\mu\text{A}$$

P 4.3  $\frac{v_b - v_a}{20} + \frac{v_b - v_o}{160} = 0$ , therefore  $v_o = 9v_b - 8v_a$

[a]  $v_a = 1.5\text{ V}$ ,  $v_b = 0\text{ V}$ ,  $v_o = -12\text{ V}$

[b]  $v_a = 3.0\text{ V}$ ,  $v_b = 0\text{ V}$ ,  $v_o = -18\text{ V}$  (sat)

[c]  $v_a = 1.0\text{ V}$ ,  $v_b = 2\text{ V}$ ,  $v_o = 10\text{ V}$

[d]  $v_a = 4.0\text{ V}$ ,  $v_b = 2\text{ V}$ ,  $v_o = -14\text{ V}$

[e]  $v_a = 6.0\text{ V}$ ,  $v_b = 8\text{ V}$ ,  $v_o = 18\text{ V}$  (sat)

[f] If  $v_b = 4.5\text{ V}$ ,  $v_o = 40.5 - 8v_a = \pm 18$

$$\therefore 2.8125 \leq v_a \leq 7.3125\text{ V}$$

P 4.4 [a]  $i_a = \frac{120}{6} \times 10^{-6} = 20\text{ }\mu\text{A}$

$$v_a = -20 \times 10^3 i_a = -400\text{ mV}$$

[b]  $\frac{v_a}{60,000} + \frac{v_a}{20,000} + \frac{v_a - v_o}{240,000} = 0$

$$\therefore v_o = 17v_a = -6.8\text{ V}$$

[c]  $i_a = 20\text{ }\mu\text{A}$

[d]  $i_o = \frac{-v_o}{80,000} + \frac{v_a - v_o}{240,000} = 111.67\text{ }\mu\text{A}$

P 4.5  $v_o = (1)(9) = 9 \text{ V}; \quad i_{15k\Omega} = \frac{9}{15,000} = 0.6 \text{ mA};$


$$i_{6k\Omega} = \frac{9}{6000} = 1.5 \text{ mA}; \quad i_{9k\Omega} = \frac{9}{9000} = 1 \text{ mA}$$

$$\therefore i_o = -0.6 - 1.5 - 1 = -3.1 \text{ mA}$$

- P 4.6 [a] First, note that  $v_n = v_p = 2.5 \text{ V}$   
Let  $v_{o1}$  equal the voltage output of the op-amp. Then


$$\frac{2.5 - v_g}{5000} + \frac{2.5 - v_{o1}}{10,000} = 0, \quad \therefore v_{o1} = 7.5 - 2v_g$$
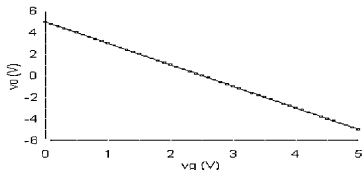
$$\text{Also note that } v_{o1} - 2.5 = v_o, \quad \therefore v_o = 5 - 2v_g$$



- [b] Yes, the circuit designer is correct!

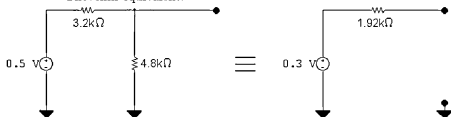- P 4.7 [a] Replace the combination of  $v_g$ ,  $3.2 \text{ k}\Omega$ , and the  $4.8 \text{ k}\Omega$  resistors with its Thévenin equivalent.



$$\text{Then } v_o = \frac{-[30 + \sigma 170]}{1.92}(0.30)$$

$$\text{At saturation } v_o = -10 \text{ V}; \quad \text{therefore}$$

$$-\left(\frac{30 + \sigma 170}{1.92}\right)(0.3) = -10, \quad \text{or } \sigma = 0.2$$

Thus for  $0 \leq \sigma < 0.20$  the operational amplifier will not saturate.

$$[b] \text{ When } \sigma = 0.12, \quad v_o = \frac{-(30 + 20.4)}{1.92}(0.30) = -7.875 \text{ V}$$

$$\text{Also } \frac{v_o}{180} + \frac{v_o}{50.4} + i_o = 0$$

$$\therefore i_o = -\frac{v_o}{180} - \frac{v_o}{50.4} = \frac{7.875}{180} + \frac{7.875}{50.4} \text{ mA} = 200 \mu\text{A}$$

P 4.8 [a] Let  $v_\Delta$  be the voltage from the potentiometer contact to ground. Then

$$\frac{0 - v_g}{5} + \frac{0 - v_\Delta}{15} = 0$$

$$-3v_g - v_\Delta = 0, \quad \therefore v_\Delta = -150 \text{ mV}$$

$$\frac{v_\Delta}{\alpha R_\Delta} + \frac{v_\Delta - 0}{15,000} + \frac{v_\Delta - v_o}{(1 - \alpha)R_\Delta} = 0$$

$$\frac{v_\Delta}{\alpha} + 10v_\Delta + \frac{v_\Delta - v_o}{1 - \alpha} = 0$$

$$v_\Delta \left( \frac{1}{\alpha} + 10 + \frac{1}{1 - \alpha} \right) = \frac{v_o}{1 - \alpha}$$

$$\therefore v_o = -0.15 \left[ 1 + 10(1 - \alpha) + \frac{(1 - \alpha)}{\alpha} \right]$$

$$\text{When } \alpha = 0.3, \quad v_o = -0.15(1 + 7 + 7/3) = -1.55 \text{ V}$$

$$\text{When } \alpha = 0.75, \quad v_o = -0.15(1 + 2.5 + 1/3) = -0.575 \text{ V}$$

$$\therefore -1.55 \text{ V} \leq v_o \leq -0.575 \text{ V}$$

$$[b] -0.15 \left[ 1 + 10(1 - \alpha) + \frac{(1 - \alpha)}{\alpha} \right] = -6$$

$$\alpha + 10\alpha(1 - \alpha) + (1 - \alpha) = 40\alpha$$

$$\alpha + 10\alpha - 10\alpha^2 + 1 - \alpha = 40\alpha$$

$$\therefore 10\alpha^2 + 30\alpha - 1 = 0 \quad \text{so} \quad \alpha \cong 0.033$$

$$P 4.9 [a] \frac{v_d - v_a}{72} + \frac{v_d - v_b}{120} + \frac{v_d - v_c}{450} + \frac{v_d}{600} + \frac{v_d - v_o}{180} = 0$$

$$v_o = 180 \left( -\frac{10}{72,000} + \frac{2}{120,000} + \frac{23}{450,000} + \frac{8}{600,000} + \frac{8}{180,000} \right) = -2.4 \text{ V}$$



$$\begin{aligned}
\text{[b]} \quad v_o &= -8.4 - 0.4v_c \\
-8.4 - 0.4v_c &= -16; \quad v_c = 19 \text{ V} \\
-8.4 - 0.4v_c &= 16; \quad v_c = -61 \text{ V} \\
-61 \text{ V} &\leq v_c \leq 19 \text{ V}
\end{aligned}$$


$$\begin{aligned}
\text{P 4.10 [a]} \quad \frac{v_d - v_a}{72,000} + \frac{v_d - v_b}{120,000} + \frac{v_d - v_c}{450,000} + \frac{v_d}{600,000} + \frac{v_d - v_o}{R_f} &= 0 \\
(25/3)v_d - (25/3)v_a + 5v_d - 5v_b + (4/3)v_d - (4/3)v_c + v_d + \\
\frac{600}{R_f}v_d &= \frac{600}{R_f}v_o \\
(47/3)v_d + \frac{600}{R_f}v_d - (25/3)v_a - 5v_b - (4/3)v_c &= \frac{600}{R_f}v_o \\
(376/3) + \frac{4800}{R_f} - 150 - 30 + 20 &= \frac{600}{R_f}v_o \\
14400 - 104R_f &= 1800v_o \quad \text{or} \quad 104R_f = 14400 - 1800v_o \\
v_o &= \pm 16 \text{ V}, \quad \text{but} \quad R_f > 0 \\
\therefore 104R_f &= 14400 - 1800(-16) \quad \text{or} \quad R_f = 415.38 \text{ k}\Omega
\end{aligned}$$

$$\begin{aligned}
\text{[b]} \quad i_f &= \frac{8 - (-16)}{415.38 \times 10^3} = 57.78 \mu\text{A} \\
i_{27 \text{ k}\Omega} &= \frac{v_o}{0.027 \times 10^6} = -592.59 \mu\text{A} \\
i_o - i_f + i_{27 \text{ k}\Omega} &= 0 \\
i_o &= 57.78 - (-592.59) = 650.37 \mu\text{A}
\end{aligned}$$

$$\begin{aligned}
\text{P 4.11 [a]} \quad v_o &= -\frac{220}{33}v_a - \frac{220}{22}v_b - \frac{220}{80}v_c = -8 + 15 - 11 = -4 \text{ V} \\
\text{[b]} \quad v_o &= -19 - 10v_b = \pm 6 \\
\therefore v_b &= -1.3 \text{ V} \quad \text{when} \quad v_o = -6 \text{ V}; \\
v_b &= -2.5 \text{ V} \quad \text{when} \quad v_o = 6 \text{ V} \\
\therefore -2.5 \text{ V} &\leq v_b \leq -1.3 \text{ V}
\end{aligned}$$

$$\begin{aligned}
\text{P 4.12} \quad v_o &= -\left[ \frac{R_f}{3000}(0.15) + \frac{R_f}{5000}(0.1) + \frac{R_f}{25,000}(0.25) \right] \\
-6 &= -8 \times 10^{-5}R_f; \quad R_f = 75 \text{ k}\Omega; \quad \therefore 0 \leq R_f \leq 75 \text{ k}\Omega
\end{aligned}$$

P 4.13

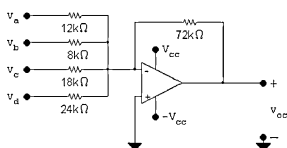


$$v_o = -(6v_a + 9v_b + 4v_c + 3v_d)$$

$$v_o = -\left[\frac{72}{R_a}v_a + \frac{72}{R_b}v_b + \frac{72}{R_c}v_c + \frac{72}{R_d}v_d\right]$$

$$\therefore R_a = 72,000/6 = 12 \text{ k}\Omega \quad R_c = 72,000/4 = 18 \text{ k}\Omega$$

$$R_b = 72,000/9 = 8 \text{ k}\Omega \quad R_d = 72,000/3 = 24 \text{ k}\Omega$$

P 4.14 [a]

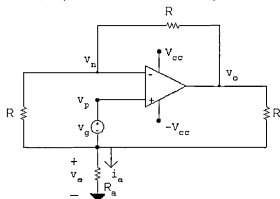

$$\frac{v_n - v_a}{R} + \frac{v_n - v_o}{R} = 0$$

$$2v_n - v_a = v_o$$

$$\frac{v_a}{R_a} + \frac{v_a - v_n}{R} + \frac{v_a - v_o}{R} = 0$$

$$v_a \left[ \frac{1}{R_a} + \frac{2}{R} \right] - \frac{v_n}{R} = \frac{v_o}{R}$$

$$v_a \left( 2 + \frac{R}{R_a} \right) - v_n = v_o$$

$$v_n = v_p = v_a + v_g$$

$$\therefore 2v_n - v_a = 2v_n + 2v_g - v_a = v_a + 2v_g$$

$$\therefore v_a - v_o = -2v_g \quad (1)$$

$$2v_a + v_a \left( \frac{R}{R_a} \right) - v_a - v_g = v_o$$

$$\therefore v_a \left( 1 + \frac{R}{R_a} \right) - v_o = v_g \quad (2)$$

Now combining equations (1) and (2) yields

$$-v_a \frac{R}{R_a} = -3v_g$$

$$\text{or } v_a = 3v_g \frac{R_a}{R}$$

$$\text{Hence } i_a = \frac{v_a}{R_a} = \frac{3v_g}{R} \quad \text{Q.E.D.}$$

[b] At saturation  $V_o = \pm V_{cc}$

$$\therefore v_a = \pm V_{cc} - 2v_g \quad (3)$$

and

$$\therefore v_a \left( 1 + \frac{R}{R_a} \right) = \pm V_{cc} + v_g \quad (4)$$

Dividing Eq (4) by Eq (3) gives

$$1 + \frac{R}{R_a} = \frac{\pm V_{cc} + v_g}{\pm V_{cc} - 2v_g}$$

$$\therefore \frac{R}{R_a} = \frac{\pm V_{cc} + v_g}{\pm V_{cc} - 2v_g} - 1 = \frac{3v_g}{\pm V_{cc} - 2v_g}$$

$$\text{or } R_a = \frac{(\pm V_{cc} - 2v_g)}{3v_g} R \quad \text{Q.E.D.}$$

P 4.15 [a] Assume the op-amp is operating within its linear range, then

$$i_L = \frac{3}{1.5} = 2 \text{ mA}$$

$$\text{For } R_L = 2.5 \text{ k}\Omega \quad v_o = (2.5 + 1.5)(2) = 8 \text{ V}$$


Now since  $v_o < 9 \text{ V}$  our assumption of linear operation is correct, therefore

$$i_L = 2 \text{ mA}$$

[b]  $9 = 2(1.5 + R_L); \quad R_L = 3 \text{ k}\Omega$

- [c] As long as the op-amp is operating in its linear region  $i_L$  is independent of  $R_L$ . From (b) we found the op-amp is operating in its linear region as long as  $R_L \leq 3 \text{ k}\Omega$ . Therefore when  $R_L = 6.5 \text{ k}\Omega$  the op-amp is saturated. We can estimate the value of  $i_L$  by assuming  $i_p = i_n \ll i_L$ . Then  $i_L = 9/(1.5 + 6.5) = 1.125 \text{ mA}$ . To justify neglecting the current into the op-amp assume the drop across the  $47 \text{ k}\Omega$  resistor is negligible, and the input resistance to the op-amp is at least  $500 \text{ k}\Omega$ . Then  $i_p = i_n = (3 - 1.5)/500 \times 10^{-3} = 3 \mu\text{A}$ . But  $3 \mu\text{A} \ll 1.125 \text{ mA}$ , hence our assumption is reasonable.

[d]

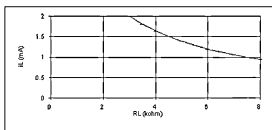

- P 4.16 [a] The output voltage of the first op-amp is  $v_{o1} = -(80/20)v_g = -4v_g$ . The output voltage of the second op-amp is  $v_{o2} = -1.6v_{o1} = 6.4v_g$ . When  $v_g$  has its largest value, i.e.,  $1.2 \text{ V}$ ,

$$v_{o1} = -4.8 \text{ V} \quad \text{and} \quad v_{o2} = 7.68 \text{ V}$$

Therefore neither op-amp saturates. The expression for  $i_g$  is

$$i_g = \frac{v_g}{20,000} + \frac{v_g - 6.4v_g}{R_o} = v_g \left[ \frac{1}{20,000} - \frac{5.4}{R_o} \right]$$

$$i_g = 0 \quad \text{when} \quad \left( \frac{1}{20,000} - \frac{5.4}{R_o} \right) = 0, \quad \text{or} \quad R_o = 108 \text{ k}\Omega$$

$$[b] \quad i_{R_o} = \frac{6.4v_g - v_g}{R_o} = \frac{5.4v_g}{R_o} = 50v_g \mu\text{A} = 50 \mu\text{A}$$

$$p_{R_o} = (50 \times 10^{-6})^2 (108 \times 10^3) = 270 \mu\text{W}$$

- P 4.17 Let  $v_{o1}$  be the output voltage of the first operational amplifier and  $v_{o2}$  the output voltage of the second operational amplifier. Then

$$\frac{0 - 1}{12,000} + \frac{0 - v_{o1}}{48,000} + \frac{0 - v_{o2}}{100,000} = 0$$

$$-50 - 12.5v_{o1} - 6v_{o2} = 0$$

$$\frac{v_{o1}}{30,000} + \frac{v_{o1} - v_{o2}}{6000} = 0$$

$$\therefore 6v_{o1} = 5v_{o2}$$

$$\therefore -50 - 12.5[(5/6)v_{o2}] - 6v_{o2} = 0 \quad \text{so} \quad v_{o2} = -3.05 \text{ V}$$

$$i_a = \frac{v_{o2}}{36,000} = -0.0846 \text{ mA}$$

$$i_a = -84.6 \mu\text{A}$$

- P 4.18 [a] Let  $v_{o1}$  = output voltage of the amplifier on the left. Let  $v_{o2}$  = output voltage of the amplifier on the right. Then

$$v_{o1} = \frac{-47}{10}(1) = -4.7 \text{ V}; \quad v_{o2} = \frac{-220}{33}(-0.15) = 1.0 \text{ V}$$

$$i_a = \frac{v_{o2} - v_{o1}}{1000} = 5.7 \text{ mA}$$

- [b]  $i_a = 0$  when  $v_{o1} = v_{o2}$  so from (a)  $v_{o2} = 1 \text{ V}$

Thus

$$\frac{-47}{10}(v_L) = 1$$

$$v_L = -\frac{10}{47} = -212.77 \text{ mV}$$

- P 4.19 [a]  $p_{16\text{k}\Omega} = \frac{(320 \times 10^{-3})^2}{(16 \times 10^3)} = 6.4 \mu\text{W}$

$$[b] \quad v_{16\text{k}\Omega} = \left(\frac{16}{64}\right)(320) = 80 \text{ mV}$$

$$p_{16\text{k}\Omega} = \frac{(80 \times 10^{-3})^2}{(16 \times 10^3)} = 0.4 \mu\text{W}$$

$$[c] \quad \frac{p_a}{p_b} = \frac{6.4}{0.4} = 16$$

- [d] Yes, the operational amplifier serves several useful purposes:

- First, it enables the source to control 16 times as much power delivered to the load resistor. When a small amount of power controls a larger amount of power, we refer to it as *power amplification*.
- Second, it allows the full source voltage to appear across the load resistor, no matter what the source resistance. This is the *voltage follower* function of the operational amplifier.

- Third, it allows the load resistor voltage (and thus its current) to be set without drawing any current from the input voltage source. This is the *current amplification* function of the circuit.

$$\text{P 4.20 [a]} \quad v_p = v_s, \quad v_n = \frac{R_1 v_o}{R_1 + R_2}, \quad v_n = v_p$$

$$\text{Therefore} \quad v_o = \left( \frac{R_1 + R_2}{R_1} \right) v_s = \left( 1 + \frac{R_2}{R_1} \right) v_s$$

$$\text{[b]} \quad v_o = v_s$$

$$\text{[c]} \quad \text{Because } v_o = v_s, \text{ thus the output voltage follows the signal voltage.}$$

$$\text{P 4.21 [a]} \quad v_p = v_n = \frac{45}{75} v_g = 0.6 v_g$$

$$\therefore \frac{0.6 v_g}{15} + \frac{0.6 v_g - v_o}{48} = 0$$

$$\therefore v_o = 2.52 v_g = 2.52(3), \quad v_o = 7.56 \text{ V}$$

$$\text{[b]} \quad v_o = 2.52 v_g = \pm 10$$

$$v_g = \pm 3.97 \text{ V}, \quad -3.97 \leq v_g \leq 3.97 \text{ V}$$

$$\text{[c]} \quad \frac{0.6 v_g}{15} + \frac{0.6 v_g - v_o}{R_f} = 0$$

$$\left( \frac{0.6 R_f}{15} + 0.6 \right) v_g = v_o = \pm 10$$

$$\therefore 3 R_f + 45 = \pm 150; \quad 3 R_f = 150 - 45; \quad R_f = 35 \text{ k}\Omega$$

$$\text{P 4.22 [a]} \quad \frac{v_p - v_a}{R_a} + \frac{v_p - v_b}{R_b} + \frac{v_p - v_c}{R_c} + \frac{v_p}{R_g} = 0$$

$$\therefore v_p = \frac{R_b R_c R_g}{D} v_a + \frac{R_a R_c R_g}{D} v_b + \frac{R_a R_b R_g}{D} v_c$$

$$\text{where } D = R_b R_c R_g + R_a R_c R_g + R_a R_b R_g + R_a R_b R_c$$

$$\frac{v_n}{R_s} + \frac{v_n - v_o}{R_f} = 0$$

$$v_n \left( \frac{1}{R_s} + \frac{1}{R_f} \right) = \frac{v_o}{R_f}$$

$$\therefore v_o = \left( 1 + \frac{R_f}{R_s} \right) v_n = k v_n$$

$$\text{where } k = \left( 1 + \frac{R_f}{R_s} \right)$$

$$v_p = v_n$$

$$\therefore v_o = kv_p$$

or

$$v_o = \frac{kR_g R_b R_c}{D} v_a + \frac{kR_g R_a R_c}{D} v_b + \frac{kR_g R_a R_b}{D} v_c$$

$$\frac{kR_g R_b R_c}{D} = 3 \quad \therefore \frac{R_b}{R_a} = 1.5$$

$$\frac{kR_g R_a R_c}{D} = 2 \quad \therefore \frac{R_c}{R_b} = 2$$

$$\frac{kR_g R_a R_b}{D} = 1 \quad \therefore \frac{R_c}{R_a} = 3$$

$$\text{Since } R_a = 2 \text{ k}\Omega \quad R_b = 3 \text{ k}\Omega \quad R_c = 6 \text{ k}\Omega$$

$$\therefore D = [(3)(6)(4) + (2)(6)(4) + (2)(3)(4) + (2)(3)(6)] \times 10^9 = 180 \times 10^9$$

$$\frac{k(4)(3)(6) \times 10^9}{180 \times 10^9} = 3$$

$$k = \frac{540 \times 10^9}{72 \times 10^9} = 7.5$$

$$\therefore 7.5 = 1 + \frac{R_f}{R_s}$$

$$\frac{R_f}{R_s} = 6.5$$

$$R_f = (6.5)(12,000) = 78 \text{ k}\Omega$$

$$[\text{b}] \quad v_o = 3(0.8) + 2(1.5) + 2.10 = 7.5 \text{ V}$$

$$v_n = v_p = \frac{7.5}{7.5} = 1.0 \text{ V}$$

$$i_a = \frac{0.8 - 1}{2000} = \frac{-0.2}{2000} = -0.1 \text{ mA} = -100 \mu\text{A}$$

$$i_b = \frac{1.5 - 1.0}{3000} = \frac{0.5}{3000} = 166.67 \mu\text{A}$$

$$i_c = \frac{2.10 - 1.0}{6000} = \frac{1.1}{6000} = 183.33 \mu\text{A}$$

$$i_g = \frac{1}{4000} = 250 \mu\text{A}$$

$$i_s = \frac{v_n}{12,000} = \frac{1}{12,000} = 83.33 \mu\text{A}$$

$$\text{P 4.23 [a]} \quad \frac{v_p - v_a}{80 \times 10^3} + \frac{v_p - v_b}{64 \times 10^3} = 0$$

$$\therefore 9v_p = 4v_a + 5v_b$$

$$\frac{v_n}{18,000} + \frac{v_n - v_o}{72,000} = 0$$

$$\therefore v_o = 5v_n = 5v_p = (20/9)v_a + (25/9)v_b = 4.44 \text{ V}$$

$$\text{[b]} \quad v_p = v_n = \frac{v_o}{5} = 0.889 \text{ V}$$

$$i_a = \frac{v_a - v_p}{80 \times 10^3} = -4.86 \mu\text{A}$$

$$i_b = \frac{v_b - v_p}{64 \times 10^3} = 4.86 \mu\text{A}$$

$$\text{[c]} \quad (20/9) \text{ for } v_a$$

$$(25/9) \text{ for } v_b$$

$$\text{P 4.24 [a]} \quad \frac{v_p - v_a}{R_a} + \frac{v_p - v_b}{R_b} + \frac{v_p - v_c}{R_c} = 0$$

$$\therefore v_p = \frac{R_b R_c}{D} v_a + \frac{R_a R_c}{D} v_b + \frac{R_a R_b}{D} v_c$$

$$\text{where } D = R_b R_c + R_a R_c + R_a R_b$$

$$\frac{v_n}{10,000} + \frac{v_n - v_o}{R_f} = 0$$

$$\left( \frac{R_f}{10,000} + 1 \right) v_n = v_o$$

$$\text{Let } \frac{R_f}{10,000} + 1 = k$$

$$v_o = kv_n = kv_p$$

$$\therefore v_o = \frac{kR_b R_c}{D} v_a + \frac{kR_a R_c}{D} v_b + \frac{kR_a R_b}{D} v_c$$

$$\therefore \frac{kR_b R_c}{D} = 5 \quad \therefore \frac{R_c}{R_a} = 5$$

$$\frac{kR_a R_c}{D} = 4$$

$$\frac{kR_a R_b}{D} = 1 \quad \therefore \frac{R_c}{R_b} = 4$$



$$\therefore R_c = 5R_a = 5 \text{ k}\Omega$$

$$R_b = R_c/4 = 1.25 \text{ k}\Omega$$

$$\therefore D = (1.25)(5) + (1)(5) + (1.25)(1) = 12.5 \times 10^6$$

$$\therefore k = \frac{5D}{R_b R_c} = \frac{(5)(12.5) \times 10^6}{(1.25)(5) \times 10^6} = 10$$

$$\therefore \frac{R_f}{10,000} + 1 = 10, \quad R_f = 90 \text{ k}\Omega$$

$$[b] \quad v_o = 5(0.5) + 4(1) + 1.5 = 8 \text{ V}$$

$$v_n = v_o/10 = 0.8 \text{ V} = v_p$$

$$i_a = \frac{v_a - v_p}{1000} = \frac{0.5 - 0.8}{1000} = -300 \mu\text{A}$$

$$i_b = \frac{v_b - v_p}{1250} = \frac{1 - 0.8}{1250} = 160 \mu\text{A}$$

$$i_c = \frac{v_c - v_p}{5000} = \frac{1.5 - 0.8}{5000} = 140 \mu\text{A}$$

$$P \ 4.25 \quad [a] \quad v_o = \frac{R_d(R_a + R_b)}{R_a(R_c + R_d)}v_b - \frac{R_b}{R_a}v_a = \frac{33(100)}{20(80)}(0.90) - 4(0.45)$$

$$v_o = 1.8563 - 1.8 = 56.25 \text{ mV}$$


$$[b] \quad v_n = v_p = \frac{(0.90)(33)}{80} = 371.25 \text{ mV}$$

$$i_a = \frac{(450 - 371.25)10^{-3}}{20 \times 10^3} = 3.9375 \mu\text{A}$$

$$R_a = \frac{v_a}{i_a} = \frac{450 \times 10^{-3}}{3.9375 \times 10^{-6}} = 114.3 \text{ k}\Omega$$

$$[c] \quad R_{inb} = R_c + R_d = 80 \text{ k}\Omega$$

P 4.26 [a]

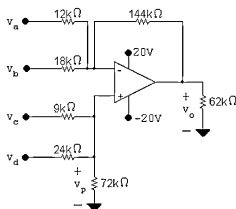

$$\frac{v_p}{72,000} + \frac{v_p - v_c}{9,000} + \frac{v_p - v_d}{24,000} = 0$$

$$\therefore v_p = (2/3)v_c + 0.25v_d = v_n$$

$$\frac{v_n - v_a}{12,000} + \frac{v_n - v_b}{18,000} + \frac{v_n - v_o}{144,000} = 0$$

$$\begin{aligned} \therefore v_o &= 21v_n - 12v_a - 8v_b \\ &= 21[(2/3)v_c + 0.25v_d] - 12v_a - 8v_b \\ &= 21(0.4 + 0.2) - 12(0.5) - 8(0.3) = 4.2 \text{ V} \end{aligned}$$

$$[b] v_o = 14v_c + 4.2 - 6 - 2.4$$

$$\pm 15 = 14v_c - 4.2$$

$$\therefore 14v_c = \pm 15 + 4.2$$


$$\therefore v_c = 1.371 \text{ V} \quad \text{and} \quad v_c = -0.771 \text{ V}$$

$$\therefore -771 \leq v_c \leq 1371 \text{ mV}$$

P 4.27 [a]

$$\begin{aligned} v_n = v_p = \alpha v_g & \quad v_o = (\alpha v_g - v_g)4 + \alpha v_g \\ \frac{v_n - v_g}{R_1} + \frac{v_n - v_o}{R_f} = 0 & \quad = [(\alpha - 1)4 + \alpha]v_g \\ (v_n - v_g)\frac{R_f}{R_1} + v_n - v_o = 0 & \quad = (5\alpha - 4)v_g \\ & \quad = (5\alpha - 4)(2) = 10\alpha - 8 \end{aligned}$$

$\alpha$	$v_o$	$\alpha$	$v_o$	$\alpha$	$v_o$
0.0	-8 V	0.4	-4 V	0.8	0 V
0.1	-7 V	0.5	-3 V	0.9	1 V
0.2	-6 V	0.6	-2 V	1.0	2 V
0.3	-5 V	0.7	-1 V		

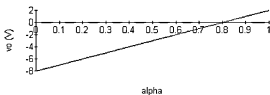

[b] Rearranging the equation for  $v_o$  from (a) gives

$$v_o = \left( \frac{R_f}{R_1} + 1 \right) v_g \alpha - \left( \frac{R_f}{R_1} \right) v_g$$

Therefore,

$$\text{slope} = \left( \frac{R_f}{R_1} + 1 \right) v_g; \quad \text{intercept} = - \left( \frac{R_f}{R_1} \right) v_g$$

[c] Using the equations from (b),

$$-6 = \left( \frac{R_f}{R_1} + 1 \right) v_g; \quad 4 = - \left( \frac{R_f}{R_1} \right) v_g$$

Solving,

$$v_g = -2 \text{ V}; \quad \frac{R_f}{R_1} = 2$$

P 4.28  $v_p = v_n = R_b i_b$

$$\frac{R_b i_b - 3000 i_a}{3000} + \frac{R_b i_b - v_o}{R_f} = 0$$

$$\left( \frac{R_b}{3000} + \frac{R_b}{R_f} \right) i_b - i_a = \frac{v_o}{R_f}$$

$$v_o = \left[ \frac{R_b R_f}{3000} + R_b \right] i_b - R_f i_a$$

$$\therefore R_f = 2000 \Omega$$

$$(2/3)R_b + R_b = 2000$$

$$\therefore R_b = 1200 \Omega$$

$$\text{P 4.29} \quad v_p = \frac{v_b R_b}{R_a + R_b} = v_n$$

$$\frac{v_n - v_a}{4700} + \frac{v_n - v_o}{R_f} = 0$$

$$v_n \left( \frac{R_f}{4700} + 1 \right) - \frac{v_a R_f}{4700} = v_o$$

$$\therefore \left( \frac{R_f}{4700} + 1 \right) \frac{R_b}{R_a + R_b} v_b - \frac{R_f}{4700} v_a = v_o$$

$$\therefore \frac{R_f}{4700} = 10; \quad R_f = 47 \text{ k}\Omega$$

$$\therefore \frac{R_f}{4700} + 1 = 11$$

$$\therefore 11 \left( \frac{R_b}{R_a + R_b} \right) = 10$$

$$11R_b = 10R_b + 10R_a \quad R_b = 10R_a$$

$$R_a + R_b = 220 \text{ k}\Omega$$

$$11R_a = 220 \text{ k}\Omega$$

$$R_a = 20 \text{ k}\Omega$$

$$R_b = 220 - 20 = 200 \text{ k}\Omega$$

$$\text{P 4.30} \quad v_o = \frac{R_d(R_a + R_b)}{R_a(R_c + R_d)} v_b - \frac{R_b}{R_a} v_a$$

$$\text{By hypothesis: } R_b/R_a = 5; \quad R_c + R_d = 600 \text{ k}\Omega; \quad \frac{R_d(R_a + R_b)}{R_a(R_c + R_d)} = 2$$

$$\therefore \frac{R_d(R_a + 5R_a)}{R_a \cdot 600,000} = 2 \quad \text{so} \quad R_d = 200 \text{ k}\Omega; \quad R_c = 400 \text{ k}\Omega$$

Also, when  $v_o = 0$  we have


$$\frac{v_n - v_a}{R_a} + \frac{v_n}{R_b} = 0$$

$$\therefore v_n \left( 1 + \frac{R_a}{R_b} \right) = v_a; \quad v_n = (5/6)v_a$$

$$i_a = \frac{v_a - (5/6)v_a}{R_a} = \frac{1}{6} \frac{v_a}{R_a}; \quad R_{in} = \frac{v_a}{i_a} = 6R_a = 18 \text{ k}\Omega$$

$$\therefore R_a = 3 \text{ k}\Omega; \quad R_b = 15 \text{ k}\Omega$$

P 4.31

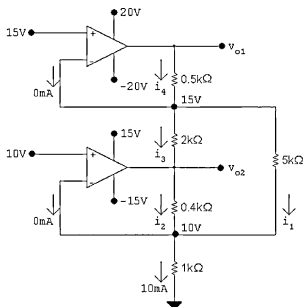

$$i_1 = \frac{15 - 10}{5000} = 1 \text{ mA}$$

$$i_2 + i_1 + 0 = 10 \text{ mA}; \quad i_2 = 9 \text{ mA}$$

$$v_{o2} = 10 + (400)(9) \times 10^{-3} = 13.6 \text{ V}$$

$$i_3 = \frac{15 - 13.6}{2000} = 0.7 \text{ mA}$$

$$i_4 = i_3 + i_1 = 1.7 \text{ mA}$$

$$v_{o1} = 15 + 1.7(0.5) = 15.85 \text{ V}$$

P 4.32 Let  $v_{o1}$  be the output voltage of the first op-amp. Then

$$\frac{0 - 1.1}{3000} + \frac{0 - v_{o1}}{18,000} + \frac{0 - v_o}{24,000} = 0$$

$$-26.4 - 4v_{o1} - 3v_o = 0$$

$$\text{But } v_{o1} = \frac{v_o}{30} (27) = 0.9v_o$$

$$\therefore -3.6v_o - 3v_o = 26.4 \quad \text{or} \quad v_o = -4 \text{ V}$$


$$i_{24\text{ k}\Omega} = \frac{0 - (-4)}{24} = (1/6) \text{ mA}$$

$$i_{3\text{ k}\Omega} = \frac{-4}{30} = (2/15) \text{ mA}$$

$$i_{4.5\text{ k}\Omega} = \frac{-4}{4.5} = (8/9) \text{ mA}$$

$$\frac{1}{6000} = i_o - \frac{2}{15,000} - \frac{8}{9000}; \quad i_o = 1.1889 \text{ mA}$$

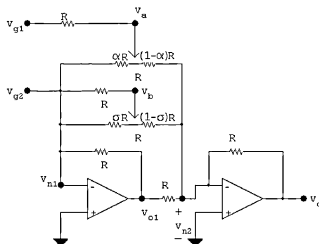P 4.33 [a] The circuit of Fig. P4.33 is redrawn with intermediate voltages defined to facilitate the analysis.



$$v_{n1} = v_{n2} = 0$$

$$\frac{0 - v_{o1}}{R} + \frac{0 - v_b}{\sigma R} + \frac{0 - v_b}{\alpha R} = 0$$

$$\text{therefore } v_{o1} = -\frac{v_a}{\alpha} - \frac{v_b}{\sigma}$$

$$\frac{0 - v_b}{(1 - \sigma)R} + \frac{0 - v_a}{(1 - \alpha)R} + \frac{0 - v_{o1}}{R} + \frac{0 - v_o}{R} = 0$$

$$\text{therefore } v_o = -v_{o1} - \frac{v_a}{1 - \alpha} - \frac{v_b}{1 - \sigma}$$

$$v_o = \frac{v_a}{\alpha} + \frac{v_b}{\sigma} - \frac{v_a}{1 - \alpha} - \frac{v_b}{1 - \sigma} = \frac{v_a(1 - 2\alpha)}{\alpha(1 - \alpha)} + v_b \frac{(1 - 2\sigma)}{\sigma(1 - \sigma)}$$

$$\frac{v_a - v_{g1}}{R} + \frac{v_a - 0}{\alpha R} + \frac{v_a - 0}{(1 - \alpha)R} = 0$$

$$v_a + \frac{v_a}{\alpha} + \frac{v_a}{1 - \alpha} = v_{g1}$$

$$v_a \left( \frac{\alpha(1 - \alpha) + (1 - \alpha) + \alpha}{\alpha(1 - \alpha)} \right) = v_{g1}$$

$$v_a = \frac{v_{g1}\alpha(1 - \alpha)}{(\alpha - \alpha^2 + 1)}$$

$$\text{By symmetry } v_b = \frac{v_{g2}\sigma(1 - \sigma)}{\sigma - \sigma^2 + 1}$$

$$\text{therefore } v_o = \frac{(1 - 2\alpha)}{(\alpha - \alpha^2 + 1)}v_{g1} + \frac{(1 - 2\sigma)}{(\sigma - \sigma^2 + 1)}v_{g2}$$

$$[\text{b}] \quad \alpha = \sigma = 1 :$$

$$v_o = -v_{g1} - v_{g2} = -(v_{g1} + v_{g2}); \quad \text{inverted summing amplifier}$$

$$[\text{c}] \quad \alpha = \sigma = 0 :$$

$$v_o = v_{g1} + v_{g2}; \quad \text{noninverted summing amplifier}$$

$$\text{P 4.34 } v_p = \frac{5.6}{8.0}v_g = 0.7v_g = 7 \sin(\pi/3)t \text{ V}$$

$$\frac{v_n}{15,000} + \frac{v_n - v_o}{75,000} = 0$$

$$6v_n = v_o; \quad v_n = v_p$$

$$\therefore v_o = 42 \sin(\pi/3)t \text{ V} \quad 0 \leq t \leq \infty$$


$$v_o = 0 \quad t \leq 0$$

At saturation

$$42 \sin\left(\frac{\pi}{3}\right)t = \pm 21; \quad \sin \frac{\pi}{3}t = \pm 0.5$$

$$\therefore \frac{\pi}{3}t = \frac{\pi}{6}, \frac{5\pi}{6}, \frac{7\pi}{6}, \frac{11\pi}{6}, \text{ etc.}$$
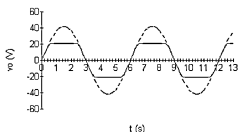
$$t = 0.50 \text{ s}, \quad 2.50 \text{ s}, \quad 3.50 \text{ s}, \quad 5.50 \text{ s}, \quad \text{etc.}$$



- P 4.35 It follows directly from the circuit that  $v_o = -16v_g$   
From the plot of  $v_g$  we have  $v_g = 0, \quad t < 0$

$$v_g = (1/4)t \quad 0 \leq t \leq 2$$

$$v_g = -(1/4)t + 1 \quad 2 \leq t \leq 6$$

$$v_g = (1/4)t - 2 \quad 6 \leq t \leq 10$$

$$v_g = -(1/4)t + 3 \quad 10 \leq t \leq 14$$

$$v_g = (1/4)t - 4 \quad 14 \leq t \leq 18, \quad \text{etc.}$$

Therefore

$$v_o = -4t \quad 0 \leq t \leq 2$$

$$v_o = 4t - 16 \quad 2 \leq t \leq 6$$


$$v_o = -4t + 32 \quad 6 \leq t \leq 10$$

$$v_o = 4t - 48 \quad 10 \leq t \leq 14$$

$$v_o = -4t + 64 \quad 14 \leq t \leq 18, \quad \text{etc.}$$

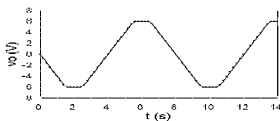
These expressions for  $v_o$  are valid as long as the op amp is not saturated. Since the peak values of  $v_o$  are  $\pm 6$ , the output is clipped at  $\pm 6$ . The plot is shown below.





P 4.36 [a]  $v_o$  will equal  $V_{CC}$  when  $v_n < v_{ref}$ . Thus
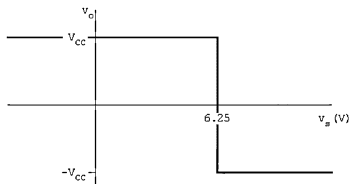
$$v_s \left( \frac{40}{50} \right) < v_{ref} \quad \text{or} \quad v_s < 6.25 \text{ V}$$




[b]  $v_o$  will equal  $V_{CC}$  when  $v_n < v_{ref}$ . Hence

$$v_s < -12.5 \text{ V}$$

$v_o$  will equal  $-V_{CC}$  when  $v_n > v_{ref}$ . Thus

$$v_s > -12.5 \text{ V}$$

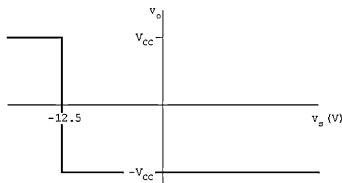

- [c] Observe that in Problem 4.36 the inputs to the comparator are interchanged with those in Example 4.2. Hence the  $v_o$  versus  $v_s$  plots in Problem 4.36 are interchanged with those in Example 4.2. For example, when  $v_{\text{ref}} = 5$  V

$$v_o = V_{\text{CC}} \quad \text{when} \quad v_s > 6.25 \text{ (Example 4.2)}$$

$$v_s < 6.25 \text{ (Problem 4.36)}$$

$$v_o = -V_{\text{CC}} \quad \text{when} \quad v_s < 6.25 \text{ (Example 4.2)}$$

$$v_s > 6.25 \text{ (Problem 4.36)}$$

$$\text{when } v_{\text{ref}} = -10 \text{ V}$$

$$v_o = V_{\text{CC}} \quad \text{when} \quad v_s > -12.5 \text{ (Example 4.2)}$$

$$v_s < -12.5 \text{ (Problem 4.36)}$$

$$v_o = -V_{\text{CC}} \quad \text{when} \quad v_s < -12.5 \text{ (Example 4.2)}$$

$$v_s > -12.5 \text{ (Problem 4.36)}$$

- P 4.37 [a] The output of the comparator will be zero when  $v_n = 0$ . Summing the currents away from the inverting input terminal yields

$$\frac{0 - v_s}{R_1} + \frac{0 - v_{\text{ref}}}{R_2} = 0$$

Solving for  $v_s$  gives

$$v_s = -\frac{R_1}{R_2} v_{\text{ref}}$$

- [b] The threshold value of  $v_s$  is

$$v_s = -\frac{10}{20}(-10) = 5 \text{ V}$$

Assume  $v_s$  is slightly less than 5 V, say

$$v_s = (5 - \epsilon) \text{ V}$$

Then

$$\frac{v_n - (5 - \epsilon)}{10} - \frac{v_n + 10}{20} = 0$$

or


$$v_n = -\frac{2}{3}\epsilon$$

With  $v_n$  slightly negative  $v_o = V_{\text{CC}}$


If  $v_s = (5 + \epsilon)$  then

$$v_n = \frac{2}{3}\epsilon$$

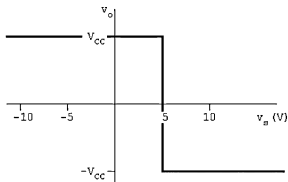Therefore, when  $v_s$  is slightly larger than the threshold value  $v_n$  goes positive and  $v_o = -V_{CC}$ . Thus, the  $v_o$  versus  $v_s$  sketch is



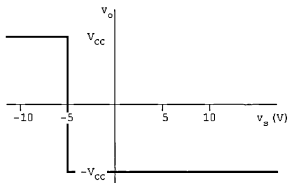[c] When  $v_{ref} = 10$  V, the threshold value of  $v_s$  is  $-5$  V and the sketch of  $v_o$  versus  $v_s$  is



P 4.38 The voltages at the inverting input terminal of the comparators, starting with the lower comparator, are: 0.875 V, 1.75 V, 2.625 V, 3.5 V, 4.375 V, 5.25 V, and 6.125 V. When  $v_s = 1$  V, all comparator output voltages are low except the lowest one. Therefore, the thermometer code is 0 0 0 0 0 0 1.

When  $v_s = 3$  V, the comparator output voltages of the three lowest comparators are high, hence the code is 0 0 0 0 1 1 1.

For  $v_s = 5$  V the code is 0 0 1 1 1 1 1 and for  $v_s = 7$  V the code is 1 1 1 1 1 1 1.

The results are summarized in the following table:

$v_s$ (V)	Thermometer Code						
1	0	0	0	0	0	0	1
3	0	0	0	0	1	1	1
5	0	0	1	1	1	1	1
7	1	1	1	1	1	1	1

- P 4.39 Since the current into the terminals of the ideal comparators is zero the current oriented down through the string of resistors is

$$i = \frac{v_{\text{ref}} - (-v_{\text{ref}})}{8R} = \frac{v_{\text{ref}}}{4R}$$

It follows that

$$v_1 = -v_{\text{ref}} + \frac{v_{\text{ref}}}{4R}(R) = -\frac{3}{4}v_{\text{ref}}$$

$$v_2 = -v_{\text{ref}} + \frac{v_{\text{ref}}}{4R}(2R) = -\frac{1}{2}v_{\text{ref}}$$

$$v_3 = -v_{\text{ref}} + \frac{v_{\text{ref}}}{4R}(3R) = -\frac{1}{4}v_{\text{ref}}$$

$$v_4 = -v_{\text{ref}} + \frac{v_{\text{ref}}}{4R}(4R) = 0$$

$$v_5 = -v_{\text{ref}} + \frac{v_{\text{ref}}}{4R}(5R) = \frac{1}{4}v_{\text{ref}}$$

$$v_6 = -v_{\text{ref}} + \frac{v_{\text{ref}}}{4R}(6R) = \frac{1}{2}v_{\text{ref}}$$

$$v_7 = -v_{\text{ref}} + \frac{v_{\text{ref}}}{4R}(7R) = \frac{3}{4}v_{\text{ref}}$$

- P 4.40 From the solution to Problem 4.39 we have

$$v_1 = (-3/4)(7) = -5.25 \text{ V}$$

$$v_2 = (-1/2)(7) = -3.5 \text{ V}$$

$$v_3 = (-1/4)(7) = -1.75 \text{ V}$$

$$v_4 = 0$$

$$v_5 = (1/4)(7) = 1.75 \text{ V}$$

$$v_6 = (1/2)(7) = 3.5 \text{ V}$$

$$v_7 = (3/4)(7) = 5.25 \text{ V}$$

When  $v_s = -7 \text{ V}$  all the comparator output voltages will be low, thus the thermometer code is 0 0 0 0 0 0.

When  $v_s = -5 \text{ V}$ , all except the first comparator (counting from the bottom up) output voltage will be low, thus the code is 0 0 0 0 0 1.

When  $v_s = -3 \text{ V}$ , all except the first two comparator output voltages will be low, hence the code is 0 0 0 0 1 1.

When  $v_s = -1 \text{ V}$ , the output voltages of the first three comparators will be high, thus the thermometer code is 0 0 0 1 1 1.

Then  $v_s = 1 \text{ V}$  the output voltages of the first four comparators will be high (0 0 0 1 1 1); when  $v_s = 3 \text{ V}$  the first five comparators will be high (0 0 1 1 1 1); when  $v_s = 5 \text{ V}$  the first six comparators will be high (0 1 1 1 1 1); and when  $v_s = 7 \text{ V}$  the output voltages of all seven comparators will be high (1 1 1 1 1 1). Our results are summarized in the following table:

$v_s$ (V)	Thermometer Code
-7	0 0 0 0 0 0 0
-5	0 0 0 0 0 0 1
-3	0 0 0 0 0 1 1
-1	0 0 0 0 1 1 1
1	0 0 0 1 1 1 1
3	0 0 1 1 1 1 1
5	0 1 1 1 1 1 1
7	1 1 1 1 1 1 1

*This page intentionally left blank*

# 5

## The Natural and Step Response of RL and RC Circuits

### Drill Exercises

DE 5.1 [a]  $i_g = 8e^{-300t} - 8e^{-1200t}$  A

$$v = L \frac{di_g}{dt} = -9.6e^{-300t} + 38.4e^{-1200t} \text{ V}, \quad t > 0^+$$

$$v(0^+) = -9.6 + 38.4 = 28.8 \text{ V}$$

[b]  $v = 0$  when  $38.4e^{-1200t} = 9.6e^{-300t}$  or  $t = (\ln 4)/900 = 1.54 \text{ ms}$

[c]  $p = vi = 384e^{-1500t} - 76.8e^{-600t} - 307.2e^{-2400t} \text{ W}$

[d]  $\frac{dp}{dt} = 0$  when  $e^{1800t} - 12.5e^{900t} + 16 = 0$

Let  $x = e^{900t}$  and solve the quadratic  $x^2 - 12.5x + 16 = 0$

$$x = 1.45, \quad x = 11.05, \quad t = \frac{\ln 1.45}{900} = 411.05 \mu\text{s}, \quad t = \frac{\ln 11.05}{900} = 2.67 \text{ ms}$$

$p$  is maximum at  $t = 411.05 \mu\text{s}$

[e]  $p_{\max} = 384e^{-1.5(0.41105)} - 76.8e^{-0.6(0.41105)} - 307.2e^{-2.4(0.41105)} = 32.72 \text{ W}$

[f]  $i_{\max} = 8[e^{-0.3(1.54)} - e^{-1.2(1.54)}] = 3.78 \text{ A}$

$$w_{\max} = (1/2)(4 \times 10^{-3})(3.78)^2 = 28.6 \text{ mJ}$$

[g]  $W$  is max when  $i$  is max,  $i$  is max when  $di/dt$  is zero.

When  $di/dt = 0$ ,  $v = 0$ , therefore  $t = 1.54 \text{ ms}$ .

DE 5.2 [a]  $i = C \frac{dv}{dt} = 24 \times 10^{-6} \frac{d}{dt} [e^{-15,000t} \sin 30,000t]$

$$= [0.72 \cos 30,000t - 0.36 \sin 30,000t] e^{-15,000t} \text{ A}, \quad i(0^+) = 0.72 \text{ A}$$

$$[b] \quad i\left(\frac{\pi}{80} \text{ ms}\right) = -31.66 \text{ mA}, \quad v\left(\frac{\pi}{80} \text{ ms}\right) = 20.505 \text{ V},$$

$$p = vi = -649.23 \text{ mW}$$

$$[c] \quad w = \left(\frac{1}{2}\right) C v^2 = 126.13 \text{ } \mu\text{J}$$

$$\begin{aligned} \text{DE 5.3} \quad [a] \quad v &= \left(\frac{1}{C}\right) \int_{0^-}^t i \, dx + v(0^-) \\ &= \frac{1}{0.6 \times 10^{-6}} \int_{0^-}^t 3 \cos 50,000x \, dx = 100 \sin 50,000t \text{ V} \end{aligned}$$

$$\begin{aligned} [b] \quad p(t) &= vi = [300 \cos 50,000t] \sin 50,000t \\ &= 150 \sin 100,000t \text{ W}, \quad p_{(\max)} = 150 \text{ W} \end{aligned}$$

$$[c] \quad w_{(\max)} = \left(\frac{1}{2}\right) C v_{\max}^2 = 0.30(100)^2 = 3000 \text{ } \mu\text{J} = 3 \text{ mJ}$$

$$\text{DE 5.4} \quad [a] \quad L_{\text{eq}} = \frac{60(240)}{300} = 48 \text{ mH}$$

$$[b] \quad i(0^+) = 3 + -5 = -2 \text{ A}$$

$$[c] \quad i = \frac{125}{6} \int_{0^+}^t (-0.03e^{-5x}) \, dx - 2 = 0.125e^{-5t} - 2.125 \text{ A}$$

$$[d] \quad i_1 = \frac{50}{3} \int_{0^+}^t (-0.03e^{-5x}) \, dx + 3 = 0.1e^{-5t} + 2.9 \text{ A}$$

$$i_2 = \frac{25}{6} \int_{0^+}^t (-0.03e^{-5x}) \, dx - 5 = 0.025e^{-5t} - 5.025 \text{ A}$$

$$i_1 + i_2 = i$$

$$\text{DE 5.5} \quad v_1 = 0.5 \times 10^6 \int_{0^+}^t 240 \times 10^{-6} e^{-10x} \, dx - 10 = -12e^{-10t} + 2 \text{ V}$$

$$v_2 = 0.125 \times 10^6 \int_{0^+}^t 240 \times 10^{-6} e^{-10x} \, dx - 5 = -3e^{-10t} - 2 \text{ V}$$

$$v_1(\infty) = 2 \text{ V}, \quad v_2(\infty) = -2 \text{ V}$$

$$W = \left[\frac{1}{2}(2)(4) + \frac{1}{2}(8)(4)\right] \times 10^{-6} = 20 \text{ } \mu\text{J}$$

$$\text{DE 5.6} \quad [a] \quad i = \left(\frac{120}{3+5}\right) \left(\frac{-30}{36}\right) = -12.5 \text{ A}$$

$$[b] \quad w = 0.5(8 \times 10^{-3})(12.5)^2 = 625 \text{ mJ}$$

$$[c] \quad \tau = \frac{L}{R} = \frac{8 \times 10^{-3}}{2} = 4 \text{ ms}$$



$$[d] \quad i = -12.5e^{-250t} \text{ A}, \quad t \geq 0$$

$$[e] \quad i(5 \text{ ms}) = -3.58 \text{ A}, \quad w(5 \text{ ms}) = (0.5)(8) \times 10^{-3}(3.58)^2 = 51.3 \text{ mJ}$$

$$w(\text{dis}) = 625 - 51.3 = 573.7 \text{ mJ}$$

$$\% \text{ dissipated} = \left( \frac{573.7}{625} \right) 100 = 91.8\%$$

$$\text{DE 5.7} \quad [a] \quad i_L(0^-) = 6.4 \left( \frac{10}{16} \right) = 4 \text{ A} = i_L(0^+), \quad t > 0$$

$$R_{\text{eq}} = \frac{(4)(16)}{20} = 3.2 \Omega, \quad \tau = \frac{0.32}{3.2} = 0.1 \text{ s}$$

$$\text{Therefore } \frac{1}{\tau} = 10, \quad i_L = 4e^{-10t} \text{ A}$$

Let  $i_1$  equal the current in the  $10 \Omega$  resistor. Let the reference direction for  $i_1$  be up. Then

$$i_1 = \left( \frac{4}{20} \right) i_L = 0.8e^{-10t} \text{ A}, \quad v_o = -10i_1 = -8e^{-10t} \text{ V}, \quad t \geq 0^+$$

$$[b] \quad v_{4\Omega} = L \frac{di_L}{dt} = 0.32(-40)e^{-10t} = -12.8e^{-10t} \text{ V}, \quad t \geq 0^+$$

$$p_{4\Omega} = \frac{v_{4\Omega}^2}{4} = 40.96e^{-20t} \text{ W}, \quad t \geq 0^+$$

$$w_{4\Omega} = \int_0^\infty 40.96e^{-20t} dt = 2.048 \text{ J}$$

$$w_i = \frac{1}{2} Li^2 = \frac{1}{2} (0.32)(16) = 2.56 \text{ J}$$

$$\% \text{ dissipated} = \left( \frac{2.048}{2.56} \right) 100 = 80\%$$

$$\text{DE 5.8} \quad [a] \quad v(0) = \left[ \frac{7.5(80)}{150} \right] 50 = 200 \text{ V}$$


$$[b] \quad \tau = RC = (50 \times 10^3)(0.4 \times 10^{-6}) = 20 \text{ ms}$$

$$[c] \quad v = 200e^{-50t} \text{ V}$$

$$[d] \quad w(0) = 0.5(0.4 \times 10^{-6})(200)^2 = 8 \text{ mJ}$$

$$[e] \quad w(t) = 0.5(0.4 \times 10^{-6})(4 \times 10^4)e^{-100t} = 8e^{-100t} \text{ mJ}$$

$$8e^{-100t} = 2, \quad t = (\ln 4)/100 = 13.86 \text{ ms}$$

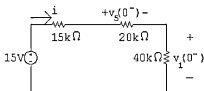DE 5.9 [a] For  $t < 0$ :

$$i = \frac{15}{75,000} = \frac{1}{5} \text{ mA}, \quad v_s(0^-) = 4 \text{ V}, \quad v_1(0^-) = 8 \text{ V}$$

$$\tau_5 = (20 \times 10^3)(5 \times 10^{-6}) = 100 \text{ ms}, \quad 1/\tau_5 = 10$$

$$\tau_1 = (40 \times 10^3)(1 \times 10^{-6}) = 40 \text{ ms}, \quad 1/\tau_1 = 25$$

$$\text{Therefore } v_5 = 4e^{-10t} \text{ V}, \quad t \geq 0; \quad v_1 = 8e^{-25t} \text{ V}, \quad t \geq 0;$$

$$v_o = v_1 + v_5 = [8e^{-25t} + 4e^{-10t}] \text{ V}, \quad t \geq 0$$

$$[b] \quad v_1(60 \text{ ms}) \cong 1.79 \text{ V}, \quad v_5(60 \text{ ms}) \cong 2.20 \text{ V}$$

$$w_1(60 \text{ ms}) = (1/2)(1)(1.79)^2 \cong 1.59 \mu\text{J}$$

$$w_5(60 \text{ ms}) = (1/2)(5)(2.20)^2 \cong 12.05 \mu\text{J}$$

$$w_1(0) = \frac{1}{2}(10^{-6})(64) + \frac{1}{2}(5 \times 10^{-6})(16) = 72 \mu\text{J}$$

$$w_{\text{diss}} = 72 - 13.64 = 58.36 \mu\text{J}$$

$$\% \text{ dissipated} = (58.36/72)(100) = 81.05 \%$$

DE 5.10 [a]  $i(0^+) = 24/2 = 12 \text{ A}$ 


$$[b] \quad v(0^+) = -10(8 + 12) = -200 \text{ V}$$

$$[c] \quad \tau = L/R = (200/10) \times 10^{-3} = 20 \text{ ms}$$

$$[d] \quad i = -8 + [12 - (-8)]e^{-50t} = [-8 + 20e^{-50t}] \text{ A}, \quad t \geq 0^+$$

$$[e] \quad v = 0 + [-200 - 0]e^{-50t} \text{ V} = -200e^{-50t} \text{ V}, \quad t \geq 0^+$$

DE 5.11 [a]

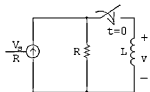

$$\frac{v}{R} + \frac{1}{L} \int_0^t v \, dx = \frac{V_s}{R}$$

$$\frac{1}{R} \frac{dv}{dt} + \frac{v}{L} = 0$$

$$\frac{dv}{dt} + \frac{R}{L} v = 0$$

$$[b] \quad \frac{dv}{dt} = -\frac{R}{L} v$$

$$\frac{dv}{dt} dt = -\frac{R}{L} v dt$$

$$\therefore \frac{dv}{v} = -\frac{R}{L} dt$$

$$\int_{v(0^+)}^{v(t)} \frac{dy}{y} = -\frac{R}{L} \int_{0^+}^t dx$$


$$\ln y \Big|_{v(0^+)}^{v(t)} = -\left(\frac{R}{L}\right) t$$

$$\ln \left[ \frac{v(t)}{v(0^+)} \right] = -\left(\frac{R}{L}\right) t$$

$$v(t) = v(0^+) e^{-(R/L)t}; \quad v(0^+) = \left(\frac{V_s}{R} - I_o\right) R = V_s - I_o R$$

$$\therefore v(t) = (V_s - I_o R) e^{-(R/L)t}$$

DE 5.12 [a]

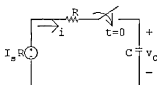

$$I_s R = Ri + \frac{1}{C} \int_{0^+}^t i dx + V_o$$

$$0 = R \frac{di}{dt} + \frac{i}{C} + 0$$

$$\therefore \frac{di}{dt} + \frac{i}{RC} = 0$$

$$[b] \quad \frac{di}{dt} = -\frac{i}{RC}; \quad \frac{di}{i} = -\frac{dt}{RC}$$


$$\int_{i(0^+)}^{i(t)} \frac{dy}{y} = -\frac{1}{RC} \int_{0^+}^t dx$$

$$\ln \frac{i(t)}{i(0^+)} = \frac{-t}{RC}$$

$$i(t) = i(0^+)e^{-t/RC}, \quad i(0^+) = \frac{I_s R - V_o}{R} = \left(I_s - \frac{V_o}{R}\right)$$

$$\therefore i(t) = \left(I_s - \frac{V_o}{R}\right)e^{-t/RC}$$

DE 5.13 [a]

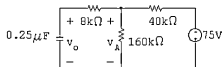

$$v_o = -60 + 90e^{-100t} \text{ V}$$

$$\frac{v_A - v_o}{8000} + \frac{v_A}{160,000} + \frac{v_A + 75}{40,000} = 0$$

$$20v_A - 20v_o + v_A + 4v_A + 300 = 0$$

$$25v_A = 20v_o - 300$$

$$v_A = 0.8v_o - 12$$

$$v_A = -48 + 72e^{-100t} - 12 = -60 + 72e^{-100t} \text{ V}, \quad t \geq 0^+$$

[b]  $t \geq 0^+$ DE 5.14 [a]  $v_c(0^+) = 50 \text{ V}$ 

$$[b] \quad v_c(\infty) = \left(-\frac{30}{25}\right)20 = -24 \text{ V}$$

[c] Find the Thévenin equivalent with respect to the terminals of the capacitor:

$$v_{Th} = -24 \text{ V}, \quad R_{Th} = 20 \parallel 5 = 4 \Omega,$$

$$\text{Therefore } \tau = 4(25 \times 10^{-9}) = 0.1 \mu\text{s}$$

$$[d] \quad i(0^+) = -\frac{50 + 24}{4} = -18.5 \text{ A}$$

$$[e] \quad v_c = -24 + [50 - (-24)]e^{-t/\tau} = -24 + 74e^{-10^7 t} \text{ V}, \quad t \geq 0$$

$$[f] \quad i = -18.5e^{-t/\tau} = -18.5e^{-10^7 t} \text{ A}, \quad t \geq 0^+$$

DE 5.15 [a]  $v_c(0^+) = (9/12)(120) = 90 \text{ V}$ 

$$[b] \quad v_c(\infty) = -1.5(40) = -60 \text{ V}$$

- [c] Find the Thévenin equivalent with respect to the terminals of the capacitor:


$$v_{Th} = -60 \text{ V}, \quad R_{Th} = 50 \text{ k}\Omega$$

$$\tau = R_{Th}C = 1 \text{ ms} = 1000 \mu\text{s}$$

- [d]  $v_c = -60 + (90 + 60)e^{-1000t} = -60 + 150e^{-1000t} \text{ V}, \quad t \geq 0$

$$\text{Therefore } t = \frac{\ln(150/60)}{1000} = 916.3 \mu\text{s}$$

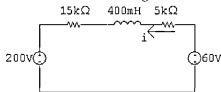
- DE 5.16 [a] For  $t < 0$ , calculate the Thévenin equivalent for the circuit to the left and right of the 400-mH inductor. We get



$$i(0^-) = -260/20 = -13 \text{ mA}$$

$$i(0^-) = i(0^+) = -13 \text{ mA}$$

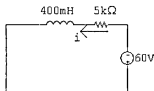- [b] For  $t > 0$ , the circuit reduces to



$$\text{Therefore } i(\infty) = -60/5 = -12 \text{ mA}$$

- [c]  $\tau = (400/5) \times 10^{-6} = 80 \mu\text{s}$

- [d]  $i(t) = -12 + [-13 + 12]e^{-12,500t} = -12 - e^{-12,500t} \text{ mA}, \quad t \geq 0$

## Problems

P 5.1  $p = vi = 40t[e^{-10t} - 10te^{-20t} - e^{-20t}]$



$$W = \int_0^\infty p \, dx = \int_0^\infty 40x[e^{-10x} - 10xe^{-20x} - e^{-20x}] \, dx = 0.2 \, \text{J}$$

This is energy stored in the inductor at  $t = \infty$ .

P 5.2  $0 \leq t < \infty$

$$i_L = \frac{10^3}{4} \int_0^t 30 \times 10^{-3} e^{-3x} \, dx + 2.5 = 7.5 \frac{e^{-3x}}{-3} \Big|_0^t + 2.5$$
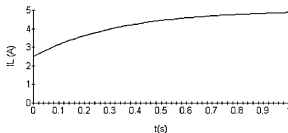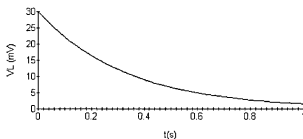
$$= 5 - 2.5e^{-3t} \, \text{A}, \quad 0 \leq t \leq \infty$$



P 5.3 [a]  $v = L \frac{di}{dt}$

$$\frac{di}{dt} = 50[t(-10e^{-10t}) + e^{-10t}] = 50e^{-10t}(1 - 10t)$$

$$\begin{aligned}
 v &= (2 \times 10^{-3})(50)e^{-10t}(1 - 10t) \\
 &= 100e^{-10t}(1 - 10t) \text{ mV}, \quad t > 0
 \end{aligned}$$

[b]  $p = vi$

$$\begin{aligned}
 v(200 \text{ ms}) &= 100e^{-2}(1 - 2) = -13.53 \text{ mV} \\
 i(200 \text{ ms}) &= 50(0.2)e^{-2} = 1.35 \text{ A} \\
 p(200 \text{ ms}) &= -13.53 \times 10^{-3}(1.35) = -18.32 \text{ mW}
 \end{aligned}$$

[c] delivering

[d]  $w = \frac{1}{2}Li^2 = \frac{1}{2}(2 \times 10^{-3})(1.35)^2 = 1.83 \text{ mJ}$

[e]  $\frac{di}{dt} = 0$  when  $t = \frac{1}{10} \text{ s} = 100 \text{ ms}$

$$i_{\max} = 50(0.1)e^{-1} = 1.84 \text{ A}$$

$$w_{\max} = \frac{1}{2}(2 \times 10^{-3})(1.84)^2 = 3.38 \text{ mJ}$$

P 5.4 [a]  $0 \leq t \leq 1 \text{ ms}$ :

$$\begin{aligned}
 i &= \frac{1}{L} \int_0^t v_s dx + i(0) = \frac{10^6}{300} \int_0^t 6 \times 10^{-3} dx + 0 \\
 &= 20x \Big|_0^t = 20t \text{ A}
 \end{aligned}$$

$1 \text{ ms} \leq t \leq 2 \text{ ms}$ :


$$i = \frac{10^6}{300} \int_{10^{-3}}^t (12 \times 10^{-3} - 6x) dx + 20 \times 10^{-3}$$

$$\therefore i = 40t - 10,000t^2 - 10 \times 10^{-3} \text{ A}$$

$2 \text{ ms} \leq t \leq \infty$ :

$$i = \frac{10^6}{300} \int_{2 \times 10^{-3}}^t (0) dx + 30 \times 10^{-3} = 30 \text{ mA}$$

[b]

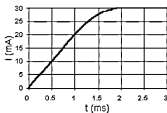

$$\text{P 5.5} \quad [\text{a}] \quad i = 0 \quad t < 0$$

$$i = 16t \text{ A} \quad 0 \leq t \leq 25 \text{ ms}$$

$$i = 0.8 - 16t \text{ A} \quad 25 \leq t \leq 50 \text{ ms}$$

$$i = 0 \quad 50 \text{ ms} < t$$

$$[\text{b}] \quad v = L \frac{di}{dt} = 375 \times 10^{-3}(16) = 6 \text{ V} \quad 0 \leq t \leq 25 \text{ ms}$$

$$v = 375 \times 10^{-3}(-16) = -6 \text{ V} \quad 25 \leq t \leq 50 \text{ ms}$$

$$v = 0 \quad t < 0$$

$$v = 6 \text{ V} \quad 0 < t < 25 \text{ ms}$$

$$v = -6 \text{ V} \quad 25 < t < 50 \text{ ms}$$

$$v = 0 \quad 50 \text{ ms} < t$$

$$p = vi$$

$$p = 0 \quad t < 0$$

$$p = (16t)(6) = 96t \text{ W} \quad 0 < t < 25 \text{ ms}$$

$$p = (0.8 - 16t)(-6) = 96t - 4.8 \text{ W} \quad 25 < t < 50 \text{ ms}$$

$$p = 0 \quad 50 \text{ ms} < t$$

$$w = 0 \quad t < 0$$

$$w = \int_0^t (16x)6 \, dx = 96 \frac{x^2}{2} \Big|_0^t = 48t^2 \text{ J} \quad 0 < t < 25 \text{ ms}$$

$$w = \int_{0.025}^t (96x - 4.8) \, dx + 0.03$$

$$= \int_{0.025}^t 96x \, dx - \int_{0.025}^t 4.8 \, dx + 0.03$$

$$= 96 \frac{x^2}{2} \Big|_{0.025}^t - 4.8x \Big|_{0.025}^t + 0.03$$

$$= 48t^2 - 4.8t + 0.12 \text{ J} \quad 25 < t < 50 \text{ ms}$$

$$w = 0 \quad 50 \text{ ms} < t$$

$$\text{P 5.6} \quad [\text{a}] \quad 0 \leq t \leq 1 \text{ s}:$$

$$v = -100t$$

$$i = \frac{1}{5} \int_0^t -100x \, dx + 0 = -20 \frac{x^2}{2} \Big|_0^t$$



$$i = -10t^2 \text{ A}$$

$$1 \text{ s} \leq t \leq 3 \text{ s} :$$

$$v = -200 + 100t$$

$$i(1) = -10 \text{ A}$$

$$\begin{aligned} \therefore i &= \frac{1}{5} \int_1^t (100x - 200) dx - 10 \\ &= 20 \int_1^t x dx - 40 \int_1^t dx - 10 \\ &= 10(t^2 - 1) - 40(t - 1) - 10 \\ &= 10t^2 - 40t + 20 \text{ A} \end{aligned}$$

$$3 \text{ s} \leq t \leq 5 \text{ s} :$$

$$v = 100$$

$$i(3) = 10(9) - 120 + 20 = -10 \text{ A}$$

$$\begin{aligned} i &= \frac{1}{5} \int_3^t 100 dx - 10 \\ &= 20t - 60 - 10 = 20t - 70 \text{ A} \end{aligned}$$

$$5 \text{ s} \leq t \leq 6 \text{ s} :$$


$$v = -100t + 600$$

$$i(5) = 100 - 70 = 30$$

$$\begin{aligned} i &= \frac{1}{5} \int_5^t (-100x + 600) dx + 30 \\ &= -20 \int_5^t x dx + 120 \int_5^t dx + 30 \\ &= -10(t^2 - 25) + 120(t - 5) + 30 \\ &= -10t^2 + 120t - 320 \text{ A} \end{aligned}$$

$$[\text{b}] \quad i(6) = -10(36) + 120(6) - 320 = 720 - 680 = 40 \text{ A}, \quad 6 \leq t \leq \infty$$

[c]

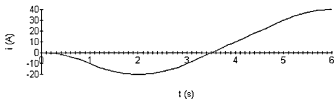

P 5.7 [a]  $i(0) = A_1 + A_2 = 0.05$

$$\frac{di}{dt} = -2500A_1e^{-2500t} - 7500A_2e^{-7500t}$$

$$v = -50A_1e^{-2500t} - 150A_2e^{-7500t} \text{ V}$$

$$v(0) = -50A_1 - 150A_2 = 10$$

$$\therefore -5A_1 - 15A_2 = 1$$

But from the equation for  $i(0)$ ,  $5A_1 + 5A_2 = 0.25$

Solving,  $A_1 = 0.175$  and  $A_2 = -0.125$

Thus,

$$i = 0.175e^{-2500t} - 0.125e^{-7500t} \text{ A}, \quad t \geq 0$$

$$v = -8.75e^{-2500t} + 18.75e^{-7500t} \text{ V}, \quad t \geq 0$$

[b]  $p = vi = 4.375e^{-10,000t} - 1.53125e^{-5000t} - 2.34375e^{-15,000t} \text{ W}$

$$p = 0 \quad \text{when} \quad 4.375e^{-10,000t} - 1.53125e^{-5000t} - 2.34375e^{-15,000t} = 0$$

Let  $x = e^{5000t}$ , then

$$4.375x - 1.53125x^2 - 2.34375 = 0$$

Solving,

$$x = 0.7143, \quad x = 2.143$$

If  $x < 1$ ,  $t$  must be negative hence the solution for  $t > 0$  must be  $x = 2.143$

$$e^{5000t} = 2.143 \quad \text{so} \quad t = 152.43 \mu\text{s}$$

P 5.8 [a] From Prob. 5.7 we have

$$i = A_1 e^{-2500t} + A_2 e^{-7500t} \text{ A}$$

$$v = -50A_1 e^{-2500t} - 150A_2 e^{-7500t} \text{ V}$$

$$i(0) = A_1 + A_2 = 0.05$$

$$v(0) = -50A_1 - 150A_2 = -100$$

$$\therefore A_1 + A_2 = 0.05 \quad \text{and} \quad A_1 + 3A_2 = 2$$

$$\therefore A_2 = 0.975 \text{ A}, \quad A_1 = -0.925 \text{ A}$$

Thus,

$$i = -0.925e^{-2500t} + 0.975e^{-7500t} \text{ A} \quad t \geq 0$$



$$v = 46.25e^{-2500t} - 146.25e^{-7500t} \text{ V} \quad t \geq 0$$

[b]  $i = 0$  when  $0.975e^{-7500t} = 0.925e^{-2500t}$

$$\therefore e^{5000t} = 1.0541$$

$$t = (\ln 1.054)/5000 = 10.53 \mu\text{s}$$

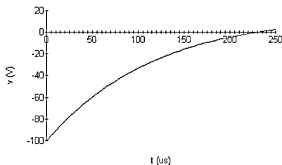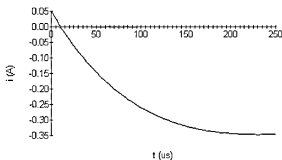$v = 0$  when  $46.25e^{-2500t} = 146.25e^{-7500t}$



$\therefore$  Energy is being stored between  $10.53 \mu\text{s}$  and  $230.25 \mu\text{s}$ ; energy is being extracted between  $0$  and  $10.53 \mu\text{s}$  and between  $230.25 \mu\text{s}$  and infinity.

$$[c] \quad p = vi = 180.375e^{-10,000t} - 42.78125e^{-5000t} - 142.59375e^{-15,000t} \text{ W}$$

$$\therefore W_{\text{stored}} = \int_{t_1}^{t_2} p \, dt + w(0)$$

$$\begin{aligned} W_{\text{stored}} &= 10^{-3} \left\{ -18.0375e^{-10,000t} \Big|_{t_1}^{t_2} + 8.55625e^{-5000t} \Big|_{t_1}^{t_2} + \right. \\ &\quad \left. 9.50625e^{-15,000t} \Big|_{t_1}^{t_2} \right\} + 25 \times 10^{-6} \\ &= 8.55625e^{-5000t_2} + 9.50625e^{-15,000t_2} - 18.0375e^{-10,000t_2} \\ &\quad - 8.55625e^{-5000t_1} - 9.50625e^{-15,000t_1} + 18.0375e^{-10,000t_1} \\ &\quad + 0.025 \text{ mJ} \end{aligned}$$

$$\text{where } t_1 = 10.52 \mu\text{s}, \quad t_2 = 230.11 \mu\text{s}$$

$$W_{\text{stored}} = 1.23 \text{ mJ.}$$

$$\begin{aligned} W_{\text{extracted}} &= \int_0^{t_1} p \, dt + \int_{t_2}^{\infty} p \, dt \\ &= \int_0^{t_1} (180.375e^{-10^4 t} - 42.78125e^{-5000t} \\ &\quad - 142.59375e^{-15,000t}) \, dt \\ &\quad + \int_{t_2}^{\infty} (180.375e^{-10^4 t} - 42.78125e^{-5000t} \\ &\quad - 142.59375e^{-15,000t}) \, dt \\ &= 10^{-3} \left\{ -18.0375e^{-10,000t} \Big|_0^{t_1} + 8.55625e^{-5000t} \Big|_0^{t_1} \right. \\ &\quad \left. + 9.50625e^{-15,000t} \Big|_0^{t_1} - 18.0375e^{-10,000t} \Big|_{t_2}^{\infty} \right. \\ &\quad \left. + 8.55625e^{-5000t} \Big|_{t_2}^{\infty} + 9.50625e^{-15,000t} \Big|_{t_2}^{\infty} \right\} \\ &= \{ 18.0375e^{-10,000t_2} - 8.55625e^{-5000t_2} - 9.50625e^{-15,000t_2} \\ &\quad + 8.55625e^{-5000t_1} + 9.50625e^{-15,000t_1} - 18.0375e^{-10,000t_1} \\ &\quad - 0.025 \} \text{ mJ} \end{aligned}$$

$$W_{\text{ext.}} = -1.23 \text{ mJ} \quad \therefore W_{\text{stored}} = W_{\text{extracted}}$$

$$\text{P 5.9} \quad [\text{a}] \quad v_L = L \frac{di}{dt} = [125 \sin 400t] e^{-200t} \text{ V}$$

$$\therefore \frac{dv_L}{dt} = 25,000(2 \cos 400t - \sin 400t) e^{-200t} \text{ V/s}$$

$$\frac{dv_L}{dt} = 0 \quad \text{when} \quad \tan 400t = 2$$

$$\therefore t = 2.77 \text{ ms}$$

$$\text{Also} \quad 400t = 1.107 + \pi \quad \text{etc.}$$

Because of the decaying exponential  $v_L$  will be maximum the first time the derivative is zero.

$$[\text{b}] \quad v_L(\text{max}) = [125 \sin 1.107] e^{-0.554} = 64.27 \text{ V}$$

$$v_{L \text{ max}} = 64.27 \text{ V}$$

$$\text{Note: When} \quad t = (1.107 + \pi)/400; \quad v_L = -13.36 \text{ V}$$

$$\text{P 5.10} \quad [\text{a}] \quad i = \frac{1000}{50} \int_0^t 250 \sin 1000x \, dx - 5$$

$$= 5000 \int_0^t \sin 1000x \, dx - 5$$

$$= 5000 \left[ \frac{-\cos 1000x}{1000} \right]_0^t - 5$$

$$= 5(1 - \cos 1000t) - 5$$

$$i = -5 \cos 1000t \text{ A}$$

$$[\text{b}] \quad p = vi = (250 \sin 1000t)(-5 \cos 1000t)$$

$$= -1250 \sin 1000t \cos 1000t$$





$$p = -625 \sin 2000t \text{ W}$$

$$w = \frac{1}{2} L i^2$$

$$= \frac{1}{2} (50 \times 10^{-3}) 25 \cos^2 1000t$$

$$= 625 \cos^2 1000t \text{ mJ}$$
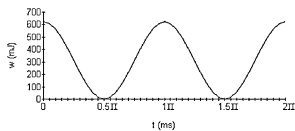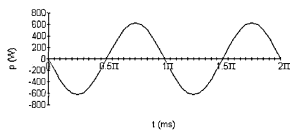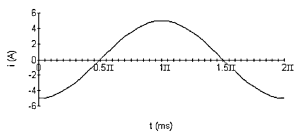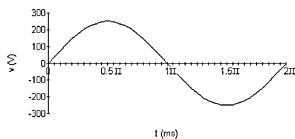
$$w = [312.5 + 312.5 \cos 2000t] \text{ mJ.}$$



[c] Absorbing power: Delivering power:

$$0.5\pi \leq t \leq \pi \text{ ms} \quad 0 \leq t \leq 0.5\pi \text{ ms}$$

$$1.5\pi \leq t \leq 2\pi \text{ ms} \quad \pi \leq t \leq 1.5\pi \text{ ms}$$

P 5.11  $i = (B_1 \cos 5t + B_2 \sin 5t)e^{-t}$

$$i(0) = B_1 = 25 \text{ A}$$

$$\frac{di}{dt} = (B_1 \cos 5t + B_2 \sin 5t)(-e^{-t}) + e^{-t}(-5B_1 \sin 5t + 5B_2 \cos 5t)$$

$$= [(5B_2 - B_1) \cos 5t - (5B_1 + B_2) \sin 5t]e^{-t}$$

$$v = 2 \frac{di}{dt} = [(10B_2 - 2B_1) \cos 5t - (10B_1 + 2B_2) \sin 5t]e^{-t}$$

$$v(0) = 100 = 10B_2 - 2B_1 = 10B_2 - 50 \quad \therefore B_2 = 150/10 = 15 \text{ A}$$

Thus,

$$i = (25 \cos 5t + 15 \sin 5t)e^{-t} \text{ A}, \quad t \geq 0$$

$$v = (100 \cos 5t - 280 \sin 5t)e^{-t} \text{ V}, \quad t \geq 0$$

$$i(0.5) = -6.70 \text{ A}; \quad v(0.5) = -150.23 \text{ V}$$

$$p(0.5) = (-6.70)(-150.23) = 1007.00 \text{ W absorbing}$$

P 5.12 [a]  $v(20 \mu\text{s}) = 12.5 \times 10^9 (20 \times 10^{-6})^2 = 5 \text{ V}$  (end of first interval)

$$v(20 \mu\text{s}) = 10^6 (20 \times 10^{-6}) - (12.5)(400) \times 10^{-3} - 10$$

$$= 5 \text{ V (start of second interval)}$$

$$v(40 \mu\text{s}) = 10^6 (40 \times 10^{-6}) - (12.5)(1600) \times 10^{-3} - 10$$

$$= 10 \text{ V (end of second interval)}$$

[b]  $p(10 \mu\text{s}) = 62.5 \times 10^{12} (10^{-5})^3 = 62.5 \text{ mW}, \quad v(10 \mu\text{s}) = 1.25 \text{ V},$

$$i(10 \mu\text{s}) = 50 \text{ mA}, \quad p(10 \mu\text{s}) = vi = 62.5 \text{ mW},$$

$$p(30 \mu\text{s}) = 437.50 \text{ mW}, \quad v(30 \mu\text{s}) = 8.75 \text{ V}, \quad i(30 \mu\text{s}) = 0.05 \text{ A}$$

$$[c] \quad w(10 \mu s) = 15.625 \times 10^{12} (10 \times 10^{-6})^4 = 0.15625 \mu J$$

$$w = 0.5 C v^2 = 0.5 (0.2 \times 10^{-6}) (1.25)^2 = 0.15625 \mu J$$

$$w(30 \mu s) = 7.65625 \mu J$$

$$w(30 \mu s) = 0.5 (0.2 \times 10^{-6}) (8.75)^2 = 7.65625 \mu J$$

$$P 5.13 \quad [a] \quad 0 \leq t \leq 50 \mu s$$

$$C = 0.5 \mu F \quad \frac{1}{C} = 2 \times 10^6$$

$$v = 2 \times 10^6 \int_0^t 20 \times 10^{-3} dx + 20$$

$$v = 40 \times 10^3 t + 20 \text{ V} \quad 0 \leq t \leq 50 \mu s$$

$$v(50 \mu s) = 2 + 20 = 22 \text{ V}$$

$$[b] \quad 50 \mu s \leq t \leq 200 \mu s$$

$$v = 2 \times 10^6 \int_{50 \times 10^{-6}}^t -40 \times 10^{-3} dx + 22 = -8 \times 10^4 t + 4 + 22$$


$$v = -8 \times 10^4 t + 26 \text{ V} \quad 50 \mu s \leq t \leq 200 \mu s$$

$$v(200 \mu s) = -8 \times 10^4 (200 \times 10^{-6}) + 26 = 10 \text{ V}$$

$$[c] \quad 200 \mu s \leq t \leq \infty$$

$$v = 2 \times 10^6 \int_{200 \times 10^{-6}}^t 0 dx + 10 = 10 \text{ V} \quad 200 \mu s \leq t \leq \infty$$

$$[d]$$

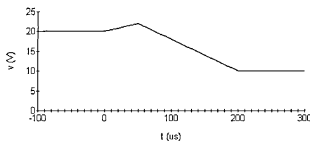

$$P 5.14 \quad i_C = C(dv/dt)$$

$$0 < t < 1:$$

$$v_c = 20t^3 \text{ V}$$


$$i_C = 0.8 \times 10^{-6} (60)t^2 = 48t^2 \mu A$$

$$1 < t < 3:$$



$$v_c = 2.5(3 - t)^3 \text{ V}$$
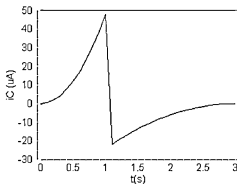
$$i_C = 0.8 \times 10^{-6}(7.5)(3 - t)^2(-1) = -6(3 - t)^2 \mu\text{A}$$



$$\text{P 5.15 [a] } v = 5 \times 10^6 \int_0^{250 \times 10^{-6}} 100 \times 10^{-3} e^{-1000t} dt - 60.6$$

$$= 500 \times 10^3 \frac{e^{-1000t}}{-1000} \bigg|_0^{250 \times 10^{-6}} - 60.6$$

$$= 500(1 - e^{-0.25}) - 60.6 = 50 \text{ V}$$

$$w = \frac{1}{2} C v^2 = \frac{1}{2} (0.2)(10^{-6})(50)^2 = 250 \mu\text{J}$$

$$\text{[b] } v = 500 - 60.6 = 439.40 \text{ V}$$

$$w = \frac{1}{2} (0.2) \times 10^{-6} (439.40)^2 = 19.31 \text{ mJ} = 19,307.24 \mu\text{J}$$

$$\text{P 5.16 [a] } w(0) = \frac{1}{2} C [v(0)]^2 = \frac{1}{2} (0.40) \times 10^{-6} (25)^2 = 125 \mu\text{J}$$

$$\text{[b] } v = (A_1 t + A_2) e^{-1500t} \quad v(0) = A_2 = 25 \text{ V}$$

$$\frac{dv}{dt} = -1500 e^{-1500t} (A_1 t + A_2) + e^{-1500t} (A_1)$$

$$= (-1500 A_1 t - 1500 A_2 + A_1) e^{-1500t}$$

$$\frac{dv}{dt}(0) = A_1 - 1500 A_2, \quad i = C \frac{dv}{dt}, \quad i(0) = C \frac{dv(0)}{dt}$$

$$\therefore \frac{dv(0)}{dt} = \frac{i(0)}{C} = \frac{90 \times 10^{-3}}{0.40 \times 10^{-6}} = 225 \times 10^3$$

$$\therefore 225 \times 10^3 = A_1 - 1500(25)$$

$$\text{Thus, } A_1 = 2.25 \times 10^5 + 3.75 \times 10^4 = 262,500 \frac{\text{V}}{\text{s}}$$

$$[c] \quad v = (262,500t + 25)e^{-1500t}$$

$$i = C \frac{dv}{dt} = 0.40 \times 10^{-6} \frac{d}{dt}(262,500t + 25)e^{-1500t}$$

$$\begin{aligned} i &= \frac{d}{dt}[(0.105t + 10 \times 10^{-6})e^{-1500t}] \\ &= (0.105t + 10 \times 10^{-6})(-1500)e^{-1500t} + e^{-1500t}(0.105) \\ &= (-157.5t - 15 \times 10^{-3} + 0.105)e^{-1500t} \\ &= (0.09 - 157.5t)e^{-1500t} \text{ A}, \quad t \geq 0 \\ &= (90 - 157,500t)e^{-1500t} \text{ mA}, \quad t \geq 0 \end{aligned}$$

$$P \ 5.17 \quad [a] \quad i = \frac{50 \times 10^{-3}}{10 \times 10^{-6}}t = 5 \times 10^3 t \quad 0 \leq t \leq 10 \mu s$$

$$i = 50 \times 10^{-3} \quad 10 \leq t \leq 30 \mu s$$

$$\begin{aligned} q &= \int_0^{10 \times 10^{-6}} 5 \times 10^3 t \, dt + \int_{10 \times 10^{-6}}^{30 \times 10^{-6}} 50 \times 10^{-3} \, dt \\ &= 5 \times 10^3 \left. \frac{t^2}{2} \right|_0^{10 \times 10^{-6}} + 50 \times 10^{-3} (20 \times 10^{-6}) \\ &= 5 \times 10^3 \left( \frac{1}{2} \right) (100 \times 10^{-12}) + 1000 \times 10^{-3} \times 10^{-6} \\ &= 1.25 \mu C \end{aligned}$$

$$[b] \quad i = 200 \times 10^{-3} - 5 \times 10^{-3}t \quad 30 \mu s \leq t \leq 50 \mu s$$

$$\begin{aligned} q &= 1.25 \times 10^{-6} + \int_{30 \times 10^{-6}}^{50 \times 10^{-6}} [200 \times 10^{-3} - 5 \times 10^3 t] \, dt \\ &= 1.25 \times 10^{-6} + 200 \times 10^{-3} (20 \times 10^{-6}) - 5 \times 10^3 \left. \frac{t^2}{2} \right|_{30 \times 10^{-6}}^{50 \times 10^{-6}} \\ &= 1.25 \times 10^{-6} + 4000 \times 10^{-9} - 5 \times 10^3 \left[ \frac{2500 - 900}{2} \right] 10^{-12} \\ &= 1.25 \mu C \end{aligned}$$

$$\text{Since } q = vC, \quad \therefore \quad v = 1.25/0.25 = 5 \text{ V.}$$

$$[c] \quad i = -300 \times 10^{-3} + 5 \times 10^{-3}t \quad 50 \mu s \leq t \leq 60 \mu s$$

$$\begin{aligned}
 q &= 1.25 \times 10^{-6} + \int_{50 \times 10^{-6}}^{60 \times 10^{-6}} [-300 \times 10^{-3} + 5 \times 10^3 t] dt \\
 &= 1.25 \times 10^{-6} - 300 \times 10^{-3} (10 \times 10^{-6}) + 5 \times 10^3 \left[ \frac{3600 - 2500}{2} \right] 10^{-12} \\
 &= 1 \mu\text{C} \\
 v &= \frac{1 \times 10^{-6}}{0.25 \times 10^{-6}} = 4 \text{ V} \\
 w &= \frac{C}{2} v^2 = \frac{1}{2} (0.25) \times 10^{-6} (16) = 2 \mu\text{J}
 \end{aligned}$$

P 5.18  $v = -60 \text{ V}, \quad t \leq 0; \quad C = 0.4 \mu\text{F}$

$$v = 15 - 15e^{-500t} (5 \cos 2000t + \sin 2000t) \text{ V}, \quad t \geq 0$$

[a]  $i = 0, \quad t < 0$

$$\begin{aligned}
 \text{[b]} \quad \frac{dv}{dt} &= -15[(5 \cos 2000t + \sin 2000t)(-500e^{-500t}) + \\
 &\quad (e^{-500t})(-10,000 \sin 2000t + 2000 \cos 2000t)] \\
 &= 15e^{-500t} (500 \cos 2000t + 10,500 \sin 2000t) \\
 i &= C \frac{dv}{dt} = 0.4 \times 10^{-6} (7500)e^{-500t} (\cos 2000t + 21 \sin 2000t) \\
 &= 3e^{-500t} (\cos 2000t + 21 \sin 2000t) \text{ mA}, \quad t > 0
 \end{aligned}$$

[c] no

[d] yes, from 0 to 3 mA

[e]  $v(\infty) = 15 \text{ V}$

$$w = \frac{1}{2} C v^2 = \frac{1}{2} (0.4) 225 \times 10^{-6} = 45 \mu\text{J}$$

P 5.19  $10 \parallel (15 + 25) = 8 \text{ H}$

$$8 \parallel 12 = 4.8 \text{ H}$$

$$44 \parallel (1.2 + 4.8) = 5.28 \text{ H}$$

$$21 \parallel 4 = 3.36 \text{ H}$$

$$5.28 + 3.36 = 8.64 \text{ H}$$

P 5.20  $6 \parallel 14 = 4.2 \text{ H}$

$$15.8 + 4.2 = 20 \text{ H}$$

$$20 \parallel 60 = 15 \text{ H}$$

$$15 + 5 = 20 \text{ H}$$

$$20 \parallel 80 = 16 \text{ H}$$

$$16 + 24 = 40 \text{ H}$$

$$40 \parallel 10 = 8 \text{ H}$$

$$L_{ab} = 12 + 8 = 20 \text{ H}$$

P 5.21 From Figure 5.17(a) we have

$$v = \frac{1}{C_1} \int_0^t i + v_1(0) + \frac{1}{C_2} \int_0^t i dx + v_2(0) + \cdots$$

$$v = \left[ \frac{1}{C_1} + \frac{1}{C_2} + \cdots \right] \int_0^t i dx + v_1(0) + v_2(0) + \cdots$$


$$\text{Therefore } \frac{1}{C_{\text{eq}}} = \left[ \frac{1}{C_1} + \frac{1}{C_2} + \cdots \right], \quad v_{\text{eq}}(0) = v_1(0) + v_2(0) + \cdots$$

P 5.22 From Fig. 5.18(a)


$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \cdots = [C_1 + C_2 + \cdots] \frac{dv}{dt}$$

Therefore  $C_{\text{eq}} = C_1 + C_2 + \cdots$ . Because the capacitors are in parallel, the initial voltage on every capacitor must be the same. This initial voltage would appear on  $C_{\text{eq}}$ .

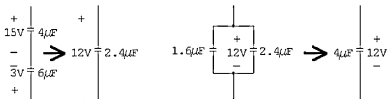
P 5.23  $\frac{1}{4} + \frac{1}{6} = \frac{5}{12} \quad \therefore C_{\text{eq}} = 2.4 \mu\text{F}$


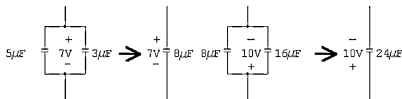
$$\frac{1}{4} + \frac{1}{12} = \frac{4}{12} \quad \therefore C_{\text{eq}} = 3 \mu\text{F}$$



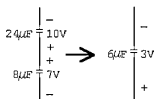
$$\frac{1}{24} + \frac{1}{8} = \frac{4}{24} \quad \therefore C_{\text{eq}} = 6 \mu\text{F}$$




P 5.24  $\frac{1}{C_1} = \frac{1}{8} + \frac{1}{32} = \frac{5}{32}; \quad C_1 = 6.4 \text{ nF}$

$$C_2 = 5.6 + 6.4 = 12 \text{ nF}$$

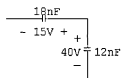


$$\frac{1}{C_3} = \frac{1}{18} + \frac{1}{12} = \frac{10}{72}; \quad C_3 = 7.2 \text{ nF}$$

$$C_4 = 12.8 + 7.2 = 20 \text{ nF}$$

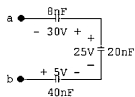

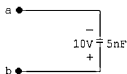
$$\frac{1}{C_5} = \frac{1}{8} + \frac{1}{20} + \frac{1}{40} = \frac{1}{5}; \quad C_5 = 5 \text{ nF}$$




P 5.25 [a]  $i_o(0) = i_1(0) + i_2(0) = 5 \text{ A}$

[b]

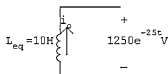

$$\begin{aligned} i_o &= -\frac{1}{10} \int_0^t 1250e^{-25x} dx + 5 = -125 \left[ \frac{e^{-25x}}{-25} \right]_0^t + 5 \\ &= 5(e^{-25t} - 1) + 5 = 5e^{-25t} \text{ A}, \quad t \geq 0 \end{aligned}$$

[c]

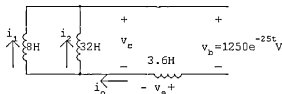

$$v_o = 3.6 \frac{d}{dt} (5e^{-25t}) = -450e^{-25t} \text{ V}$$

$$\begin{aligned} v_c &= v_a + v_b = -450e^{-25t} + 1250e^{-25t} \\ &= 800e^{-25t} \text{ V} \end{aligned}$$

$$\begin{aligned} i_1 &= -\frac{1}{8} \int_0^t 800e^{-25x} dx + 10 \\ &= 4e^{-25t} - 4 + 10 \end{aligned}$$

$$i_1 = 4e^{-25t} + 6 \text{ A} \quad t \geq 0$$

[d] 
$$\begin{aligned} i_2 &= -\frac{1}{32} \int_0^t 800e^{-25x} dx - 5 \\ &= e^{-25t} - 1 - 5 \\ i_2 &= e^{-25t} - 6 \text{ A}, \quad t \geq 0 \end{aligned}$$

$$[\text{e}] \quad w(0) = \frac{1}{2}(8)(100) + \frac{1}{2}(32)(25) + \frac{1}{2}(3.6)(25) = 845 \text{ J}$$

$$[\text{f}] \quad w_{\text{del}} = \frac{1}{2}(10)(25) = 125 \text{ J}$$

$$[\text{g}] \quad w_{\text{trapped}} = 845 - 125 = 720 \text{ J}$$

$$\text{P 5.26} \quad v_b = 1250e^{-25t} \text{ V}$$

$$i_o = 5e^{-25t} \text{ A}$$

$$p = 6250e^{-50t} \text{ W}$$

$$w = \int_0^t 6250e^{-50x} dx = 6250 \left. \frac{e^{-50x}}{-50} \right|_0^t = 125(1 - e^{-50t}) \text{ W}$$


$$w_{\text{total}} = 125 \text{ J}$$

$$80\%w_{\text{total}} = 100 \text{ J}$$

Thus,

$$125 - 125e^{-50t} = 100; \quad e^{50t} = 5; \quad \therefore t = 32.19 \text{ ms}$$

$$\text{P 5.27} \quad [\text{a}]$$

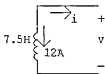

$$i(t) = -\frac{1}{7.5} \int_0^t -1800e^{-20x} dx - 12$$

$$= 240 \left. \frac{e^{-20x}}{-20} \right|_0^t - 12$$

$$= -12(e^{-20t} - 1) - 12$$

$$i(t) = -12e^{-20t} \text{ A}$$

$$[\text{b}] \quad i_1(t) = -\frac{1}{10} \int_0^t -1800e^{-20x} dx + 4$$

$$= 180 \left. \frac{e^{-20x}}{-20} \right|_0^t + 4$$

$$= -9(e^{-20t} - 1) + 4$$

$$i_1(t) = -9e^{-20t} + 13 \text{ A}$$


$$\begin{aligned}
[\text{c}] \quad i_2(t) &= -\frac{1}{30} \int_0^t -1800e^{-20x} dx - 16 \\
&= 60 \frac{e^{-20x}}{-20} \Big|_0^t - 16 \\
&= -3(e^{-20t} - 1) - 16 \\
i_2(t) &= -3e^{-20t} - 13 \text{ A} \\
[\text{d}] \quad p &= vi = (-1800e^{-20t})(-12e^{-20t}) = 21,600e^{-40t} \text{ W} \\
w &= \int_0^\infty p dt = \int_0^\infty 21,600e^{-40t} dt \\
&= 21,600 \frac{e^{-40t}}{-40} \Big|_0^\infty \\
&= 540 \text{ J}
\end{aligned}$$

$$[\text{e}] \quad w = \frac{1}{2}(10)(16) + \frac{1}{2}(30)(256) = 3920 \text{ J}$$

$$\begin{aligned}
[\text{f}] \quad w_{\text{trapped}} &= \frac{1}{2}(10)(13)^2 + \frac{1}{2}(30)(13)^2 = 3380 \text{ J} \\
w_{\text{trapped}} &= 3920 - 540 = 3380 \text{ J} \quad \text{checks}
\end{aligned}$$

[g] Yes, they agree.

P 5.28 [a]

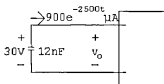

$$\begin{aligned}
v_o &= -\frac{10^9}{12} \int_0^t 900 \times 10^{-6} e^{-2500x} dx + 30 \\
&= -75,000 \frac{e^{-2500x}}{-2500} \Big|_0^t + 30 \\
&= 30e^{-2500t} \text{ V}, \quad t \geq 0 \\
[\text{b}] \quad v_1 &= -\frac{10^9}{20} (900 \times 10^{-6}) \frac{e^{-2500x}}{-2500} \Big|_0^t + 45 \\
&= 18e^{-2500t} + 27 \text{ V}, \quad t \geq 0 \\
[\text{c}] \quad v_2 &= -\frac{10^9}{30} (900 \times 10^{-6}) \frac{e^{-2500x}}{-2500} \Big|_0^t - 15 \\
&= 12e^{-2500t} - 27 \text{ V}, \quad t \geq 0
\end{aligned}$$



$$\begin{aligned}
\text{[d]} \quad p &= vi = (30e^{-2500t})(900 \times 10^{-6})e^{-2500t} \\
&= 27 \times 10^{-3} e^{-5000t} \\
w &= \int_0^\infty 27 \times 10^{-3} e^{-5000t} dt \\
&= 27 \times 10^{-3} \left. \frac{e^{-5000t}}{-5000} \right|_0^\infty \\
&= -5.4 \times 10^{-6} (0 - 1) = 5.4 \mu\text{J}
\end{aligned}$$

$$\begin{aligned}
\text{[e]} \quad w &= \frac{1}{2}(20 \times 10^{-9})(45)^2 + \frac{1}{2}(30 \times 10^{-9})(15)^2 \\
&= 20.25 \times 10^{-6} + 3.375 \times 10^{-6} \\
&= 23.625 \mu\text{J}
\end{aligned}$$

$$\begin{aligned}
\text{[f]} \quad w_{\text{trapped}} &= \frac{1}{2}(20 \times 10^{-9})(27)^2 + \frac{1}{2}(30 \times 10^{-9})(27)^2 \\
&= (10 + 15)(27)^2 \times 10^{-9} \\
&= 18.225 \mu\text{J}
\end{aligned}$$

CHECK:  $18.225 + 5.4 = 23.625 \mu\text{J}$

[g] Yes, they agree.


P 5.29  $C_1 = 1 + 1.5 = 2.5 \text{ nF}$

$$\frac{1}{C_2} = \frac{1}{2.5} + \frac{1}{12.5} + \frac{1}{50} = \frac{1}{2}$$

$$\therefore C_2 = 2 \text{ nF}$$

$$v_a(0) + v_b(0) - v_c(0) = 40 + 15 + 45 = 100 \text{ V}$$

[a]

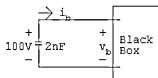

$$\begin{aligned}
v_b &= -\frac{10^9}{2} \int_0^t 50 \times 10^{-6} e^{-250x} dx + 100 \\
&= -25,000 \left. \frac{e^{-250x}}{-250} \right|_0^t + 100 \\
&= 100(e^{-250t} - 1) + 100 \\
&= 100e^{-250t} \text{ V}, \quad t \geq 0
\end{aligned}$$

$$\begin{aligned}
\text{[b]} \quad v_a &= -\frac{10^9}{12.5} \int_0^t 50 \times 10^{-6} e^{-250x} dx + 15 \\
&= -4000 \frac{e^{-250x}}{-250} \Big|_0^t + 15 \\
&= 16(e^{-250t} - 1) + 15 \\
&= 16e^{-250t} - 1 \text{ V}
\end{aligned}$$

$$\begin{aligned}
\text{[c]} \quad v_c &= \frac{10^9}{50} \int_0^t 50 \times 10^{-6} e^{-250x} dx - 45 \\
&= 1000 \frac{e^{-250x}}{-250} \Big|_0^t - 45 \\
&= -4(e^{-250t} - 1) - 45 \\
&= -4e^{-250t} - 41 \text{ V}, \quad t \geq 0
\end{aligned}$$

$$\begin{aligned}
\text{[d]} \quad v_d &= -\frac{10^9}{2.5} \int_0^t 50 \times 10^{-6} e^{-250x} dx + 40 \\
&= -20,000 \frac{e^{-250x}}{-250} \Big|_0^t + 40 \\
&= 80(e^{-250t} - 1) + 40 \\
&= 80e^{-250t} - 40 \text{ V}, \quad t \geq 0
\end{aligned}$$

$$\begin{aligned}
\text{CHECK: } v_b &= v_d + v_a - v_c \\
&= 80e^{-250t} - 40 + 16e^{-250t} - 1 + 4e^{-250t} + 41 \\
&= 100e^{-250t} \text{ V} \quad (\text{checks})
\end{aligned}$$

$$\begin{aligned}
\text{[e]} \quad i_1 &= -10^{-9} \frac{d}{dt} [80e^{-250t} - 40] \\
&= -10^{-9} (-20,000e^{-250t}) \\
&= 20e^{-250t} \mu\text{A}, \quad t \geq 0
\end{aligned}$$

$$\begin{aligned}
\text{[f]} \quad i_2 &= -1.5 \times 10^{-9} \frac{d}{dt} [80e^{-250t} - 40] \\
&= -1.5 \times 10^{-9} (-20,000e^{-250t}) \\
&= 30e^{-250t} \mu\text{A}, \quad t \geq 0
\end{aligned}$$

$$\text{CHECK: } i_1 + i_2 = 50e^{-250t} \mu\text{A} = i_b$$

$$\begin{aligned}\text{P 5.30 [a]} \quad w(0) &= [\tfrac{1}{2}(2.5)(40)^2 + \tfrac{1}{2}(12.5)(15)^2 + \tfrac{1}{2}(50)(45)^2] \times 10^{-9} \\ &= 54,031.25 \text{ nJ}\end{aligned}$$

$$\begin{aligned}\text{[b]} \quad v_a(\infty) &= -1 \text{ V} \\ v_c(\infty) &= -41 \text{ V} \\ v_d(\infty) &= -40 \text{ V} \\ w(\infty) &= [\tfrac{1}{2}(2.5)(40)^2 + \tfrac{1}{2}(12.5)(1)^2 + \tfrac{1}{2}(50)(41)^2] \times 10^{-9} \\ &= 44,031.25 \text{ nJ}\end{aligned}$$

$$\begin{aligned}\text{[c]} \quad w &= \int_0^\infty (100e^{-250t})(50e^{-250t}) \times 10^{-6} dt = 10,000 \text{ nJ} \\ \text{CHECK: } 54,031.25 - 44,031.25 &= 10,000\end{aligned}$$

$$\text{[d]} \quad \% \text{ delivered} = \frac{10,000}{54,031.25} \times 100 = 18.51\%$$

$$\begin{aligned}\text{[e]} \quad w &= 5 \times 10^{-3} \int_0^t e^{-500x} dx \\ &= 10^4(1 - e^{-500t}) \text{ nJ} \\ \therefore 10^4(1 - e^{-500t}) &= 5000; \quad e^{-500t} = 0.5 \\ \text{Thus, } t &= (\ln 2)/500 = 1.39 \text{ ms.}\end{aligned}$$

$$\text{P 5.31 [a]} \quad \frac{v}{i} = R = \frac{100e^{-80t}}{4e^{-80t}} = 25 \Omega$$

$$\text{[b]} \quad \tau = \frac{1}{80} = 12.5 \text{ ms}$$

$$\text{[c]} \quad \tau = \frac{L}{R} = 12.5 \times 10^{-3}$$

$$L = (12.5)(25) \times 10^{-3} = 312.5 \text{ mH}$$


$$\text{[d]} \quad w(0) = \frac{1}{2}L[i(0)]^2 = \frac{1}{2}(0.3125)(16) = 2.5 \text{ J}$$

$$\text{[e]} \quad w_{\text{diss}} = \int_0^t 400e^{-160x} dx = 2.5 - 2.5e^{-160t}$$


$$0.8w(0) = (0.8)(2.5) = 2 \text{ J}$$

$$2.5 - 2.5e^{-160t} = 2 \quad \therefore e^{-160t} = 0.5$$

$$\text{Solving, } t = 10.06 \text{ ms.}$$

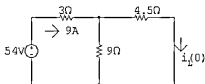P 5.32 [a]  $t < 0$ :


$$\frac{(9)(4.5)}{13.5} = 3\Omega; \quad i_L(0) = 9 \frac{9}{13.5} = 6\text{ A}$$

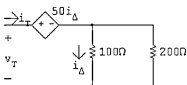 $t > 0$ :

$$i_D = \frac{i_T(200)}{300} = \frac{2}{3}i_T$$

$$v_T = 50i_D + i_T \frac{(100)(200)}{300} = 50i_T \frac{2}{3} + \frac{200}{3}i_T$$
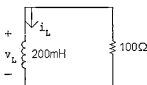
$$\frac{v_T}{i_T} = R_{Th} = \frac{100}{3} + \frac{200}{3} = 100\Omega$$




$$\tau = \frac{L}{R} = \frac{200}{100} \times 10^{-3} \quad \frac{1}{\tau} = 500$$

$$i_L = 6e^{-500t} \text{ A}, \quad t \geq 0$$

[b]  $v_L = 200 \times 10^{-3}(-3000e^{-500t}) = -600e^{-500t} \text{ V}, \quad t \geq 0^+$

[c]

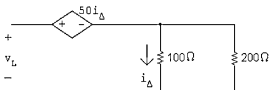

$$v_L = 50i_D + 100i_D = 150i_D$$

$$i_{\Delta} = \frac{v_L}{150} = -4e^{-500t} \text{ A} \quad t \geq 0^+$$

P 5.33  $w(0) = \frac{1}{2}(200 \times 10^{-3})(36) = 3.6 \text{ J}$

$$p_{50i_{\Delta}} = -50i_{\Delta}i_L = -50(-4e^{-500t})(6e^{-500t}) = 1200e^{-1000t} \text{ W}$$

$$w_{50i_{\Delta}} = \int_0^{\infty} 1200e^{-1000t} dt = 1200 \frac{e^{-1000t}}{-1000} \Big|_0^{\infty} = 1.2 \text{ J}$$

$$\% \text{ dissipated} = \frac{1.2}{3.6}(100) = 33.33\%$$

P 5.34 [a]  $i(0) = 125/25 = 5 \text{ A}$

[b]  $\tau = \frac{L}{R} = \frac{4}{100} = 40 \text{ ms}$

[c]  $i = 5e^{-25t} \text{ A}, \quad t \geq 0$

$$v_1 = L \frac{di_1}{dt} = 4(-125e^{-25t}) = -500e^{-25t} \text{ V} \quad t \geq 0^+$$

$$v_2 = -80i = -400e^{-25t} \text{ V} \quad t \geq 0$$

[d]  $p_{\text{diss}} = i^2(20) = 25e^{-50t}(20) = 500e^{-50t} \text{ W}$


$$w_{\text{diss}} = \int_0^t 500e^{-50x} dx = 500 \frac{e^{-50x}}{-50} \Big|_0^t = 10 - 10e^{-50t} \text{ J}$$

$$w_{\text{diss}}(12 \text{ ms}) = 10 - 10e^{-0.6} = 4.51 \text{ J}$$

$$w(0) = \frac{1}{2}(4)(25) = 50 \text{ J}$$

$$\% \text{ dissipated} = \frac{4.51}{50}(100) = 9.02\%$$

P 5.35 [a]  $t < 0$

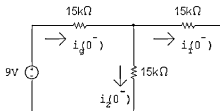

$$15 \text{ k}\Omega \parallel 15 \text{ k}\Omega = 7.5 \text{ k}\Omega$$

$$i_g(0^-) = \frac{9}{(15 + 7.5) \times 10^3} = 0.4 \text{ mA}$$

$$i_1(0^-) = i_2(0^-) = (0.4 \times 10^{-3}) \left( \frac{15}{30} \right) = 0.2 \text{ mA}$$

[b]  $i_1(0^+) = i_1(0^-) = 0.2 \text{ mA}$

$i_2(0^+) = -i_1(0^+) = -0.2 \text{ mA}$  (when switch is open)

[c]  $\tau = \frac{L}{R} = \frac{30 \times 10^{-3}}{30 \times 10^3} = 10^{-6}; \quad \frac{1}{\tau} = 10^6$

$i_1(t) = i_1(0^+)e^{-t/\tau}$


$i_1(t) = 0.2e^{-10^6 t} \text{ mA}, \quad t \geq 0$

[d]  $i_2(t) = -i_1(t)$  when  $t \geq 0^+$

$\therefore i_2(t) = -0.2e^{-10^6 t} \text{ mA}, \quad t \geq 0^+$

[e] The current in a resistor can change instantaneously. The switching operation forces  $i_2(0^-)$  to equal  $0.2 \text{ mA}$  and  $i_2(0^+) = -0.2 \text{ mA}$ .


P 5.36 [a] For  $t < 0$

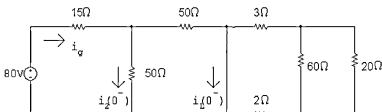

$i_g = \frac{80}{40} = 2 \text{ A}$

$i_L(0^-) = \frac{2(50)}{(100)} = 1 \text{ A} = i_L(0^+)$

For  $t > 0$

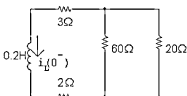

$i_L(t) = i_L(0^+)e^{-t/\tau} \text{ A}, \quad t \geq 0$

$\tau = \frac{L}{R} = \frac{0.20}{5 + 15} = \frac{1}{100} = 0.01 \text{ s}$

$i_L(0^+) = 1 \text{ A}$

$$i_L(t) = e^{-100t} \text{ A}, \quad t \geq 0$$

$$v_o(t) = -15i_L(t)$$

$$v_o(t) = -15e^{-100t} \text{ V}, \quad t \geq 0^+$$


P 5.37  $P_{20\Omega} = \frac{v_o^2}{20} = 11.25e^{-200t} \text{ W}$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{0.01} 11.25e^{-200t} dt \\ &= \frac{11.25}{-200} e^{-200t} \Big|_0^{0.01} \\ &= 56.25 \times 10^{-3} (1 - e^{-2}) = 48.64 \text{ mJ} \end{aligned}$$

$$w_{\text{stored}} = \frac{1}{2} (0.2)(1)^2 = 100 \text{ mJ}.$$


$$\% \text{ diss} = \frac{48.64}{100} \times 100 = 48.64\%$$

P 5.38  $t < 0$

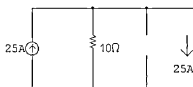


$$i_L(0^-) = i_L(0^+) = 25 \text{ A}$$

$t > 0$

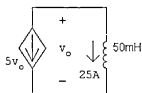


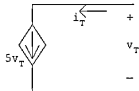Find Thévenin resistance seen by inductor



$$i_T = 5v_T; \quad \frac{v_T}{i_T} = R_{\text{Th}} = \frac{1}{5} = 0.2 \Omega$$

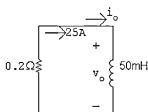
$$\tau = \frac{L}{R} = \frac{50 \times 10^{-3}}{0.2} = 250 \text{ ms}; \quad 1/\tau = 4$$




$$i_o = 25e^{-4t} \text{ A}, \quad t \geq 0$$

$$v_o = L \frac{di_o}{dt} = (50 \times 10^{-3})(-100e^{-4t}) = -5e^{-4t} \text{ V}, \quad t \geq 0^+$$

P 5.39 [a]  $t < 0$ :

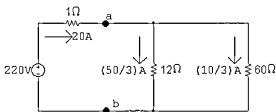


$t = 0^+$ :

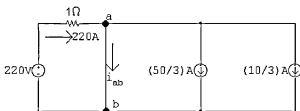


$$220 = i_{ab} + (50/3) + (10/3), \quad i_{ab} = 200 \text{ A}, \quad t = 0^+$$



[b] At  $t = \infty$ :

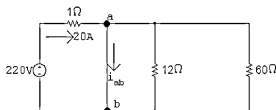
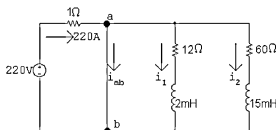
$$i_{ab} = 220/1 = 220 \text{ A}, \quad t = \infty$$



$$[c] \quad i_1(0) = 50/3, \quad \tau_1 = \frac{2}{12} \times 10^{-3} = 0.167 \text{ ms}$$

$$i_2(0) = 10/3, \quad \tau_2 = \frac{15}{60} \times 10^{-3} = 0.25 \text{ ms}$$

$$i_1(t) = (50/3)e^{-6000t} \text{ A}, \quad t \geq 0$$

$$i_2(t) = (10/3)e^{-4000t} \text{ A}, \quad t \geq 0$$

$$i_{ab} = 220 - (50/3)e^{-6000t} - (10/3)e^{-4000t} \text{ A}, \quad t \geq 0$$

$$220 - (50/3)e^{-6000t} - (10/3)e^{-4000t} = 210$$

$$30 = 50e^{-6000t} + 10e^{-4000t}$$


$$3 = 5e^{-6000t} + e^{-4000t}$$

By trial and error

$$t = 123.1 \mu\text{s}$$

P 5.40 [a]  $i_o(0^-) = 0$  since the switch is open for  $t < 0$ .

[b] For  $t = 0^-$  the circuit is:

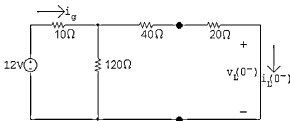


$$120\Omega // 60\Omega = 40\Omega$$

$$\therefore i_g = \frac{12}{10 + 40} = 0.24\text{ A} = 240\text{ mA}$$

$$i_L(0^-) = \left(\frac{120}{180}\right) i_g = 160\text{ mA}$$

[c] For  $t = 0^+$  the circuit is:

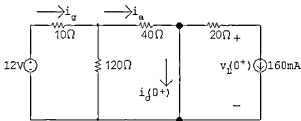

$$120\Omega // 40\Omega = 30\Omega$$

$$\therefore i_g = \frac{12}{10 + 30} = 0.30\text{ A} = 300\text{ mA}$$

$$i_a = \left(\frac{120}{160}\right) 300 = 225\text{ mA}$$

$$\therefore i_o(0^+) = 225 - 160 = 65\text{ mA}$$

[d]  $i_L(0^+) = i_L(0^-) = 160\text{ mA}$

[e]  $i_o(\infty) = i_a = 225\text{ mA}$

[f]  $i_L(\infty) = 0$ , since the switch short circuits the branch containing the  $20\Omega$  resistor and the  $100\text{ mH}$  inductor.

[g]  $\tau = \frac{L}{R} = \frac{100 \times 10^{-3}}{20} = 5\text{ ms}; \quad \frac{1}{\tau} = 200$

$$\therefore i_L = 0 + (160 - 0)e^{-200t} = 160e^{-200t}\text{ mA}, \quad t \geq 0$$

[h]  $v_L(0^-) = 0$  since for  $t < 0$  the current in the inductor is constant

[i] Refer to the circuit at  $t = 0^+$  and note:


$$20(0.16) + v_L(0^+) = 0; \quad \therefore v_L(0^+) = -3.2 \text{ V}$$

[j]  $v_L(\infty) = 0$ , since the current in the inductor is a constant at  $t = \infty$ .


$$[k] \quad v_L(t) = 0 + (-3.2 - 0)e^{-200t} = -3.2e^{-200t} \text{ V}, \quad t \geq 0^+$$

$$[l] \quad i_o = i_a - i_L = 225 - 160e^{-200t} \text{ mA}, \quad t \geq 0^+$$


P 5.41 [a]  $t < 0$ :

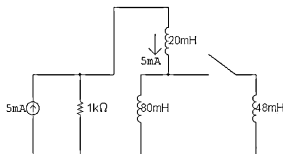

$t = 0^+$ :

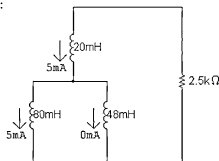


$t > 0$ :

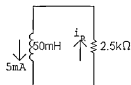

$$i_R = 5e^{t/\tau} \text{ mA}; \quad \tau = \frac{L}{R} = 20 \times 10^{-6}$$

$$i_R = 5e^{-50,000t} \text{ mA}$$

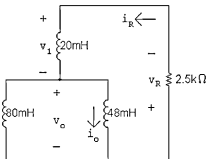

$$v_R = (2.5 \times 10^3)(5 \times 10^{-3})e^{-50,000t} = 12.5e^{-50,000t} \text{ V}$$

$$v_1 = 20 \times 10^{-3}[5 \times 10^{-3}(-50,000)e^{-50,000t}] = -5e^{-50,000t} \text{ V}$$

$$v_o = -v_1 - v_R = -7.5e^{-50,000t} \text{ V}$$

$$[b] \quad i_o = \frac{10^3}{48} \int_0^t -7.5e^{-50,000x} dx + 0 = 3.125e^{-50,000t} - 3.125 \text{ mA}$$

P 5.42 [a] From the solution to Problem 5.41,

$$i_R = 5 \times 10^{-3}e^{-50,000t} \text{ A}$$

$$p_R = (25 \times 10^{-6}e^{-100,000t})(2.5 \times 10^3) = 62.5 \times 10^{-3}e^{-100,000t} \text{ W}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^\infty 62.5 \times 10^{-3}e^{-100,000t} dt \\ &= 62.5 \times 10^{-3} \frac{e^{-100,000t}}{-10^5} \Big|_0^\infty = 625 \text{ nJ} \end{aligned}$$

$$[b] \quad w_{\text{trapped}} = \frac{1}{2} L_{\text{eq}} i_R^2(0) = \frac{1}{2} (50 \times 10^{-3})(5 \times 10^{-3})^2 = 625 \text{ nJ}$$

CHECK:

$$w(0) = \frac{1}{2}(20)(25 \times 10^{-6}) \times 10^{-3} + \frac{1}{2}(80)(25 \times 10^{-6}) \times 10^{-3} = 1250 \text{ nJ}$$

$$\therefore w(0) = w_{\text{diss}} + w_{\text{trapped}}$$

$$P 5.43 [a] \quad i_L(0) = \frac{80}{40} = 2 \text{ A}$$

$$i_o(0^+) = \frac{80}{20} - 2 = 4 - 2 = 2 \text{ A}$$

$$i_o(\infty) = \frac{80}{20} = 4 \text{ A}$$

$$[b] \quad i_L = 2e^{-t/\tau}; \quad \tau = \frac{L}{R} = \frac{20}{20} \times 10^{-3} = 1 \text{ ms}$$

$$i_L = 2e^{-1000t} \text{ A}$$


$$i_o = 4 - i_L = 4 - 2e^{-1000t} \text{ A}, \quad t \geq 0^+$$

$$[c] \quad 4 - 2e^{-1000t} = 3.8$$

$$0.2 = 2e^{-1000t}$$


$$e^{1000t} = 10 \quad \therefore t = 2.30 \text{ ms}$$

P 5.44 [a]  $t < 0$

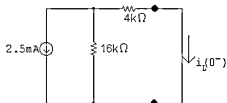

$$i_L(0^-) = \frac{-2.5(16)}{(20)} = -2 \text{ mA}$$

$$t \geq 0$$

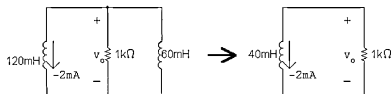

$$\tau = \frac{40 \times 10^{-3}}{10^3} = 40 \times 10^{-6}; \quad 1/\tau = 25,000$$

$$v_o = -1000(-2 \times 10^{-3})e^{-25,000t} = 2e^{-25,000t} \text{ V}, \quad t \geq 0^+$$

$$[b] \quad w_{\text{del}} = \frac{1}{2}(40 \times 10^{-3})(4 \times 10^{-6}) = 80 \text{ nJ}$$

$$[c] \quad 0.95w_{\text{del}} = 76 \text{ nJ}$$


$$\therefore 76 \times 10^{-9} = \int_0^{t_o} \frac{4e^{-50,000t}}{1000} dt$$

$$\therefore 76 \times 10^{-9} = 80 \times 10^{-9} e^{-50,000t} \Big|_0^{t_o} = 80 \times 10^{-9} (1 - e^{-50,000t_o})$$


$$\therefore e^{-50,000t_o} = 0.05$$

$$50,000t_o = \ln 20 \quad \text{so} \quad t_o = 59.9 \mu\text{s}$$

$$\therefore \frac{t_o}{\tau} = \frac{59.9}{40} = 1.498 \quad \text{so} \quad t_o \approx 1.5\tau$$

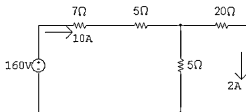P 5.45  $t < 0$ :

$$i_L(0^+) = 2 \text{ A}$$

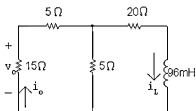 $t > 0$ :

$$R_e = \frac{(20)(5)}{25} + 20 = 24 \Omega$$

$$\tau = \frac{L}{R_e} = \frac{96}{24} \times 10^{-3} = 4 \text{ ms}; \quad \frac{1}{\tau} = 250$$

$$\therefore i_L = 2e^{-250t} \text{ A}$$

$$\therefore i_o = \frac{5}{25} i_L = 0.4e^{-250t} \text{ A}$$

$$v_o = -15i_o = -6e^{-250t} \text{ V}, \quad t \geq 0^+$$

P 5.46  $p_{20\Omega} = 20i_L^2 = 20(4)(e^{-250t})^2 = 80e^{-500t} \text{ W}$ 

$$w_{20\Omega} = \int_0^\infty 80e^{-500t} dt = 80 \frac{e^{-500t}}{-500} \bigg|_0^\infty = 160 \text{ mJ}$$

$$w(0) = \frac{1}{2}(96)(10^{-3})(4) = 192 \text{ mJ}$$

$$\% \text{ diss} = \frac{160}{192}(100) = 83.33\%$$

$$\text{P 5.47} \quad w(0) = \frac{1}{2}(20 \times 10^{-3})(10^2) = 1 \text{ J}$$

$$0.5w(0) = 0.5 \text{ J}$$

$$i_R = 10e^{-t/\tau}$$

$$p_{\text{diss}} = i_R^2 R = 100Re^{-2t/\tau}$$

$$w_{\text{diss}} = \int_0^t R(100)e^{-2x/\tau} dx$$

$$w_{\text{diss}} = 100R \frac{e^{-2x/\tau}}{-2/\tau} \Big|_0^{t_o} = -50\tau R(e^{-2t_o/\tau} - 1) = 50L(1 - e^{-2t_o/\tau})$$

$$50L = (50)(20) \times 10^{-3} = 1; \quad t_o = 10 \mu\text{s}$$

$$1 - e^{-2t_o/\tau} = 0.5$$

$$e^{2t_o/\tau} = 2; \quad \frac{2t_o}{\tau} = \frac{2t_o R}{L} = \ln 2$$

$$R = \frac{L \ln 2}{2t_o} = \frac{20 \times 10^{-3} \ln 2}{20 \times 10^{-6}} = 693.15 \Omega$$

$$\text{P 5.48} \quad [\text{a}] \quad w(0) = \frac{1}{2}LI_g^2$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{t_o} I_g^2 R e^{-2t/\tau} dt = I_g^2 R \frac{e^{-2t/\tau}}{(-2/\tau)} \Big|_0^{t_o} \\ &= \frac{1}{2} I_g^2 R \tau (1 - e^{-2t_o/\tau}) = \frac{1}{2} I_g^2 L (1 - e^{-2t_o/\tau}) \end{aligned}$$

$$w_{\text{diss}} = \sigma w(0)$$

$$\therefore \frac{1}{2} LI_g^2 (1 - e^{-2t_o/\tau}) = \tau \left( \frac{1}{2} LI_g^2 \right)$$

$$1 - e^{-2t_o/\tau} = \sigma; \quad e^{2t_o/\tau} = \frac{1}{(1 - \sigma)}$$

$$\frac{2t_o}{\tau} = \ln \left[ \frac{1}{(1 - \sigma)} \right]; \quad \frac{R(2t_o)}{L} = \ln[1/(1 - \sigma)]$$

$$R = \frac{L \ln[1/(1 - \sigma)]}{2t_o}$$

$$[b] R = \frac{(20 \times 10^{-3}) \ln[1/0.5]}{20 \times 10^{-6}}$$

$$R = 693.15 \Omega$$

P 5.49 [a]  $v_o(t) = v_o(0^+)e^{-t/\tau}$

$$\therefore v_o(0^+)e^{-5 \times 10^{-3}/\tau} = 0.25v_o(0^+)$$

$$\therefore e^{5 \times 10^{-3}/\tau} = 4$$

$$\therefore \tau = \frac{L}{R} = \frac{5 \times 10^{-3}}{\ln 4}$$

$$\therefore L = \frac{250 \times 10^{-3}}{\ln 4} = 180.34 \text{ mH}$$

[b]  $i_L(0^-) = 60 \left( \frac{1}{6} \right) = 10 \text{ mA} = i_L(0^+)$

$$w_{\text{stored}} = \frac{1}{2} L i_L(0^+)^2 = \frac{1}{2} (R\tau) (100 \times 10^{-6}) = 2500\tau \mu\text{J}.$$

$$i_L(t) = 10e^{-t/\tau} \text{ mA}$$

$$p_{50\Omega} = i_L^2(50) = 5000 \times 10^{-6} e^{-2t/\tau}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{5 \times 10^{-3}} 5000 \times 10^{-6} e^{-2t/\tau} dt \\ &= 5000 \times 10^{-6} \left. \frac{e^{-2t/\tau}}{(-2/\tau)} \right|_0^{5 \times 10^{-3}} \\ &= 2500 \times 10^{-6} \tau \left[ 1 - e^{-\frac{10 \times 10^{-3}}{\tau}} \right] \end{aligned}$$


$$e^{-\frac{10 \times 10^{-3}}{\tau}} = e^{-2 \ln 4} = 0.0625$$

$$w_{\text{diss}} = 2500 \times 10^{-6} \tau (0.9375)$$

$$\% \text{ diss} = \frac{2500 \times 10^{-6} \tau (0.9375)}{2500 \times 10^{-6} \tau} \times 100$$

$$w_{\text{diss}} = 93.75\%$$

P 5.50 [a]  $t < 0$

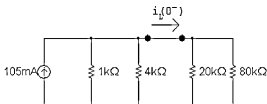


$$1 \text{ k}\Omega \parallel 4 \text{ k}\Omega = 0.8 \text{ k}\Omega$$




$$20\text{ k}\Omega \parallel 80\text{ k}\Omega = 16\text{ k}\Omega$$

$$(105)(0.8) = 84\text{ V}$$

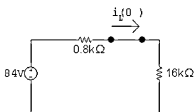

$$i_L(0^-) = \frac{84}{16.8} = 5\text{ mA}$$

$$t > 0$$

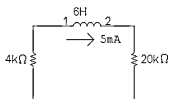

$$\tau = \frac{L}{R} = \frac{6}{24} \times 10^{-3} = 250\text{ }\mu\text{s}; \quad \frac{1}{\tau} = 4000$$

$$i_L(t) = 5e^{-4000t}\text{ mA}, \quad t \geq 0$$

$$p_{4k} = 25 \times 10^{-6} e^{-8000t} (4000) = 0.10e^{-8000t}\text{ W}$$

$$w_{\text{diss}} = \int_0^t 0.10e^{-8000x} dx = 12.5 \times 10^{-6} [1 - e^{-8000t}]\text{ J}$$

$$w(0) = \frac{1}{2}(6)(25 \times 10^{-6}) = 75\text{ }\mu\text{J}$$

$$0.10w(0) = 7.5\text{ }\mu\text{J}$$

$$12.5(1 - e^{-8000t}) = 7.5; \quad \therefore e^{-8000t} = 2.5$$

$$t = \frac{\ln 2.5}{8000} = 114.54\text{ }\mu\text{s}$$

$$[\text{b}] \quad w_{\text{diss}}(\text{total}) = 75(1 - e^{-8000t})\text{ }\mu\text{J}$$

$$w_{\text{diss}}(114.54\text{ }\mu\text{s}) = 45\text{ }\mu\text{J}$$

$$\% = (45/75)(100) = 60\%$$

$$\text{P 5.51} \quad [\text{a}] \quad R = \frac{v}{i} = 20\text{ k}\Omega$$

$$[b] \frac{1}{\tau} = \frac{1}{RC} = 1000; \quad C = \frac{1}{(10^3)(20 \times 10^3)} = 0.05 \mu\text{F}$$

$$[c] \tau = \frac{1}{1000} = 1 \text{ ms}$$

$$[d] w(0) = \frac{1}{2}(0.05 \times 10^{-6})(10^4) = 250 \mu\text{J}$$

[e]

$$\begin{aligned} W_{\text{diss}} &= \int_0^{t_o} \frac{v^2}{R} dt = \int_0^{t_o} \frac{(10^4)e^{-2000t}}{(20 \times 10^3)} dt \\ &= 0.5 \frac{e^{-2000t}}{-2000} \Big|_0^{t_o} = 250(1 - e^{-2000t_o}) \mu\text{J} \end{aligned}$$


$$200 = 250(1 - e^{-2000t_o})$$

$$\therefore e^{-2000t_o} = 0.2; \quad e^{2000t_o} = 5$$

$$t_o = \frac{1}{2000} \ln 5; \quad t_o \cong 804.72 \mu\text{s}$$


P 5.52 [a]  $v_1(0^-) = v_1(0^+) = 75 \text{ V} \quad v_2(0^+) = 0$
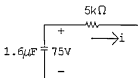
$$C_{\text{eq}} = 2 \times 8/10 = 1.6 \mu\text{F}$$



$$\tau = (5)(1.6) \times 10^{-3} = 8 \text{ ms}; \quad \frac{1}{\tau} = 125$$
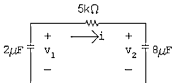
$$i = \frac{75}{5} \times 10^{-3} e^{-125t} = 15e^{-125t} \text{ mA}, \quad t \geq 0^+$$



$$v_1 = \frac{-10^6}{2} \int_0^t 15 \times 10^{-3} e^{-125x} dx + 75 = 60e^{-125t} + 15 \text{ V}, \quad t \geq 0$$

$$v_2 = \frac{10^6}{8} \int_0^t 15 \times 10^{-3} e^{-125x} dx + 0 = -15e^{-125t} + 15 \text{ V}, \quad t \geq 0$$


$$[b] \quad w(0) = \frac{1}{2}(2 \times 10^{-6})(5625) = 5625 \mu\text{J}$$

$$[c] \quad w_{\text{trapped}} = \frac{1}{2}(2 \times 10^{-6})(225) + \frac{1}{2}(8 \times 10^{-6})225 = 1125 \mu\text{J}.$$

$$w_{\text{diss}} = \frac{1}{2}(1.6 \times 10^{-6})(5625) = 4500 \mu\text{J}.$$

$$\text{Check: } w_{\text{trapped}} + w_{\text{diss}} = 1125 + 4500 = 5625 \mu\text{J}; \quad w(0) = 5625 \mu\text{J}.$$

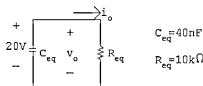P 5.53 [a] The equivalent circuit for  $t > 0$ :



$$\tau = 0.4 \text{ ms}; \quad 1/\tau = 2500$$

$$v_o = 20e^{-2500t} \text{ V}, \quad t \geq 0$$

$$i_o = 2e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

$$i_{25\text{k}\Omega} = 2e^{-2500t} \left( \frac{15}{40} \right) = 0.75e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

$$p_{25\text{k}\Omega} = (0.5625 \times 10^{-6} e^{-5000t})(25,000) = 14,062.5 \times 10^{-6} e^{-5000t} \text{ W}$$

$$w_{25\text{k}\Omega} = \int_0^\infty 14,062.5 \times 10^{-6} e^{-5000t} dt = -2.8125 \times 10^{-6} (0 - 1) = 2.8125 \mu\text{J}$$

$$w(0) = \frac{1}{2}(0.2 \times 10^{-6})(100) + \frac{1}{2}(0.05 \times 10^{-6})(900) = 32.5 \mu\text{J}$$

$$\% \text{ diss } (25 \text{ k}\Omega) = \frac{2.8125}{32.5} \times 100 = 8.65\%$$

$$[b] \quad p_{625\Omega} = 625(2 \times 10^{-3} e^{-2500t})^2 = 2.5 \times 10^{-3} e^{-5000t}$$

$$w_{625\Omega} = \int_0^\infty p_{625\Omega} dt = 0.50 \mu\text{J}$$

$$\% \text{ diss } (625\Omega) = \frac{0.5}{32.5} \times 100 = 1.54\%$$

$$i_{15\text{k}\Omega} = 2e^{-2500t} \left( \frac{25}{40} \right) = 1.25e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

$$p_{15\text{k}\Omega} = (1.25 \times 10^{-3} e^{-2500t})^2 (15,000) = 23.4375 \times 10^{-3} e^{-5000t} \text{ W}$$

$$w_{15\text{k}\Omega} = \int_0^\infty 23.4375 \times 10^{-3} e^{-5000t} dt = 4.6875 \mu\text{J}$$

$$\% \text{ diss } (15\text{k}\Omega) = 14.42\%$$

$$[c] \sum w_{\text{diss}} = 2.8125 + 0.50 + 4.6875 = 8 \mu\text{J}$$

$$w_{\text{trapped}} = w(0) - \sum w_{\text{diss}} = 32.5 - 8 = 24.5 \mu\text{J}$$


$$\% \text{ trapped} = \frac{24.5}{32.5} \times 100 = 75.38\%$$

$$\text{Check: } 8.65 + 1.54 + 14.42 + 75.38 = 99.99 \approx 100\%$$

$$\text{P 5.54 } [a] \frac{1}{C_e} = 1 + \frac{1}{4} = 1.25$$

$$\therefore C_e = 0.8 \mu\text{F}; \quad v_o(0) = 60 - 10 = 50 \text{ V}$$
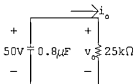
$$\tau = (0.8)(25) \times 10^{-3} = 20 \text{ ms}; \quad \frac{1}{\tau} = 50$$



$$v_o = 50e^{-50t} \text{ V}, \quad t > 0^+$$

$$[b] w_o = \frac{1}{2}(1 \times 10^{-6})(3600) + \frac{1}{2}(4 \times 10^{-6})(100) = 2 \text{ mJ}$$

$$w_{\text{diss}} = \frac{1}{2}(0.8 \times 10^{-6})(2500) = 1 \text{ mJ}$$

$$\% \text{ diss} = \frac{1}{2} \times 100 = 50\%$$

$$[c] i_o = \frac{v_o}{25} \times 10^{-3} - 2e^{-50t} \text{ mA}$$

$$\begin{aligned} v_1 &= -\frac{10^6}{4} \int_0^t 2 \times 10^{-3} e^{-50x} dx - 10 = -500 \int_0^t e^{-50x} dx - 10 \\ &= -500 \left. \frac{e^{-50x}}{-50} \right|_0^t - 10 = 10e^{-50t} - 20 \text{ V} \quad t \geq 0 \end{aligned}$$


$$[d] v_1 + v_2 = v_o$$

$$v_2 = v_o - v_1 = 50e^{-50t} - 10e^{-50t} + 20 = 40e^{-50t} + 20 \text{ V} \quad t \geq 0$$

$$[e] w_{\text{trapped}} = \frac{1}{2}(4 \times 10^{-6})(400) + \frac{1}{2}(1 \times 10^{-6})(400) = 1 \text{ mJ}$$

$$w_{\text{diss}} + w_{\text{trapped}} = 2 \text{ mJ} \quad (\text{check})$$

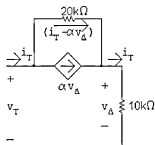P 5.55 [a]  $\tau = RC = R_{Th}(0.2) \times 10^{-6} = 10^{-3}$ ;  $\therefore R_{Th} = \frac{1000}{0.2} = 5 \text{ k}\Omega$



$$v_T = 20 \times 10^3(i_T - \alpha v_\Delta) + 10 \times 10^3 i_T$$


$$v_\Delta = 10 \times 10^3 i_T$$

$$v_T = 30 \times 10^3 i_T - 20 \times 10^3 \alpha 10 \times 10^3 i_T$$


$$\frac{v_T}{i_T} = 30 \times 10^3 - 200 \times 10^6 \alpha = 5 \times 10^3$$

$$\therefore 30 - 200,000\alpha = 5; \quad \alpha = 125 \times 10^{-6} \text{ A/V}$$

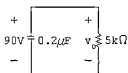[b]  $v_o(0) = (0.018)(5000) = 90 \text{ V} \quad t < 0$   
 $t > 0$ :


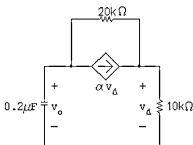
$$v_o = 90e^{-1000t} \text{ V}, \quad t \geq 0$$




$$\frac{v_\Delta}{10 \times 10^3} + \frac{v_\Delta - v_o}{20,000} - 125 \times 10^{-6} v_\Delta = 0$$

$$2v_\Delta + v_\Delta - v_o - 2500 \times 10^{-3} v_\Delta = 0$$

$$\therefore v_\Delta = 2v_o = 180e^{-1000t} \text{ V}$$

P 5.56 [a]

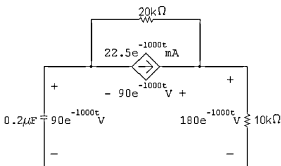

$$p_{ds} = (-90e^{-1000t})(22.5 \times 10^{-3}e^{-1000t}) = -2025 \times 10^{-3}e^{-2000t} \text{ W}$$

$$w_{ds} = \int_0^{\infty} p_{ds} dt = -1012.5 \mu\text{J}.$$

$\therefore$  dependent source is delivering  $1012.5 \mu\text{J}$

$$[b] p_{10k} = \frac{(180)^2 e^{-2000t}}{10 \times 10^3}$$

$$w_{10k} = \int_0^{\infty} p_{10k} dt = 1620 \mu\text{J}$$


$$p_{20k} = \frac{(90)^2 e^{-2000t}}{20 \times 10^3}$$

$$w_{20k} = \int_0^{\infty} p_{20k} dt = 202.5 \mu\text{J}$$

$$w_c(0) = \frac{1}{2}(0.2) \times 10^{-6}(90)^2 = 810 \mu\text{J}$$


$$\sum w_{dev} = 810 + 1012.5 = 1822.5 \mu\text{J}$$

$$\sum w_{diss} = 202.5 + 1620 = 1822.5 \mu\text{J}.$$

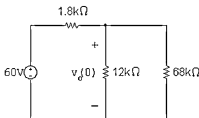P 5.57 [a]  $t < 0$ :

$$v_o(0) = \frac{(60)(10.2)}{12} = 51 \text{ V}$$

$t > 0$ :

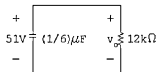

$$\tau = \frac{1}{6}(12) \times 10^{-3} = 2 \text{ ms}; \quad \frac{1}{\tau} = 500$$

$$v_o = 51e^{-500t} \text{ V}, \quad t \geq 0$$

$$p = \frac{v_o^2}{12} \times 10^{-3} = 216.75 \times 10^{-3} e^{-1000t} \text{ W}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{2 \times 10^{-3}} 216.75 \times 10^{-3} e^{-1000t} dt = 216.75 \times 10^{-6} (1 - e^{-2}) \\ &= 187.42 \mu\text{J} \end{aligned}$$

[b]  $w(0) = \left(\frac{1}{2}\right) \left(\frac{1}{6}\right) (51)^2 \times 10^{-6} = 216.75 \mu\text{J}$


$$0.95w(0) = 205.9125 \mu\text{J}$$

$$\int_0^{t_o} 216.75 \times 10^{-3} e^{-1000x} dx = 205.9125 \times 10^{-6}$$

$$\int_0^{t_o} e^{-1000x} dx = 0.95 \times 10^{-3}$$

$$\therefore 1 - e^{-1000t_o} = 0.95; \quad e^{1000t_o} = 20; \quad \text{so } t_o = 3 \text{ ms}$$

P 5.58 [a]  $t < 0$ :

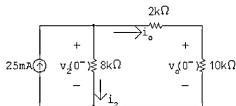


$$i_o(0^-) = \frac{(25)(8)}{(20)} = 10 \text{ mA}$$


$$v_o(0^-) = (10)(10) = 100 \text{ V}$$

$$i_2(0^-) = 25 - 10 = 15 \text{ mA}$$

$$v_2(0^-) = 15(8) = 120 \text{ V}$$

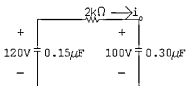
$t > 0$ 
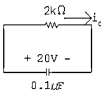
$$\tau = RC = 0.2 \text{ ms} = 200 \mu\text{s}; \quad \frac{1}{\tau} = 5000$$



$$i_o(t) = \frac{20}{2 \times 10^3} e^{-t/\tau} = 10e^{-5000t} \text{ mA}, \quad t \geq 0^+$$

[b]

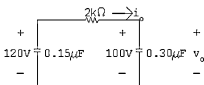

$$\begin{aligned} v_o &= \frac{10^6}{0.3} \int_0^t 10 \times 10^{-3} e^{-5000x} dx + 100 \\ &= \frac{10^5}{3} \frac{e^{-5000x}}{-5000} \Big|_0^t + 100 \\ &= -(20/3)e^{-5000t} + (20/3) + 100 \\ v_o &= [-(20/3)e^{-5000t} + (320/3)] \text{ V}, \quad t \geq 0 \end{aligned}$$

$$[c] \quad w_{\text{trapped}} = (1/2)(0.15) \times 10^{-6}(320/3)^2 + (1/2)(0.3) \times 10^{-6}(320/3)^2$$

$$w_{\text{trapped}} = 2560 \mu\text{J}.$$

Check:

$$w_{\text{diss}} = \frac{1}{2}(0.1 \times 10^{-6})(20)^2 = 20 \mu\text{J}$$

$$w(0) = \frac{1}{2}(0.15) \times 10^{-6}(120)^2 + \frac{1}{2}(0.3 \times 10^{-6})(100)^2 = 2580 \mu\text{J}.$$

$$w_{\text{trapped}} + w_{\text{diss}} = w(0)$$

$$2560 + 20 = 2580 \quad \text{OK.}$$



P 5.59 [a]  $v(0) = \frac{(8)(27)(33)}{60} = 118.80 \text{ V}$

$$R_e = \frac{(3)(6)}{9} = 2 \text{ k}\Omega$$

$$\tau = R_e C = (2000)(0.25) \times 10^{-6} = 500 \mu\text{s}; \quad \frac{1}{\tau} = 2000$$

$$v = 118.80e^{-2000t} \text{ V} \quad t \geq 0$$

$$i_o = \frac{v}{3000} = 39.6e^{-2000t} \text{ mA}, \quad t \geq 0^+$$

[b]  $w(0) = \frac{1}{2}(0.25)(118.80)^2 = 1764.18 \mu\text{J}$

$$i_{4k} = \frac{118.80e^{-2000t}}{6} = 19.8e^{-2000t} \text{ mA}$$


$$p_{4k} = [(19.8)e^{-2000t}]^2(4000) \times 10^{-6} = 1568.16 \times 10^{-3}e^{-4000t}$$

$$w_{4k} = 1568.16 \times 10^{-3} \frac{e^{-4000t}}{-4000} \bigg|_0^{250 \times 10^{-6}} = 392.04(1 - e^{-1}) \mu\text{J}$$

$$= 247.82 \mu\text{J}$$

$$\% = \frac{247.82}{1764.18} \times 100 = 14.05\%$$

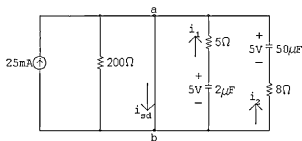P 5.60 [a] At  $t = 0^-$  the voltage on each capacitor will be  $5 \text{ V}(25 \times 10^{-3} \times 200)$ , positive at the upper terminal. Hence at  $t \geq 0^+$  we have



$$\therefore i_{sd}(0^+) = 0.025 + \frac{5}{5} + \frac{5}{8} = 1.65 \text{ A}$$

At  $t = \infty$ , both capacitors will have completely discharged.

$$\therefore i_{sd}(\infty) = 25 \text{ mA}$$

$$[b] \quad i_{sd}(t) = 0.025 + i_1(t) + i_2(t)$$

$$\tau_1 = (5)(2) \times 10^{-6} = 10 \mu s$$


$$\tau_2 = (8)(50 \times 10^{-6}) = 400 \mu s$$

$$\therefore i_1(t) = e^{-10^5 t} \text{ A}, \quad t \geq 0^+$$


$$i_2(t) = 0.625e^{-2500t} \text{ A}, \quad t \geq 0$$

$$\therefore i_{sd} = 25 + 1000e^{-100,000t} + 625e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

P 5.61  $t < 0$

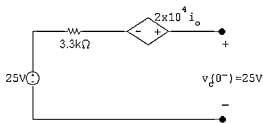


$t > 0$

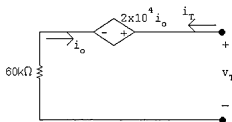

$$v_T = 2 \times 10^4 i_o + 60,000 i_T$$

$$= 20,000(-i_T) + 60,000 i_T = 40,000 i_T$$
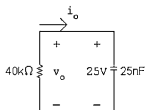
$$\therefore \frac{v_T}{i_T} = R_{Th} = 40 \text{ k}\Omega$$




$$\tau = RC = 1 \text{ ms}; \quad \frac{1}{\tau} = 1000$$

$$v_o = 25e^{-1000t} \text{ V}, \quad t \geq 0$$

$$i_o = 25 \times 10^{-9} \frac{d}{dt} [25e^{-1000t}] = -625e^{-1000t} \mu\text{A}, \quad t \geq 0^+$$

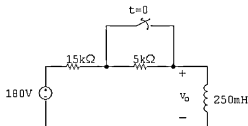P 5.62 After making a Thévenin equivalent we have



$$I_o = 180/15 = 12 \text{ mA}$$

$$\tau = (0.25/20) \times 10^{-3} = 0.125 \times 10^{-4}; \quad \frac{1}{\tau} = 80,000$$

$$\frac{V_s}{R} = \frac{180}{20} = 9 \text{ mA}$$

$$i_o = 9 + (12 - 9)e^{-80,000t} = 9 + 3e^{-80,000t} \text{ mA}$$

$$v = [180 - 12(20)]e^{-80,000t} = -60e^{-80,000t} \text{ V}$$

P 5.63 [a]  $v_o(0^+) = -I_g R_2; \quad \tau = \frac{L}{R_1 + R_2}$

$$v_o(\infty) = 0$$

$$v_o(t) = -I_g R_2 e^{-[(R_1 + R_2)/L]t} \text{ V}, \quad t \geq 0$$

[b]  $v_o = -(12 \times 10^{-3})(5 \times 10^3)e^{-[\frac{15,000 + 5000}{0.25}]t} = -60e^{-80,000t} \text{ V}, \quad t \geq 0$

[c]  $v_o(0^+) \rightarrow \infty$ , and the duration of  $v_o(t) \rightarrow 0$

[d]  $v_{sw} = R_2 i_o; \quad \tau = \frac{L}{R_1 + R_2}$


$$i_o(0^+) = I_g; \quad i_o(\infty) = I_g \frac{R_1}{R_1 + R_2}$$

$$\text{Therefore} \quad i_o(t) = \frac{I_g R_1}{R_1 + R_2} + \left[ I_g - \frac{I_g R_1}{R_1 + R_2} \right] e^{-[(R_1 + R_2)/L]t}$$

$$i_o(t) = \frac{R_1 I_g}{(R_1 + R_2)} + \frac{R_2 I_g}{(R_1 + R_2)} e^{-[(R_1 + R_2)/L]t}$$

$$\text{Therefore} \quad v_{sw} = \frac{R_1 I_g}{(1 + R_1/R_2)} + \frac{R_2 I_g}{(1 + R_1/R_2)} e^{-[(R_1 + R_2)/L]t}, \quad t \geq 0$$

$$[e] \quad |v_{sw}(0^+)| \rightarrow \infty; \quad \text{duration} \rightarrow 0$$

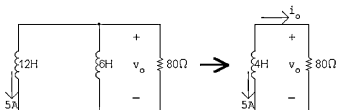P 5.64  $t > 0$ 

$$\tau = \frac{4}{80} = \frac{1}{20}$$

$$i_o = -5e^{-20t} \text{ A}, \quad t \geq 0$$

$$v_o = 80i_o = -400e^{-20t} \text{ V}, \quad t > 0^+$$

$$-400e^{-20t} = -80; \quad e^{20t} = 5$$

$$\therefore t = \frac{1}{20} \ln 5 = 80.47 \text{ ms}$$

P 5.65 [a]  $w_{\text{diss}} = \frac{1}{2} L_e \dot{i}^2(0) = \frac{1}{2} (4) (25) = 50 \text{ J}$


[b]

$$\begin{aligned} i_{12H} &= \frac{1}{12} \int_0^t (-400) e^{-20x} dx + 5 \\ &= \frac{-100}{3} \frac{e^{-20x}}{-20} \Big|_0^t + 5 = \frac{5}{3} e^{-20t} + \frac{10}{3} \text{ A} \end{aligned}$$

$$\begin{aligned} i_{6H} &= \frac{1}{6} \int_0^t (-400) e^{-20x} dx + 0 \\ &= \frac{-200}{3} \frac{e^{-20x}}{-20} \Big|_0^t + 0 = \frac{10}{3} e^{-20t} - \frac{10}{3} \text{ A} \end{aligned}$$

$$w_{\text{trapped}} = \frac{1}{2} (18) (100/9) = 100 \text{ J}$$

[c]  $w(0) = \frac{1}{2} (12) (25) = 150 \text{ J}$

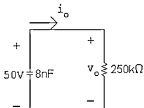P 5.66 [a] For  $t > 0$ :

$$\tau = RC = 250 \times 10^3 \times 8 \times 10^{-9} = 2 \text{ ms}; \quad \frac{1}{\tau} = 500$$

$$v_o = 50e^{-500t} \text{ V}, \quad t \geq 0^+$$

$$[b] \quad i_o = \frac{v_o}{250} \times 10^{-3} = \frac{50e^{-500t}}{250} \times 10^{-3} = 200e^{-500t} \mu\text{A}$$


$$v_1 = -\frac{10^9}{40} \times 200 \times 10^{-6} \int_0^t e^{-500x} dx + 50 = 10e^{-500t} + 40 \text{ V}, \quad t \geq 0$$

$$\text{P 5.67 [a]} \quad w = \frac{1}{2} C_e v_e^2 = \frac{1}{2} (8 \times 10^{-9}) (2500) = 10 \mu\text{J}$$

$$[b] \quad w_{\text{trapped}} = \frac{1}{2} (40)^2 (50) \times 10^{-9} = 40 \mu\text{J}$$

$$[c] \quad w(0) = \frac{1}{2} (40 \times 10^{-9}) (2500) = 50 \mu\text{J}$$

P 5.68 For  $t < 0$

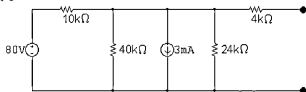


$$80/10,000 = 8 \text{ mA}, \quad 10 \text{ k}\Omega \parallel 40 \text{ k}\Omega \parallel 24 \text{ k}\Omega = 6 \text{ k}\Omega$$

$$8 \text{ mA} - 3 \text{ mA} = 5 \text{ mA}$$


$$5 \text{ mA} \times 6 \text{ k}\Omega = 30 \text{ V}$$

$t < 0$

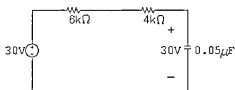


$$\therefore v_o(0^-) = v_o(0^+) = 30 \text{ V}$$

$t > 0$

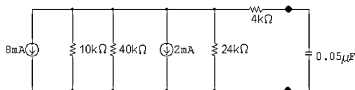
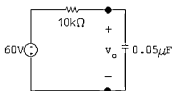
$$v_o(\infty) = -10 \times 10^{-3} (6 \times 10^3) = -60 \text{ V}$$




$$\tau = 0.5 \text{ ms}; \quad \frac{1}{\tau} = 2000$$


$$v_o = -60 + (30 - (-60))e^{-2000t}$$

$$v_o = -60 + 90e^{-2000t} \text{ V} \quad t \geq 0$$

P 5.69 [a]  $t < 0$

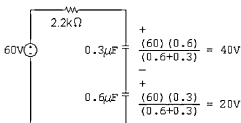

$t > 0$

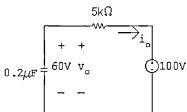

$$v_o(0^-) = v_o(0^+) = 60 \text{ V}$$

$$v_o(\infty) = 100 \text{ V}$$

$$\tau = (0.2)(5) \times 10^{-3} = 1 \text{ ms}; \quad 1/\tau = 1000$$

$$v_o = 100 - 40e^{-1000t} \text{ V}, \quad t \geq 0$$

$$[b] \quad i_o = -C \frac{dv_o}{dt} = -0.2 \times 10^{-6} [40,000e^{-1000t}]$$


$$= -8e^{-1000t} \text{ mA}; \quad t \geq 0^+$$

$$\begin{aligned}
 \text{[c]} \quad v_1 &= \frac{-10^6}{0.3} \int_0^t -8 \times 10^{-3} e^{-1000x} dx + 40 \\
 &= 66.67 - 26.67e^{-1000t} \text{ V}, \quad t \geq 0
 \end{aligned}$$

$$\begin{aligned}
 \text{[d]} \quad v_2 &= \frac{-10^6}{0.6} \int_0^t -8 \times 10^{-3} e^{-1000x} dx + 20 \\
 &= 33.33 - 13.33e^{-1000t} \text{ V}, \quad t \geq 0
 \end{aligned}$$

$$\begin{aligned}
 \text{[e]} \quad w_{\text{trapped}} &= \frac{1}{2}(0.3)10^{-6}(66.67)^2 + \frac{1}{2}(0.6)10^{-6}(33.33)^2 \\
 &= 666.67 + 333.33 = 1000 \mu\text{J}.
 \end{aligned}$$

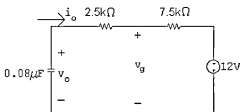P 5.70 [a]  $v_o(0^-) = v_o(0^+) = 48 \text{ V}$



$$v_o(\infty) = -12 \text{ V}; \quad \tau = 0.8 \text{ ms}; \quad \frac{1}{\tau} = 1250$$

$$v_o = -12 + (48 - (-12))e^{-1250t}$$

$$v_o = -12 + 60e^{-1250t} \text{ V}, \quad t \geq 0$$

$$\text{[b]} \quad i_o = -0.08 \times 10^{-6} [-75,000e^{-1250t}]$$

$$i_o = 6e^{-1250t} \text{ mA}, \quad t \geq 0^+$$

$$\text{[c]} \quad v_g = v_o - 2.5 \times 10^3 i_o$$

$$v_g = -12 + 45e^{-1250t} \text{ V}$$

$$\text{[d]} \quad v_g(0^+) = -12 + 45 = 33 \text{ V}$$

Checks:

$$v_g(0^+) = i_o(0^+)7.5 \times 10^3 - 12 = 45 - 12 = 33 \text{ V}$$

$$i_{10k} = \frac{v_g}{10k} = -1.2 + 4.5e^{-1250t} \text{ mA}$$

$$i_{30k} = \frac{v_g}{30k} = -0.4 + 1.5e^{-1250t} \text{ mA}$$

$$-i_o + i_{10} + i_{30} + 1.6 = 0 \quad (\text{ok})$$

P 5.71 [a]  $0 \leq t \leq 1 \text{ ms}$ :

$$v_c(0^+) = 0; \quad v_c(\infty) = 50 \text{ V};$$

$$RC = 400 \times 10^3(0.01 \times 10^{-6}) = 4 \text{ ms}; \quad 1/RC = 250$$

$$v_c = 50 - 50e^{-250t}$$

$$v_o = 50 - 50 + 50e^{-250t} = 50e^{-250t} \text{ V}, \quad 0 \leq t \leq 1 \text{ ms}$$

$$1 \text{ ms} \leq t \leq \infty:$$

$$v_c(1 \text{ ms}) = 50 - 50e^{-0.25} = 11.06 \text{ V}$$


$$v_c(\infty) = 0 \text{ V}$$

$$\tau = 4 \text{ ms}; \quad 1/\tau = 250$$

$$v_c = 11.06e^{-250(t-0.001)} \text{ V}$$

$$v_o = -v_c = -11.06e^{-250(t-0.001)} \text{ V}, \quad 1 \text{ ms} \leq t \leq \infty$$

[b]

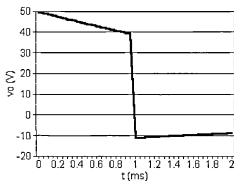P 5.72 [a]  $t < 0$ ;  $v_o = 0$ 

$$0 \leq t \leq 10 \text{ ms}:$$

$$\tau = (50)(0.4) \times 10^{-3} = 20 \text{ ms}; \quad 1/\tau = 50$$

$$v_o = 40 - 40e^{-50t} \text{ V}, \quad 0 \leq t \leq 10 \text{ ms}$$

$$v_o(10 \text{ ms}) = 40(1 - e^{-0.5}) = 15.74 \text{ V}$$

$$10 \text{ ms} \leq t \leq 20 \text{ ms}:$$

$$v_o = -40 + 55.74e^{-50(t-0.01)} \text{ V}$$


$$v_o(20 \text{ ms}) = -40 + 55.74e^{-0.5} = -6.19 \text{ V}$$

$$20 \text{ ms} \leq t \leq \infty:$$

$$v_o = -6.19e^{-50(t-0.02)} \text{ V}$$



[b]

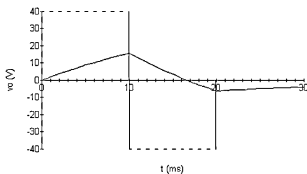[c]  $t \leq 0$ :  $v_o = 0$  $0 \leq t \leq 10$  ms:

$$\tau = 10(0.4 \times 10^{-3}) = 4 \text{ ms}$$

$$v_o = 40 - 40e^{-250t} \text{ V}, \quad 0 \leq t \leq 10 \text{ ms}$$

$$v_o(10 \text{ ms}) = 40 - 40e^{-2.5} = 36.72 \text{ V}$$


 $10 \text{ ms} \leq t \leq 20$  ms:

$$v_o = -40 + 76.72e^{-250(t-0.01)} \text{ V}, \quad 10 \text{ ms} \leq t \leq 20 \text{ ms}$$

$$v_o(20 \text{ ms}) = -40 + 76.72e^{-2.5} = -33.7 \text{ V}$$

 $20 \text{ ms} \leq t \leq \infty$ :
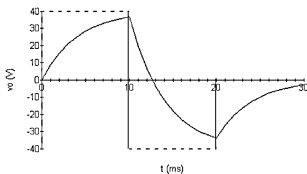
$$v_o = -33.7e^{-250(t-0.02)} \text{ V}, \quad 20 \text{ ms} \leq t \leq \infty$$



$$\text{P 5.73} \quad \frac{1}{R_s C_f} = \frac{10^6}{50 \times 10^3(0.05)} = 400$$

Therefore,

$$\begin{aligned}v_o &= -400 \int_0^t 75 \cos 5000x \, dx + 0 \\&= -30,000 \left[ \frac{1}{5000} \sin 5000x \right]_0^t \\&= -6 \sin 5000t \text{ V}\end{aligned}$$

P 5.74 [a] For  $0 \leq t \leq 25$  ms:

$$\begin{aligned}v_s &= \frac{600}{25}t = 24t \\ \frac{1}{R_s C_f} &= \frac{(10^6)(10^{-3})}{(7.5)(0.16)} = \frac{1000}{1.2} \\ \therefore v_o &= -\frac{1000}{1.2} \int_0^t 24x \, dx + 0 \\&= -20,000 \left[ \frac{x^2}{2} \right]_0^t \\&= -10^4 t^2 \text{ V} \quad 0 \leq t \leq 25 \text{ ms}\end{aligned}$$


[b] For  $25 \text{ ms} \leq t \leq 75 \text{ ms}$ :

$$\begin{aligned}v_s &= 1.2 - 24t \\ v_o(25 \text{ ms}) &= -10^4(625 \times 10^{-6}) = -6.25 \text{ V} \\ \therefore v_o &= -\frac{1000}{1.2} \int_{25 \times 10^{-3}}^t (1.2 - 24x) \, dx - 6.25 \\&= -\frac{1000}{1.2} \left[ 1.2x - \frac{24x^2}{2} \right]_{25 \times 10^{-3}}^t - 6.25 \\&= 10^4 t^2 - 10^3 t + 12.5 \text{ V} \quad 25 \text{ ms} \leq t \leq 75 \text{ ms} \\ v_o(75 \text{ ms}) &= -10^4(5625 \times 10^{-6}) - 75 + 12.5 = -6.25 \text{ V}\end{aligned}$$

[c] For  $75 \text{ ms} \leq t \leq 100 \text{ ms}$ :

$$\begin{aligned}v_o &= -\frac{1000}{1.2} \int_{75 \times 10^{-3}}^t (-2.4 + 24x) \, dx - 6.25 \\&= -10^4 t^2 + 2000t - 100 \text{ V} \quad 75 \text{ ms} \leq t \leq 100 \text{ ms}\end{aligned}$$

[d]

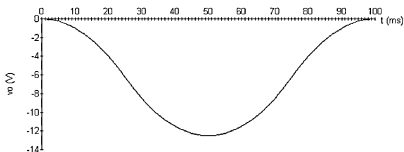

P 5.75 [a]  $v_o(t_1) = \frac{4 \times 10^6}{0.8R}(0.25) = 10$

$$\therefore R = \frac{10^6}{8} = 125 \text{ k}\Omega$$

[b]  $t_2 - t_1 = \frac{4}{10}(250) = 100 \text{ ms}$

P 5.76 [a]  $t_2 - t_1 = \frac{3.6}{10}(250) = 90 \text{ ms}$

$$N_2 = \frac{90}{1000}(10^5) = 9000 \text{ pulses}$$

[b] From (a) we have 9000/3.6 or 2500 pulses/volt.

$$\therefore 7000 \text{ pulses corresponds to } 7000/2500 = 2.8 \text{ V}$$

$$\therefore v_a = 2.8 \text{ V}$$

P 5.77 Summing the currents at the inverting input terminal yields

$$\frac{0 - v_{\text{ref}}}{R_{\text{ref}}} + \frac{0 - v_x}{R_x} = 0$$

Solving for  $v_x$  gives

$$v_x = -\left(\frac{V_{\text{ref}}}{R_{\text{ref}}}\right) R_x$$

Since  $(V_{\text{ref}}/R_{\text{ref}})$  is a constant fixed by the circuit designer we see that  $v_x$  is directly proportional to the unknown resistance  $R_x$ .

*This page intentionally left blank*

# 6

## Natural and Step Responses of *RLC* Circuits

### Drill Exercises

DE 6.1 [a]  $\frac{1}{(2RC)^2} = \frac{1}{LC}$ , therefore  $C = 500 \text{ nF}$

[b]  $\alpha = 5000 = \frac{1}{2RC}$ , therefore  $C = 1 \mu\text{F}$

$$s_{1,2} = -5000 \pm \sqrt{25 \times 10^6 - \frac{(10^3)(10^6)}{20}} = (-5000 \pm j5000) \text{ rad/s}$$

[c]  $\frac{1}{\sqrt{LC}} = 20,000$ , therefore  $C = 125 \text{ nF}$

$$s_{1,2} = \left[ -40 \pm \sqrt{(40)^2 - 20^2} \right] 10^3,$$

$$s_1 = -5.36 \text{ krad/s}, \quad s_2 = -74.64 \text{ krad/s}$$

$$\begin{aligned} \text{DE 6.2} \quad i_L &= \frac{1000}{50} \int_0^t [-14e^{-5000x} + 26e^{-20,000x}] dx + 30 \times 10^{-3} \\ &= 20 \left\{ \left. \frac{-14e^{-5000x}}{-5000} \right|_0^t + \left. \frac{26e^{-20,000x}}{-20,000} \right|_0^t \right\} + 30 \times 10^{-3} \\ &= 56 \times 10^{-3} (e^{-5000t} - 1) - 26 \times 10^{-3} (e^{-20,000t} - 1) + 30 \times 10^{-3} \\ &= [56e^{-5000t} - 56 - 26e^{-20,000t} + 26 + 30] \text{ mA} \\ &= 56e^{-5000t} - 26e^{-20,000t} \text{ mA}, \quad t \geq 0 \end{aligned}$$

DE 6.3 From the given values of  $R$ ,  $L$ , and  $C$ ,  $s_1 = -10 \text{ krad/s}$  and  $s_2 = -40 \text{ krad/s}$ .

[a]  $v(0^-) = v(0^+) = 0$ , therefore  $i_R(0^+) = 0$

$$[b] \quad i_C(0^+) = 4 \text{ A}$$

$$[c] \quad C \frac{dv_C(0^+)}{dt} = 4, \quad \text{therefore} \quad \frac{dv_C(0^+)}{dt} = 4 \times 10^8 \text{ V/s}$$

$$[d] \quad v = [A_1 e^{-10,000t} + A_2 e^{-40,000t}] \text{ V}, \quad t \geq 0^+$$

$$v(0^+) = A_1 + A_2, \quad \frac{dv(0^+)}{dt} = -10,000A_1 - 40,000A_2$$

$$\text{Therefore} \quad A_1 + A_2 = 0, \quad -A_1 - 4A_2 = 40,000, \quad A_1 = 40,000/3$$

$$[e] \quad A_2 = -40,000/3$$

$$[f] \quad v = [40,000/3][e^{-10,000t} - e^{-40,000t}] \text{ V}, \quad t \geq 0^+$$

$$\text{DE 6.4} \quad [a] \quad \frac{1}{2RC} = 8000, \quad \text{therefore} \quad R = 62.5 \, \Omega$$

$$[b] \quad i_R(0^+) = \frac{10}{62.5} = 160 \text{ mA}$$

$$i_C(0^+) = -80 - 160 = -240 \text{ mA}, \quad i_C(0^+) = C \frac{dv(0^+)}{dt}$$

$$\text{Therefore} \quad \frac{dv(0^+)}{dt} = -240 \text{ kV/s}$$

$$[c] \quad B_1 = v(0^+) = 10 \text{ V}, \quad \frac{dv_C(0^+)}{dt} = \omega_d B_2 - \alpha B_1$$

$$\text{Therefore} \quad 6000B_2 - 8000B_1 = -240,000, \quad B_2 = (-80/3) \text{ V}$$

$$[d] \quad i_L = -(i_R + i_C); \quad i_R = v/R; \quad i_C = C \frac{dv}{dt}$$

$$v = e^{-8000t} [10 \cos 6000t - \frac{80}{3} \sin 6000t] \text{ V}$$

$$\text{Therefore} \quad i_R = e^{-8000t} [160 \cos 6000t - \frac{1280}{3} \sin 6000t] \text{ mA}$$

$$i_C = e^{-8000t} [-240 \cos 6000t + \frac{460}{3} \sin 6000t] \text{ mA}$$

$$i_L = 10e^{-8000t} [8 \cos 6000t + \frac{82}{3} \sin 6000t] \text{ mA}, \quad t \geq 0$$

$$\text{DE 6.5} \quad [a] \quad \left( \frac{1}{2RC} \right)^2 = \frac{1}{LC} = \frac{10^6}{4}, \quad \text{therefore} \quad \frac{1}{2RC} = 500, \quad R = 100 \, \Omega$$

$$[b] \quad 0.5CV_0^2 = 12.5 \times 10^{-3}, \quad \text{therefore} \quad V_0 = 50 \text{ V}$$

$$[c] \quad 0.5LI_0^2 = 12.5 \times 10^{-3}, \quad I_0 = 250 \text{ mA}$$

$$[d] \quad D_2 = v(0^+) = 50, \quad \frac{dv(0^+)}{dt} = D_1 - \alpha D_2$$

$$i_R(0^+) = \frac{50}{100} = 500 \text{ mA}$$

$$\text{Therefore } i_C(0^+) = -(500 + 250) = -750 \text{ mA}$$

$$\text{Therefore } \frac{dv(0^+)}{dt} = -750 \times \frac{10^{-3}}{C} = -75,000 \text{ V/s}$$

$$\text{Therefore } D_1 - \alpha D_2 = -75,000;$$

$$\alpha = \frac{1}{2RC} = 500, \quad D_1 = -50,000 \text{ V/s}$$

$$[e] \quad v = [50e^{-500t} - 50,000te^{-500t}] \text{ V}$$

$$i_R = \frac{v}{R} = [0.5e^{-500t} - 500te^{-500t}] \text{ A}, \quad t \geq 0^+$$

$$\text{DE 6.6 [a]} \quad i_R(0^+) = \frac{V_0}{R} = \frac{40}{500} = 0.08 \text{ A}$$

$$[b] \quad i_C(0^+) = I - i_R(0^+) - i_L(0^+) = -1 - 0.08 - 0.5 = -1.58 \text{ A}$$

$$[c] \quad \frac{di_L(0^+)}{dt} = \frac{40}{0.64} = 62.5 \text{ A/s}$$

$$[d] \quad \alpha = \frac{1}{2RC} = 1000; \quad \frac{1}{LC} = 1,562,500;$$

$$s_{1,2} = -1000 \pm j750 \text{ rad/s}$$

$$[e] \quad i_L = i_f + B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t, \quad i_f = -1 \text{ A}$$

$$i_L(0^+) = 0.5 = i_f + B'_1, \quad \text{therefore } B'_1 = 1.5 \text{ A}$$

$$\frac{di_L(0^+)}{dt} = 62.5 = -\alpha B'_1 + \omega_d B'_2, \quad \text{therefore } B'_2 = (25/12) \text{ A}$$

$$\therefore i_L(t) = -1 + e^{-1000t} [1.5 \cos 750t + (25/12) \sin 750t] \text{ A}, \quad t \geq 0^+$$

$$[f] \quad v(t) = \frac{L di_L}{dt} = 40e^{-1000t} [\cos 750t - (154/3) \sin 750t] \text{ V} \quad t \geq 0$$

$$\text{DE 6.7 [a]} \quad i(0^+) = 0$$

$$[b] \quad v_C(0^+) = v_C(0^-) = \left(\frac{80}{24}\right)(15) = 50 \text{ V}$$

$$[c] \quad 50 + L \frac{di(0^+)}{dt} = 100, \quad \frac{di(0^+)}{dt} = 10,000 \text{ A/s}$$

$$[d] \quad \alpha = 8000; \quad \frac{1}{LC} = 100 \times 10^6; \quad s_{1,2} = -8000 \pm j6000 \text{ rad/s}$$

$$[\text{e}] \quad i = i_f + e^{-\alpha t} [B'_1 \cos \omega_d t + B'_2 \sin \omega_d t]; \quad i_f = 0, \quad i(0^+) = 0$$

$$\text{Therefore} \quad B'_1 = 0; \quad \frac{di(0^+)}{dt} = 10,000 = -\alpha B'_1 + \omega_d B'_2$$

$$\text{Therefore} \quad B'_2 = 1.67 \text{ A}; \quad i = 1.67 e^{-8000t} \sin 6000t \text{ A}, \quad t \geq 0$$

$$\text{DE 6.8} \quad v_c(t) = v_f + e^{-\alpha t} [B'_1 \cos \omega_d t + B'_2 \sin \omega_d t], \quad v_f = 100 \text{ V}$$

$$v_c(0^+) = 50 \text{ V}; \quad \frac{dv_c(0^+)}{dt} = 0; \quad \text{therefore} \quad 50 = 100 + B'_1$$

$$B'_1 = -50 \text{ V}; \quad 0 = -\alpha B'_1 + \omega_d B'_2$$

$$\text{Therefore} \quad B'_2 = \frac{\alpha}{\omega_d} B'_1 = \left( \frac{8000}{6000} \right) (-50) = -66.67 \text{ V}$$

$$\text{Therefore} \quad v_c(t) = 100 - e^{-8000t} [50 \cos 6000t + 66.67 \sin 6000t] \text{ V}, \quad t \geq 0$$

## Problems

$$\text{P 6.1} \quad [\text{a}] \quad \alpha = \frac{1}{2RC} = 1 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = 10$$

$$\omega_d = \sqrt{10 - 1} = 3 \text{ rad/s}$$

$$\therefore v = B_1 e^{-t} \cos 3t + B_2 e^{-t} \sin t$$

$$v(0) = B_1 = 0; \quad v = B_2 e^{-t} \sin 3t$$

$$i_R(0^+) = 0 \text{ A}; \quad i_C(0^+) = 3 \text{ A}; \quad \frac{dv}{dt}(0^+) = \frac{3}{0.25} = 12 \text{ V/s}$$

$$12 = -\alpha B_1 + \omega_d B_2 = -1(0) + 3B_2$$

$$\therefore B_2 = 4$$

$$\therefore v = 4e^{-t} \sin 3t \text{ V}, \quad t \geq 0$$



$$[b] \frac{dv}{dt} = 4e^{-t}(3 \cos 3t - \sin 3t)$$

$$\frac{dv}{dt} = 0 \quad \text{when} \quad 3 \cos 3t = \sin 3t \quad \text{or} \quad \tan 3t = 3$$

$$\therefore 3t_1 = 1.25, \quad t_1 = 416.35 \text{ ms}$$

$$3t_2 = 1.25 + \pi, \quad t_2 = 1463.55 \text{ ms}$$

$$3t_3 = 1.25 + 2\pi, \quad t_3 = 2510.74 \text{ ms}$$

$$[c] \quad t_3 - t_1 = 2094.40 \text{ ms}; \quad T_d = \frac{2\pi}{\omega_d} = \frac{2\pi}{3} = 2094.40 \text{ ms}$$


$$[d] \quad t_2 - t_1 = 1047.20 \text{ ms}; \quad \frac{T_d}{2} = \frac{2094.40}{2} = 1047.20 \text{ ms}$$

$$[e] \quad v(t_1) = 4e^{-(0.41635)} \sin 3(0.41635) = 2.50 \text{ V}$$

$$v(t_2) = 4e^{-(1.46355)} \sin 3(1.46355) = -0.88 \text{ V}$$

$$v(t_3) = 4e^{-(2.51074)} \sin 3(2.51074) = 0.31 \text{ V}$$

[f]

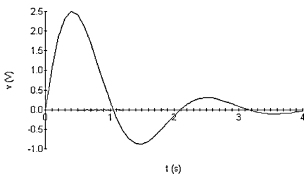

$$P 6.2 \quad [a] \quad \alpha = 0; \quad \omega_d = \omega_o = \sqrt{10} = 3.16 \text{ rad/s}$$

$$v = B_1 \cos \omega_o t + B_2 \sin \omega_o t; \quad v(0) = B_1 = 0; \quad v = B_2 \sin \omega_o t$$

$$C \frac{dv}{dt}(0) = -i_L(0) = 3$$

$$12 = -\alpha B_1 + \omega_d B_2 = -0 + \sqrt{10} B_2$$

$$\therefore B_2 = 12/\sqrt{10} = 3.79 \text{ V}$$

$$v = 3.79 \sin 3.16t \text{ V}, \quad t \geq 0$$

$$[\text{b}] \quad 2\pi f = 3.16; \quad f = \frac{3.16}{2\pi} \cong 0.50 \text{ Hz}$$

$$[\text{c}] \quad 3.79 \text{ V}$$

$$\text{P 6.3} \quad [\text{a}] \quad \alpha = 4000; \quad \omega_d = 3000$$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$$

$$\therefore \omega_o^2 = \omega_d^2 + \alpha^2 = 9 \times 10^6 + 16 \times 10^6 = 25 \times 10^6$$

$$\frac{1}{LC} = 25 \times 10^6$$

$$L = \frac{1}{(25 \times 10^6)(50 \times 10^{-9})} = 0.8 \text{ H} = 800 \text{ mH}$$

$$[\text{b}] \quad \alpha = \frac{1}{2RC}$$

$$\therefore R = \frac{1}{2\alpha C} = \frac{10^9}{(8000)(50)} = 2500 \, \Omega$$

$$[\text{c}] \quad V_o = v(0) = 125 \text{ V}$$

$$[\text{d}] \quad I_o = i_L(0) = -i_R(0) - i_C(0)$$

$$i_R(0) = \frac{V_o}{R} = \frac{125}{2.5} \times 10^{-3} = 50 \text{ mA}$$

$$i_C(0) = C \frac{dv}{dt}(0)$$

$$\frac{dv}{dt} = 125 \{ e^{-4000t} [-3000 \sin 3000t - 6000 \cos 3000t] -$$

$$4000 e^{-4000t} [\cos 3000t - 2 \sin 3000t]$$

$$\frac{dv}{dt}(0) = 125 \{ 1(-6000) - 4000 \} = -125 \times 10^4$$

$$C \frac{dv}{dt}(0) = -125 \times 10^4 (40 \times 10^{-9}) = -6250 \times 10^{-5} = -62.5 \text{ mA}$$

$$\therefore I_o = -50 + 62.5 = 12.5 \text{ mA}$$

$$[\text{e}] \quad \frac{dv}{dt} = 125 e^{-4000t} [5000 \sin 3000t - 10,000 \cos 3000t]$$

$$= 625 \times 10^3 e^{-4000t} [\sin 3000t - 2 \cos 3000t]$$

$$C \frac{dv}{dt} = 31,250 \times 10^{-6} e^{-4000t} (\sin 3000t - 2 \cos 3000t)$$

$$i_C(t) = 31.25e^{-4000t}(\sin 3000t - 2 \cos 3000t) \text{ mA}$$

$$i_R(t) = 50e^{-4000t}(\cos 3000t - 2 \sin 3000t) \text{ mA}$$

$$\begin{aligned} i_L(t) &= -i_R(t) - i_C(t) \\ &= e^{-4000t}(12.5 \cos 3000t + 68.75 \sin 3000t) \text{ mA}, \quad t \geq 0 \end{aligned}$$

CHECK:

$$\begin{aligned} \frac{di_L}{dt} &= \{-4000e^{-4000t}[12.5 \cos 3000t + 68.75 \sin 3000t] \\ &\quad + e^{-4000t}[-37.5 \times 10^3 \sin 3000t \\ &\quad + 206.25 \times 10^3 \cos 3000t] \times 10^{-3} \\ &= e^{-4000t}[156.25 \cos 3000t - 312.5 \sin 3000t] \\ L \frac{di_L}{dt} &= e^{-4000t}[125 \cos 3000t - 250 \sin 3000t] \\ &= 125e^{-4000t}[\cos 3000t - 2 \sin 3000t] \text{ V} \end{aligned}$$

$$\begin{aligned} \text{P 6.4 [a]} \quad \left(\frac{1}{2RC}\right)^2 &= \frac{1}{LC} = (4000)^2 \\ \therefore C &= \frac{1}{(16 \times 10^9)(5)} = 12.5 \text{ nF} \end{aligned}$$

$$\frac{1}{2RC} = 4000$$

$$\therefore R = \frac{10^9}{(8000)(12.5)} = 10 \text{ k}\Omega$$

$$v(0) = D_2 = 25 \text{ V}$$

$$i_R(0) = \frac{25}{10} = 2.5 \text{ mA}$$

$$i_C(0) = -2.5 - 5 = -7.5 \text{ mA}$$

$$\frac{dv}{dt}(0) = D_1 - 4000D_2 = \frac{-7.5 \times 10^{-3}}{12.5 \times 10^{-9}} = -6 \times 10^5$$

$$\therefore D_1 = -6 \times 10^5 + 4000(25) = -5 \times 10^5 \text{ V/s}$$

$$\text{[b]} \quad v = -5 \times 10^5 te^{-4000t} + 25e^{-4000t}$$

$$\frac{dv}{dt} = [20 \times 10^8 t - 6 \times 10^5]e^{-4000t}$$

$$\begin{aligned} i_C &= C \frac{dv}{dt} = 12.5 \times 10^{-9} [20 \times 10^8 t - 6 \times 10^5] e^{-4000t} \\ &= (25,000t - 7.5)e^{-4000t} \text{ mA}, \quad t > 0 \end{aligned}$$

$$\text{P 6.5} \quad [\text{a}] \quad -\alpha + \sqrt{\alpha^2 - \omega_o^2} = -5000$$

$$-\alpha - \sqrt{\alpha^2 - \omega_o^2} = -20,000$$

$$\therefore -2\alpha = -25,000$$

$$\alpha = 12,500 \text{ rad/s}$$

$$\frac{1}{2RC} = \frac{10^6}{2R(0.05)} = 12,500$$

$$R = 800 \Omega$$

$$2\sqrt{\alpha^2 - \omega_o^2} = 15,000$$

$$4(\alpha^2 - \omega_o^2) = 225 \times 10^6$$

$$\therefore \omega_o = 10,000 \text{ rad/s}$$

$$\omega_o^2 = 10^8 = \frac{1}{LC}$$

$$\therefore L = \frac{1}{10^8 C} = 200 \text{ mH}$$

$$[\text{b}] \quad i_R = \frac{v(t)}{R} = -6.25e^{-5000t} + 25e^{-20,000t} \text{ mA}, \quad t \geq 0^+$$

$$i_C = C \frac{dv(t)}{dt} = 1.25e^{-5000t} - 20e^{-20,000t} \text{ mA}, \quad t \geq 0^+$$

$$i_L = -(i_R + i_C) = 5e^{-5000t} - 5e^{-20,000t} \text{ mA}, \quad t \geq 0^+$$

$$\text{P 6.6} \quad [\text{a}] \quad \omega_o^2 = \frac{1}{LC} = \frac{10^9}{40} = 25 \times 10^6$$

$$\omega_o = 5000 \text{ rad/s}$$

$$\frac{1}{2RC} = 5000; \quad R = \frac{1}{10,000C}$$

$$R = \frac{10^9}{8 \times 10^4} = 12.5 \text{ k}\Omega$$

$$[\text{b}] \quad v(t) = D_1 t e^{-5000t} + D_2 e^{-5000t}$$

$$v(0) = -25 \text{ V} = D_2$$

$$\frac{dv}{dt} = (D_1 t - 25)(-5000e^{-5000t}) + D_1 e^{-5000t}$$

$$\frac{dv}{dt}(0) = 125 \times 10^3 + D_1 = \frac{i_C(0)}{C}$$

$$i_C(0) = -i_R(0) - i_L(0)$$

$$i_R(0) = \frac{-25}{12.5} = -2 \text{ mA}$$

$$\therefore i_C(0) = 2 - (-1) = 3 \text{ mA}$$

$$\therefore \frac{dv}{dt}(0) = \frac{3 \times 10^{-3}}{8 \times 10^{-9}} = 0.375 \times 10^6 = 3.75 \times 10^5$$

$$\therefore 1.25 \times 10^5 + D_1 = 3.75 \times 10^5$$

$$D_1 = 2.5 \times 10^5 = 25 \times 10^4 \text{ V/s}$$

$$\therefore v(t) = (25 \times 10^4 t - 25)e^{-5000t} \text{ V}, \quad t \geq 0$$

[c]  $i_C(t) = 0$  when  $\frac{dv}{dt}(t) = 0$

$$\frac{dv}{dt} = (25 \times 10^4 t - 25)(-5000)e^{-5000t} + e^{-5000t}(25 \times 10^4)$$

$$= (375,000 - 125 \times 10^7 t)e^{-5000t}$$

$$\frac{dv}{dt} = 0 \text{ when } 125 \times 10^7 t_1 = 375,000; \quad \therefore t_1 = 300 \mu\text{s}$$

$$v(300 \mu\text{s}) = 50e^{-1.5} = 11.16 \text{ V}$$

[d]  $i_L(300 \mu\text{s}) = -i_R(300 \mu\text{s}) = \frac{11.16}{12.5} = 0.89 \text{ mA}$

$$\omega_C(300 \mu\text{s}) = 4 \times 10^{-9} (11.16)^2 = 497.87 \text{ nJ}$$

$$\omega_L(300 \mu\text{s}) = (2.5)(0.89)^2 \times 10^{-6} = 1991.48 \text{ nJ}$$

$$\omega(300 \mu\text{s}) = \omega_C + \omega_L = 2489.35 \text{ nJ}$$

$$\omega(0) = 4 \times 10^{-9} (625) + 2.5(10^{-6}) = 5000 \text{ nJ}$$

$$\% \text{ remaining} = \frac{2489.35}{5000}(100) = 49.79\%$$

P 6.7 [a]  $i_R(0) = \frac{90}{2000} = 45 \text{ mA}$

$$i_L(0) = -30 \text{ mA}$$

$$i_C(0) = -i_L(0) - i_R(0) = 30 - 45 = -15 \text{ mA}$$

$$[\text{b}] \quad \alpha = \frac{1}{2RC} = \frac{10^9}{(4000)(10)} = 25,000$$

$$\omega_o^2 = \frac{1}{LC} = \frac{(10^3)(10^9)}{(250)(10)} = 4 \times 10^8$$

$$s_{1,2} = -25,000 \pm \sqrt{6.25 \times 10^8 - 10^8(4)} = -25,000 \pm 15,000$$

$$s_1 = -10,000 \text{ rad/s}; \quad s_2 = -40,000 \text{ rad/s}$$

$$v = A_1 e^{-10,000t} + A_2 e^{-40,000t}$$

$$v(0) = A_1 + A_2 = 90$$

$$\frac{dv}{dt}(0) = -10^4 A_1 - 4A_2 \times 10^4 = \frac{-15 \times 10^{-3}}{10 \times 10^{-9}} = -1.5 \times 10^6 \text{ V/s}$$

$$-A_1 - 4A_2 = -150$$

$$\therefore -3A_2 = -60; \quad A_2 = 20; \quad A_1 = 70$$

$$v = 70e^{-10,000t} + 20e^{-40,000t} \text{ V}, \quad t \geq 0$$

$$\begin{aligned} [\text{c}] \quad i_C &= C \frac{dv}{dt} \\ &= 10 \times 10^{-9} [-70 \times 10^4 e^{-10,000t} - 80 \times 10^4 e^{-40,000t}] \\ &= -7e^{-10,000t} - 8e^{-40,000t} \text{ mA} \\ i_R &= 35e^{-10,000t} + 10e^{-40,000t} \text{ mA} \\ i_L &= -i_C - i_R = -28e^{-10,000t} - 2e^{-40,000t} \text{ mA}, \quad t \geq 0 \end{aligned}$$

$$\text{P 6.8} \quad \frac{1}{2RC} = \frac{3 \times 10^9}{(25,000)(10)} = 12,000$$

$$\frac{1}{LC} = 4 \times 10^8$$

$$s_{1,2} = -12,000 \pm j16,000 \text{ rad/s}$$

$\therefore$  response is underdamped

$$v(t) = B_1 e^{-12,000t} \cos 16,000t + B_2 e^{-12,000t} \sin 16,000t$$

$$v(0^+) = 90 \text{ V} = B_1; \quad i_R(0^+) = \frac{90}{(12,500/3)} = 21.6 \text{ mA}$$

$$i_C(0^+) = [-i_L(0^+) + i_R(0^+)] = -[-30 + 21.6] = 8.4 \text{ mA}$$

$$\frac{dv(0^+)}{dt} = \frac{8.4 \times 10^{-3}}{10 \times 10^{-9}} = 840,000 \text{ V/s}$$

$$\frac{dv(0)}{dt} = -12,000B_1 + 16,000B_2 = 840,000$$

$$\text{or } -3B_1 + 4B_2 = 210; \quad \therefore B_2 = 120 \text{ V}$$

$$v(t) = 90e^{-12,000t} \cos 16,000t + 120e^{-12,000t} \sin 16,000t \text{ V}, \quad t \geq 0$$

$$\text{P 6.9} \quad \alpha = \frac{1}{2RC} = \frac{10^9}{(5000)(10)} = 2 \times 10^4$$

$$\alpha^2 = 4 \times 10^8; \quad \therefore \alpha^2 = \omega_o^2$$

Critical damping:

$$v = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

$$i_R(0^+) = \frac{90}{2500} = 36 \text{ mA}$$

$$i_C(0^+) = [-i_L(0^+) + i_R(0^+)] = -[-30 + 36] = -6 \text{ mA}$$

$$v(0) = D_2 = 90$$

$$\frac{dv}{dt} = D_1[t(-\alpha e^{-\alpha t}) + e^{-\alpha t}] - \alpha D_2 e^{-\alpha t}$$

$$\frac{dv}{dt}(0) = D_1 - \alpha D_2 = \frac{i_C(0)}{C} = \frac{-6 \times 10^{-3}}{10 \times 10^{-9}} = -6 \times 10^5$$

$$D_1 = \alpha D_2 - 6 \times 10^5 = (2 \times 10^4)(90) - 6 \times 10^5 = 120 \times 10^4$$

$$v = (120 \times 10^4 t + 90)e^{-20,000t} \text{ V}, \quad t \geq 0$$

$$\text{P 6.10 [a]} \quad \alpha = \frac{1}{2RC} = \frac{10^9}{(10,000)(8)} = 12,500$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(1.25)(8)} = 10^8$$

$$s_{1,2} = -12,500 \pm \sqrt{(1.5625 - 1)10^8} = -12,500 \pm 7500$$

$$s_1 = -5000 \text{ rad/s}$$

$$s_2 = -20,000 \text{ rad/s}$$

[b] overdamped

[c]  $\omega_d = \sqrt{\omega_o^2 - \alpha^2}$

$$\therefore \alpha^2 = \omega_o^2 - \omega_d^2 = 10^8 - 36 \times 10^6 = 0.64 \times 10^8$$

$$\alpha = 0.8 \times 10^4 = 8000$$

$$\frac{1}{2RC} = 8000; \quad \therefore R = \frac{10^9}{(16,000)(8)} = 7812.5 \Omega$$

[d]  $s_1 = -8000 + j6000 \text{ rad/s}; \quad s_2 = -8000 - j6000 \text{ rad/s}$

[e]  $\alpha = 10^4 = \frac{1}{2RC}; \quad \therefore R = \frac{1}{2C(10^4)} = 6250 \Omega$

P 6.11  $\alpha = 2000/2 = 1000$

$$R = \frac{1}{2\alpha C} = \frac{10^6}{(2000)(18)} = 27.78 \Omega$$

$$v(0^+) = -24 \text{ V}$$

$$i_R(0^+) = \frac{-24}{27.78} = -864 \text{ mA}$$

$$\frac{dv}{dt} = 2400e^{-200t} + 21,600e^{-1800t}$$

$$\frac{dv(0^+)}{dt} = 2400 + 21,600 = 24,000 \text{ V/s}$$

$$i_C(0^+) = 18 \times 10^{-6}(24,000) = 432 \text{ mA}$$

$$i_L(0^+) = -[i_R(0^+) + i_C(0^+)] = -[-864 + 432] = 432 \text{ mA}$$

P 6.12 [a]  $2\alpha = 200; \quad \alpha = 100 \text{ rad/s}$

$$2\sqrt{\alpha^2 - \omega_o^2} = 120; \quad \omega_o = 80 \text{ rad/s}$$

$$C = \frac{1}{2\alpha R} = \frac{1}{200(200)} = 25 \mu\text{F}$$

$$L = \frac{1}{\omega_o^2 C} = \frac{10^6}{(80)^2(25)} = 6.25 \text{ H}$$

$$i_C(0^+) = A_1 + A_2 = 15 \text{ mA}$$



$$\frac{di_C}{dt} + \frac{di_L}{dt} + \frac{di_R}{dt} = 0$$

$$\frac{di_C(0)}{dt} = -\frac{di_L(0)}{dt} - \frac{di_R(0)}{dt}$$

$$\frac{di_L(0)}{dt} = \frac{0}{6.25} = 0 \text{ A/s}$$

$$\frac{di_R(0)}{dt} = \frac{1}{R} \frac{dv(0)}{dt} = \frac{1}{R} \frac{i_C(0)}{C} = \frac{15 \times 10^{-3}}{(200)(25 \times 10^{-6})} = 3 \text{ A/s}$$

$$\therefore \frac{di_C(0)}{dt} = -3 \text{ A/s}$$

$$\therefore 40A_1 + 160A_2 = 3$$

$$A_1 + 4A_2 = 75 \times 10^{-3}; \quad \therefore A_1 = -5 \text{ mA}; \quad A_2 = 20 \text{ mA}$$

$$\therefore i_C = 20e^{-160t} - 5e^{-40t} \text{ mA}, \quad t \geq 0$$

[b] By hypothesis

$$v = A_3e^{-160t} + A_4e^{-40t}, \quad t \geq 0$$

$$v(0) = A_3 + A_4 = 0$$

$$\frac{dv(0)}{dt} = \frac{15 \times 10^{-3}}{25 \times 10^{-6}} = 600 \text{ V/s}$$

$$-160A_3 - 40A_4 = 600; \quad \therefore A_3 = -5 \text{ V}; \quad A_4 = 5 \text{ V}$$

$$v = -5e^{-160t} + 5e^{-40t} \text{ V}, \quad t \geq 0$$

$$[c] i_R(t) = \frac{v}{200} = -25e^{-160t} + 25e^{-40t} \text{ mA}, \quad t \geq 0^+$$

$$[d] i_L = -i_R - i_C$$

$$i_L = 5e^{-160t} - 20e^{-40t} \text{ mA}, \quad t \geq 0$$

P 6.13 From the form of the solution we have

$$v(0) = A_1 + A_2$$

$$\frac{dv(0^+)}{dt} = -\alpha(A_1 + A_2) + j\omega_d(A_1 - A_2)$$

We know both  $v(0)$  and  $dv(0^+)/dt$  will be real numbers. To facilitate the algebra we let these numbers be  $K_1$  and  $K_2$ , respectively. Then our two simultaneous equations are

$$K_1 = A_1 + A_2$$

$$K_2 = (-\alpha + j\omega_d)A_1 + (-\alpha - j\omega_d)A_2$$

The characteristic determinate is

$$\Delta = \begin{vmatrix} 1 & 1 \\ (-\alpha + j\omega_d) & (-\alpha - j\omega_d) \end{vmatrix} = -j2\omega_d$$

The numerator determinates are

$$N_1 = \begin{vmatrix} K_1 & 1 \\ K_2 & (-\alpha - j\omega_d) \end{vmatrix} = -(\alpha + j\omega_d)K_1 - K_2$$

$$\text{and } N_2 = \begin{vmatrix} 1 & K_1 \\ (-\alpha + j\omega_d) & K_2 \end{vmatrix} = K_2 + (\alpha - j\omega_d)K_1$$

$$\text{It follows that } A_1 = \frac{N_1}{\Delta} = \frac{\omega_d K_1 - j(\alpha K_1 + K_2)}{2\omega_d}$$

$$\text{and } A_2 = \frac{N_2}{\Delta} = \frac{\omega_d K_1 + j(\alpha K_1 + K_2)}{2\omega_d}$$

We see from these expressions that  $A_1 = A_2^*$

P 6.14 By definition,  $B_1 = A_1 + A_2$ . From the solution to Problem 6.13 we have

$$A_1 + A_2 = \frac{2\omega_d K_1}{2\omega_d} = K_1$$

But  $K_1$  is  $v(0)$ , therefore,  $B_1 = v(0)$ , which is identical to Eq. (6.30).

By definition,  $B_2 = j(A_1 - A_2)$ . From Problem 6.13 we have

$$B_2 = j(A_1 - A_2) = \frac{j[-2j(\alpha K_1 + K_2)]}{2\omega_d} = \frac{\alpha K_1 + K_2}{\omega_d}$$

It follows that


$$K_2 = -\alpha K_1 + \omega_d B_2, \quad \text{but } K_2 = \frac{dv(0^+)}{dt} \quad \text{and } K_1 = B_1$$

Thus we have

$$\frac{dv}{dt}(0^+) = -\alpha B_1 + \omega_d B_2,$$

which is identical to Eq. (6.31).

P 6.15

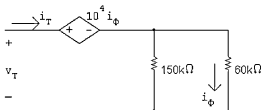

$$v_T = 10^4 \frac{i_T(150 \times 10^3)}{210 \times 10^3} + \frac{(150)(60)10^6}{210 \times 10^3} i_T$$

$$\frac{v_T}{i_T} = \frac{1500 \times 10^3}{210} + \frac{9000 \times 10^3}{210} = \frac{10,500}{210} \times 10^3 = 50 \text{ k}\Omega$$

$$V_o = \frac{75}{10}(6) = 45 \text{ V}; \quad I_o = 0$$

$$i_C(0) = -i_R(0) - i_L(0) = -\frac{45}{50,000} = -0.9 \text{ mA}$$

$$\frac{i_C(0)}{C} = \frac{-0.9}{1.25} \times 10^6 = -720 \times 10^3$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(8)(1.25)} = 10^8; \quad \omega_o = 10^4 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{10^9}{(2)(50)(1.25) \times 10^3} = 8000 \text{ rad/s}$$

$$\omega_d = \sqrt{(100 - 64) \times 10^6} = 6000 \text{ rad/s}$$

$$v_o = B_1 e^{-8000t} \cos 6000t + B_2 e^{-8000t} \sin 6000t$$

$$v_o(0) = B_1 = 45 \text{ V}$$

$$\frac{dv_o}{dt}(0) = 6000B_2 - 8000B_1 = -720 \times 10^3$$

$$\therefore 6000B_2 = 8000(45) - 720 \times 10^3; \quad \therefore B_2 = -60 \text{ V}$$

$$v_o = 45e^{-8000t} \cos 6000t - 60e^{-8000t} \sin 6000t \text{ V}, \quad t \geq 0$$

P 6.16 [a]  $\alpha = \frac{1}{2RC} = 1250$ ,  $\omega_o = 10^3$ , therefore overdamped

$$s_1 = -500, \quad s_2 = -2000$$

therefore  $v = A_1 e^{-500t} + A_2 e^{-2000t}$


$$v(0^+) = 0 = A_1 + A_2; \quad \left[ \frac{dv(0^+)}{dt} \right] = \frac{i_C(0^+)}{C} = 98,000 \text{ V/s}$$

Therefore  $-500A_1 - 2000A_2 = 98,000$

$$A_1 = \frac{+980}{15}, \quad A_2 = \frac{-980}{15}$$

$$v(t) = \left[ \frac{980}{15} \right] [e^{-500t} - e^{-2000t}] \text{ V}, \quad t \geq 0$$

[b]

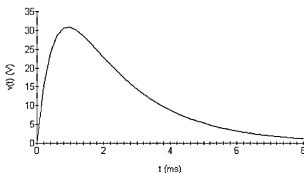

Example 6.4:  $v_{\max} \cong 74 \text{ V}$  at 1.4 ms

Example 6.5:  $v_{\max} \cong 36.1 \text{ V}$  at 1.0 ms

Problem 6.16:  $v_{\max} \cong 30.9$  at 0.92 ms

P 6.17 [a]  $v = L \left( \frac{di_L}{dt} \right) = 16[e^{-20,000t} - e^{-80,000t}] \text{ V}, \quad t \geq 0$

[b]  $i_R = \frac{v}{R} = 40[e^{-20,000t} - e^{-80,000t}] \text{ mA}, \quad t \geq 0^+$


[c]  $i_C = I - i_L - i_R = [-8e^{-20,000t} + 32e^{-80,000t}] \text{ mA}, \quad t \geq 0^+$

P 6.18 [a]  $v = L \left( \frac{di_L}{dt} \right) = 40e^{-32,000t} \sin 24,000t \text{ V}, \quad t \geq 0$


[b]  $i_C(t) = I - i_R - i_L = 24 \times 10^{-3} - \frac{v}{625} - i_L$   
 $= [24e^{-32,000t} \cos 24,000t - 32e^{-32,000t} \sin 24,000t] \text{ mA}, \quad t \geq 0^+$

$$\text{P 6.19} \quad v = L \left( \frac{di_L}{dt} \right) = 960,000te^{-40,000t} \text{ V}, \quad t \geq 0$$
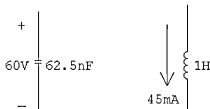
$$\text{P 6.20} \quad t < 0: \quad V_o = 60 \text{ V}, \quad I_o = 45 \text{ mA}$$



$t > 0$ :

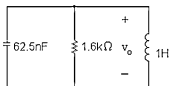

$$i_R(0) = \frac{60}{1600} = 37.5 \text{ mA}; \quad i_L(0) = 45 \text{ mA}$$

$$i_C(0) = -37.5 - 45 = -82.5 \text{ mA}$$

$$\alpha = \frac{1}{2RC} = \frac{10^9}{3200(62.5)} = 5000 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{62.5} = 16 \times 10^6$$

$$s_{1,2} = -5000 \pm \sqrt{25 \times 10^6 - 16 \times 10^6} = -5000 \pm 3000$$

$$s_1 = -2000 \text{ rad/s}; \quad s_2 = -8000 \text{ rad/s}$$

$$\therefore v_o = A_1 e^{-2000t} + A_2 e^{-8000t}$$

$$A_1 + A_2 = v_o(0) = 60$$

$$\frac{dv_o}{dt}(0) = -2000A_1 - 8000A_2 = \frac{-82.5 \times 10^{-3}}{62.5 \times 10^{-9}} = -1320 \times 10^3$$

$$\text{Solving,} \quad A_1 = -140 \text{ V}, \quad A_2 = 200 \text{ V}$$

$$\therefore v_o = -140e^{-2000t} + 200e^{-8000t} \text{ V}, \quad t \geq 0$$

$$\text{P 6.21} \quad \omega_o^2 = \frac{1}{LC} = \frac{16 \times 10^6}{0.64} = 25 \times 10^6$$

$$\alpha = \frac{1}{2RC} = \frac{16 \times 10^6}{4000} = 4000 \text{ nepers}; \quad \alpha^2 = 16 \times 10^3$$

$$\omega_d = \sqrt{(25 - 16) \times 10^6} = 3000 \text{ rad/s}$$

$$s_{1,2} = -4000 \pm j3000 \text{ rad/s}$$

$$v_o(t) = B_1 e^{-4000t} \cos 3000t + B_2 e^{-4000t} \sin 3000t$$

$$v_o(0) = B_1 = 60 \text{ V}$$

$$i_R(0) = \frac{60}{2000} = 30 \text{ mA}$$

$$i_L(0) = 45 \text{ mA}$$

$$i_C(0) = -i_R(0) - i_L(0) = -75 \text{ mA}$$

$$\frac{i_C(0)}{C} = (-75 \times 10^{-3})(16 \times 10^6) = -12 \times 10^5$$

$$\frac{dv_o}{dt}(0) = -4000B_1 + 3000B_2 = -12 \times 10^5$$

$$\therefore 3B_2 = 4B_1 - 1200 = 240 - 1200 = -960; \quad \therefore B_2 = -320 \text{ V}$$

$$v_o(t) = 60e^{-4000t} \cos 3000t - 320e^{-4000t} \sin 3000t \text{ V}, \quad t \geq 0$$

$$\text{P 6.22} \quad \omega_o^2 = \frac{1}{LC} = \frac{16 \times 10^6}{0.16} = 10^8; \quad \omega_o = 10^4$$

$$\alpha = \frac{1}{2RC} = \frac{16 \times 10^6}{1600} = 10^4$$

$$\therefore \alpha^2 = \omega_o^2 \text{ (critical damping)}$$

$$v_o(t) = D_1 t e^{-10,000t} + D_2 e^{-10,000t}$$

$$v_o(0) = D_2 = 60 \text{ V}$$

$$i_R(0) = \frac{60}{800} = 75 \text{ mA}$$

$$i_L(0) = 45 \text{ mA}$$

$$i_C(0) = -120 \text{ mA}$$

$$\frac{dv_o}{dt}(0) = -10,000D_2 + D_1$$

$$\frac{i_C(0)}{C} = (-120 \times 10^{-3})(16 \times 10^6) = -1920 \times 10^3$$

$$D_1 - 10,000D_2 = -1920 \times 10^3; \quad D_1 = -1320 \times 10^3 \text{ V/s}$$

$$v_o(t) = (60 - 132 \times 10^4 t)e^{-10,000t} \text{ V}, \quad t > 0$$

P 6.23 [a]  $2\alpha = 5000; \quad \alpha = 2500 \text{ rad/s}$

$$\sqrt{\alpha^2 - \omega_o^2} = 1500; \quad \omega_o^2 = 4 \times 10^6; \quad \omega_o = 2000 \text{ rad/s}$$

$$\alpha = \frac{R}{2L} = 2500; \quad R = 5000L$$

$$\omega_o^2 = \frac{1}{LC} = 4 \times 10^6; \quad L = \frac{10^9}{4 \times 10^6(50)} = 5 \text{ H}$$

$$R = 25,000 \Omega$$

[b]  $i(0) = 0$

$$L \frac{di(0)}{dt} = v_c(0); \quad \frac{1}{2}(50) \times 10^{-9} v_c^2(0) = 90 \times 10^{-6}$$

$$\therefore v_c^2(0) = 3600; \quad v_c(0) = 60 \text{ V}$$

$$\frac{di(0)}{dt} = \frac{60}{5} = 12 \text{ A/s}$$

[c]  $i(t) = A_1 e^{-1000t} + A_2 e^{-4000t}$

$$i(0) = A_1 + A_2 = 0$$

$$\frac{di(0)}{dt} = -1000A_1 - 4000A_2 = 12$$

$$\therefore A_1 + 4A_2 = -12 \times 10^{-3}$$

$$\therefore A_2 = -4 \text{ mA}; \quad A_1 = +4 \text{ mA}$$

$$i(t) = +4e^{-1000t} - 4e^{-4000t} \text{ mA} \quad t \geq 0$$

$$[d] \quad \frac{di(t)}{dt} = -4e^{-1000t} + 16e^{-4000t}$$

$$\frac{di}{dt} = 0 \text{ when } 16e^{-4000t} = 4e^{-1000t}$$

$$\text{or } e^{3000t} = 4$$


$$\therefore t = \frac{\ln 4}{3000} \mu\text{s} = 462.10 \mu\text{s}$$

$$[e] \quad i_{\max} = 4e^{-0.4621} - 4e^{-1.8484} = 1.89 \text{ mA}$$

$$[f] \quad v_L(t) = 5 \frac{di}{dt} = [-20e^{-1000t} + 80e^{-4000t}] \text{ V}, \quad t \geq 0^+$$

P 6.24  $i_L(0^-) = i_L(0^+) = 37.5 \text{ mA}$

For  $t > 0$

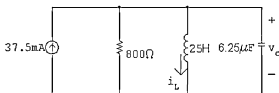

$$i_L(0^-) = i_L(0^+) = 37.5 \text{ mA}$$

$$\alpha = \frac{1}{2RC} = 100 \text{ rad/s}; \quad \omega_o^2 = \frac{1}{LC} = 6400$$

$$s_1 = -40 \text{ rad/s} \quad s_2 = -160 \text{ rad/s}$$

$$v_o(\infty) = 0 = V_f$$

$$v_o = A'_1 e^{-40t} + A'_2 e^{-160t}$$

$$i_C(0^+) = -37.5 + 37.5 + 0 = 0$$

$$\therefore \frac{dv_o}{dt} = 0$$

$$\frac{dv_o}{dt}(0) = -40A'_1 - 160A'_2$$

$$\therefore A'_1 + 4A'_2 = 0; \quad A'_1 + A'_2 = 0$$



$$\therefore A'_1 = 0; \quad A'_2 = 0$$

$$\therefore v_o = 0 \text{ for } t \geq 0$$

$$\text{Note: } v_o(0) = 0; \quad v_o(\infty) = 0; \quad \frac{dv_o(0)}{dt} = 0$$

Hence the 37.5 mA current circulates between the current source and the ideal inductor in the equivalent circuit. In the original circuit the 30 V source sustains a current of 37.5 mA in the inductor. This is an example of a circuit going directly into steady state when the switch is closed. There is no transient period, or interval.

$$\text{P 6.25 } i_C(0) = 0; \quad v_o(0) = 200 \text{ V}$$

$$\alpha = \frac{R}{2L} = \frac{4}{2(0.04)} = 50 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^3}{0.4} = 2500$$

$$\therefore \alpha^2 = \omega_o^2; \quad \text{critical damping}$$

$$v_o(t) = V_f + D'_1 t e^{-50t} + D'_2 e^{-50t}$$

$$V_f = 100 \text{ V}$$

$$v_o(0) = 100 + D'_2 = 200; \quad D'_2 = 100 \text{ V}$$

$$\frac{dv_o}{dt}(0) = -50D'_2 + D'_1 = 0$$

$$D'_1 = 50D'_2 = 5000 \text{ V/s}$$

$$v_o = 100 + 5000te^{-50t} + 100e^{-50t} \text{ V, } t \geq 0$$

$$\text{P 6.26 } \alpha = 800 \text{ rad/s; } \quad \omega_d = 600 \text{ rad/s}$$


$$\omega_o^2 - \alpha^2 = 36 \times 10^4; \quad \omega_o^2 = 100 \times 10^4; \quad \omega_o = 1000 \text{ rad/s}$$

$$\alpha = \frac{R}{2L} = 800; \quad R = 1600L$$

$$\frac{1}{LC} = 100 \times 10^4; \quad L = \frac{10^6}{(100 \times 10^4)(500)} = 2 \text{ mH}$$

$$\therefore R = 3.2 \Omega$$
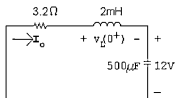
$$i(0^+) = B_1 = 0 \text{ A}; \quad \text{at } t = 0^+$$



$$12 + 0 + v_L(0^+) = 0; \quad v_L(0^+) = -12 \text{ V}$$

$$\frac{di(0^+)}{dt} = \frac{-12}{0.002} = -6000 \text{ A/s}$$

$$\therefore \frac{di(0^+)}{dt} = 600B_2 - 800B_1 = -6000$$

$$\therefore 600B_2 = 800B_1 - 6000; \quad \therefore B_2 = -10 \text{ A}$$

$$\therefore i = -10e^{-800t} \sin 600t \text{ A}, \quad t \geq 0$$

P 6.27 From Prob. 6.26 we know  $v_c$  will be of the form

$$v_c = B_3 e^{-800t} \cos 600t + B_4 e^{-800t} \sin 600t$$

From Prob. 6.26 we have

$$v_c(0) = -12 \text{ V} = B_3$$

and

$$\frac{dv_c(0)}{dt} = \frac{i_C(0)}{C} = 0$$

$$\frac{dv_c(0)}{dt} = 600B_4 - 800B_3$$

$$\therefore 600B_4 = 800B_3 + 0; \quad B_4 = -16 \text{ V}$$

$$v_c(t) = -12e^{-800t} \cos 600t - 16e^{-800t} \sin 600t \text{ V} \quad t \geq 0$$

$$\text{P 6.28} \quad v_C(0^+) = \frac{1}{2}(240) = 120 \text{ V}$$

$$i_L(0^+) = 60 \text{ mA}; \quad i_L(\infty) = \frac{240}{5} \times 10^{-3} = 48 \text{ mA}$$

$$\alpha = \frac{1}{2RC} = \frac{10^6}{2(2500)(5)} = 40$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{400} = 2500$$

$$\alpha^2 = 1600; \quad \alpha^2 < \omega_o^2; \quad \therefore \text{ underdamped}$$

$$s_{1,2} = -40 \pm j\sqrt{2500 - 1600} = -40 \pm j30 \text{ rad/s}$$

$$\begin{aligned} i_L &= I_f + B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t \\ &= 48 + B'_1 e^{-40t} \cos 30t + B'_2 e^{-40t} \sin 30t \end{aligned}$$

$$i_L(0) = 48 + B'_1; \quad B'_1 = 60 - 48 = 12 \text{ mA}$$

$$\frac{di_L}{dt}(0) = 30B'_2 - 40B'_1 = \frac{120}{80} = 1.5 = 1500 \times 10^{-3}$$

$$\therefore 30B'_2 = 40(12) \times 10^{-3} + 1500 \times 10^{-3}; \quad B'_2 = 66 \text{ mA}$$

$$\therefore i_L = 48 + 12e^{-40t} \cos 30t + 66e^{-40t} \sin 30t \text{ mA}, \quad t \geq 0$$

$$\text{P 6.29} \quad \alpha = \frac{R}{2L} = 5000 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{200} = 50 \times 10^6$$

$$s_{1,2} = -5000 \pm \sqrt{25 \times 10^6 - 50 \times 10^6} = -5000 \pm j5000 \text{ rad/s}$$

$$v_o = V_f + B'_1 e^{-5000t} \cos 5000t + B'_2 e^{-5000t} \sin 5000t$$

$$v_o(0) = 0 = V_f + B'_1$$

$$v_o(\infty) = 40 \text{ V}; \quad \therefore B'_1 = -40 \text{ V}$$

$$\frac{dv_o(0)}{dt} = 0 = 5000B'_2 - 5000B'_1$$

$$\therefore B'_2 = B'_1 = -40 \text{ V}$$

$$v_o = 40 - 40e^{-5000t} \cos 5000t - 40e^{-5000t} \sin 5000t \text{ V}, \quad t \geq 0$$

$$\text{P 6.30} \quad \alpha = \frac{1}{2RC} = \frac{10^6}{(1600)(6.25)} = 100; \quad \alpha^2 = 10^4$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{(25)(6.25)} = 6400$$

$$s_{1,2} = -200 \pm \sqrt{10^4 - 6400} = -100 \pm 60$$

$$s_1 = -40 \text{ rad/s}; \quad s_2 = -160 \text{ rad/s}$$

$$v_o(\infty) = 0 = V_f$$

$$\therefore v_o = A'_1 e^{-40t} + A'_2 e^{-160t}$$

$$v_o(0) = 30 = A'_1 + A'_2$$

$$\text{Note:} \quad i_C(0^+) = 0$$

$$\therefore \frac{dv_o}{dt}(0) = 0 = -40A'_1 - 160A'_2$$

$$\text{Solving,} \quad A'_1 = 40 \text{ V}, \quad A'_2 = -10 \text{ V}$$

$$v_o(t) = 40e^{-40t} - 10e^{-160t} \text{ V}, \quad t > 0^+$$

$$\text{P 6.31 [a]} \quad i_o = I_f + A'_1 e^{-40t} + A'_2 e^{-160t}$$

$$I_f = \frac{30}{800} = 37.5 \text{ mA}; \quad i_o(0) = 0$$

$$0 = 37.5 \times 10^{-3} + A'_1 + A'_2, \quad \therefore A'_1 + A'_2 = -37.5 \times 10^{-3}$$

$$\frac{di_o}{dt}(0) = \frac{30}{25} = -40A'_1 - 160A'_2$$

$$\text{Solving,} \quad A'_1 = -40 \text{ mA}; \quad A'_2 = 2.5 \text{ mA}$$


$$i_o = 37.5 - 40e^{-40t} + 2.5e^{-160t} \text{ mA}, \quad t \geq 0$$

$$\text{[b]} \quad \frac{di_o}{dt} = [1600e^{-40t} - 400e^{-160t}] \times 10^{-3}$$

$$L \frac{di_o}{dt} = 25(1.6)e^{-40t} - 25(0.4)e^{-160t}$$

$$\therefore v_o = 40e^{-40t} - 10e^{-160t} \text{ V}, \quad t \geq 0$$

This agrees with the solution to Problem 6.30.

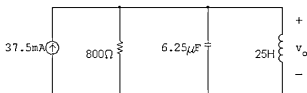P 6.32 For  $t > 0$ 

$$\alpha = \frac{1}{2RC} = 100; \quad \frac{1}{LC} = 6400$$

$$s_{1,2} = -100 \pm 60$$

$$s_1 = -40 \text{ rad/s}; \quad s_2 = -160 \text{ rad/s}$$

$$v_o = V_f + A'_1 e^{-40t} + A'_2 e^{-160t}$$

$$V_f = 0; \quad v_o(0^+) = 0; \quad i_C(0^+) = 37.5 \text{ mA}$$

$$\therefore A'_1 + A'_2 = 0$$

$$\frac{dv_o(0^+)}{dt} = \frac{i_C(0^+)}{6.25 \times 10^{-6}} = 6000 \text{ V/s}$$

$$\frac{dv_o(0^+)}{dt} = -40A'_1 - 160A'_2$$

$$-40A'_1 - 160A'_2 = 6000$$

$$A'_1 + 4A'_2 = -150$$

$$A'_1 + A'_2 = 0$$

$$\therefore A'_1 = 50 \text{ V}; \quad A'_2 = -50 \text{ V}$$

$$v_o = 50e^{-40t} - 50e^{-160t} \text{ V}, \quad t \geq 0$$

- P 6.33 [a] From the solution to Prob. 6.32  $s_1 = -40 \text{ rad/s}$  and  $s_2 = -160 \text{ rad/s}$ , therefore

$$i_o = I_f + A'_1 e^{-40t} + A'_2 e^{-160t}$$

$$I_f = 37.5 \text{ mA}; \quad i_o(0^+) = 0; \quad \frac{di_o(0^+)}{dt} = 0$$

$$\therefore 0 = 37.5 + A'_1 + A'_2; \quad -40A'_1 - 160A'_2 = 0$$

It follows that

$$A'_1 = -50 \text{ mA}; \quad A'_2 = 12.5 \text{ mA}$$

$$\therefore i_o = 37.5 - 50e^{-40t} + 12.5e^{-160t} \text{ mA}, \quad t \geq 0$$


[b]  $\frac{di_o}{dt} = 2e^{-40t} - 2e^{-160t}$

$$v_o = L \frac{di_o}{dt} = 25[2e^{-40t} - 2e^{-160t}]$$


$$v_o = 50e^{-40t} - 50e^{-160t} \text{ V}, \quad t \geq 0$$

This agrees with the solution to Problem 6.32

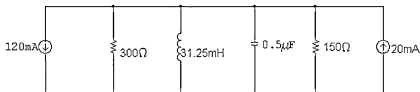- P 6.34  $t < 0$ :  $i_L = 3/150 = 20 \text{ mA}$   
 $t > 0$ :



$$300 \parallel 150 = 100 \Omega$$

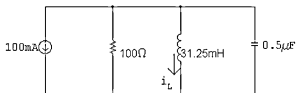

$$i_L(0) = 20 \text{ mA}, \quad i_L(\infty) = -100 \text{ mA}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(31.25)(0.5)} = 64 \times 10^6; \quad \omega_o = 8000 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{10^6}{(200)(0.5)} = 10^4; \quad \alpha^2 = 100 \times 10^6$$

$$\alpha^2 - \omega_o^2 = (100 - 64)10^6 = 36 \times 10^6$$

$$s_{1,2} = -10,000 \pm 6000$$

$$s_1 = -4000 \text{ rad/s}; \quad s_2 = -16,000 \text{ rad/s}$$

$$i_L = I_f + A'_1 e^{-4000t} + A'_2 e^{-16,000t}$$

$$i_L(\infty) = I_f = -100 \text{ mA}$$

$$i_L(0) = A'_1 + A'_2 + I_f = 20 \text{ mA}$$

$$\therefore A'_1 + A'_2 - 100 = 20 \quad \text{so} \quad A'_1 + A'_2 = 120 \text{ mA}$$

$$\frac{di_L}{dt}(0) = 0 = -4000A'_1 - 16,000A'_2$$

$$\text{Solving,} \quad A'_1 = 160 \text{ mA}, \quad A'_2 = -40 \text{ mA}$$

$$i_L = -100 + 160e^{-4000t} - 40e^{-16,000t} \text{ mA}, \quad t \geq 0$$

$$\text{P 6.35} \quad \omega_o^2 = \frac{1}{LC} = \frac{10^6}{200} = 5000$$

$$\alpha = \frac{R}{2L} = \frac{400}{40} = 10; \quad \alpha^2 = 100$$

$$\alpha^2 < \omega_o^2 \quad \therefore \quad \text{underdamped}$$

$$s_{1,2} = -10 \pm j\sqrt{4900} = -10 \pm j70 \text{ rad/s}$$


$$i = B_1 e^{-10t} \cos 70t + B_2 e^{-10t} \sin 70t$$

$$i(0) = B_1 = 147/420 = 350 \text{ mA}$$

$$\frac{di}{dt}(0) = 70B_2 - 10B_1 = 0$$


$$\therefore B_2 = 50 \text{ mA}$$

$$i = 50e^{-10t}(7 \cos 70t + \sin 70t) \text{ mA}, \quad t \geq 0^+$$

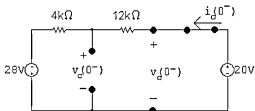P 6.36 [a]  $t < 0$ :

$$i_o(0^-) = \frac{48}{16,000} = 3 \text{ mA}$$

$$v_C(0^-) = 20 - (12,000)(0.003) = -16 \text{ V}$$

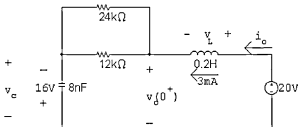 $t = 0^+$ :

$$12 \text{ k}\Omega \parallel 24 \text{ k}\Omega = 8 \text{ k}\Omega$$

$$\therefore v_o(0^+) = (0.003)(8000) - 16 = 24 - 16 = 8 \text{ V}$$

$$\text{and } v_L(0^+) = 20 - 8 = 12 \text{ V}$$

[b]  $v_o(t) = 8000i_o + v_C$ 

$$\frac{dv_o}{dt}(t) = 8000 \frac{di_o}{dt} + \frac{dv_C}{dt}$$

$$\frac{dv_o}{dt}(0^+) = 8000 \frac{di_o}{dt}(0^+) + \frac{dv_C}{dt}(0^+)$$

$$20 = L \frac{di_o}{dt} + 8000i_o + v_C$$

$$20 = 0.2 \frac{di_o}{dt}(0^+) + 24 - 16$$

$$\therefore 0.2 \frac{di_o}{dt}(0^+) = 20 - 8 = 12$$

$$\frac{di_o}{dt}(0^+) = \frac{12}{0.2} = 60 \text{ A/s}$$

$$C \frac{dv_C}{dt}(0^+) = i_o(0^+)$$



$$\therefore \frac{dv_c}{dt}(0^+) = \frac{3 \times 10^{-3}}{8 \times 10^{-9}} = 375,000$$

$$\therefore \frac{dv_o}{dt}(0^+) = 8000(60) + 375,000 = 855,000 \text{ V/s}$$

$$[c] \quad \omega_o^2 = \frac{1}{LC} = \frac{10^9}{1.6} = 625 \times 10^6; \quad \omega_o = 25,000 \text{ rad/s}$$

$$\alpha = \frac{R}{2L} = \frac{8000}{0.4} = 20,000 \text{ rad/s}; \quad \alpha^2 = 400 \times 10^6$$

$$\alpha^2 < \omega_o^2 \quad \text{underdamped}$$

$$s_{1,2} = -20,000 \pm j15,000 \text{ rad/s}$$

$$v_o(t) = V_f + B'_1 e^{-20,000t} \cos 15,000t + B'_2 e^{-20,000t} \sin 15,000t$$

$$V_f = v_o(\infty) = 20 \text{ V}$$

$$8 = 20 + B'_1; \quad B'_1 = -12 \text{ V}$$

$$-20,000B'_1 + 15,000B'_2 = 855,000$$

$$\text{Solving,} \quad B'_2 = 41 \text{ V}$$

$$\therefore v_o(t) = 20 - 12e^{-20,000t} \cos 15,000t + 41e^{-20,000t} \sin 15,000t \text{ V}, \quad t \geq 0^+$$

P 6.37 [a]  $t < 0$ :

$$i_o = \frac{120}{8000} = 15 \text{ mA}; \quad v_o = (5000)(0.015) = 75 \text{ V}$$

$t > 0$ :

$$\alpha = \frac{R}{2L} = \frac{5000}{2(1)} = 2500 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(1)(250)} = 4 \times 10^6 = 400 \times 10^4$$

$$\alpha^2 - \omega_o^2 = 625 \times 10^4 - 400 \times 10^4 = 225 \times 10^4$$

$$\therefore s_{1,2} = -2500 \pm 1500$$

$$s_1 = -1000 \text{ rad/s} \quad s_2 = -4000 \text{ rad/s}$$

$$\therefore i_o(t) = A_1 e^{-1000t} + A_2 e^{-4000t}$$

$$i_o(0) = A_1 + A_2 = 15 \times 10^{-3}$$

$$\frac{di_o}{dt}(0) = -1000A_1 - 4000A_2 = 0$$

$$\text{Solving,} \quad A_1 = 20 \text{ mA}; \quad A_2 = -5 \text{ mA}$$

$$i_o(t) = 20e^{-1000t} - 5e^{-4000t} \text{ mA}, \quad t \geq 0^+$$

$$[\mathbf{b}] \quad v_o(t) = A_1 e^{-1000t} + A_2 e^{-4000t}$$

$$v_o(0) = A_1 + A_2 = 75$$

$$\frac{dv_o}{dt}(0) = -1000A_1 - 4000A_2 = \frac{-15 \times 10^{-3}}{250 \times 10^{-9}}$$

$$\text{Solving,} \quad A_1 = 80 \text{ V}; \quad A_2 = -5 \text{ V}$$

$$v_o(t) = 80e^{-1000t} - 5e^{-4000t} \text{ V}, \quad t \geq 0^+$$

Check:

$$5000i_o + 1 \frac{di_o}{dt} = v_o$$

$$5000i_o = 100e^{-1000t} - 25e^{-4000t}$$

$$\frac{di_o}{dt} = -20e^{-1000t} + 20e^{-4000t}$$

$$\therefore 5000i_o + \frac{di_o}{dt} = 80e^{-1000t} - 5e^{-4000t} \text{ V} \quad (\text{checks})$$

$$\text{P 6.38} \quad \omega_o^2 = \frac{1}{LC} = \frac{10^6}{(20)(5)} = 10^4; \quad \omega_o = 100 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{10^5}{(1600)(5)} = \frac{10^4}{80} = 125 \text{ rad/s}$$

$$s_{1,2} = -125 \pm \sqrt{(125)^2 - 10^4} = -125 \pm 75$$

$$s_1 = -50 \text{ rad/s}; \quad s_2 = -200 \text{ rad/s}$$

$$I_f = 15 \text{ mA}$$

$$i_L = 15 + A'_1 e^{-50t} + A'_2 e^{-200t}$$

$$\therefore -30 = 15 + A'_1 + A'_2; \quad A'_1 + A'_2 = -45 \times 10^{-3}$$

$$\frac{di_L}{dt} = -50A'_1 - 200A'_2 = \frac{60}{20} = 3$$

$$\text{Solving,} \quad A'_1 = -40 \text{ mA}; \quad A'_2 = -5 \text{ mA}$$

$$i_L = 15 - 40e^{-50t} - 5e^{-200t} \text{ mA}, \quad t \geq 0$$

$$\text{P 6.39} \quad \alpha = \frac{1}{2RC} = \frac{10^6}{(2500)(5)} = 80; \quad \alpha^2 = 6400$$

$$\omega_o^2 = 10^4$$

$$s_{1,2} = -80 \pm j\sqrt{10^4 - 6400} = -80 \pm j60 \text{ rad/s}$$

$$i_L = 15 + B'_1 e^{-80t} \cos 60t + B'_2 e^{-80t} \sin 60t$$

$$-30 = 15 + B'_1 \quad \therefore B'_1 = -45 \text{ mA}$$

$$\frac{di_L}{dt}(0) = -80B'_1 + 60B'_2 = 3$$

$$\therefore B'_2 = -10 \text{ mA}$$

$$i_L = 15 - 45e^{-80t} \cos 60t - 10e^{-80t} \sin 60t \text{ mA}, \quad t \geq 0$$

$$\text{P 6.40} \quad \alpha = \frac{1}{2RC} = \frac{10^6}{(2000)(5)} = 100$$

$$\alpha^2 = 10^4 = \omega_o^2 \quad \text{critical damping}$$


$$i_L = I_f + D'_1 t e^{-100t} + D'_2 e^{-100t} = 15 + D'_1 t e^{-100t} + D'_2 e^{-100t}$$

$$i_L(0) = -30 = 15 + D'_2; \quad \therefore D'_2 = -45 \text{ mA}$$

$$\frac{di_L}{dt}(0) = -100D'_2 + D'_1 = 3000 \times 10^{-3}$$


$$\therefore D'_1 = 3000 \times 10^{-3} + 100(-45 \times 10^{-3}) = -1500 \times 10^{-3}$$

$$i_L = 15 - 1500t e^{-100t} - 45e^{-100t} \text{ mA}, \quad t \geq 0$$

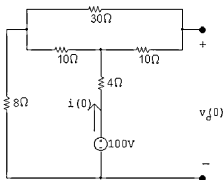P 6.41  $t < 0$ :

$$i(0) = \frac{100}{4 + 8 + 8} = \frac{100}{20} = 5 \text{ A}$$

$$v_o(0) = 100 - 5(4) - 10(5) \left( \frac{10}{50} \right) = 70 \text{ V}$$

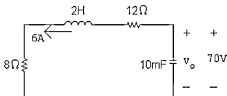 $t > 0$ :

$$\alpha = \frac{R}{2L} = \frac{20}{4} = 5, \quad \alpha^2 = 25$$

$$\omega_o^2 = \frac{1}{LC} = \frac{100}{2} = 50$$

$$\omega_o^2 > \alpha^2 \text{ underdamped}$$

$$v_o = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t; \quad \omega_d = \sqrt{50 - 25} = 5$$

$$v_o = B_1 e^{-5t} \cos 5t + B_2 e^{-5t} \sin 5t$$

$$v_o(0) = B_1 = 70 \text{ V}$$

$$C \frac{dv_o}{dt}(0) = -5, \quad \frac{dv_o}{dt} = \frac{-5}{10} \times 10^3 = -500 \text{ V/s}$$

$$\frac{dv_o}{dt}(0) = -5B_1 + 5B_2 = -500$$

$$5B_2 = -500 + 5B_1 = -500 + 350; \quad B_2 = -150/5 = -30 \text{ V}$$

$$\therefore v_o = 70e^{-5t} \cos 5t - 30e^{-5t} \sin 5t \text{ V}, \quad t \geq 0$$

P 6.42 [a] Let  $i$  be the current in the direction of the voltage drop  $v_o(t)$ . Then by hypothesis

$$i = i_f + B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t$$

$$i_f = i(\infty) = 0, \quad i(0) = \frac{V_g}{R} = B'_1$$

$$\text{Therefore } i = B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t$$

$$L \frac{di(0)}{dt} = 0, \quad \text{therefore } \frac{di(0)}{dt} = 0$$

$$\frac{di}{dt} = [(\omega_d B'_2 - \alpha B'_1) \cos \omega_d t - (\alpha B'_2 + \omega_d B'_1) \sin \omega_d t] e^{-\alpha t}$$

$$\text{Therefore } \omega_d B'_2 - \alpha B'_1 = 0; \quad B'_2 = \frac{\alpha}{\omega_d} B'_1 = \frac{\alpha}{\omega_d} \frac{V_g}{R}$$

Therefore

$$v_o = L \frac{di}{dt} = - \left\{ L \left( \frac{\alpha^2 V_g}{\omega_d R} + \frac{\omega_d V_g}{R} \right) \sin \omega_d t \right\} e^{-\alpha t}$$

$$= - \left\{ \frac{LV_g}{R} \left( \frac{\alpha^2}{\omega_d} + \omega_d \right) \sin \omega_d t \right\} e^{-\alpha t}$$

$$= - \frac{V_g L}{R} \left( \frac{\alpha^2 + \omega_d^2}{\omega_d} \right) e^{-\alpha t} \sin \omega_d t$$

$$v_o = - \frac{V_g}{RC \omega_d} e^{-\alpha t} \sin \omega_d t \text{ V, } t \geq 0^+$$

$$[b] \frac{dv_o}{dt} = - \frac{V_g}{\omega_d RC} \{ \omega_d \cos \omega_d t - \alpha \sin \omega_d t \} e^{-\alpha t}$$

$$\frac{dv_o}{dt} = 0 \quad \text{when} \quad \tan \omega_d t = \frac{\omega_d}{\alpha}$$

$$\text{Therefore } \omega_d t = \tan^{-1}(\omega_d/\alpha) \quad (\text{smallest } t)$$

$$t = \frac{1}{\omega_d} \tan^{-1} \left( \frac{\omega_d}{\alpha} \right)$$

P 6.43 [a] From Problem 6.42 we have

$$v_o = \frac{-V_g}{RC \omega_d} e^{-\alpha t} \sin \omega_d t$$

$$\alpha = \frac{R}{2L} = \frac{120}{0.01} = 12,000 \text{ rad/s}$$

$$\omega_d^2 = \frac{1}{LC} = \frac{10^{12}}{2500} = 400 \times 10^6$$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2} = 16 \text{ krad/s}$$

$$\frac{-V_g}{RC\omega_d} = \frac{-(-600)10^9}{(120)(500)(16) \times 10^3} = 625$$

$$\therefore v_o = 625e^{-12,000t} \sin 16,000t \text{ V}$$

[b] From Problem 6.42

$$t_d = \frac{1}{\omega_d} \tan^{-1} \left( \frac{\omega_d}{\alpha} \right) = \frac{1}{16,000} \tan^{-1} \left( \frac{16,000}{12,000} \right)$$

$$t_d = 57.96 \mu\text{s}$$

[c]  $v_{\max} = 625e^{-0.012(57.96)} \sin[(0.016)(57.96)] = 249.42 \text{ V}$

[d]  $R = 12 \Omega$ ;  $\alpha = 1200 \text{ rad/s}$

$$\omega_d = 19,963.97 \text{ rad/s}$$

$$v_o = 5009.02e^{-1200t} \sin 19,963.97t \text{ V}, \quad t \geq 0$$

$$t_d = 75.67 \mu\text{s}$$


$$v_{\max} = 4565.96 \text{ V}$$

P 6.44  $t < 0$ :

$$v_o(0^-) = v_o(0^+) = \frac{1000}{1250}(25) = 20 \text{ V}$$

$$i_L(0^-) = i_L(0^+) = 0$$

$t > 0$

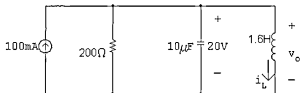

$$-100 + \frac{20}{0.2} + i_C(0^+) + 0 = 0; \quad \therefore i_C(0^+) = 0$$

$$\frac{1}{2RC} = \frac{10^6}{(400)(10)} = 250 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{10(1.6)} = 62,500$$

$$\therefore \alpha^2 = \omega_o^2 \text{ critically damped}$$

$$[\text{a}] \quad v_o = V_f + D'_1 t e^{-250t} + D'_2 e^{-250t}$$

$$V_f = 0$$

$$\frac{dv_o(0)}{dt} = -250D'_2 + D'_1 = 0$$

$$v_o(0^+) = 20 = D'_2$$

$$D'_1 = 250D'_2 = 5000 \text{ V/s}$$

$$\therefore v_o = 5000te^{-250t} + 20e^{-250t} \text{ V}, \quad t \geq 0^+$$

$$[\text{b}] \quad i_L = I_f + D'_3 t e^{-250t} + D'_4 e^{-250t}$$

$$i_L(0^+) = 0; \quad I_f = 100 \text{ mA}; \quad \frac{di_L(0^+)}{dt} = \frac{20}{1.6} = 12.5 \text{ A/s}$$

$$\therefore 0 = 100 + D'_4; \quad D'_4 = -100 \text{ mA};$$

$$-250D'_4 + D'_3 = 12.5; \quad D'_3 = -12.5 \text{ A/s}$$

$$\therefore i_L = 100 - 12,500te^{-250t} - 100e^{-250t} \text{ mA} \quad t \geq 0$$

$$\text{P 6.45} \quad [\text{a}] \quad w_L = \int_0^\infty p dt = \int_0^\infty v_o i_L dt$$

$$v_o = 5000te^{-250t} + 20e^{-250t} \text{ V}$$

$$i_L = 0.1 - 12.5te^{-250t} - 0.1e^{-250t} \text{ A}$$

$$p = 2e^{-250t} + 500te^{-250t} - 750te^{-500t} - 62,500t^2e^{-500t} - 2e^{-500t} \text{ W}$$

$$\frac{w_L}{2} = \int_0^\infty e^{-250t} dt + 250 \int_0^\infty te^{-250t} dt - 375 \int_0^\infty te^{-500t} dt -$$

$$31,250 \int_0^\infty t^2 e^{-500t} dt - \int_0^\infty e^{-500t} dt$$

$$= \frac{e^{-250t}}{-250} \Big|_0^\infty + \frac{250}{(250)^2} e^{-250t} (-250t - 1) \Big|_0^\infty -$$

$$\frac{375}{(500)^2} e^{-500t} (-500t - 1) \Big|_0^\infty -$$

$$\frac{31,250}{(-500)^3} e^{-500t} (500^2 t^2 + 1000t + 2) \Big|_0^\infty -$$

$$\frac{e^{-500t}}{(-500)} \Big|_0^\infty$$

All the upper limits evaluate to zero hence

$$\frac{w_L}{2} = \frac{1}{250} + \frac{250}{62,500} - \frac{375}{25 \times 10^4} - \frac{(31,250)(2)}{(5)^3 10^6} - \frac{1}{500}$$

$$w_L = 8 + 8 - 3 - 1 - 4 = 8 \text{ mJ}$$

Note this value corresponds to the final energy stored in the inductor, i.e.

$$w_L(\infty) = \frac{1}{2}(1.6)(0.1)^2 = 8 \text{ mJ}.$$

$$[\text{b}] \quad v = 5000te^{-250t} + 20e^{-250t} \text{ V}$$

$$i_R = \frac{v}{200} = 25te^{-250t} + 0.1e^{-250t} \text{ A}$$

$$p_R = vi_R = 2e^{-500t}[62,500t^2 + 500t + 1]$$

$$w_R = \int_0^\infty p_R dt$$

$$\begin{aligned} \frac{w_R}{2} &= 62,500 \int_0^\infty t^2 e^{-500t} dt + 500 \int_0^\infty t e^{-500t} dt + \int_0^\infty e^{-500t} dt \\ &= \frac{62,500e^{-500t}}{-125 \times 10^6} [25 \times 10^4 t^2 + 1000t + 2] \Big|_0^\infty + \\ &\quad \frac{500e^{-500t}}{25 \times 10^4} (-500t - 1) \Big|_0^\infty + \frac{e^{-500t}}{(-500)} \Big|_0^\infty \end{aligned}$$

Since all the upper limits evaluate to zero we have

$$\frac{w_R}{2} = \frac{62,500(2)}{125 \times 10^6} + \frac{500}{25 \times 10^4} + \frac{1}{500}$$

$$w_R = 2 + 4 + 4 = 10 \text{ mJ}$$

$$[\text{c}] \quad 100 = i_R + i_C + i_L \quad (\text{mA})$$

$$\begin{aligned} i_R + i_L &= 25,000te^{-250t} + 100e^{-250t} + 100 \\ &\quad - 12,500te^{-250t} - 100e^{-250t} \text{ mA} \\ &= 100 + 12,500te^{-250t} \text{ mA} \end{aligned}$$

$$\therefore i_C = 100 - (i_R + i_L) = -12,500te^{-250t} \text{ mA} = -12.5te^{-250t} \text{ A}$$

$$\begin{aligned} p_C &= vi_C = [5000te^{-250t} + 20e^{-250t}][-12.5te^{-250t}] \\ &= -250[250t^2e^{-500t} + te^{-500t}] \end{aligned}$$

$$\frac{w_C}{-250} = 250 \int_0^\infty t^2 e^{-500t} dt + \int_0^\infty te^{-500t} dt$$



$$\frac{w_C}{-250} = \frac{250e^{-500t}}{-125 \times 10^6} [25 \times 10^4 t^2 + 1000t + 2] \Big|_0^\infty + \frac{e^{-500t}}{25 \times 10^4} (-500t - 1) \Big|_0^\infty$$

Since all upper limits evaluate to zero we have

$$w_C = \frac{-250(250)(2)}{125 \times 10^6} - \frac{250(1)}{25 \times 10^4} = -1000 \times 10^{-6} - 10 \times 10^{-4} = -2 \text{ mJ}$$

Note this 2 mJ corresponds to the initial energy stored in the capacitor, i.e.,

$$w_C(0) = \frac{1}{2} (10 \times 10^{-6})(20)^2 = 2 \text{ mJ}.$$

Thus  $w_C(\infty) = 0 \text{ mJ}$  which agrees with the final value of  $v = 0$ .

[d]  $i_s = 100 \text{ mA}$

$$\begin{aligned} p_s(\text{del}) &= 100v_o \text{ mW} \\ &= 0.1[5000te^{-250t} + 20e^{-250t}] \\ &= 2e^{-250t} + 500te^{-250t} \text{ W} \\ \frac{w_s}{2} &= \int_0^\infty e^{-250t} dt + \int_0^\infty 250te^{-250t} dt \\ &= \frac{e^{-250t}}{-250} \Big|_0^\infty + \frac{250e^{-250t}}{62,500} (-250t - 1) \Big|_0^\infty \\ &= \frac{1}{250} + \frac{1}{250} \\ w_s &= \frac{2(2)}{250} = \frac{4}{250} = 16 \text{ mJ} \end{aligned}$$

[e]  $w_L = 8 \text{ mJ}$  (absorbed)

$w_R = 10 \text{ mJ}$  (absorbed)

$w_C = 2 \text{ mJ}$  (delivered)

$w_S = 16 \text{ mJ}$  (delivered)

$$\sum w_{\text{del}} = w_{\text{abs}} = 18 \text{ mJ}.$$

$$\text{P 6.46 [a]} \quad \omega_o^2 = \frac{1}{LC} = \frac{10^9}{(0.25)(160)} = \frac{10^8}{4} = 25 \times 10^6$$

$$\alpha = \frac{R}{2L} = \omega_o = 5000 \text{ rad/s}$$

$$\therefore R = (5000)(2)L = 2500 \Omega$$

[b]  $i(0) = i_L(0) = 24 \text{ mA}$

$$v_L(0) = 90 - (0.024)(2500) = 30 \text{ V}$$

$$\frac{di}{dt}(0) = \frac{30}{0.25} = 120 \text{ A/s}$$

[c]  $v_C = D_1 te^{-5000t} + D_2 e^{-5000t}$

$$v_C(0) = D_2 = 90 \text{ V}$$


$$\frac{dv_C}{dt}(0) = D_1 - 5000D_2 = \frac{i_C(0)}{C} = \frac{-i_L(0)}{C}$$

$$D_1 - 450,000 = -\frac{24 \times 10^{-3}}{160 \times 10^{-9}} = -150,000$$

$$\therefore D_1 = 300,000 \text{ V/s}$$

$$v_C = 300,000te^{-5000t} + 90e^{-5000t} \text{ V}, \quad t \geq 0^+$$


P 6.47  $t < 0$ :

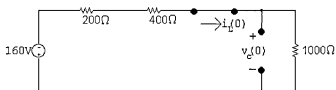

$$i_L(0) = \frac{-160}{1600} = -100 \text{ mA}$$

$$v_C(0) = 1000i_L(0) = -100 \text{ V}$$

$t > 0$ :

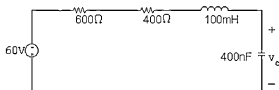

$$\alpha = \frac{R}{2L} = \frac{1000}{200} \times 10^3 = 5000 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{(10^9)(10^3)}{(100)(400)} = \frac{10^8}{4} = 25 \times 10^6$$

$$\omega_o = 5000 \text{ rad/s} \quad \therefore \text{critical damping}$$

$$v_C(t) = V_f + D'_1 t e^{-5000t} + D'_2 e^{-5000t}$$

$$v_C(0) = -100 \text{ V}; \quad V_f = -60 \text{ V}$$

$$\therefore -100 = -60 + D'_2; \quad D'_2 = -40 \text{ V}$$


$$C \frac{dv_C}{dt}(0) = i_L(0) = -100 \times 10^{-3}$$

$$\frac{dv_C}{dt}(0) = \frac{-100 \times 10^{-3}}{400 \times 10^{-9}} = -250,000 \text{ V/s}$$

$$\therefore D'_1 = 5000(-40) - 250,000 = -450,000$$

$$v_C(t) = -60 - 450,000 t e^{-5000t} - 40 e^{-5000t} \text{ V}, \quad t \geq 0$$

P 6.48 [a] For  $t > 0$ :

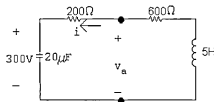

$$\text{Since } i(0^-) = i(0^+) = 0$$

$$v_a(0^+) = 300 \text{ V}$$

$$\text{[b] } v_a = 200i + 5 \times 10^4 \int_0^t i \, dx + 300$$

$$\frac{dv_a}{dt} = 200 \frac{di}{dt} + 5 \times 10^4 i$$

$$\frac{dv_a(0^+)}{dt} = 200 \frac{di(0^+)}{dt} + 5 \times 10^4 i(0^+) = 200 \frac{di(0^+)}{dt}$$

$$-L \frac{di(0^+)}{dt} = 300$$

$$\frac{di(0^+)}{dt} = -0.2(300) = -60 \text{ A/s}$$

$$\therefore \frac{dv_a(0^+)}{dt} = -12,000 \text{ V/s}$$

$$[c] \quad \alpha = \frac{R}{2L} = \frac{800}{10} = 80 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{(5)(20)} = 10^4$$

$$s_{1,2} = -80 \pm \sqrt{6400 - 10^4} = -80 \pm j60 \text{ rad/s}$$

Underdamped:

$$v_o = B_1 e^{-80t} \cos 60t + B_2 e^{-80t} \sin 60t$$

$$v_o(0) = B_1 = 300 \text{ V}$$

$$\frac{dv_o(0)}{dt} = -80B_1 + 60B_2 = -12,000; \quad \therefore B_2 = 200$$

$$v_o = 300e^{-80t} \cos 60t + 200e^{-80t} \sin 60t \text{ V}, \quad t \geq 0^+$$

P 6.49 [a] When  $L = 1.6 \text{ nH}$ ,

$$\begin{aligned} s_{1,2} &= -\frac{100}{3.2 \times 10^{-9}} \pm \sqrt{\left(\frac{100}{3.2} \times 10^9\right)^2 - \frac{10^{12}}{1.6 \times 10^{-9}}} \\ &= -3.125 \times 10^{10} \pm 1.875 \times 10^{10} \end{aligned}$$

$$s_1 = -12.5 \times 10^9 \text{ rad/s} \quad s_2 = -50 \times 10^9 \text{ rad/s}$$

$$\therefore v_o = V_f + A'_1 e^{-12.5 \times 10^9 t} + A'_2 e^{-50 \times 10^9 t}$$

$$V_f = 5 \text{ V}$$

$$v_o(0) = 1 \text{ V} = A'_1 + A'_2 + 5$$

$$\frac{dv_o(0)}{dt} = 0 = -12.5 \times 10^9 A'_1 - 50 \times 10^9 A'_2$$

$$\therefore A'_1 + A'_2 = -4; \quad A'_1 = -4A'_2$$

$$\therefore A'_1 = -\frac{16}{3} \text{ V}; \quad A'_2 = \frac{4}{3} \text{ V}$$

$$\therefore v_o = 5 - \frac{16}{3} e^{-12.5 \times 10^9 t} + \frac{4}{3} e^{-50 \times 10^9 t} \text{ V} \quad t \geq 0$$

[b] When  $L = 2.5 \text{ nH}$ ,

$$\frac{R}{2L} = 2 \times 10^{10}; \quad \left(\frac{R}{2L}\right)^2 = 4 \times 10^{20}$$

$$\frac{1}{LC} = \frac{10^{12}}{2.5 \times 10^{-9}} = 4 \times 10^{20}$$

$$\therefore \left(\frac{R}{2L}\right)^2 = \frac{1}{LC}; \quad s_{1,2} = -2 \times 10^{10} \text{ rad/s}$$

$$\therefore v_o = V_f + D'_1 t e^{-2 \times 10^{10} t} + D'_2 e^{-2 \times 10^{10} t}$$

$$V_f = 5 \text{ V}$$

$$v_o(0) = 5 + D'_2 = 1; \quad D'_2 = -4 \text{ V}$$

$$\frac{dv_o(0)}{dt} = 0 = D'_1 - 2 \times 10^{10} D'_2$$

$$\therefore D'_1 = -8 \times 10^{10} \text{ V/s}$$

$$\therefore v_o = 5 - 8 \times 10^{10} t e^{-2 \times 10^{10} t} - 4 e^{-2 \times 10^{10} t} \text{ V}, \quad t \geq 0$$

[c] When  $L = 5 \text{ nH}$ ,

$$\frac{R}{2L} = \frac{50}{5} \times 10^9 = 10^{10}$$

$$\frac{1}{LC} = \frac{10^{12} \times 10^9}{5} = 2 \times 10^{20}$$

$$s_{1,2} = -10^{10} \pm \sqrt{10^{20} - 2 \times 10^{20}} = -10^{10} \pm j10^{10} \text{ rad/s}$$

$$v_o = 5 + B'_1 e^{-10^{10} t} \cos 10^{10} t + B'_2 e^{10^{10} t} \sin 10^{10} t$$

$$v_o(0) = 5 + B'_1 = 1; \quad B'_1 = -4 \text{ V}$$

$$\frac{dv_o(0)}{dt} = -10^{10} B'_1 + 10^{10} B'_2 = 0; \quad B'_1 = B'_2 = -4 \text{ V}$$

$$v_o = 5 - 4 e^{-10^{10} t} (\cos 10^{10} t + \sin 10^{10} t) \text{ V}, \quad t \geq 0$$

[d] When  $L = 25 \text{ nH}$ ,

$$\frac{R}{2L} = \frac{50}{25} \times 10^9 = 2 \times 10^9 \left(\frac{R}{2L}\right)^2 = 4 \times 10^{18}$$

$$\frac{1}{LC} = \frac{10^{12} \times 10^9}{25} = 40 \times 10^{18}$$

$$s_{1,2} = -2 \times 10^9 \pm j6 \times 10^9 \text{ rad/s}$$

$$v_o = 5 + B'_1 e^{-2 \times 10^9 t} \cos 6 \times 10^9 t + B'_2 e^{-2 \times 10^9 t} \sin 6 \times 10^9 t$$

$$v_o(0) = 1 = 5 + B'_1; \quad B'_1 = -4 \text{ V}$$

$$\frac{dv_o(0)}{dt} = -2 \times 10^9 B'_1 + 6 \times 10^9 B'_2 = 0; \quad B'_2 = -\frac{4}{3} \text{ V}$$

$$v_o = 5 - 4 e^{-2 \times 10^9 t} (\cos 6 \times 10^9 t + (1/3) \sin 6 \times 10^9 t) \text{ V}, \quad t \geq 0$$

- P 6.50 Use the  $L = 0$  value of  $t_x$  as a first estimate. Then by successive approximations find that:

$$t_x = 133.79 \text{ ps} \quad \text{when} \quad L = 1.6 \text{ nH}$$

$$t_x = 134.64 \text{ ps} \quad \text{when} \quad L = 2.5 \text{ nH}$$

$$t_x = 147.41 \text{ ps} \quad \text{when} \quad L = 5 \text{ nH}$$

$$t_x = 268.64 \text{ ps} \quad \text{when} \quad L = 25 \text{ nH}$$

# Sinusoidal Steady State Analysis

## Drill Exercises

DE 7.1 [a]  $\omega = 2\pi f = 3769.91 \text{ rad/s}$ ,  $f = 600 \text{ Hz}$

[b]  $T = 1/f = 1.67 \text{ ms}$

[c]  $V_m = 10 \text{ V}$

[d]  $v(0) = 10(0.6) = 6 \text{ V}$

[e]  $\phi = -53.13^\circ$ ;  $\phi = \frac{-53.13^\circ(2\pi)}{360^\circ} = -0.9273 \text{ rad}$

[f]  $3769.91t = 143.13/57.3 = 2.498 \text{ rad}$ ,  $t = 662.62 \mu\text{s}$

[g]  $(dv/dt) = (-10)3769.91 \sin(3769.91t - 53.13^\circ)$

$(dv/dt) = 0$  when  $3769.91t - 53.13^\circ = 0^\circ$

or  $3769.91t = 0.9273 \text{ rad}$

Therefore  $t = 245.97 \mu\text{s}$

DE 7.2  $V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^{T/2} V_m^2 \sin^2 \frac{2\pi}{T} t dt}$

$$\int_0^{T/2} V_m^2 \sin^2 \left( \frac{2\pi}{T} t \right) dt = \frac{V_m^2}{2} \int_0^{T/2} \left( 1 - \cos \frac{4\pi}{T} t \right) dt = \frac{V_m^2 T}{4}$$

Therefore  $V_{\text{rms}} = \sqrt{\frac{1}{T} \frac{V_m^2 T}{4}} = \frac{V_m}{2}$

DE 7.3 [a] The numerical values of the terms in Eq. 7.9 are

$V_m = 20$ ,  $R/L = 1066.67$ ,  $\omega L = 60$

$\sqrt{R^2 + \omega^2 L^2} = 100$

$\phi = 25^\circ$ ,  $\theta = \tan^{-1} 60/80$ ,  $\theta = 36.87^\circ$

$i = \left[ -195.72e^{-1066.67t} + 200 \cos(800t - 11.87^\circ) \right] \text{ mA}, \quad t \geq 0$

- [b] Transient component  $= -195.72e^{-1066.67t}$  mA  
 Steady-state component  $= 200 \cos(800t - 11.87^\circ)$  mA  
 [c] By direct substitution into Eq 7.9,  $i(1.875 \text{ ms}) = 28.39 \text{ mA}$   
 [d]  $0.2 \text{ A}$ ,  $800 \text{ rad/s}$ ,  $-11.87^\circ$   
 [e] The current lags the voltage by  $36.87^\circ$ .

DE 7.4 [a]  $\mathbf{V} = 170/\underline{-40^\circ} \text{ V}$

[b]  $\mathbf{I} = 10/\underline{-70^\circ} \text{ A}$

[c]  $\mathbf{I} = 5/\underline{36.87^\circ} + 10/\underline{-53.13^\circ}$   
 $= 4 + j3 + 6 - j8 = 10 - j5 = 11.18/\underline{-26.57^\circ} \text{ A}$

[d]  $\mathbf{V} = 300/\underline{45^\circ} - 100/\underline{-60^\circ} = 212.13 + j212.13 - (50 - j86.60)$   
 $= 162.13 + j298.73 = 339.90/\underline{61.51^\circ} \text{ mV}$

DE 7.5 [a]  $v = 18.6 \cos(\omega t - 54^\circ) \text{ V}$

[b]  $\mathbf{I} = 20/\underline{45^\circ} - 50/\underline{-30^\circ} = 14.14 + j14.14 - 43.3 + j25$   
 $= -29.16 + j39.14 = 48.81/\underline{126.68^\circ}$

Therefore  $i = 48.81 \cos(\omega t + 126.68^\circ) \text{ mA}$

[c]  $\mathbf{V} = 20 + j80 - 30/\underline{15^\circ} = 20 + j80 - 28.98 - j7.76$   
 $= -8.98 + j72.24 = 72.79/\underline{97.08^\circ}$

$v = 72.79 \cos(\omega t + 97.08^\circ) \text{ V}$

DE 7.6 [a]  $\omega L = (10^4)(20 \times 10^{-3}) = 200 \Omega$

[b]  $Z_L = j200 \Omega$

[c]  $\mathbf{V}_L = \mathbf{I}Z_L = (10/\underline{30^\circ})(200/\underline{90^\circ}) \times 10^{-3} = 2/\underline{120^\circ} \text{ V}$

[d]  $v_L = 2 \cos(10,000t + 120^\circ) \text{ V}$

DE 7.7 [a]  $X_C = \frac{-1}{\omega C} = -\frac{10^6}{4000(5)} = -50 \Omega$

[b]  $Z_C = jX_C = -j50 \Omega$

[c]  $\mathbf{I} = \frac{30/\underline{25^\circ}}{50/\underline{-90^\circ}} = 0.6/\underline{115^\circ} \text{ A}$

[d]  $i = 0.6 \cos(4000t + 115^\circ) \text{ A}$



$$\text{DE 7.8 } \mathbf{I}_1 = 100/\underline{25^\circ} = 90.63 + j42.26$$

$$\mathbf{I}_2 = 100/\underline{145^\circ} = -81.92 + j57.36$$

$$\mathbf{I}_3 = 100/\underline{-95^\circ} = -8.71 - j99.62$$

$$\mathbf{I}_4 = -(\mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3) = (0 + j0) \text{ A,} \quad \text{therefore } i_4 = 0 \text{ A}$$

$$\text{DE 7.9 [a] } \mathbf{I} = \frac{125/\underline{-60^\circ}}{|Z|/\theta_z} = \frac{125}{|Z|} \angle (-60 - \theta_z)^\circ$$

$$\text{But } -60 - \theta_z = -105^\circ \quad \therefore \theta_z = 45^\circ$$


$$Z = 90 + j160 + jX_C$$

$$\therefore X_C = -70 \Omega; \quad -\frac{1}{\omega C} = -70$$

$$\therefore C = \frac{1}{(70)(5000)} = 2.86 \mu\text{F}$$

$$\text{[b] } \mathbf{I} = \frac{125/\underline{-60^\circ}}{(90 + j90)} = 0.982/\underline{-105^\circ} \text{ A;} \quad \therefore |\mathbf{I}| = 0.982 \text{ A}$$

DE 7.10 [a]

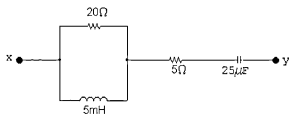

$$\omega = 2000 \text{ rad/s}$$

$$\omega L = 10 \Omega, \quad \frac{-1}{\omega C} = -20 \Omega$$

$$Z_{xy} = \frac{20(j10)}{(20 + j10)} + 5 - j20 = 4 + j8 + 5 - j20 = (9 - j12) \Omega$$

$$\text{[b] } \omega L = 40 \Omega, \quad \frac{-1}{\omega C} = -5 \Omega$$

$$Z_{xy} = 5 - j5 + \left[ \frac{(20)(j40)}{20 + j40} \right] = 5 - j5 + 16 + j8 = (21 + j3) \Omega$$

$$\begin{aligned}
 \text{[c]} \quad Z_{xy} &= \left[ \frac{20(j\omega L)}{20 + j\omega L} \right] + \left( 5 - \frac{j10^6}{25\omega} \right) \\
 &= \frac{20\omega^2 L^2}{400 + \omega^2 L^2} + \frac{j400\omega L}{400 + \omega^2 L^2} + 5 - \frac{j10^6}{25\omega}
 \end{aligned}$$

The impedance will be purely resistive when the  $j$  terms cancel, i.e.,

$$\frac{400\omega L}{400 + \omega^2 L^2} = \frac{10^6}{25\omega}$$

Solving for  $\omega$  yields  $\omega = 4000$  rad/s.

$$\text{[d]} \quad Z_{xy} = \frac{20\omega^2 L^2}{400 + \omega^2 L^2} + 5 = 10 + 5 = 15 \Omega$$

DE 7.11

$$\mathbf{V} = 150\angle 0^\circ, \quad \mathbf{I}_s = \frac{150\angle 0^\circ}{15} = 10\angle 0^\circ \text{ A}$$

$$\mathbf{I}_L = \frac{10(20)}{20 + j20} = 5 - j5 = 7.07\angle -45^\circ \text{ A}$$

$$i_L = 7.07 \cos(4000t - 45^\circ) \text{ A}, \quad I_m = 7.07 \text{ A}$$

DE 7.12

$$\begin{aligned}
 \text{[a]} \quad Y &= \frac{1}{3 + j4} + \frac{1}{16 - j12} + \frac{1}{-j4} \\
 &= 0.12 - j0.16 + 0.04 + j0.03 + j0.25 \\
 &= 0.16 + j0.12 = 200\angle 36.87^\circ \text{ mS}
 \end{aligned}$$

$$\text{[b]} \quad G = 160 \text{ mS}$$


$$\text{[c]} \quad B = 120 \text{ mS}$$

$$\text{[d]} \quad \mathbf{I} = 8\angle 0^\circ \text{ A}, \quad \mathbf{V} = \frac{\mathbf{I}}{Y} = \frac{8}{0.2\angle 36.87^\circ} = 40\angle -36.87^\circ \text{ V}$$

$$\mathbf{I}_C = \frac{\mathbf{V}}{Z_C} = \frac{40\angle -36.87^\circ}{4\angle -90^\circ} = 10\angle 53.13^\circ \text{ A}$$

$$i_C = 10 \cos(\omega t + 53.13^\circ) \text{ A}, \quad I_m = 10 \text{ A}$$

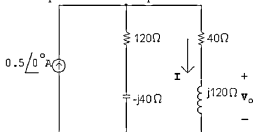DE 7.13 Construct the phasor domain equivalent circuit:



$$\mathbf{I} = \frac{0.5(120 - j40)}{160 + j80} = 0.25 - j0.25 \text{ A}$$

$$V_o = j120I = 30 + j30 = 42.43\angle 45^\circ$$

$$v_o = 42.43 \cos(2000t + 45^\circ) \text{ V}$$


DE 7.14 Use the lower node as the reference node. Let  $V_1$  = node voltage across the  $20\Omega$  resistor and  $V_{Th}$  = node voltage across the capacitor. Writing the node voltage equations gives us

$$\frac{V_1}{20} - 2\angle 45^\circ + \frac{V_1 - 10I_x}{j10} = 0 \quad \text{and} \quad V_{Th} = \frac{-j10}{10 - j10}(10I_x)$$

We also have

$$I_x = \frac{V_1}{20}$$

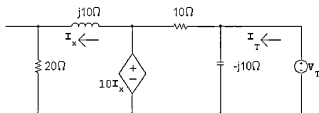Solving these equations for  $V_{Th}$  gives  $V_{Th} = 10\angle 45^\circ \text{ V}$ . To find the Thévenin impedance, we remove the independent current source and apply a test voltage source at the terminals a, b. Thus



It follows from the circuit that


$$10I_x = (20 + j10)I_x$$

Therefore

$$I_x = 0 \quad \text{and} \quad I_T = \frac{V_T}{-j10} + \frac{V_T}{10}$$

$$Z_{Th} = \frac{V_T}{I_T}, \quad \text{therefore} \quad Z_{Th} = (5 - j5)\Omega$$

DE 7.15 Short circuit current

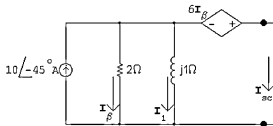


With the short circuit

$$\mathbf{I}_\beta = \frac{-6\mathbf{I}_\beta}{2}$$

$$2\mathbf{I}_\beta = -6\mathbf{I}_\beta; \quad \therefore \mathbf{I}_\beta = 0$$

$$\mathbf{I}_1 = 0; \quad \therefore \mathbf{I}_{sc} = 10/\underline{-45^\circ} \text{ A} = \mathbf{I}_N$$

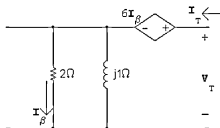The Norton impedance is the same as the Thévenin impedance. Thus



$$\mathbf{V}_T = 6\mathbf{I}_\beta + 2\mathbf{I}_\beta = 8\mathbf{I}_\beta, \quad \mathbf{I}_\beta = \frac{j1}{2+j1}\mathbf{I}_T$$


$$\mathbf{Z}_{Th} = \frac{\mathbf{V}_T}{\mathbf{I}_T} = \frac{8\mathbf{I}_\beta}{[(2+j1)/j1]\mathbf{I}_\beta} = \frac{j8}{2+j1} = 1.6 + j3.2\Omega$$

DE 7.16 The phasor domain circuit is as shown in the following diagram. The node voltage equation is

$$-10 + \frac{\mathbf{V}}{5} + \frac{9\mathbf{V}}{-j20} + \frac{\mathbf{V}}{j5} + \frac{\mathbf{V} - 100/\underline{-90^\circ}}{20} = 0$$

$$\text{Therefore } \mathbf{V} = 10 - j30 = 31.62/\underline{-71.57^\circ}$$

$$\text{Therefore } v = 31.62 \cos(50,000t - 71.57^\circ) \text{ V}$$

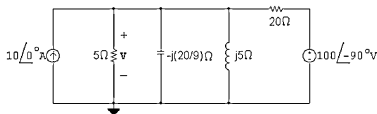

DE 7.17 Let  $\mathbf{I}_a$ ,  $\mathbf{I}_b$ , and  $\mathbf{I}_c$  be the three clockwise mesh currents going from left to right. Summing the voltages around meshes a and b gives

$$33.8 = (1 + j2)\mathbf{I}_a + (3 - j5)(\mathbf{I}_a - \mathbf{I}_b)$$

and

$$0 = (3 - j5)(\mathbf{I}_b - \mathbf{I}_a) + 2(\mathbf{I}_b - \mathbf{I}_c).$$

But

$$\mathbf{V}_x = -j5(\mathbf{I}_a - \mathbf{I}_b),$$

therefore

$$\mathbf{I}_c = -0.75[-j5(\mathbf{I}_a - \mathbf{I}_b)].$$

Solving for  $\mathbf{I} = \mathbf{I}_a = 29 + j2 = 29.07\angle 3.95^\circ \text{ A}$ .

DE 7.18 [a]  $\mathbf{V} = 100\angle -45^\circ \text{ V}$ ,  $\mathbf{I} = 20\angle 15^\circ \text{ A}$

Therefore

$$P = \frac{1}{2}(100)(20)\cos[-45 - (15)] = 500 \text{ W}, \quad \mathbf{A} \rightarrow \mathbf{B}$$

$$Q = 1000\sin -60^\circ = -866.03 \text{ VAR}, \quad \mathbf{B} \rightarrow \mathbf{A}$$

[b]  $\mathbf{V} = 100\angle -45^\circ$ ,  $\mathbf{I} = 20\angle 165^\circ$

$$P = 1000\cos(-210^\circ) = -866.03 \text{ W}, \quad \mathbf{B} \rightarrow \mathbf{A}$$

$$Q = 1000\sin(-210^\circ) = 500 \text{ VAR}, \quad \mathbf{A} \rightarrow \mathbf{B}$$

[c]  $\mathbf{V} = 106\angle -45^\circ$ ,  $\mathbf{I} = 20\angle -105^\circ$

$$P = 1000\cos(60^\circ) = 500 \text{ W}, \quad \mathbf{A} \rightarrow \mathbf{B}$$

$$Q = 1000\sin(60^\circ) = 866.03 \text{ VAR}, \quad \mathbf{A} \rightarrow \mathbf{B}$$

[d]  $P = 1000\cos(-120^\circ) = -500 \text{ W}$ ,  $\mathbf{B} \rightarrow \mathbf{A}$

$$Q = 1000\sin(-120^\circ) = -866.03 \text{ VAR}, \quad \mathbf{B} \rightarrow \mathbf{A}$$

DE 7.19

$$p_f = \cos(\theta_v - \theta_i) = \cos[15 - (75)] = \cos -60^\circ = 0.5 \text{ leading}$$

$$r_f = \sin(\theta_v - \theta_i) = \sin -60^\circ = -0.866$$

DE 7.20 From Example 7.4,

$$\begin{aligned}
 I_{\text{eff}} &= \frac{0.18}{\sqrt{3}} \\
 P &= I_{\text{eff}}^2 R \\
 &= \left( \frac{0.0324}{3} \right) (5000) \\
 &= 54 \text{ W}
 \end{aligned}$$

DE 7.21 [a]  $Z = (39 + j26) \parallel (-j52) = 48 - j20 = 52 \angle -22.62^\circ \Omega$ 

$$\text{Therefore } \mathbf{I}_\ell = \frac{250 \angle 0^\circ}{48 - j20 + 1 + j4} = 4.85 \angle 18.08^\circ \text{ A(rms)}$$

$$\mathbf{V}_L = Z \mathbf{I}_\ell = (52 \angle -22.62^\circ)(4.85 \angle 18.08^\circ) = 252.20 \angle -4.54^\circ \text{ V(rms)}$$

$$\mathbf{I}_L = \frac{\mathbf{V}_L}{39 + j26} = 5.38 \angle -38.23^\circ \text{ A(rms)}$$

$$\begin{aligned}
 \text{[b] } S_L &= (252.20 \angle -4.54^\circ)(5.38 \angle +38.23^\circ) = 1357 \angle 33.69^\circ \\
 &= (1129.09 + j752.73) \text{ VA}
 \end{aligned}$$

$$P_L = 1129.09 \text{ W}; \quad Q_L = 752.73 \text{ VAR}$$

$$\text{[c] } P_\ell = |\mathbf{I}_\ell|^2 1 = (4.85)^2 \cdot 1 = 23.52 \text{ W}; \quad Q_\ell = |\mathbf{I}_\ell|^2 4 = 94.09 \text{ VAR}$$

$$\text{[d] } S_g(\text{delivering}) = 250 \mathbf{I}_\ell^* = (1152.62 - j376.36) \text{ VA}$$

Therefore the source is delivering 1152.62 W and absorbing 376.36 magnetizing VAR.

$$\text{[e] } Q_{\text{cap}} = \frac{|\mathbf{V}_L|^2}{-52} = \frac{(252.20)^2}{-52} = -1223.18 \text{ VAR}$$

Therefore the capacitor is delivering 1223.18 magnetizing VAR.

$$\text{Check: } 94.09 + 752.73 + 376.36 = 1223.18 \text{ VAR} \quad \text{and}$$

$$1129.09 + 23.52 = 1152.62 \text{ W}$$

DE 7.22 Series circuit derivation:

$$250 \mathbf{I}^* = (40,000 - j30,000)$$

$$\text{Therefore } \mathbf{I}^* = 160 - j120 = 200 \angle -36.87^\circ \text{ A(rms)}$$

$$\mathbf{I} = 200 \angle 36.87^\circ \text{ A(rms)}$$

$$Z = \frac{250}{200/\underline{36.87^\circ}} = 1.25/\underline{-36.87^\circ} = (1 - j0.75) \Omega$$

$$\text{Therefore } R = 1 \Omega, \quad X_C = -0.75 \Omega$$

Parallel circuit derivation:

$$P = \frac{(250)^2}{R}; \quad \text{therefore } R = \frac{(250)^2}{40,000} = 1.5625 \Omega$$

$$Q = \frac{(250)^2}{X_C}; \quad \text{therefore } X_C = \frac{(250)^2}{-30,000} = -2.083 \Omega$$

DE 7.23

$$S_1 = 15,000(0.6) + j15,000(0.8) = 9000 + j12,000 \text{ VA}$$

$$S_2 = 6000(0.8) + j6000(0.6) = 4800 - j3600 \text{ VA}$$

$$S_T = S_1 + S_2 = 13,800 + j8400 \text{ VA}$$

$$S_T = 200\mathbf{I}^*; \quad \text{therefore } \mathbf{I}^* = 69 + j42 \quad \mathbf{I} = 69 - j42 \text{ A}$$

$$\mathbf{V}_s = 200 + j\mathbf{I} = 200 + j69 + 42 = 242 + j69 = 251.64/\underline{15.91^\circ} \text{ V(rms)}$$

## Problems

P 7.1 [a] By hypothesis

$$i = 10 \cos(\omega t + \theta)$$

$$\frac{di}{dt} = -10\omega \sin(\omega t + \theta)$$


$$\therefore 10\omega = 20,000\pi; \quad \omega = 2000\pi \text{ rad/s}$$

$$[b] f = \frac{\omega}{2\pi} = 1000 \text{ Hz}; \quad T = \frac{1}{f} = 1 \text{ ms} = 1000 \mu\text{s}$$

$$\frac{150}{1000} = \frac{3}{20}, \quad \therefore \theta = -90 - \frac{3}{20}(360) = -144^\circ$$

$$\therefore i = 10 \cos(2000\pi t - 144^\circ) \text{ A}$$

P 7.2

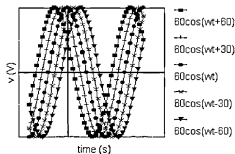[a] Left as  $\phi$  becomes more positive

[b] Right

P 7.3 [a] 170 V

$$[b] 2\pi f = 120\pi; \quad f = 60 \text{ Hz}$$

$$[c] \omega = 120\pi = 376.99 \text{ rad/s}$$

$$[d] \theta(\text{rad}) = \frac{-\pi}{180}(60) = \frac{-\pi}{3} = -1.05 \text{ rad}$$

$$[e] \theta = -60^\circ$$

$$[f] T = \frac{1}{f} = \frac{1}{60} = 16.67 \text{ ms}$$

$$[g] 120\pi t - \frac{\pi}{3} = 0; \quad \therefore t = \frac{1}{360} = 2.78 \text{ ms}$$



$$\begin{aligned}
 \text{[h]} \quad v &= 170 \cos \left[ 120\pi \left( t + \frac{0.125}{18} \right) - \frac{\pi}{3} \right] \\
 &= 170 \cos[120\pi t + (15\pi/18) - (\pi/3)] \\
 &= 170 \cos[120\pi t + (\pi/2)] \\
 &= -170 \sin 120\pi t \text{ V}
 \end{aligned}$$

$$\text{[i]} \quad 120\pi(t - t_o) - (\pi/3) = 120\pi t - (\pi/2)$$

$$\therefore 120\pi t_o = \frac{\pi}{6}; \quad t_o = \frac{25}{18} \text{ ms}$$

$$\text{[j]} \quad 120\pi(t - t_o) - (\pi/3) = 120\pi t$$

$$\therefore 120\pi t_o = \frac{\pi}{3}; \quad t_o = \frac{25}{9} \text{ ms}$$

$$\text{P 7.4 [a]} \quad \frac{T}{2} = \frac{1250}{6} + \frac{250}{6} = 250 \mu\text{s}; \quad T = 500 \mu\text{s}$$

$$f = \frac{1}{T} = \frac{10^6}{500} = 2000 \text{ Hz}$$

$$\text{[b]} \quad v = V_m \sin(\omega t + \theta)$$

$$\omega = 2\pi f = 4000\pi \text{ rad/s}$$

$$4000\pi \left( \frac{-250}{6} \times 10^{-6} \right) + \theta = 0; \quad \therefore \theta = \frac{\pi}{6} \text{ rad} = 30^\circ$$

$$v = V_m \sin[4000\pi t + 30^\circ]$$

$$75 = V_m \sin 30^\circ; \quad V_m = 150 \text{ V}$$

$$v = 150 \sin[4000\pi t + 30^\circ] = 150 \cos[4000\pi t - 60^\circ] \text{ V}$$

$$\text{P 7.5 [a]} \quad \text{From Eq. 7.9 we have}$$

$$L \frac{di}{dt} = \frac{V_m R \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} e^{-(R/L)t} - \frac{\omega L V_m \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}}$$

$$Ri = \frac{-V_m R \cos(\phi - \theta) e^{-(R/L)t}}{\sqrt{R^2 + \omega^2 L^2}} + \frac{V_m R \cos(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}}$$

$$L \frac{di}{dt} + Ri = V_m \left[ \frac{R \cos(\omega t + \phi - \theta) - \omega L \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} \right]$$

But

$$\frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \cos \theta \quad \text{and} \quad \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} = \sin \theta$$

Therefore the right-hand side reduces to

$$V_m \cos(\omega t + \phi)$$

At  $t = 0$ , Eq. 7.9 reduces to

$$i(0) = \frac{-V_m \cos(\phi - \theta)}{\sqrt{R^2 - \omega^2 L^2}} + \frac{V_m \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} = 0$$

$$[b] \quad i_{ss} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

Therefore

$$L \frac{di_{ss}}{dt} = \frac{-\omega L V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi - \theta)$$

and

$$Ri_{ss} = \frac{V_m R}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

$$L \frac{di_{ss}}{dt} + Ri_{ss} = V_m \left[ \frac{R \cos(\omega t + \phi - \theta) - \omega L \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} \right]$$

$$= V_m \cos(\omega t + \phi)$$

P 7.6 [a]  $Y = 100/\underline{45^\circ} + 500/\underline{-60^\circ} = 483.86/\underline{-48.48^\circ}$

$$y = 483.86 \cos(300t - 48.48^\circ)$$

[b]  $Y = 250/\underline{30^\circ} - 150/\underline{50^\circ} = 120.51/\underline{4.8^\circ}$

$$y = 120.51 \cos(377t + 4.8^\circ)$$

[c]  $Y = 60/\underline{60^\circ} - 120/\underline{-215^\circ} + 100/\underline{90^\circ} = 152.88/\underline{32.94^\circ}$

$$y = 152.88 \cos(100t + 32.94^\circ)$$

[d]  $Y = 100/\underline{40^\circ} + 100/\underline{160^\circ} + 100/\underline{-80^\circ} = 0$

$$y = 0$$

P 7.7  $u = \int_{t_o}^{t_o+T} V_m^2 \cos^2(\omega t + \phi) dt$

$$= V_m^2 \int_{t_o}^{t_o+T} \frac{1}{2} + \frac{1}{2} \cos(2\omega t + 2\phi) dt$$

$$= \frac{V_m^2}{2} \left\{ \int_{t_o}^{t_o+T} dt + \int_{t_o}^{t_o+T} \cos(2\omega t + 2\phi) dt \right\}$$

$$= \frac{V_m^2}{2} \left\{ T + \frac{1}{2\omega} [\sin(2\omega t + 2\phi)]_{t_o}^{t_o+T} \right\}$$


$$= \frac{V_m^2}{2} \left\{ T + \frac{1}{2\omega} [\sin(2\omega t_o + 4\pi + 2\phi) - \sin(2\omega t_o + 2\phi)] \right\}$$

$$= V_m^2 \left( \frac{T}{2} \right) + \frac{1}{2\omega} (0) = V_m^2 \left( \frac{T}{2} \right)$$

P 7.8  $V_m = \sqrt{2}V_{\text{rms}} = \sqrt{2}(120) = 169.71 \text{ V}$

P 7.9 [a]  $j\omega L = j(5 \times 10^4)(40 \times 10^{-6}) = j2 \Omega$
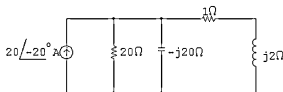
$$\frac{1}{j\omega C} = -j\frac{10^6}{5 \times 10^4} = -j20 \Omega; \quad \mathbf{I}_g = 20/-20^\circ \text{ A}$$



[b]  $\mathbf{V}_o = 20/-20^\circ Z_e$

$$Z_e = \frac{1}{Y_e}; \quad Y_e = \frac{1}{20} + j\frac{1}{20} + \frac{1}{1+j2}$$


$$Y_e = 0.05 + j0.05 + 0.20 - j0.40 = 0.25 - j0.35 \text{ S}$$

$$Z_e = \frac{1}{0.25 - j0.35} = 2.32/54.46^\circ \Omega$$

$$\mathbf{V}_o = (20/-20^\circ)(2.32/54.46^\circ) = 46.4/34.46^\circ \text{ V}$$

[c]  $v_o = 46.4 \cos(5 \times 10^4 t + 34.46^\circ) \text{ V}$

P 7.10 [a]

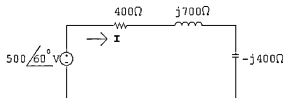

[b]  $\mathbf{I} = \frac{500/60^\circ}{400 + j700 - j400} = 1/23.13^\circ \text{ A}$

[c]  $i = 1 \cos(8000t + 23.13^\circ) \text{ A}$

P 7.11 [a] 50 Hz

[b]  $\theta_o = 0^\circ$

[c]  $\mathbf{I} = \frac{340/0^\circ}{j\omega L} = \frac{340}{\omega L} \angle -90^\circ = 8.5 \angle -90^\circ; \quad \theta_i = -90^\circ$

[d]  $\frac{340}{\omega L} = 8.5; \quad \omega L = 40 \Omega$

[e]  $L = \frac{40}{100\pi} = \frac{400}{\pi} \text{ mH} = 127.32 \text{ mH}$

[f]  $Z_L = j\omega L = j40 \Omega$

P 7.12 [a]  $\omega = 2\pi f = 80\pi \times 10^3 = 251.33 \text{ krad/s} = 251,327.41 \text{ rad/s}$

[b]  $\mathbf{I} = \frac{2.5 \times 10^{-3} \angle 0^\circ}{1/j\omega C} = j\omega C(2.5 \times 10^{-3}) \angle 0^\circ = 2.5 \times 10^{-3} \omega C \angle 90^\circ$

$\therefore \theta_i = 90^\circ$

[c]  $125.66 \times 10^{-6} = 2.5 \times 10^{-3} \omega C$

$\frac{1}{\omega C} = \frac{2.5 \times 10^{-3}}{125.66 \times 10^{-6}} = 19.89 \Omega, \quad \therefore X_C = -19.89 \Omega$

[d]  $C = \frac{1}{19.89(\omega)} = \frac{1}{(19.89)(80\pi \times 10^3)}$


$C = 0.2 \times 10^{-6} = 0.2 \mu\text{F}$

[e]  $Z_c = j \left( \frac{-1}{\omega C} \right) = -j19.89 \Omega$

P 7.13  $\frac{1}{j\omega C} = \frac{10^9}{(31.25)(8000)} = -j4000 \Omega$

$j\omega L = j8000(500)10^{-3} = j4000 \Omega$

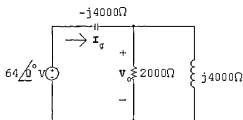$\mathbf{V}_g = 64 \angle 0^\circ \text{ V}$



$Z_e = \frac{(2000)(j4000)}{2000 + j4000} = 1600 + j800 \Omega$

$Z_T = 1600 + j800 - j4000 = 1600 - j3200 \Omega$

$\mathbf{I}_g = \frac{64 \angle 0^\circ}{1600 - j3200} = 8 + j16 \text{ mA}$

$\mathbf{V}_o = Z_e \mathbf{I}_g = (1600 + j800)(0.008 + j0.016) = j32 = 32 \angle 90^\circ \text{ V}$

$v_o = 32 \cos(8000t + 90^\circ) \text{ V}$

$$\text{P 7.14} \quad Z = 400 + j(5)(40) - j \frac{1000}{(5)(0.4)} = 500 / -36.87^\circ \Omega$$

$$I_o = \frac{750 / 0^\circ \times 10^{-3}}{500 / -36.87^\circ} = 1.5 / 36.87^\circ \text{ mA}$$

$$i_o(t) = 1.5 \cos(5000t + 36.87^\circ) \text{ mA}$$

$$\text{P 7.15} \quad [\text{a}] \quad Z_p = \frac{\frac{R}{j\omega C}}{R + (1/j\omega C)} = \frac{R}{1 + j\omega RC}$$

$$= \frac{12,500}{1 + j(1000)(12,500)C} = \frac{12,500}{1 + j12.5 \times 10^6 C}$$

$$= \frac{12,500(1 - j12.5 \times 10^6 C)}{1 + 156.25 \times 10^{12} C^2}$$

$$= \frac{12,500}{1 + 156.25 \times 10^{12} C^2} - j \frac{156.25 \times 10^9 C}{1 + 156.25 \times 10^{12} C^2}$$

$$j\omega L = j1000(5) = j5000$$

$$\therefore 5000 = \frac{156.25 \times 10^9 C}{1 + 156.25 \times 10^{12} C^2}$$

$$\therefore 781.25 \times 10^{15} C^2 - 156.25 \times 10^9 C + 5000 = 0$$

$$\therefore C^2 - 20 \times 10^{-8} C + 64 \times 10^{-16} = 0$$

$$\therefore C_{1,2} = 10 \times 10^{-8} \pm \sqrt{100 \times 10^{-16} - 64 \times 10^{-16}}$$

$$C_1 = 10 \times 10^{-8} + 6 \times 10^{-8} = 16 \times 10^{-8} = 160 \text{ nF} = 0.16 \mu\text{F}$$

$$C_2 = 10 \times 10^{-8} - 6 \times 10^{-8} = 4 \times 10^{-8} = 40 \text{ nF} = 0.04 \mu\text{F}$$

$$[\text{b}] \quad R_e = \frac{12,500}{1 + 156.25 \times 10^{12} C^2}$$

$$\text{When } C = 160 \text{ nF} \quad R_e = 2500 \Omega;$$

$$I_g = \frac{250 / 0^\circ}{2500} = 0.1 / 0^\circ \text{ A}; \quad i_g = 100 \cos 1000t \text{ mA}$$

$$\text{When } C = 40 \text{ nF} \quad R_e = 10,000 \Omega;$$

$$I_g = \frac{250 / 0^\circ}{10,000} = 0.025 / 0^\circ \text{ A}; \quad i_g = 25 \cos 1000t \text{ mA}$$

$$\begin{aligned}
 \text{P 7.16 [a]} \quad Y_p &= \frac{1}{10 + j2\omega} + j4 \times 10^{-3}\omega \\
 &= \frac{10 - j2\omega}{100 + 4\omega^2} + j4 \times 10^{-3}\omega \\
 &= \frac{10}{100 + 4\omega^2} - \frac{j2\omega}{100 + 4\omega^2} + j4 \times 10^{-3}\omega
 \end{aligned}$$

$Y_p$  is real when

$$4 \times 10^{-3}\omega = \frac{2\omega}{100 + 4\omega^2}$$

$$\text{or} \quad \omega^2 = 100; \quad \omega = 10 \text{ rad/s}; \quad f = 5/\pi = 1.59\text{Hz}$$

$$\text{[b]} \quad Y_p(10 \text{ rad/s}) = \frac{10}{500} = 20 \text{ mS}$$

$$Z_p(10 \text{ rad/s}) = \frac{10^3}{20} = 50 \Omega$$

$$Z(10 \text{ rad/s}) = 50 + 150 = 200 \Omega$$

$$\mathbf{I}_o = \frac{\mathbf{V}_g}{200} \text{ A} = \frac{10\angle 0^\circ}{200} = 50\angle 0^\circ \text{ mA}$$

$$i_o = 50 \cos 10t \text{ mA}$$

$$\text{P 7.17} \quad \mathbf{V}_g = 50\angle -45^\circ \text{ V}; \quad \mathbf{I}_g = 100\angle -8.13^\circ \text{ mA}$$

$$Z = \frac{\mathbf{V}_g}{\mathbf{I}_g} = 500\angle -36.87^\circ \Omega = 400 - j300 \Omega$$

$$Z = 400 + j \left( 0.04\omega - \frac{2.5 \times 10^6}{\omega} \right)$$

$$\therefore 0.04\omega - \frac{2.5 \times 10^6}{\omega} = -300$$


$$\therefore \omega^2 + 7500\omega - 62.5 \times 10^6 = 0$$

$$\therefore \omega = -3750 \pm \sqrt{(3750)^2 + 62.5 \times 10^6} = -3750 \pm 8750$$

$$\omega > 0, \quad \therefore \omega = 5000 \text{ rad/s}$$

P 7.18  $j\omega L = j1.6 \times 10^6(25 \times 10^{-6}) = j40 \Omega$
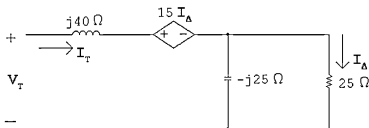
$$\frac{1}{j\omega C} = \frac{10^{-6} \times 10^9}{j1.6(25)} = -j25 \Omega$$



$$V_T = j40I_T + 15I_\Delta + 25I_\Delta$$

$$I_\Delta = \frac{I_T(-j25)}{25 - j25} = \frac{-jI_T}{1 - j1}$$

$$V_T = j40I_T + 40 \frac{(-jI_T)}{1 - j1}$$

$$\frac{V_T}{I_T} = Z_{ab} = j40 + 20(-j)(1 + j) = 20 + j20 \Omega = 28.28 \angle 45^\circ \Omega$$

P 7.19 First find the admittance of the parallel branches

$$Y_p = \frac{1}{6 - j2} + \frac{1}{4 + j12} + \frac{1}{5} + \frac{1}{j10} = 0.375 - j0.125 \text{ S}$$

$$Z_p = \frac{1}{Y_p} = \frac{1}{0.375 - j0.125} = 2.4 + j0.8 \Omega$$

$$Z_{ab} = -j12.8 + 2.4 + j0.8 + 13.6 = 16 - j12 \Omega$$

$$Y_{ab} = \frac{1}{Z_{ab}} = \frac{1}{16 - j12} = 0.04 + j0.03 \text{ S}$$

$$= 40 + j30 \text{ mS} = 50 \angle 36.87^\circ \text{ mS}$$

$$\begin{aligned}
 \text{P 7.20 [a]} \quad Z_g &= 4000 - j\frac{10^9}{25\omega} + \frac{10^4(j2\omega)}{10^4 + j2\omega} \\
 &= 4000 - j\frac{10^9}{25\omega} + \frac{2 \times 10^4 j\omega(10^4 - j2\omega)}{10^8 + 4\omega^2} \\
 &= 4000 - j\frac{10^9}{25\omega} + \frac{4 \times 10^4 \omega^2}{10^8 + 4\omega^2} + j\frac{2 \times 10^8 \omega}{10^8 + 4\omega^2} \\
 \therefore \quad \frac{10^9}{25\omega} &= \frac{0.2 \times 10^9 \omega}{10^8 + 4\omega^2} \\
 10^8 + 4\omega^2 &= 5\omega^2 \\
 \omega^2 &= 10^8; \quad \omega = 10,000 \text{ rad/s}
 \end{aligned}$$

[b] When  $\omega = 10,000 \text{ rad/s}$

$$\begin{aligned}
 Z_g &= 4000 + \frac{4 \times 10^4 (10^4)^2}{10^8 + 4(10^4)^2} = 12,000 \Omega \\
 \therefore \quad I_g &= \frac{45\angle 0^\circ}{12,000} = 3.75\angle 0^\circ \text{ mA} \\
 \mathbf{V}_o &= \mathbf{V}_g - \mathbf{I}_g Z_1 \\
 Z_1 &= 4000 - j\frac{10^9}{25 \times 10^4} = 4000 - j4000 \Omega \\
 \mathbf{V}_o &= 45\angle 0^\circ - (3.75 \times 10^{-3})(4000 - j4000) = 45 - (15 - j15) \\
 &= 30 + j15 = 33.54\angle 26.57^\circ \text{ V} \\
 v_o &= 33.54 \cos(10,000t + 26.57^\circ) \text{ V}
 \end{aligned}$$

$$\text{P 7.21 [a]} \quad Z_1 = 1600 - j\frac{10^9}{10^4(62.5)} = 1600 - j1600 \Omega$$

$$\begin{aligned}
 Z_1 &= \frac{4000(j10^4 L)}{4000 + j10^4 L} = \frac{4 \times 10^5 L^2 + j16 \times 10^4 L}{16 + 100L^2} \\
 Z_T &= Z_1 + Z_2 = 1600 + \frac{4 \times 10^5 L^2}{16 + 100L^2} - j1600 + j\frac{16 \times 10^4 L}{16 + 100L^2} \\
 Z_T &\text{ is resistive when} \\
 \frac{16 \times 10^4 L}{16 + 100L^2} &= 1600 \quad \text{or} \\
 L^2 - L + 0.16 &= 0
 \end{aligned}$$

Solving,  $L_1 = 0.8 \text{ H}$  and  $L_2 = 0.2 \text{ H}$ .



[b] When  $L = 0.8 \text{ H}$ :

$$Z_T = 1600 + \frac{4 \times 10^5(0.64)}{16 + 64} = 4800 \Omega$$

$$I_g = \frac{96/\underline{0^\circ}}{4.8} \times 10^{-3} = 20/\underline{0^\circ} \text{ mA}$$

$$i_g = 20 \cos 10,000t \text{ mA}$$

When  $L = 0.2 \text{ H}$ :

$$Z_T = 1600 + \frac{4 \times 10^5(0.04)}{16 + 4} = 2400 \Omega$$

$$i_g = 40 \cos 10,000t \text{ mA}$$

$$\begin{aligned} \text{P 7.22 [a]} \quad Z_{ab} &= j5\omega + \frac{(4000)(10^9/j\omega 625)}{4000 + (10^9/j625\omega)} \\ &= j5\omega + \frac{4 \times 10^{12}}{2500 \times 10^3 j\omega + 10^9} \\ &= j5\omega + \frac{4 \times 10^7}{10^4 + j25\omega} \\ &= j5\omega + \frac{4 \times 10^{11}}{10^8 + 625\omega^2} - j \frac{100 \times 10^7 \omega}{10^8 + 625\omega^2} \\ \therefore 5 &= \frac{10^9}{10^8 + 625\omega^2} \\ 5 \times 10^8 + 3125\omega^2 &= 10^9 \\ \omega &= 4 \times 10^2 = 400 \text{ rad/s} \end{aligned}$$

$$[\text{b}] \quad Z_{ab}(400) = j2000 + \frac{(4000)(-j4000)}{4000 - j4000} = 2 \text{ k}\Omega$$

$$\text{P 7.23} \quad Z_1 = 10 - j40 \Omega$$

$$Z_2 = \frac{(5 - j10)(10 + j30)}{15 + j20} = 10 - j10 \Omega$$

$$Z_3 = \frac{20(j20)}{20 + j20} = 10 + j10 \Omega$$

$$\therefore Z_{ab} = Z_1 + Z_2 + Z_3 = 30 - j40 \Omega = 50/\underline{-53.13^\circ} \Omega$$

P 7.24 [a]  $Y_1 = \frac{1}{5000} = 0.2 \times 10^{-3} \text{ S}$

$$Y_2 = \frac{1}{1200 + j0.2\omega}$$

$$= \frac{1200}{1.44 \times 10^6 + 0.04\omega^2} - j \frac{0.2\omega}{1.44 \times 10^6 + 0.04\omega^2}$$

$$Y_3 = j\omega 50 \times 10^{-9}$$

$$Y_T = Y_1 + Y_2 + Y_3$$

For  $i_g$  and  $v_o$  to be in phase the  $j$  component of  $Y_T$  must be zero; thus,

$$\omega 50 \times 10^{-9} = \frac{0.2\omega}{1.44 \times 10^6 + 0.04\omega^2}$$

or

$$0.04\omega^2 + 1.44 \times 10^6 = \frac{0.2 \times 10^9}{50} = 4 \times 10^6$$

$$\therefore 0.04\omega^2 = 2.56 \times 10^6 \quad \therefore \omega = 8000 \text{ rad/s} = 8 \text{ krad/s}$$

[b]  $Y_T = 0.2 \times 10^{-3} + \frac{1200}{1.44 \times 10^6 + 0.04(64) \times 10^6} = 0.5 \times 10^{-3} \text{ S}$

$$\therefore Z_T = 2000 \Omega$$

$$\mathbf{V}_o = (2.5 \times 10^{-3} \angle 0^\circ)(2000) = 5 \angle 0^\circ$$

$$v_o = 5 \cos 8000t \text{ V}$$

P 7.25 [a]  $Z_1 = R_1 + j\omega L_1$

$$Z_2 = \frac{R_2(j\omega L_2)}{R_2 + j\omega L_2} = \frac{\omega^2 L_2^2 R_2 + j\omega L_2 R_2^2}{R_2^2 + \omega^2 L_2^2}$$

$$Z_1 = Z_2 \quad \text{when} \quad R_1 = \frac{\omega^2 L_2^2 R_2}{R_2^2 + \omega^2 L_2^2} \quad \text{and} \quad L_1 = \frac{R_2^2 L_2}{R_2^2 + \omega^2 L_2^2}$$

[b]  $R_1 = \frac{(4 \times 10^8)(6.25)(5 \times 10^4)}{25 \times 10^8 + (4 \times 10^8)(6.25)} = 2.5 \times 10^4$

$$\therefore R_1 = 25 \text{ k}\Omega$$

$$L_1 = \frac{(25 \times 10^8)2.5}{50 \times 10^8} = 1.25 \text{ H}$$

$$\text{P 7.26 [a]} \quad Y_2 = \frac{1}{R_2} - \frac{j}{\omega L_2}$$

$$Y_1 = \frac{1}{R_1 + j\omega L_1} = \frac{R_1 - j\omega L_1}{R_1^2 + \omega^2 L_1^2}$$

$$\text{Therefore} \quad Y_2 = Y_1 \quad \text{when}$$

$$R_2 = \frac{R_1^2 + \omega^2 L_1^2}{R_1} \quad \text{and} \quad L_2 = \frac{R_1^2 + \omega^2 L_1^2}{\omega^2 L_1}$$

$$\text{[b]} \quad R_2 = \frac{25 \times 10^6 + 10^8(0.25)}{5 \times 10^3} = 10 \times 10^3$$

$$\therefore R_2 = 10 \text{ k}\Omega$$

$$L_2 = \frac{50 \times 10^6}{10^8(0.5)} = 1 \text{ H}$$

$$\text{P 7.27 [a]} \quad Z_1 = R_1 - j\frac{1}{\omega C_1}$$

$$Z_2 = \frac{R_2/j\omega C_2}{R_2 + (1/j\omega C_2)} = \frac{R_2}{1 + j\omega R_2 C_2} = \frac{R_2 - j\omega R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2}$$

$$Z_1 = Z_2 \quad \text{when} \quad R_1 = \frac{R_2}{1 + \omega^2 R_2^2 C_2^2} \quad \text{and}$$

$$\frac{1}{\omega C_1} = \frac{\omega R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2} \quad \text{or} \quad C_1 = \frac{1 + \omega^2 R_2^2 C_2^2}{\omega^2 R_2^2 C_2}$$

$$\text{[b]} \quad R_1 = \frac{500}{1 + (64 \times 10^8)(25 \times 10^4)(625 \times 10^{-18})} = 250 \Omega$$

$$C_1 = \frac{2}{(64 \times 10^8)(25 \times 10^4)(25 \times 10^{-9})} = 50 \text{ nF}$$

$$\text{P 7.28 [a]} \quad Y_2 = \frac{1}{R_2} + j\omega C_2$$

$$Y_1 = \frac{1}{R_1 + (1/j\omega C_1)} = \frac{j\omega C_1}{1 + j\omega R_1 C_1} = \frac{\omega^2 R_1 C_1^2 + j\omega C_1}{1 + \omega^2 R_1^2 C_1^2}$$

$$\text{Therefore} \quad Y_1 = Y_2 \quad \text{when}$$

$$R_2 = \frac{1 + \omega^2 R_1^2 C_1^2}{\omega^2 R_1 C_1^2} \quad \text{and} \quad C_2 = \frac{C_1}{1 + \omega^2 R_1^2 C_1^2}$$

$$\text{[b]} \quad R_2 = \frac{1 + (4 \times 10^8)(4 \times 10^6)(2500 \times 10^{-18})}{(4 \times 10^8)(2 \times 10^3)(2500 \times 10^{-18})} = 2500 = 2.5 \text{ k}\Omega$$

$$C_2 = \frac{50 \times 10^{-9}}{5} = 10 \text{ nF}$$

$$\text{P 7.29} \quad [\text{a}] \quad \mathbf{V}_g = 150\angle 20^\circ; \quad \mathbf{I}_g = 30\angle -52^\circ$$

$$\therefore Z = \frac{\mathbf{V}_g}{\mathbf{I}_g} = 5\angle 72^\circ \Omega$$

$$[\text{b}] \quad i_g \text{ lags } v_g \text{ by } 72^\circ:$$

$$2\pi f = 8000\pi; \quad f = 4000 \text{ Hz}; \quad T = 1/f = 250 \mu\text{s}$$

$$\therefore i_g \text{ lags } v_g \text{ by } \frac{72}{360}(250) = 50 \mu\text{s}$$

$$\text{P 7.30} \quad \frac{1}{j\omega C} = -j\frac{10^6}{10^4} = -j100 \Omega$$

$$j\omega L = j(500)(1) = j500 \Omega$$

$$\text{Let } Z_1 = 50 - j100 \Omega; \quad Z_2 = 250 + j500 \Omega$$

$$\mathbf{I}_g = 125\angle 0^\circ \text{ mA}$$

$$\mathbf{I}_o = \frac{\mathbf{I}_g Z_1}{Z_1 + Z_2} = \frac{125\angle 0^\circ (50 - j100)}{(300 + j400)}$$

$$= -12.5 - j25 \text{ mA} = 27.95\angle -116.57^\circ \text{ mA}$$

$$i_o = 27.95 \cos(500t - 116.57^\circ) \text{ mA}$$

$$\text{P 7.31} \quad Z_o = 600 - j\frac{10^6}{(5000)(0.25)} = 600 - j800 \Omega$$

$$Z_T = 300 + j2000 + 600 - j800 = 900 + j1200 \Omega = 1500\angle 53.13^\circ \Omega$$

$$\mathbf{V}_o = \mathbf{V}_g \frac{Z_o}{Z_T} = \frac{(75\angle 0^\circ)(1000\angle -53.13^\circ)}{1500\angle 53.13^\circ} = 50\angle -106.26^\circ \text{ V}$$

$$v_o = 50 \cos(5000t - 106.26^\circ) \text{ V}$$

$$\text{P 7.32} \quad \mathbf{V}_1 = 240\angle 53.13^\circ = 144 + j192 \text{ V}$$


$$\mathbf{V}_2 = 96\angle -90^\circ = -j96 \text{ V}$$

$$j\omega L = j(4000)(15 \times 10^{-3}) = j60 \Omega$$

$$\frac{1}{j\omega C} = -j \frac{6 \times 10^6}{(4000)(25)} = -j60 \Omega$$


$$\frac{\mathbf{V}_1}{j60} = \frac{144 + j192}{j60} = 3.2 - j2.4 \text{ A}$$
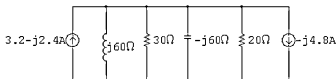
$$\frac{\mathbf{V}_2}{20} = -j \frac{96}{20} = -j4.8 \text{ A}$$



$$Y = \frac{1}{j60} + \frac{1}{30} + \frac{1}{-j60} + \frac{1}{20} = \frac{j5}{j60} = \frac{1}{12}$$


$$Z = \frac{1}{Y} = 12 \Omega$$

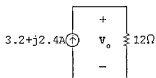

$$\mathbf{V}_o = 12(3.2 + j2.4) = 38.4 + j28.8 \text{ V} = 48 \angle 36.87^\circ \text{ V}$$

$$v_o = 48 \cos(4000t + 36.87^\circ) \text{ V}$$

P 7.33 [a]

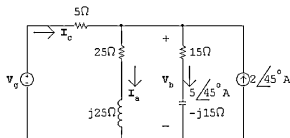

$$\mathbf{V}_b = (15 - j15)5 \angle 45^\circ = 75\sqrt{2} \angle 0^\circ \text{ V}$$

$$\mathbf{I}_a = \frac{75\sqrt{2}}{25 + j25} = 3/\underline{-45^\circ} \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_a + 5/\underline{45^\circ} - 2/\underline{45^\circ} = 3\sqrt{2} \text{ A}$$

$$\mathbf{V}_g = 5\mathbf{I}_c + \mathbf{V}_b = 15\sqrt{2} + 75\sqrt{2} = 90\sqrt{2} \text{ V} = 127.28/\underline{0^\circ} \text{ V}$$

[b]  $i_a = 3 \cos(800t - 45^\circ) \text{ A}$

$$i_c = 4.24 \cos 800t \text{ A}$$


$$v_g = 127.28 \cos 800t \text{ V}$$

P 7.34  $\mathbf{I}_s = 15/\underline{0^\circ} \text{ mA}$

$$\frac{1}{j\omega C} = \frac{10^6}{j0.05(8000)} = -j2500 \Omega$$

$$j\omega L = j8000(1.25) = j10,000 \Omega$$

After two source transformations we have

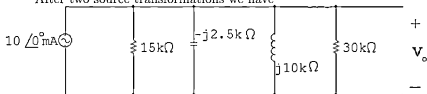

$$15 \text{ k}\Omega \parallel 30 \text{ k}\Omega = 10 \text{ k}\Omega$$


$$\mathbf{Y}_o = \frac{10^{-3}}{10} + \frac{1}{-j2500} + \frac{1}{j10^4} = 10^{-4}(1 + j3)$$

$$\mathbf{Z}_o = \frac{10^4}{1 + j3} = (1 - j3) \text{ k}\Omega$$

$$\mathbf{V}_o = \mathbf{I}_g \mathbf{Z}_o = (10)(1 - j3) = 10 - j30 = 31.62/\underline{-71.57^\circ} \text{ V}$$

$$v_o = 31.62 \cos(8000t - 71.57^\circ) \text{ V}$$

P 7.35

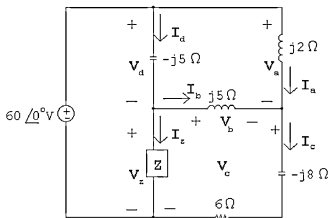

$$\mathbf{V}_a = j2\mathbf{I}_a = j2(-j5) = 10\angle 0^\circ \text{ V}$$

$$\mathbf{V}_c = 60\angle 0^\circ - \mathbf{V}_a = 50\angle 0^\circ \text{ V}$$

$$\mathbf{I}_c = \frac{\mathbf{V}_c}{6 - j8} = \frac{50\angle 0^\circ}{10\angle -53.13^\circ} = 5\angle 53.13^\circ = 3 + j4 \text{ A}$$

$$\mathbf{I}_b = \mathbf{I}_c - \mathbf{I}_a = 3 + j4 - (-j5) = 3 + j9 \text{ A} = 9.49\angle 71.57^\circ \text{ A}$$

$$\mathbf{V}_b = \mathbf{I}_b(j5) = (3 + j9)(j5) = -45 + j15 \text{ V}$$

$$\mathbf{V}_z = \mathbf{V}_b + \mathbf{V}_c = -45 + j15 + 50 + j0 = 5 + j15 \text{ V}$$

$$\mathbf{V}_d + \mathbf{V}_z = 60\angle 0^\circ; \quad \therefore \mathbf{V}_d = 60 - 5 - j15 = 55 - j15 \text{ V}$$


$$\mathbf{I}_d = \frac{\mathbf{V}_d}{-j5} = 3 + j11 \text{ A}$$

$$\mathbf{I}_z = \mathbf{I}_d - \mathbf{I}_b = 3 + j11 - 3 - j9 = j2 \text{ A}$$

$$\mathbf{Z} = \frac{\mathbf{V}_z}{\mathbf{I}_z} = \frac{5 + j15}{j2} = 7.5 - j2.5 \Omega$$

$$\text{P 7.36} \quad \frac{1}{\omega C_1} = \frac{(10^{-3})(10^9)}{25(10/3)} = 12 \text{ k}\Omega$$
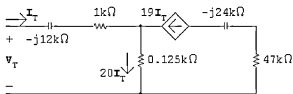
$$\frac{1}{\omega C_2} = \frac{(10^{-3})(10^9)}{25(5/3)} = 24 \text{ k}\Omega$$




$$\mathbf{V}_T = (1 - j12)\mathbf{I}_T + 20\mathbf{I}_T(0.125)$$

$$\mathbf{Z}_{Th} = \frac{\mathbf{V}_T}{\mathbf{I}_T} = 3.5 - j12 \text{ k}\Omega$$

P 7.37 [a]  $j\omega L = j(1000)(100) \times 10^{-3} = j100 \Omega$
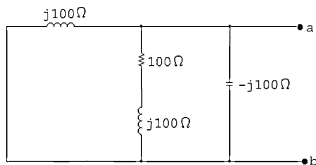
$$\frac{1}{j\omega C} = -j \frac{10^6}{(1000)(10)} = -j100 \Omega$$



$$\mathbf{Y}_{ab} = \frac{1}{j100} + \frac{1}{100 + j100} + \frac{1}{-j100}$$

$$= \frac{1}{100} \left[ \frac{1}{j} + \frac{1}{1 + j1} + \frac{j}{1} \right]$$

$$\mathbf{Y}_{ab} = \frac{1}{100} \left[ -j + \frac{1 - j1}{2} + j \right]$$

$$= \frac{1 - j1}{200}; \quad \mathbf{Z}_{ab} = \frac{200}{1 - j1} = 100(1 + j1)$$

$$\therefore \mathbf{V}_{ab} = 100(1 + j1) \left[ \frac{247.49 \angle 45^\circ}{j100} \right]$$


$$= \sqrt{2} \angle 45^\circ \cdot 1 \angle -90^\circ \cdot 247.49 \angle 45^\circ$$

$$\mathbf{V}_{Th} = 350 \angle 0^\circ \text{ V}$$




[b]  $Z_{Th} = Z_{ab} = 100 + j100 \Omega$

[c]

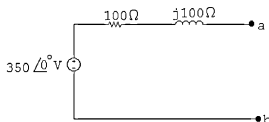

P 7.38

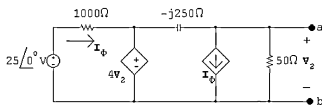

$$\frac{V_2}{50} + \frac{25 - 4V_2}{1000} + \frac{V_2 - 4V_2}{-j250} = 0$$

Solving,


$$V_2 = -10 - j0.75 \text{ V} = 1.25 \angle 216.87^\circ \text{ V}$$

$$I_{sc} = -I_\phi = \frac{-25 \angle 0^\circ}{1000} = -25 \angle 0^\circ \text{ mA}$$

$$Z_{Th} = \frac{1.25 \angle 216.87^\circ}{-25 \times 10^{-3} \angle 0^\circ} = 50 \angle 36.87^\circ \Omega = 40 + j30 \Omega$$


$$I_N = I_{sc} = -25 \angle 0^\circ \text{ mA}$$
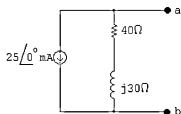
$$Z_N = Z_{Th} = 50 \angle 36.87^\circ = 40 + j30 \Omega$$




$$\text{P 7.39} \quad \mathbf{I}_N = \mathbf{I}_{sc} = \frac{(16/\underline{0^\circ})(25)}{25 + 15 + j30} = 6.4 - j4.8 \text{ A} = 8/\underline{-36.87^\circ} \text{ A}$$

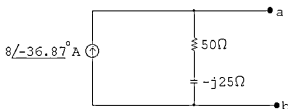
$$\mathbf{Z}_N = \frac{(-j50)(40 + j30)}{40 + j30 - j50} = 50 - j25 \Omega$$



P 7.40

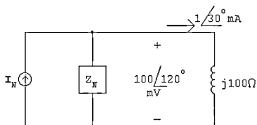
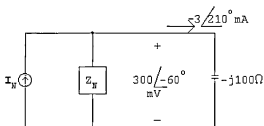
$$\mathbf{I}_N = \frac{0.1/\underline{120^\circ}}{\mathbf{Z}_N} + 1/\underline{30^\circ} \text{ mA}, \quad \mathbf{Z}_N \text{ in k}\Omega$$




$$\mathbf{I}_N = \frac{0.3/\underline{-60^\circ}}{\mathbf{Z}_N} + (-3/\underline{210^\circ}) \text{ mA}, \quad \mathbf{Z}_N \text{ in k}\Omega$$

$$\frac{0.1/\underline{120^\circ}}{\mathbf{Z}_N} + 1/\underline{30^\circ} = \frac{0.3/\underline{-60^\circ}}{\mathbf{Z}_N} + (-3/\underline{210^\circ})$$

$$\frac{0.3/\underline{-60^\circ} - 0.1/\underline{120^\circ}}{\mathbf{Z}_N} = 1/\underline{30^\circ} + 3/\underline{210^\circ}$$


$$Z_N = \frac{0.3/-60^\circ - 0.1/120^\circ}{1/30^\circ + 3/210^\circ} = 0.2/90^\circ = j0.2 \text{ k}\Omega$$
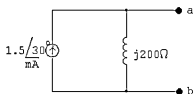
$$I_N = \frac{0.1/120^\circ}{0.2/90^\circ} + 1/30^\circ = 1.5/30^\circ \text{ mA}$$




P 7.41  $V_{Th} = \frac{75(24)}{24 + j18} = 60/-36.87^\circ \text{ V}$
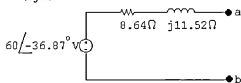
$$Z_{Th} = \frac{(24)(j18)}{24 + j18} = 8.64 + j11.52 \Omega$$



P 7.42

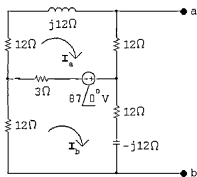

$$(27 + j12)I_a - 3I_b = -87/0^\circ$$


$$-3I_a + (27 - j12)I_b = 87/0^\circ$$

Solving,

$$I_a = -2.4167 + j1.21; \quad I_b = 2.4167 + j1.21$$

$$\mathbf{V}_{Th} = 12\mathbf{I}_a + (12 - j12)\mathbf{I}_b = 14.5\angle 0^\circ \text{ V}$$

Short Circuit Test:

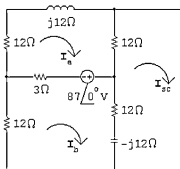

$$(27 + j12)\mathbf{I}_a - 3\mathbf{I}_b - 12\mathbf{I}_{sc} = -87$$

$$-3\mathbf{I}_a + (27 - j12)\mathbf{I}_b - (12 - j12)\mathbf{I}_{sc} = 87$$


$$-12\mathbf{I}_a - (12 - j12)\mathbf{I}_b + (24 - j12)\mathbf{I}_{sc} = 0$$

Solving,

$$\mathbf{I}_{sc} = 1\angle 0^\circ$$

$$\mathbf{Z}_{Th} = \frac{\mathbf{V}_{Th}}{\mathbf{I}_{sc}} = \frac{14.5\angle 0^\circ}{1\angle 0^\circ} = 14.5 \Omega$$

P 7.43

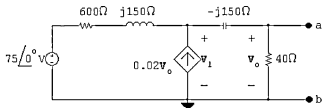


$$\frac{\mathbf{V}_1 - 75}{150(4 + j1)} - \frac{0.02\mathbf{V}_1(40)}{40 - j150} + \frac{\mathbf{V}_1}{40 - j150} = 0$$

$$\therefore \mathbf{V}_1 = \frac{75(4 - j15)}{16 - j12}$$


$$\begin{aligned} V_{Th} &= \frac{40V_1}{40 - j150} = \frac{4}{4 - j15} \cdot \frac{75(4 - j15)}{16 - j12} \\ &= \frac{75}{4 - j3} = 15\angle 36.87^\circ \text{ V} \end{aligned}$$

$$I_{sc} = \frac{75}{600} = \frac{1}{8} \text{ A}$$
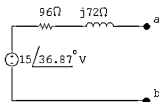
$$Z_{Th} = \frac{V_{Th}}{I_{sc}} = 120\angle 36.87^\circ = 96 + j72 \Omega$$



P 7.44 [a]

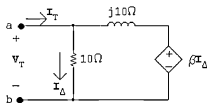

$$I_T = \frac{V_T}{10} + \frac{V_T + \beta V_T / 10}{j10}$$

$$\frac{I_T}{V_T} = \frac{1}{10} + \frac{(1 - \beta/10)}{j10} = \frac{(10 - \beta) + j10}{j100}$$

$$\therefore Z_{Th} = \frac{V_T}{I_T} = \frac{1000 + j100(10 - \beta)}{(10 - \beta)^2 + 100}$$

$Z_{Th}$  is real when  $\beta = 10$ .

[b]  $Z_{Th} = \frac{1000}{100} = 10 \Omega$

[c]  $Z_{Th} = 5 + j5$

$$\frac{1000}{(10 - \beta)^2 + 100} = 5; \quad (10 - \beta)^2 = 100$$

$$\therefore 10 - \beta = \pm 10; \quad \beta = 10 \mp 10$$


$$\beta = 0; \quad \beta = 20$$

But the  $j$  term can only equal the real term with  $\beta = 0$ . Thus,  $\beta = 0$ .

[d]  $Z_{Th}$  will be capacitive when  $\beta > 10$ :

$$\therefore 10 < \beta \leq 50$$

P 7.45

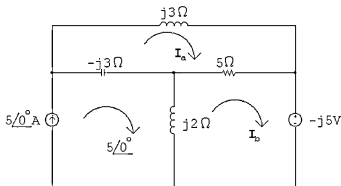


$$j3I_a + 5(I_a - I_b) - j3(I_a - 5) = 0$$

$$j2(I_b - 5) + 5(I_b - I_a) - j5 = 0$$

Solving,

$$I_a = -j3; \quad I_b = -j3 = 3/\underline{-90^\circ} \text{ A}$$

P 7.46

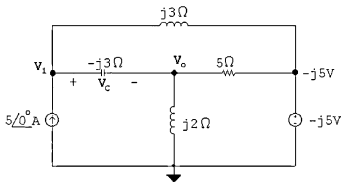

$$\frac{V_o}{j2} + \frac{V_o + j5}{5} + \frac{V_o - V_1}{-j3} = 0$$


$$(5 + j6)V_o + 10V_1 = 30$$

$$-5 + \frac{V_1 - V_o}{-j3} + \frac{V_1 + j5}{j3} = 0$$

$$V_o = j10; \quad V_1 = 9 - j5$$

$$V_c = V_1 - V_o = 9 - j5 - j10 = 9 - j15 = 17.49/\underline{-59.04^\circ} \text{ V}$$

P 7.47

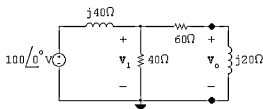

$$\frac{V_1 - 100}{j40} + \frac{V_1}{40} + \frac{V_1}{60 + j20} = 0$$

Solving for  $V_1$  yields


$$V_1 = 30 - j40 \text{ V}$$

$$V_o = \frac{V_1}{60 + j20}(j20) = \left(\frac{j}{3 + j}\right)V_1$$

$$V_o = 15 + j5 \text{ V} = 15.81\angle18.43^\circ \text{ V}$$

P 7.48  $j\omega L = j5000(14 \times 10^{-3}) = j70 \Omega$ 
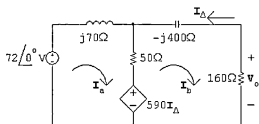
$$\frac{1}{j\omega C} = \frac{-j}{(5000)(0.5 \times 10^{-6})} = -j400 \Omega$$



$$72\angle0^\circ = (50 + j70)I_a - 50I_b + 590(-I_b)$$

$$0 = -50I_a - 590(-I_b) + (210 - j400)I_b$$

Solving,

$$I_b = (50 - j50) \text{ mA}$$

$$V_o = 160I_b = 8 - j8 = 11.31\angle-45^\circ$$


$$v_o = 11.31 \cos(5000t - 45^\circ) \text{ V}$$

P 7.49  $j\omega L = j(5000)(0.4 \times 10^{-3}) = j2\ \Omega$

$$\frac{1}{j\omega C} = -j \frac{10^6}{(5000)(50)} = -j4\ \Omega$$

$$\mathbf{V}_{g1} = 10/\underline{53.13^\circ} = 6 + j8\ \text{V}$$
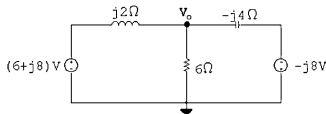
$$\mathbf{V}_{g2} = 8/\underline{-90^\circ} = -j8\ \text{V}$$




$$\frac{\mathbf{V}_o - 6 - j8}{j2} + \frac{\mathbf{V}_o}{6} + \frac{\mathbf{V}_o + (-j8)}{-j4} = 0$$

Solving,


$$\mathbf{V}_o = 12/\underline{0^\circ}$$

$$v_o(t) = 12 \cos 5000t\ \text{V}$$

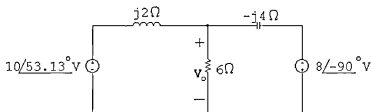P 7.50 From the solution to Problem 7.49 the phasor-domain circuit is



Making two source transformations yields

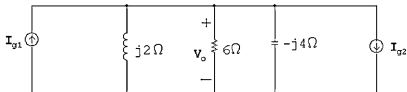

$$\mathbf{I}_{g1} = \frac{10/\underline{53.13^\circ}}{j2} = 5/\underline{-36.87^\circ} = 4 - j3\ \text{A}$$




$$\mathbf{I}_{g2} = \frac{8\angle -90^\circ}{-j4} = 2\angle 0^\circ = 2 \text{ A}$$

$$\mathbf{Y} = \frac{1}{j2} + \frac{1}{6} + \frac{1}{-j4} \text{ S}$$

$$\mathbf{Z} = \frac{1}{\mathbf{Y}} = \frac{1}{(1/6) - j(1/4)} = 1.85 + j2.77 \Omega$$

$$\mathbf{I}_e = \mathbf{I}_{g1} - \mathbf{I}_{g2} = 4 - j3 - 2 = 2 - j3 \text{ A}$$


Hence the circuit reduces to

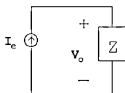

$$\mathbf{V}_o = \mathbf{Z}\mathbf{I}_e = (1.85 + j2.77)(2 - j3) = 12\angle 0^\circ$$

$$\therefore v_o(t) = 12 \cos 5000t \text{ V}$$

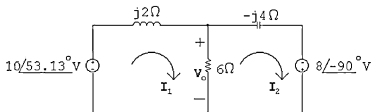P 7.51 From the solution to Problem 7.49 the phasor-domain circuit is



$$10\angle 53.13^\circ = (6 + j2)\mathbf{I}_1 - 6\mathbf{I}_2$$

$$8\angle -90^\circ = -6\mathbf{I}_1 + (6 - j4)\mathbf{I}_2$$


$$\mathbf{V}_o = (\mathbf{I}_1 - \mathbf{I}_2)6$$

Solving,

$$\mathbf{V}_o = 12\angle 0^\circ \text{ V}$$

$$v_o(t) = 12 \cos 5000t \text{ V}$$

P 7.52

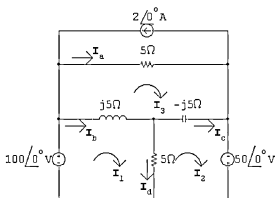

$$100\angle 0^\circ = (5 + j5)I_1 - 5I_2 - j5I_3$$

$$50\angle 0^\circ = -5I_1 + (5 - j5)I_2 + j5I_3$$

$$-10\angle 0^\circ = -j5I_1 + j5I_2 + 5I_3$$

Solving,

$$I_1 = 58 - j20 \text{ A}; \quad I_2 = 58 + j10 \text{ A}; \quad I_3 = 28 + j0 \text{ A}$$

$$I_a = I_3 + 2 = 30 + j0 \text{ A}$$

$$I_b = I_1 - I_3 = 58 - j20 - 28 = 30 - j20 \text{ A}$$

$$I_c = I_2 - I_3 = 58 + j10 - 28 = 30 + j10 \text{ A}$$

$$I_d = I_1 - I_2 = 58 - j20 - 58 - j10 = -j30 \text{ A}$$

P 7.53  $V_2$  is the voltage across the  $-j10\Omega$  impedance.

$$\frac{V_1 - V_g}{20} + \frac{V_1}{j5} + \frac{V_1 - V_2}{Z} = 0$$

$$\frac{(40 + j30) - (100 - j50)}{20} + \frac{40 + j30}{j5} + \frac{(40 + j30) - V_2}{Z} = 0$$

$$\therefore V_2 = 40 + j30 + (3 - j4)Z$$

$$\frac{V_2 - V_1}{Z} + \frac{V_L}{-j10} - I_g + \frac{V_2 - V_g}{3 + j1} = 0$$

$$\frac{V_2 - (40 + j30)}{Z} + \frac{V_2}{-j10} - (20 + j30) + \frac{V_2 - (100 - j50)}{3 + j1} = 0$$


Substituting the expression for  $V_2$  found at the start and simplifying yields

$$Z = 12 + j16\Omega$$

P 7.54  $V_a = 60\angle 0^\circ \text{ V}; \quad V_b = 90\angle 90^\circ \text{ V}$

$$j\omega L = j(4 \times 10^4)(125 \times 10^{-6}) = j5\Omega$$
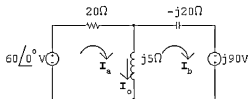
$$\frac{-j}{\omega C} = \frac{-j10^6}{40,000(1.25)} = -j20\Omega$$



$$60 = (20 + j5)I_a - j5I_b$$

$$j90 = -j5I_a - j15I_b$$

Solving,

$$I_a = 2.25 - j2.25 \text{ A}; \quad I_b = -6.75 + j0.75 \text{ A}$$

$$I_o = I_a - I_b = 9 - j3 = 9.49\angle -18.43^\circ \text{ A}$$

$$i_o(t) = 9.49 \cos(40,000t - 18.43^\circ) \text{ A}$$


P 7.55 [a]  $\frac{1}{j\omega C} = \frac{10^9}{j8 \times 10^5(125)} = -j10\Omega$

$$j\omega L = j8 \times 10^5(25 \times 10^{-6}) = j20\Omega$$

$$Z_e = \frac{(-j10)(20)}{20 - j10} = 4 - j8\Omega$$

$$I_g = 5\angle 0^\circ$$
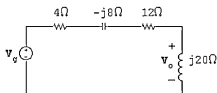
$$V_g = I_g Z_e = 5(4 - j8) = 20 - j40 \text{ V}$$



$$V_o = \frac{(20 - j40)(j20)}{(16 + j12)} = 44 - j8 = 44.72\angle -10.30^\circ \text{ V}$$

$$v_o = 44.72 \cos(8 \times 10^5 t - 10.30^\circ) \text{ V}$$


$$[b] \quad \omega = 2\pi f = 8 \times 10^5; \quad f = \frac{4 \times 10^5}{\pi}$$

$$T = \frac{1}{f} = \frac{\pi}{4 \times 10^5} = 2.5\pi \mu s$$

$$\therefore \frac{10.30}{360}(2.5\pi) = 224.82 \text{ ns}$$

$$\therefore v_o \text{ lags } i_g \text{ by } 224.82 \text{ ns}$$

P 7.56

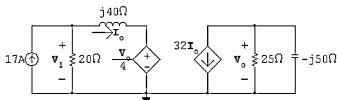

$$\frac{V_o}{25} + \frac{V_o}{-j50} + 32I_o = 0$$

$$(2 + j)V_o = -1600I_o$$

$$V_o = (-640 + j320)I_o$$

$$I_o = \frac{V_1 - (V_o/4)}{j40}$$

$$\therefore V_1 = (-160 + j120)I_o$$

$$17 = \frac{V_1}{20} + I_o = (-8 + j6)I_o + I_o = (-7 + j6)I_o$$

$$\therefore I_o = \frac{17}{(-7 + j6)} = -1.4 - j1.2 \text{ A} = 1.84 \angle -139.40^\circ \text{ A}$$

$$V_o = (-640 + j320)I_o = 1280 + j320 = 1319.39 \angle 14.04^\circ \text{ V}$$

$$P 7.57 \quad -15 \angle 0^\circ + \frac{V_o}{8} + \frac{V_o - 2.5I_\Delta}{j5} + \frac{V_o}{-j10} = 0$$

$$I_\Delta = \frac{V_o}{-j10}$$

Solving,


$$V_o = 72 + j96 = 120 \angle 53.13^\circ \text{ V}$$

$$\text{P 7.58} \quad j\omega L = j10^4(1.2 \times 10^{-3}) = j12 \Omega$$

$$\frac{1}{j\omega C} = \frac{-j10^6}{5 \times 10^4} = -j20 \Omega$$

$$\mathbf{V}_a = 100/\underline{-90^\circ} = -j100 \text{ V}$$
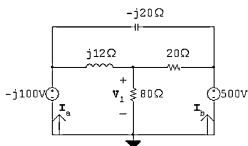
$$\mathbf{V}_b = 500/\underline{0^\circ} = 500 \text{ V}$$



$$\frac{\mathbf{V}_1}{80} + \frac{\mathbf{V}_1 - 500}{20} + \frac{\mathbf{V}_1 + j100}{j12} = 0$$

Solving,

$$\mathbf{V}_1 = 160/\underline{53.13^\circ} \text{ V} = 96 + j128 \text{ V}$$


$$\begin{aligned} \mathbf{I}_a &= \frac{-j100 - 96 - j128}{j12} + \frac{-j100 - 500}{-j20} \\ &= 14 - j17 = 22.02/\underline{-129.47^\circ} \text{ A} \end{aligned}$$

$$i_a = 22.02 \cos(10,000t - 129.47^\circ) \text{ A}$$

$$\begin{aligned} \mathbf{I}_b &= \frac{500 - 96 - j128}{20} + \frac{500 + j100}{-j20} \\ &= 15.2 + j18.6 = 24.02/\underline{50.74^\circ} \text{ A} \end{aligned}$$

$$i_b = 24.02 \cos(10,000t + 50.74^\circ) \text{ A}$$

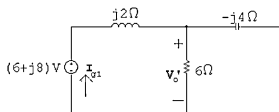
- P 7.59 From the solution to Problem 7.49 the phasor-domain circuit with the right-hand source removed is



$$Z_{e1} = \frac{6(-j4)}{(6-j4)} = \frac{-j24}{6-j4} \Omega$$

$$\mathbf{V}'_o = \frac{Z_{e1}}{Z_{e1} + j2} (6 + j8) = \frac{192 - j144}{8 - j12} \text{ V}$$

With the left hand source removed

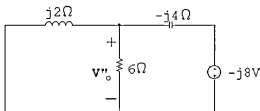

$$Z_{e2} = \frac{6(j2)}{6 + j2} = \frac{j12}{6 + j2} \Omega$$

$$\mathbf{V}''_o = \frac{Z_{e2}}{-j4 + Z_{e2}} (j8) = \frac{-96}{8 - j12} \text{ V}$$

$$\mathbf{V}_o = \mathbf{V}'_o + \mathbf{V}''_o = \frac{192 - j144 - 96}{8 - j12} = 12 + j0 \text{ V}$$

$$v_o(t) = 12 \cos 5000t \text{ V}$$

- P 7.60 [a]  $P = \frac{1}{2}(340)(20) \cos(60 - 15) = 2400 \cos 45^\circ = 2404.16 \text{ W (abs)}$

$$Q = 2400 \sin 45^\circ = 2404.16 \text{ VAR (abs)}$$

$$[\text{b}] \quad P = \frac{1}{2}(16)(75) \cos(-15 - 60) = 600 \cos(-75^\circ) = 155.29 \text{ W} \quad (\text{abs})$$

$$Q = 600 \sin(-75^\circ) = -579.56 \text{ VAR} \quad (\text{del})$$

$$[\text{c}] \quad P = \frac{1}{2}(625)(4) \cos(40 - 150) = 1250 \cos(-110^\circ) = -427.53 \text{ W} \quad (\text{del})$$


$$Q = 1250 \sin(-110^\circ) = -1174.62 \text{ VAR} \quad (\text{del})$$

$$[\text{d}] \quad P = \frac{1}{2}(180)(10) \cos(130 - 20) = 900 \cos(110^\circ) = -307.82 \text{ W} \quad (\text{del})$$

$$Q = 900 \sin(110^\circ) = 845.72 \text{ VAR} \quad (\text{abs})$$

$$\text{P 7.61} \quad p = P + P \cos 2\omega t - Q \sin 2\omega t; \quad \frac{dp}{dt} = -2\omega P \sin 2\omega t - 2\omega Q \cos 2\omega t$$
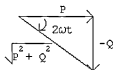
$$\frac{dp}{dt} = 0 \quad \text{when} \quad -2\omega P \sin 2\omega t = 2\omega Q \cos 2\omega t \quad \text{or} \quad \tan 2\omega t = -\frac{Q}{P}$$



$$\cos 2\omega t = \frac{P}{\sqrt{P^2 + Q^2}}; \quad \sin 2\omega t = -\frac{Q}{\sqrt{P^2 + Q^2}}$$

Let  $\theta = \tan^{-1}(-Q/P)$ , then  $p$  is maximum when  $2\omega t = \theta$  and  $p$  is minimum when  $2\omega t = (\theta + \pi)$ .

$$\text{Therefore} \quad p_{\max} = P + P \cdot \frac{P}{\sqrt{P^2 + Q^2}} - \frac{Q(-Q)}{\sqrt{P^2 + Q^2}} = P + \sqrt{P^2 + Q^2}$$

$$\text{and} \quad p_{\min} = P - P \cdot \frac{P}{\sqrt{P^2 + Q^2}} - Q \cdot \frac{Q}{\sqrt{P^2 + Q^2}} = P - \sqrt{P^2 + Q^2}$$

$$\text{P 7.62} \quad W_{\text{dc}} = \frac{V_{\text{dc}}^2}{R} T; \quad W_s = \int_{t_o}^{t_o+T} \frac{v_s^2}{R} dt$$

$$\therefore \frac{V_{\text{dc}}^2}{R} T = \int_{t_o}^{t_o+T} \frac{v_s^2}{R} dt$$

$$V_{\text{dc}}^2 = \frac{1}{T} \int_{t_o}^{t_o+T} v_s^2 dt$$

$$V_{\text{dc}} = \sqrt{\frac{1}{T} \int_{t_o}^{t_o+T} v_s^2 dt} = V_{\text{rms}} = V_{\text{eff}}$$

P 7.63 [a] Area under one cycle of  $v_g^2$ :

$$\begin{aligned} A &= (400)(4)(20 \times 10^{-6}) + 10,000(2)(20 \times 10^{-6}) \\ &= 21,600(20 \times 10^{-6}) \end{aligned}$$

Mean value of  $v_g^2$ :

$$\text{M.V.} = \frac{A}{120 \times 10^{-6}} = \frac{21,600(20 \times 10^{-6})}{120 \times 10^{-6}} = 3600$$

$$\therefore V_{\text{rms}} = \sqrt{3600} = 60 \text{ V(rms)}$$

[b]  $P = \frac{V_{\text{rms}}^2}{R} = \frac{3600}{12} = 300 \text{ W}$

P 7.64  $i(t) = \frac{30}{40} \times 10^3 t = 750t \quad 0 \leq t \leq 40 \text{ ms}$

$$i(t) = M - \frac{30}{10} \times 10^3 t \quad 40 \text{ ms} \leq t \leq 50 \text{ ms}$$

$$i(t) = 0 \text{ when } t = 50 \text{ ms}$$

$$\therefore M = 3000(50 \times 10^{-3}) = 150$$

$$i(t) = 150 - 3000t \quad 40 \text{ ms} \leq t \leq 50 \text{ ms}$$

$$\therefore I_{\text{rms}} = \sqrt{\frac{1000}{50} \left\{ \int_0^{0.04} (750)^2 t^2 dt + \int_{0.04}^{0.05} (150 - 3000t)^2 dt \right\}}$$

$$\int_0^{0.04} (750)^2 t^2 dt = (750)^2 \frac{t^3}{3} \bigg|_0^{0.04} = 12$$

$$(150 - 3000t)^2 = 22,500 - 9 \times 10^5 t + 9 \times 10^6 t^2$$

$$\int_{0.04}^{0.05} 22,500 dt = 225$$

$$\int_{0.04}^{0.05} 9 \times 10^5 t dt = 45 \times 10^4 t^2 \bigg|_{0.04}^{0.05} = 405$$

$$9 \times 10^6 \int_{0.04}^{0.05} t^2 dt = 3 \times 10^6 t^3 \bigg|_{0.04}^{0.05} = 183$$

$$\therefore I_{\text{rms}} = \sqrt{20\{12 + (225 - 405 + 183)\}} = \sqrt{300} = 17.32 \text{ A}$$



$$\text{P 7.65} \quad P = I_{\text{rms}}^2 R \quad \therefore R = \frac{24 \times 10^3}{300} = 80 \, \Omega$$

$$\text{P 7.66} \quad \frac{1}{\omega C} = \frac{10^9}{(5000)(80)} = 2500 \, \Omega$$

$$Z_{\text{f}} = \frac{-j2500(7500)}{7500 - j2500} = 750 - j2250 \, \Omega$$

$$Z_{\text{i}} = 1500 \, \Omega$$

$$\therefore \frac{Z_{\text{f}}}{Z_{\text{i}}} = \frac{750 - j2250}{1500} = 0.5 - j1.5$$


$$\mathbf{V}_o = -\frac{Z_{\text{f}}}{Z_{\text{i}}} \mathbf{V}_g; \quad \mathbf{V}_g = 4\angle 0^\circ \text{ V}$$

$$\mathbf{V}_o = (-0.5 + j1.5)(4) = -2 + j6 = 6.32\angle 108.43^\circ \text{ V}$$

$$P = \frac{1}{2} \frac{V_{\text{m}}^2}{R} = \frac{1}{2} \frac{(4)(10)}{1000} = 20 \times 10^{-3} = 20 \text{ mW}$$

$$\text{P 7.67} \quad \mathbf{I}_g = 30\angle 0^\circ \text{ mA}$$
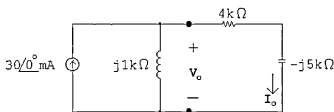
$$j\omega L = j(100)(10) = j1000 \, \Omega; \quad \frac{1}{j\omega C} = \frac{10^6}{j(100)(2)} = -j5000 \, \Omega$$



$$\mathbf{I}_o = \frac{30\angle 0^\circ (j1000)}{4000 - j4000} = 3.75\sqrt{2}\angle 135^\circ \text{ mA}$$


$$P = |\mathbf{I}_o|_{\text{rms}}^2 (4000) = (3.75)^2 (4000) = 56.25 \text{ mW}$$

$$Q = |\mathbf{I}_o|_{\text{rms}}^2 (-5000) = -70.3125 \text{ mVAR}$$

$$S = P + jQ = 56.25 - j70.3125 \text{ mVA}$$

$$|S| = 90.044 \text{ mVA}$$

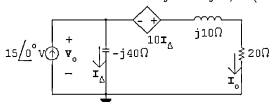P 7.68  $j\omega L = j10,000(10^{-3}) = j10\Omega$ ;  $\frac{1}{j\omega C} = \frac{10^6}{j10,000(2.5)} = -j40\Omega$



$$-15 + \frac{V_o}{-j40} + \frac{V_o + 10(V_o / -j40)}{20 + j10} = 0$$

$$\therefore V_o \left[ \frac{1}{-j40} + \frac{1 + j0.25}{20 + j10} \right] = 15$$

$$\therefore V_o = 300 - j100 \text{ V}$$

$$\therefore I_{\Delta} = \frac{V_o}{-j40} = 2.5 + j7.5 \text{ A}$$

$$I_o = 15\angle 0^\circ - I_{\Delta} = 15 - 2.5 - j7.5 = 12.5 - j7.5 = 14.58\angle -30.9^\circ \text{ A}$$

$$P_{20\Omega} = \frac{1}{2}|I_o|^2 20 = 2125 \text{ W}$$

P 7.69 [a]  $Z_1 = 240 + j70 = 250\angle 16.26^\circ \Omega$

$$\text{pf} = \cos(16.26^\circ) = 0.96 \text{ lagging}$$

$$\text{rf} = \sin(16.26^\circ) = 0.28$$

$$Z_2 = 160 - j120 = 200\angle -36.87^\circ \Omega$$

$$\text{pf} = \cos(-36.87^\circ) = 0.80 \text{ leading}$$

$$\text{rf} = \sin(-36.87^\circ) = -0.60$$

$$Z_3 = 30 - j40 = 50\angle -53.13^\circ \Omega$$

$$\text{pf} = \cos(-53.13^\circ) = 0.6 \text{ leading}$$

$$\text{rf} = \sin(-53.13^\circ) = -0.8$$

$$[b] Y = Y_1 + Y_2 + Y_3$$

$$Y_1 = \frac{1}{250/16.26^\circ}; \quad Y_2 = \frac{1}{200/-36.87^\circ}; \quad Y_3 = \frac{1}{50/-53.13^\circ}$$


$$Y = 19.84 + j17.88 \text{ mS}$$

$$Z = \frac{1}{Y} = 37.44/-42.03^\circ \Omega$$

$$\text{pf} = \cos(-42.03^\circ) = 0.74 \text{ leading}$$

$$\text{rf} = \sin(-42.03^\circ) = -0.67$$

P 7.70 [a]

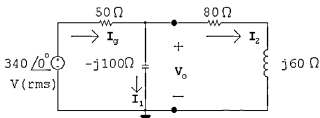

$$\frac{V_o}{-j100} + \frac{V_o - 340}{50} + \frac{V_o}{80 + j60} = 0$$

$$\therefore V_o = 238 - j34 \text{ V}$$

$$I_g = \frac{340 - 238 + j34}{50} = 2.04 + j0.68 \text{ A}$$

$$\begin{aligned} S_g &= \mathbf{V}_g \mathbf{I}_g^* = (340)(2.04 - j0.68) \\ &= 693.6 - j231.2 \text{ VA} \end{aligned}$$

[b] Source is delivering 693.6 W.

[c] Source is absorbing 231.2 magnetizing VAR.

$$[d] I_1 = \frac{V_o}{-j100} = 0.34 + j2.38 \text{ A}$$

$$\begin{aligned} S_1 &= \mathbf{V}_o \mathbf{I}_1^* = (238 - j34)(0.34 - j2.38) \\ &= 0 - j578 \text{ VA} \end{aligned}$$

$$I_2 = \frac{V_o}{80 + j60} = \frac{238 - j34}{80 + j60} = 1.7 - j1.7 \text{ A}$$

$$\begin{aligned} S_2 &= \mathbf{V}_o \mathbf{I}_2^* = (238 - j34)(1.7 + j1.7) \\ &= 462.4 + j346.8 \text{ VA} \end{aligned}$$

$$S_{50\Omega} = |\mathbf{I}_g|^2(50) + j0 = (2.15)^2(50) = 231.2 \text{ W}$$

$$[\text{e}] \quad \sum P_{\text{del}} = 693.6 \text{ W}$$

$$\sum P_{\text{diss}} = 462.4 + 231.2 = 693.6 \text{ W}$$

$$\therefore \sum P_{\text{del}} = \sum P_{\text{diss}} = 693.6 \text{ W}$$


$$[\text{f}] \quad \sum Q_{\text{abs}} = 231.2 + 346.8 = 578 \text{ VAR}$$

$$\sum Q_{\text{dev}} = 578 \text{ VAR}$$

$$\therefore \sum \text{mag VAR dev} = \sum \text{mag VAR abs} = 578$$

$$\text{P 7.71} \quad \mathbf{I}_g = 30 \angle 0^\circ \text{ mA}; \quad \frac{1}{j\omega C} = \frac{10^6}{j(25 \times 10^3)(40)} = -j1 \Omega$$
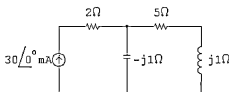
$$j\omega L = j(25 \times 10^3)(40) \times 10^{-6} = j1 \Omega$$



$$Z_1 = j1 \parallel (5 + j1) = 0.2 - j1 \Omega$$

$$Z_{\text{eq}} = 2 + Z_1 = 2.2 - j1 \Omega$$

$$P_g = |I_{\text{rms}}|^2 \text{Re}\{Z_{\text{eq}}\} = \left(\frac{30}{\sqrt{2}} \times 10^{-3}\right)^2 (2.2) = 990 \mu\text{W}$$

$$\text{P 7.72} \quad [\text{a}] \quad P = \frac{1}{2} \frac{(240)^2}{480} = 60 \text{ W}$$

$$-\frac{1}{\omega C} = \frac{-9 \times 10^6}{(5000)(5)} = -360 \Omega$$

$$Q = \frac{1}{2} \frac{(240)^2}{(-360)} = -80 \text{ VAR}$$

$$p_{\text{max}} = P + \sqrt{P^2 + Q^2} = 60 + \sqrt{(60)^2 + (80)^2} = 160 \text{ W (del)}$$

$$[\text{b}] \quad p_{\text{min}} = 60 - 100 = -40 \text{ W (abs)}$$

$$[\text{c}] \quad P = 60 \text{ W}$$

$$[\text{d}] \quad Q = -80 \text{ VAR}$$

[e] generate

[f]  $\text{pf} = \cos(\theta_v - \theta_i)$


$$\mathbf{I} = \frac{240}{480} + \frac{240}{-j360} = 0.5 + j0.67 = 0.83/\underline{53.13^\circ} \text{ A}$$

$$\therefore \text{pf} = \cos(0 - 53.13^\circ) = 0.6 \text{ leading}$$

[g]  $\text{rf} = \sin(-53.13^\circ) = -0.8$

P 7.73 [a]  $\frac{1}{j\omega C} = \frac{10^6}{j10^5} = -j10 \Omega$
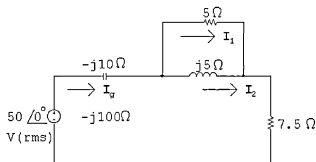
$$j\omega L = j10^5(50 \times 10^{-6}) = j5 \Omega$$



$$Z = -j10 + \frac{(5)(j5)}{5 + j5} + 7.5 = 10 - j7.5 \Omega$$

$$\mathbf{I}_g = \frac{50/\underline{0^\circ}}{10 - j7.5} = 3.2 + j2.4 \text{ A}$$

$$S_g = \frac{1}{2} \mathbf{V}_g \mathbf{I}_g^* = 25(3.2 - j2.4) = 80 - j60 \text{ VA}$$

$$P = 80 \text{ W (del)}; \quad Q = 60 \text{ VAR (abs)}$$

$$|S| = |S_g| = 100 \text{ VA}$$

[b]  $\mathbf{I}_1 = \frac{\mathbf{I}_g(j5)}{5 + j5} = \frac{1}{2}(3.2 + j2.4)(1 + j1) = 0.4 + j2.8 \text{ A}$

$$P_{5\Omega} = \frac{1}{2} |\mathbf{I}_1|^2 (5) = 20 \text{ W}$$

$$P_{7.5\Omega} = \frac{1}{2} |\mathbf{I}_g|^2 (7.5) = 60 \text{ W}$$

$$\sum P_{\text{diss}} = 20 + 60 = 80 \text{ W} = \sum P_{\text{dev}}$$

$$[c] \quad I_{j5} = \frac{I_g 5}{5 + j5} = \frac{1}{2}(3.2 + j2.4)(1 - j1) = 2.8 - j0.4 \text{ A}$$

$$Q_{j5\Omega} = \frac{1}{2}|I_{j5}|^2(5) = 20 \text{ VAR(abc)}$$

$$Q_{-j10\Omega} = \frac{1}{2}|I_g|^2(-10) = -80 \text{ VAR(dev)}$$

$$\sum Q_{\text{abs}} = 20 + 60 = 80 \text{ VAR} = \sum Q_{\text{dev}}$$

P 7.74 [a]  $S_1 = 24,960 + j47,040 \text{ VA}$

$$S_2 = \frac{|\mathbf{V}_L|^2}{Z_2} = \frac{(480)^2}{5 + j5} = 23,040 - j23,040 \text{ VA}$$

$$S_1 + S_2 = 48,000 + j24,000 \text{ VA}$$

$$480\mathbf{I}_L^* = 48,000 + j24,000; \quad \therefore \mathbf{I}_L = 100 - j50 \text{ A(rms)}$$


$$\begin{aligned} \mathbf{V}_g &= \mathbf{V}_L + \mathbf{I}_L(0.02 + j0.20) = 480 + (100 - j50)(0.02 + j0.20) \\ &= 492 + j19 = 492.37 \angle 2.21^\circ \text{ Vrms} \end{aligned}$$

$$|\mathbf{V}_g| = 492.37 \text{ Vrms}$$

[b]  $T = \frac{1}{f} = \frac{1}{60} = 16.67 \text{ ms}$

$$\frac{2.21^\circ}{360^\circ} = \frac{t}{16.67 \text{ ms}}; \quad \therefore t = 102.39 \mu\text{s}$$

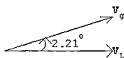[c]  $\mathbf{V}_L$  lags  $\mathbf{V}_g$  by  $2.21^\circ$  or  $102.31 \mu\text{s}$



P 7.75 [a]  $S_1 = 18 + j24 \text{ kVA}; \quad S_2 = 36 - j48 \text{ kVA}; \quad S_3 = 18 + j0 \text{ kVA}$

$$S_T = S_1 + S_2 + S_3 = 72 - j24 \text{ kVA}$$

$$2400\mathbf{I}^* = (72 - j24) \times 10^3; \quad \therefore \mathbf{I} = 30 + j10 \text{ A}$$

$$Z = \frac{2400}{30 + j10} = 72 - j24 \Omega = 75.89 \angle -18.43^\circ \Omega$$

[b]  $\text{pf} = \cos(-18.43^\circ) = 0.9487 \text{ leading}$

P 7.76 [a] From the solution to Problem 7.75 we have

$$\mathbf{I}_L = 30 + j10 \text{ A (rms)}$$

$$\begin{aligned}\therefore \mathbf{V}_s &= 2400\angle 0^\circ + (30 + j10)(0.2 + j1.6) = 2390 + j50 \\ &= 2390.52\angle 1.20^\circ \text{ V (rms)}\end{aligned}$$


[b]  $|\mathbf{I}_L| = \sqrt{1000}$

$$P_\ell = (1000)(0.2) = 200 \text{ W} \quad Q_\ell = (1000)(1.6) = 1600 \text{ VAR}$$

[c]  $P_s = 72,000 + 200 = 72.2 \text{ kW} \quad Q_s = -24,000 + 1600 = -22.4 \text{ kVAR}$

[d]  $\eta = \frac{72}{72.2}(100) = 99.72\%$

P 7.77

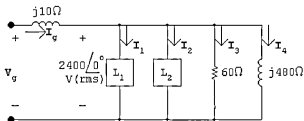

$$2400\mathbf{I}_1^* = 24,000 + j18,000$$

$$\mathbf{I}_1^* = 10 + j7.5; \quad \therefore \mathbf{I}_1 = 10 - j7.5 \text{ A (rms)}$$

$$2400\mathbf{I}_2^* = 48,000 - j30,000$$

$$\mathbf{I}_2^* = 20 - j12.5; \quad \therefore \mathbf{I}_2 = 20 + j12.5 \text{ A (rms)}$$

$$\mathbf{I}_3 = \frac{2400\angle 0^\circ}{60} = 40 + j0 \text{ A}; \quad \mathbf{I}_4 = \frac{2400\angle 0^\circ}{j480} = 0 - j5 \text{ A}$$

$$\mathbf{I}_g = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 + \mathbf{I}_4 = 70 \text{ A}$$

$$\mathbf{V}_g = 2400 + (70)(j10) = 2400 + j700 = 2500\angle 16.26^\circ \text{ V (rms)}$$

P 7.78  $S_T = 52,800 - j\frac{52,800}{0.8}(0.6) = 52,800 - j39,600 \text{ VA}$

$$S_1 = 40,000(0.96 + j0.28) = 38,400 + j11,200 \text{ VA}$$

$$S_2 = S_T - S_1 = 14,400 - j50,800 = 52,801.52\angle -74.17^\circ \text{ VA}$$

$$\text{pf} = \cos(-74.17^\circ) = 0.2727 \text{ leading}$$

$$\text{P 7.79 [a] } \mathbf{I} = \frac{7200 \angle 0^\circ}{140 + j480} = 14.4 \angle -73.74^\circ \text{ A (rms)}$$

$$P = (14.4)^2(2) = 414.72 \text{ W}$$

$$\text{[b] } \mathbf{Y}_L = \frac{1}{138 + j460} = \frac{138 - j460}{230,644}$$

$$\therefore -j\omega C = -j \frac{460}{230,644} \quad \therefore X_C = \frac{-230,644}{460} = -501.40 \Omega$$

$$\text{[c] } \mathbf{Z}_L = \frac{230,644}{138} = 1671.33 \Omega$$


$$\text{[d] } \mathbf{I} = \frac{7200}{1673.33 + j20} = 4.30 \angle -0.68^\circ \text{ A}$$

$$P = (4.30)^2(2) = 37.02 \text{ W}$$

$$\text{[e] } \% = \frac{37.02}{414.72}(100) = 8.93\%$$

Thus the power loss after the capacitor is added is 8.93% of the power loss before the capacitor is added.

P 7.80 [a]

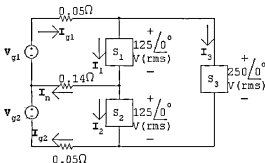

$$\mathbf{I}_1 = \frac{5000 - j2000}{125} = 40 - j16 \text{ A (rms)}$$

$$\mathbf{I}_2 = \frac{3750 - j1500}{125} = 30 - j12 \text{ A (rms)}$$

$$\mathbf{I}_3 = \frac{8000 + j0}{250} = 32 + j0 \text{ A (rms)}$$

$$\therefore \mathbf{I}_{g1} = 72 - j16 \text{ A (rms)}$$

$$\mathbf{I}_n = \mathbf{I}_1 - \mathbf{I}_2 = 10 - j4 \text{ A (rms)}$$

$$\mathbf{I}_{g2} = 62 - j12 \text{ A}$$

$$\mathbf{V}_{g1} = 0.05\mathbf{I}_{g1} + 125 + j0 + 0.14\mathbf{I}_n = 130 - j1.36 \text{ V (rms)}$$



$$\mathbf{V}_{g2} = -0.14\mathbf{I}_n + 125 + j0 + 0.05\mathbf{I}_{g2} = 126.7 - j0.04\text{ V(rms)}$$

$$S_{g1} = [(130 - j1.36)(72 + j16)] = [9381.76 + j1982.08]\text{ VA}$$

$$S_{g2} = [(126.7 - j0.04)(62 + j12)] = [7855.88 + j1517.92]\text{ VA}$$

Note: Both sources are delivering average power and magnetizing VAR to the circuit.

$$[\text{b}] P_{0.05} = |\mathbf{I}_{g1}|^2(0.05) = 272\text{ W}$$

$$P_{0.14} = |\mathbf{I}_n|^2(0.14) = 16.24\text{ W}$$

$$P_{0.05} = |\mathbf{I}_{g2}|^2(0.05) = 199.4\text{ W}$$


$$\sum P_{\text{dis}} = 272 + 16.24 + 199.4 + 5000 + 3750 + 8000 = 17,237.64\text{ W}$$

$$\sum P_{\text{dev}} = 9381.76 + 7855.88 = 17,237.64\text{ W} = \sum P_{\text{dis}}$$

$$\sum Q_{\text{abs}} = 2000 + 1500 = 2500\text{ VAR}$$

$$\sum Q_{\text{del}} = 1982.08 + 1517.92 = 3500\text{ VAR} = \sum Q_{\text{abs}}$$

P 7.81 [a]

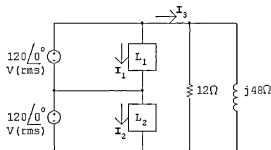

$$120\mathbf{I}_1^* = 1800 + j600; \quad \therefore \mathbf{I}_1 = 15 - j5\text{ A(rms)}$$

$$120\mathbf{I}_2^* = 1200 - j900; \quad \therefore \mathbf{I}_2 = 10 + j7.5\text{ A(rms)}$$

$$\mathbf{I}_3 = \frac{240}{12} + \frac{240}{j48} = 20 - j5\text{ A(rms)}$$

$$\mathbf{I}_{g1} = \mathbf{I}_1 + \mathbf{I}_3 = 35 - j10\text{ A}$$

$$S_{g1} = 120(35 + j10) = 4200 + j1200\text{ VA}$$

Thus the  $\mathbf{V}_{g1}$  source is delivering 4200 W and 1200 magnetizing vars.

$$\mathbf{I}_{g2} = \mathbf{I}_2 + \mathbf{I}_3 = 30 + j2.5\text{ A(rms)}$$

$$S_{g2} = 120(30 - j2.5) = 3600 - j300\text{ VA}$$

Thus the  $\mathbf{V}_{g2}$  source is delivering 3600 W and absorbing 300 magnetizing vars.

$$[b] \sum P_{\text{gen}} = 4200 + 3600 = 7800 \text{ W}$$

$$\sum P_{\text{abs}} = 1800 + 1200 + \frac{(240)^2}{12} = 7800 \text{ W} = \sum P_{\text{gen}}$$

$$\sum Q_{\text{del}} = 1200 + 900 = 2100 \text{ VAR}$$

$$\sum Q_{\text{abs}} = 300 + 600 + \frac{(240)^2}{48} = 2100 \text{ VAR} = \sum Q_{\text{del}}$$

P 7.82 [a]  $S_L = 24 + j7 \text{ kVA}$

$$125 \mathbf{I}_L^* = (24 + j7) \times 10^3; \quad \mathbf{I}_L^* = 192 + j56 \text{ A(rms)}$$

$$\therefore \mathbf{I}_L = 192 - j56 \text{ A(rms)}$$

$$\begin{aligned} \mathbf{V}_s &= 125 + (192 - j56)(0.006 + j0.048) = 128.84 + j8.88 \\ &= 129.15 \angle 3.94^\circ \text{ V(rms)} \end{aligned}$$

$$|\mathbf{V}_s| = 129.15 \text{ V(rms)}$$

$$[b] P_\ell = |\mathbf{I}_\ell|^2 (0.006) = (200)^2 (0.006) = 240 \text{ W}$$

$$[c] \frac{(125)^2}{X_C} = -7000; \quad X_C = -2.23 \Omega$$

$$-\frac{1}{\omega C} = -2.23; \quad C = \frac{1}{(2.23)(120\pi)} = 1188.36 \mu\text{F}$$

[d]  $\mathbf{I}_\ell = 192 + j0 \text{ A(rms)}$

$$\begin{aligned} \mathbf{V}_s &= 125 + 192(0.006 + j0.048) = 126.152 + j9.216 \\ &= 126.49 \angle 4.18^\circ \text{ V(rms)} \end{aligned}$$

$$|\mathbf{V}_s| = 126.49 \text{ V(rms)}$$

$$[e] P_\ell = (192)^2 (0.006) = 221.184 \text{ W}$$

P 7.83 [a]  $\Delta = R_a R_b R_c - R_1^2 R_b - R_2^2 R_a - R_n (2R_1 R_2 + R_n R_c)$

$$R_a = R_1 + R_n + R_t = 30 + 1 + 0.5 = 31.5 \Omega$$

$$R_b = R_2 + R_n + R_t = 300 + 1 + 0.5 = 301.5 \Omega$$

$$R_c = R_1 + R_2 + R_3 = 30 + 300 + 15 = 345 \Omega$$

$$\begin{aligned} \Delta &= (31.5)(301.5)(345) - 900(301.5) - 9 \times 10^4(31.5) \\ &\quad - 1[2(30)(300) + 1(345)] \\ &= 151,856.25 \end{aligned}$$

$$\begin{aligned}
 N_a &= \mathbf{V}_{g1}[(R_b R_c - R_2^2) + R_n R_c + R_1 R_2] \\
 &= 120[(301.5)(345) - 9 \times 10^4 + 345 + 30(300)] \\
 &= 2,803,500
 \end{aligned}$$

$$\begin{aligned}
 N_b &= \mathbf{V}_{g1}[R_n R_c + R_1 R_2 + R_a R_c - R_1^2] \\
 &= 120[345 + (30)(300) + 31.5(345) - 900] \\
 &= 2,317,500
 \end{aligned}$$

$$\mathbf{I}_a = \frac{N_a}{\Delta}; \quad \mathbf{I}_b = \frac{N_b}{\Delta}$$

$$\mathbf{I}_n = \mathbf{I}_a - \mathbf{I}_b = \frac{N_a - N_b}{\Delta} = 3.2/\underline{0^\circ} \text{A(rms)}$$

[b]

$$\begin{aligned}
 N_c &= \mathbf{V}_{g1}[R_2 R_n + R_1 R_b + R_2 R_a + R_1 R_n] \\
 &= 120[300 + 30(301.5) + 31.5(300) + 30] \\
 &= 2,259,000
 \end{aligned}$$

$$\mathbf{I}_{L1} = \frac{N_a - N_c}{\Delta}$$

$$\mathbf{V}_1 = 30\mathbf{I}_{L1} = \frac{30(N_a - N_c)}{\Delta} = 107.57/\underline{0^\circ} \text{V(rms)}$$

$$[c] \quad \mathbf{I}_{L2} = \frac{N_b - N_c}{\Delta}$$

$$\mathbf{V}_2 = 300\mathbf{I}_{L2} = \frac{300(N_b - N_c)}{\Delta} = 115.57/\underline{0^\circ} \text{V(rms)}$$

$$[d] \quad \mathbf{V}_3 = 15\mathbf{I}_c = 15\frac{N_c}{\Delta} = 233.14/\underline{0^\circ} \text{V(rms)}$$

CHECK:

$$\mathbf{V}_3 = \mathbf{V}_1 + \mathbf{V}_2 = 107.57/\underline{0^\circ} + 115.57/\underline{0^\circ} = 233.14/\underline{0^\circ} \text{V(rms)}$$

$$[e] \quad P_1 = \frac{|\mathbf{V}_1|^2}{R_1} = \frac{(107.57)^2}{30} = 385.70 \text{ W}$$

$$P_2 = \frac{|\mathbf{V}_2|^2}{R_2} = \frac{(115.57)^2}{300} = 44.52 \text{ W}$$

$$P_3 = \frac{|\mathbf{V}_3|^2}{R_3} = \frac{(233.14)^2}{15} = 3319.39 \text{ W}$$

$$[\text{f}] \quad \mathbf{I}_a = \frac{N_a}{\Delta} = 18.46/\underline{0^\circ} \text{ A (rms)}$$

$$\mathbf{I}_b = \frac{N_b}{\Delta} = 15.26/\underline{0^\circ} \text{ A (rms)}$$

$$P_a = (120)(18.46) \cos 0^\circ$$

$$P_b = (120)(15.26) \cos 0^\circ$$

$$\sum P_{\text{gen}} = 120(18.46 + 15.26) = 4046.72 \text{ W}$$

$$[\text{g}] \quad P_a = |\mathbf{I}_a|^2(0.5) = 170.41 \text{ W}$$


$$P_n = |\mathbf{I}_n|^2(1) = 10.24 \text{ W}$$

$$P_b = |\mathbf{I}_b|^2(0.5) = 116.45 \text{ W}$$

$$\begin{aligned} \sum P_{\text{diss}} &= 170.41 + 10.24 + 116.45 + 385.70 \\ &\quad + 44.52 + 3319.39 \\ &= 4046.72 \text{ W} \end{aligned}$$

P 7.84 [a]  $\mathbf{I}_n = 0$  by hypothesis.

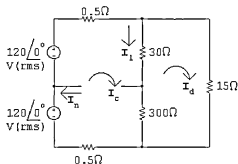[b] With the neutral conductor open the circuit becomes:



The two mesh current equations are

$$240/\underline{0^\circ} = 331\mathbf{I}_c - 330\mathbf{I}_d$$

$$0 = -330\mathbf{I}_c + 345\mathbf{I}_d$$

$$\therefore \mathbf{I}_c = \frac{82,800}{5295} + 15.64/\underline{0^\circ} \text{ A (rms)}$$

$$\mathbf{I}_d = \frac{79,200}{5295} + 14.96/\underline{0^\circ} \text{ A (rms)}$$

$$\mathbf{I}_1 = \mathbf{I}_c - \mathbf{I}_d = 0.68/\underline{0^\circ} \text{ A (rms)}$$

$$\mathbf{V}_1 = 30\mathbf{I}_1 = 20.40/\underline{0^\circ} \text{ V (rms)}$$

$$[\text{c}] \quad \mathbf{V}_2 = 300\mathbf{I}_1 = 203.97/\underline{0^\circ}\text{V}(\text{rms})$$

$$[\text{d}] \quad \mathbf{V}_3 = 15\mathbf{I}_d = 224.36/\underline{0^\circ}\text{V}(\text{rms})$$

$$[\text{e}] \quad P_{R_1} = (20.40)^2/30 = 13.87 \text{ W}$$

$$P_{R_2} = (203.97)^2/300 = 138.67 \text{ W}$$

$$P_{R_3} = (224.36)^2/15 = 3355.91 \text{ W}$$

$$[\text{f}] \quad \sum P_{\text{gen}} = 240|\mathbf{I}_e| \cos 0^\circ = (240)(15.64)(1) = 3752.97 \text{ W}$$

$$[\text{g}] \quad \sum P_{\text{diss}} = (15.64)^2(1) + 13.87 + 138.67 + 3355.91 = 3752.97 \text{ W}$$