



Joint Programme Examinations 2016/17

BBO4102 Introduction to Electronic Systems

Paper A

Time allowed 2 hours

Questions 1- 8 are for All Students.
Questions 7- 8 are for only Classes 1~16.
Questions 9~10 are for only Classes 17~22.


1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
Total	

Complete the information below about yourself very carefully.

QM student number

BUPT student number

Class number



INSTRUCTIONS

- INSTRUCTIONS**
1. You must not take answer books, used or unused, from the examination room.
 2. Write only in black or blue pen and in English.
 3. Do all rough work in the answer book – do not tear out any pages.
 4. If you use Supplementary Answer Books, tie them to the end of this book.
 5. Write clearly and legibly.
 6. Read the instructions on the inside cover.

Examiners

Hongxiang Wang, Minglun Zhang, Dong Liang, Yong Zuo, Jinnan Zhang, Hongtao Zhang, Dao Yang

BBC4102 2016/2017


Introduction to Electronic Systems Paper A

Solutions & Analysis

By Puyuan Zheng, BUPTIS.

(写在前面的话：解答题给分点均根据解析者本人对题目的理解认为的采分点。与实际若有不同，请以实际判分为准，本解析写出的采分点仅供参考。本解析若有问题错误，欢迎批评指正。)

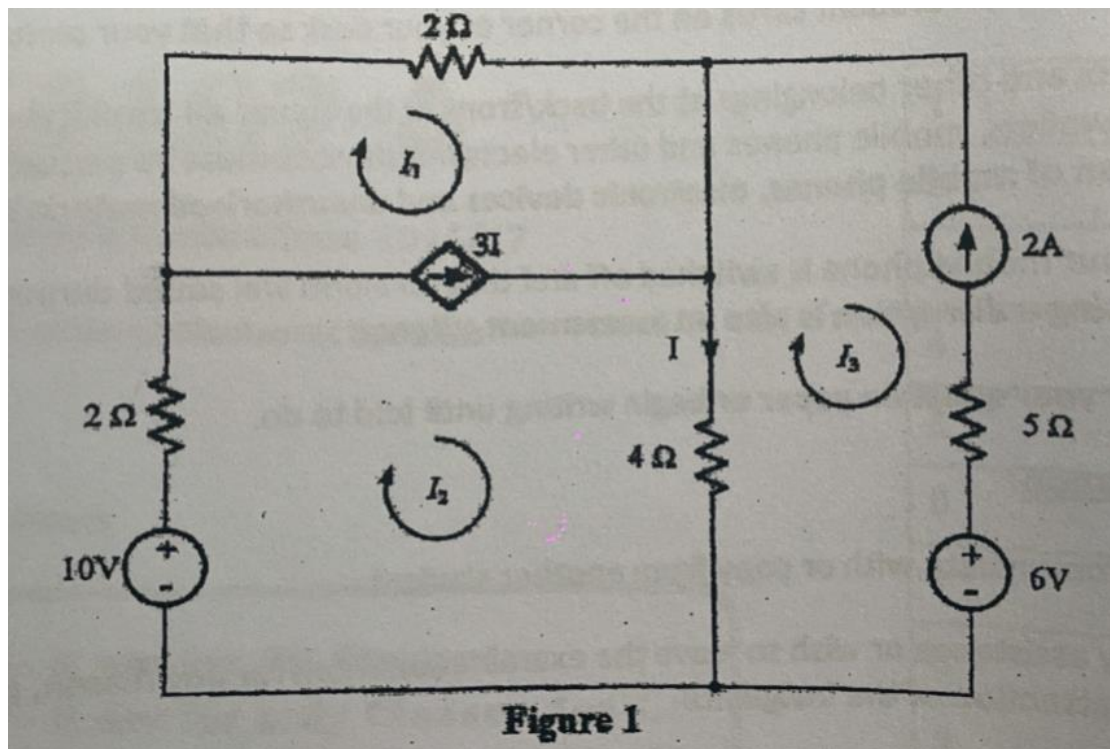Question 1 (12 Marks): Use the mesh-current method to find the power dissipated by the 4Ω resistor in the circuit in Figure 1.



【考点 Point】

网孔电流法 Mesh-current method

电阻功率计算 Find the power of a resistor

Answer: 324W.

【解析 Analysis】

先用网孔电流法解出通过 4Ω 电阻的电流 I ，然后根据电阻功率的公式计算即

可。

Solution:

By mesh-current method, we have the equations

$$\begin{cases} 10 - 2I_2 - 2I_1 - 4I = 0 \\ 4I + V_{2A} - 5I_3 - 6 = 0 \end{cases}$$

Since $I = I_2 - I_3$ and $I_3 = -2A$, we have

$$\begin{cases} 10 - 2I_2 - 2I_1 - 4(I_2 + 2) = 0 \\ 4I_2 + V_{2A} + 12 = 0 \end{cases}$$

Since $3I = I_2 - I_1$, then we have $2I_2 + I_1 = -6A$

That is,

$$10 - 2I_2 - 2(-6A - 2I_2) - 4(I_2 + 2) = 0$$

$$14 - 2I_2 = 0$$

By solving the equations, we have

$$\begin{cases} I_1 = -20A \\ I_2 = 7A \end{cases}$$


Then $I = I_2 - I_3 = 9A$

The power dissipated by the 4Ω resistor is:

$$P = I^2 \cdot 4\Omega = (9A)^2 \cdot 4\Omega = 324W$$

Finish.

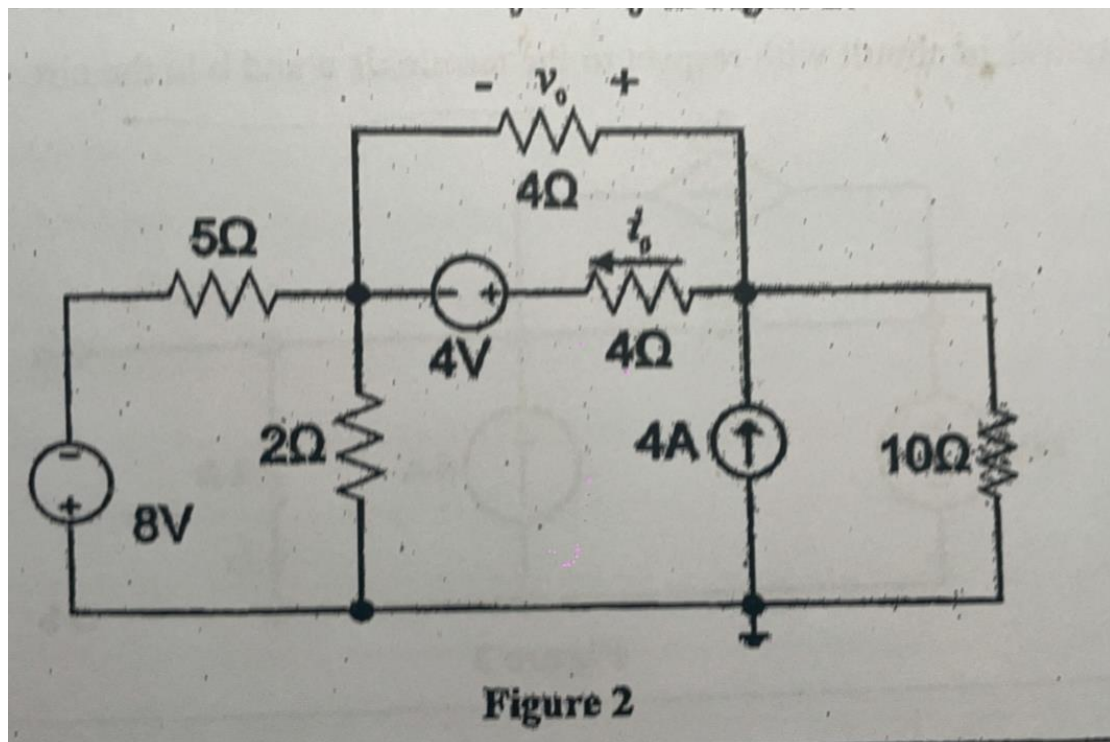Question 2 (12 Marks): Use the Node-Voltage method to find the value of v_0 and i_0 in Figure 2.



【考点 Point】

节点电压法 Node-voltage method


Answer: 8V, 1A.

【解析 Analysis】

直接节点电压法求解就可以了，注意参考点的选择。

Solution:

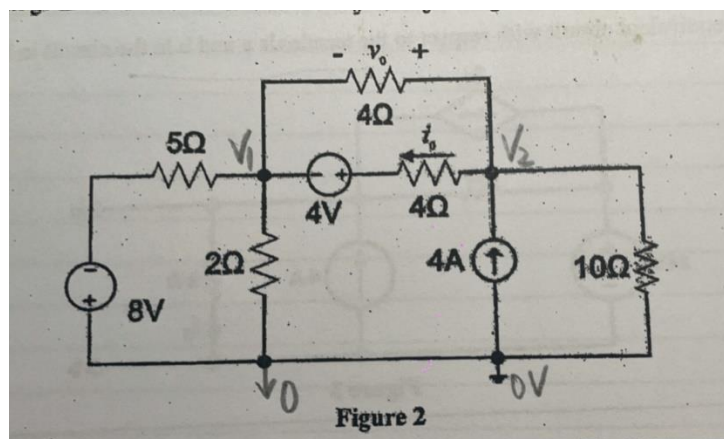We set the reference point and the node point as the picture below.



By node-voltage method, we have the equations

$$\begin{cases} \frac{v_1 - (-8)}{5} + \frac{v_1}{2} + \frac{v_1 - v_2}{4} + \frac{v_1 + 4 - v_2}{4} = 0 \\ -4 + \frac{v_2}{10} + \frac{v_2 - v_1}{4} + \frac{v_2 - v_1 - 4}{4} = 0 \end{cases}$$

That is,


$$\begin{cases} \frac{6}{5}v_1 - \frac{1}{2}v_2 + \frac{13}{5} = 0 \\ -\frac{1}{2}v_1 + \frac{3}{5}v_2 - 5 = 0 \end{cases}$$

By solving the equations, we have

$$\begin{cases} v_1 = 2V \\ v_2 = 10V \end{cases}$$


Then $v_0 = v_2 - v_1 = 8V$, $i_0 = \frac{v_2 - v_1 - 4}{4} = 1A$ Finish.

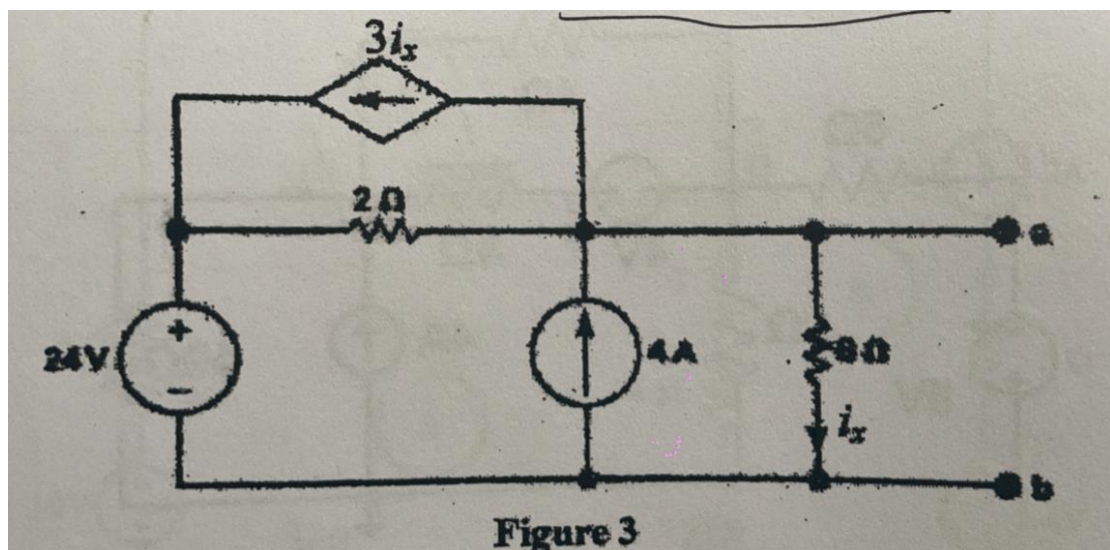Question 3 (13 Marks): Find the Thevenin equivalent circuit with respect to the terminals a and b in the circuit in Figure 3.



【考点 Point】

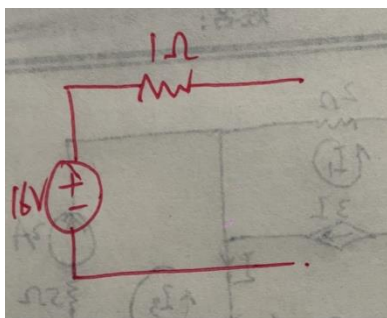求解戴维南等效电路 Find the Thevenin Equivalent circuit



Answer:

【解析 Analysis】

本题为求解戴维南等效电路，要解的是两个量，戴维南电压和戴维南电阻 R_{Th} 。

戴维南电压即开路电压，直接用平常解电压的方法求解即可。（节点/网孔）


对于戴维南电阻，本题既有受控源又有独立源，故使用开路电压短路电流的方法。

Solution:

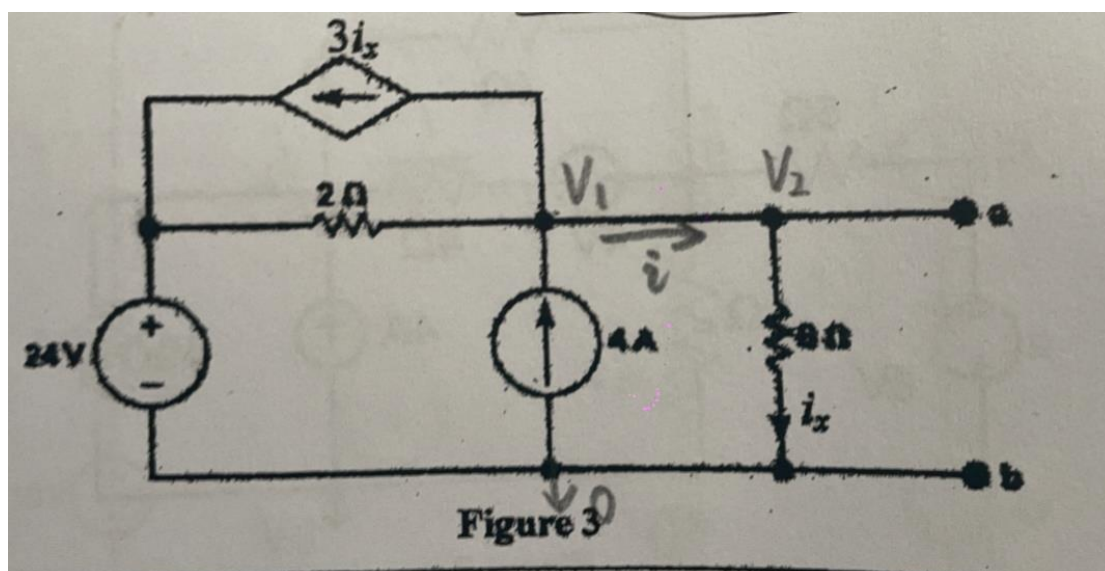Part 1: 求解戴维南电压 V_{Th}

Method 1: 节点电压法

We set the reference point and the node point as the picture below.



By node-voltage method, we have the equations

$$\begin{cases} \frac{v_1 - 24}{2} + i - 4 + 3i_x = 0 \\ \frac{v_a}{8} - i = 0 \end{cases}$$

Then, we have $i = \frac{v_a}{8}$.

Since $i = i_x$, $v_1 = v_a$, $v_b = 0$, then ,

That is,

$$\frac{v_1 - 24}{2} - 4 + 4i_x = 0$$

$$v_1 - 16 = 0$$


By solving the equations, we have

$$\begin{cases} v_1 = 16V \\ v_a = v_1 = 16V \\ v_b = 0V \end{cases}$$

Then $v_{TH} = v_a - v_b = 16V - 0V = 16V$

Method 2: 网孔电流法

We set the meshes as the picture below.

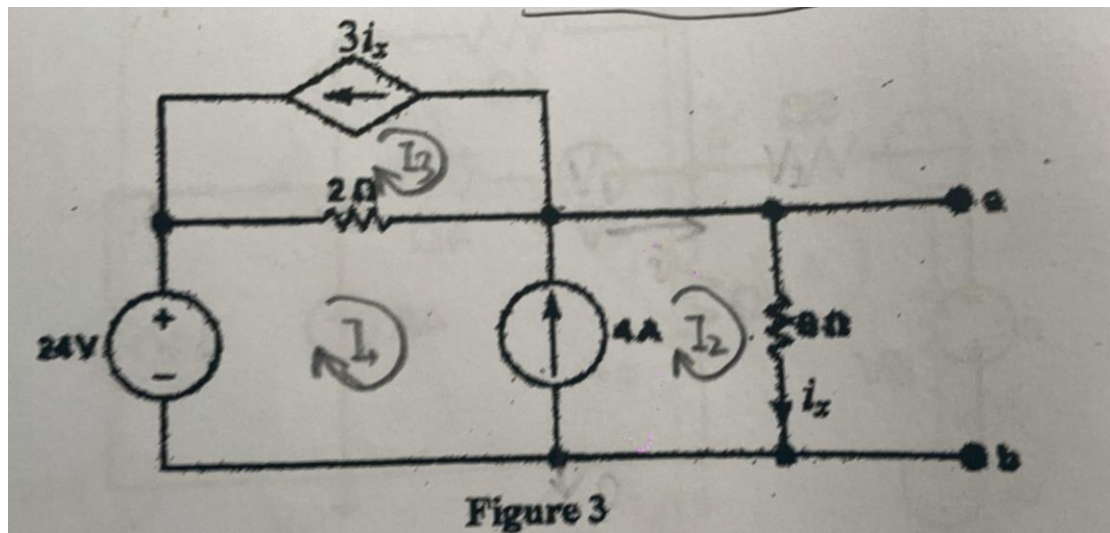

By mesh-current method, we have the equations

$$\begin{cases} 24 - 2(I_1 - I_3) - 8I_2 = 0 \\ -2(I_3 - I_1) + V_{3i_x} = 0 \end{cases}$$

Since $4A = I_2 - I_1$, $I_2 = I_x$, $I_3 = -3I_x$, we have

$$24 - 2(I_x - 4 + 3I_x) - 8I_x = 0$$

$$32 - 16I_x = 0$$


By solving the equations, we have $I_x = 2A$

$$\text{Then } V_{TH} = I_x \cdot 8\Omega = 2A \cdot 8\Omega = 16V$$

Next, we find the Thevenin equivalent resistor.

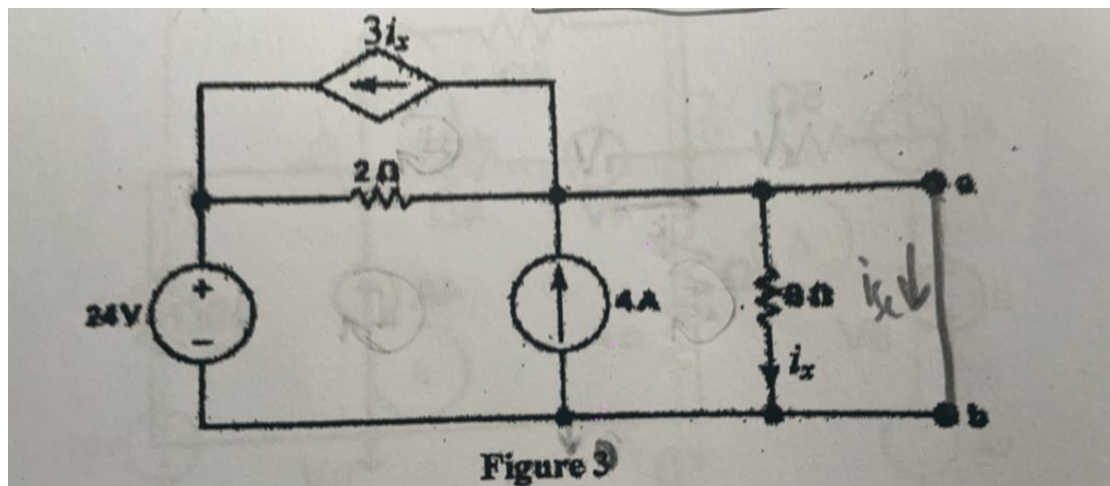
Part 2: 求解戴维南电阻 R_{Th}

By the method of short-circuit current, we have the circuit:



(这里只给了节点电压法，网孔电流就不再赘述了~)

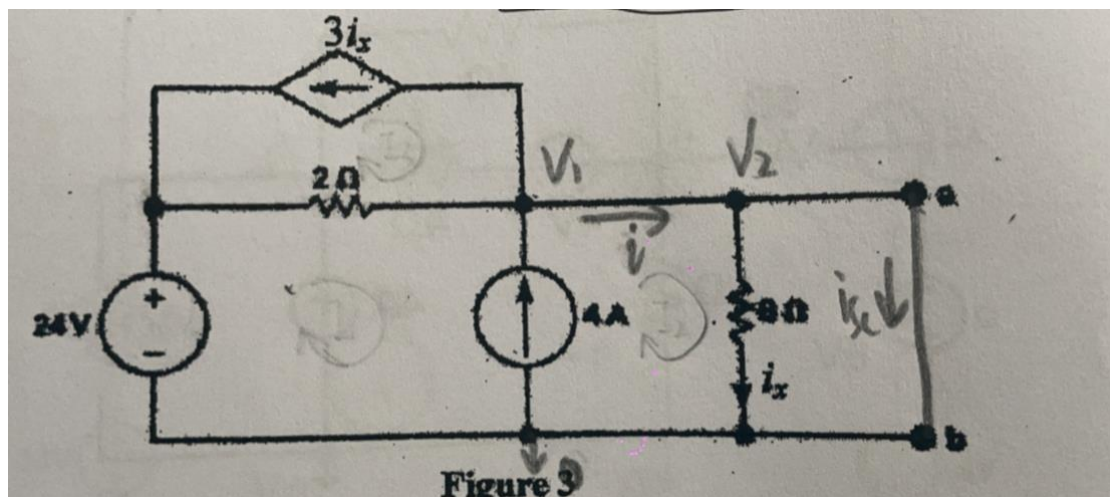By node-voltage method, we set the reference point and the node point as the picture below:



We have the equations:

$$\begin{cases} \frac{v_1 - 24}{2} + i - 4 + 3i_x = 0 \\ i_x - i + i_{sc} = 0 \end{cases}$$


Since $i_x = \frac{v_a}{8}$, $v_1 = v_a$, $v_b = 0$, then we have

$$\begin{cases} \frac{v_1 - 24}{2} - 4 + i + \frac{3v_a}{8} = 0 \\ \frac{v_a}{8} - i + i_{sc} = 0 \end{cases}$$

Since $v_b = v_a$, then $v_b = v_a = v_1 = 0$, By solving the equations, we have


$$\begin{cases} i = 16A \\ i_{sc} = 16A \end{cases}$$

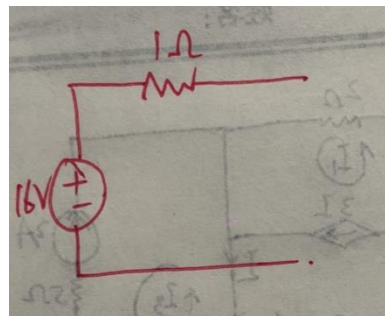Then $R_{TH} = \frac{V_{th}}{I_{sc}} = \frac{16V}{16A} = 1\Omega$



Finally, we find the Thevenin equivalent circuit.

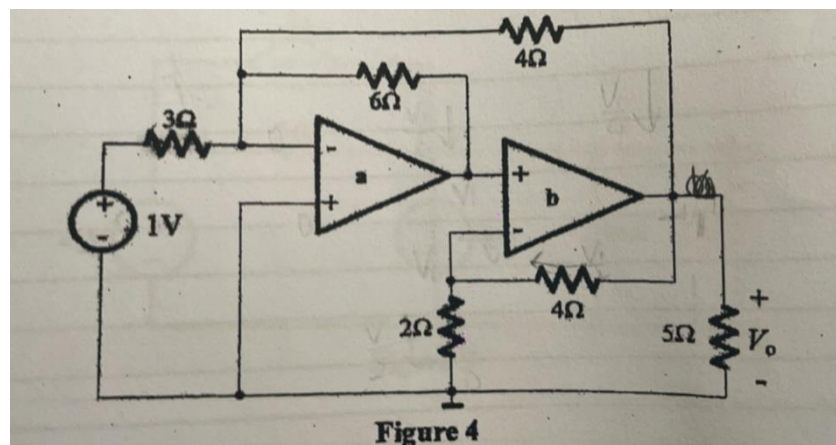Question 4 (12 Marks): The operational amplifiers in the circuit shown in Figure 4 are ideal. Find the voltage V_0 .



【考点 Point】

运算放大器 Op amp

Answer: $-\frac{12}{11}V$.


【解析 Analysis】

本题考察运算放大器。核心在于“虚短路，虚开路。”

别看是级联，电路很复杂，其实处处藏关系。靠上述六个字就能够化简绝大多数的部分。不要恐惧哦~

级联注意各放大器之间电压数值的联系。

Solution:

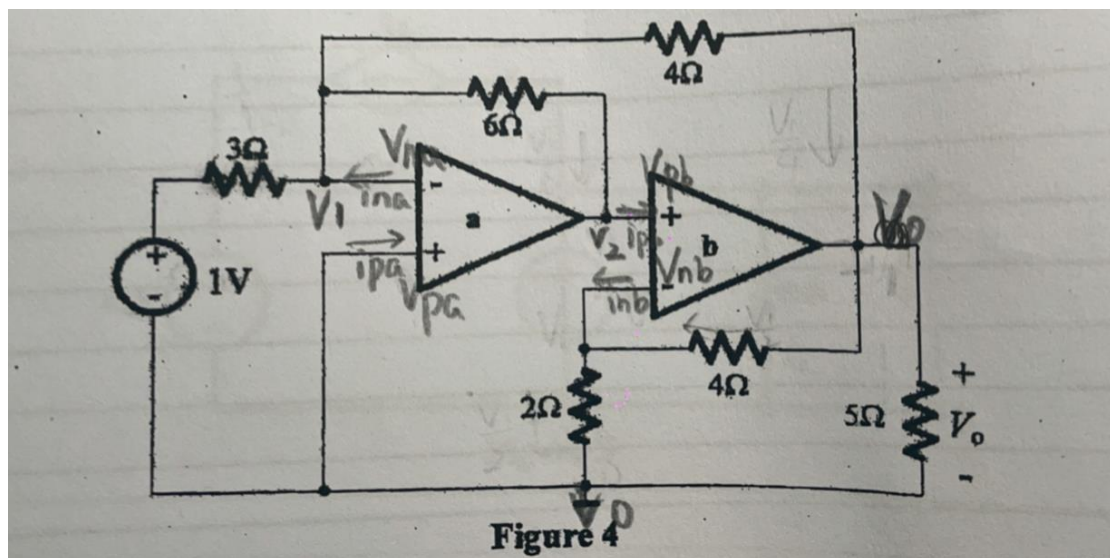

$$v_{pa} = v_{na} = 0V, v_{pb} = v_{nb}.$$

$$i_{pa} = i_{na} = i_{pb} = i_{nb} = 0$$

(记住! 碰到运算放大器看着电路就不想做的, 别怕, 先把上面所有的虚短路虚开路写上, 有分的!!!!)

Also, $v_1 = v_{na} = 0V, v_{pb} = v_{nb} = v_2$.

下面用节点电压法解需要的电压 V_o .

By node-voltage method, we have the equations

$$\begin{cases} \frac{v_1 - 1}{3} + \frac{v_1 - v_2}{6} + \frac{v_1 - v_0}{4} = 0 \\ \frac{v_2 - v_0}{4} + \frac{v_2}{2} = 0 \end{cases}$$

That is,


$$\begin{cases} \frac{3}{4}v_1 - \frac{1}{6}v_2 - \frac{1}{4}v_0 - \frac{1}{3} = 0 \\ \frac{3}{4}v_2 - \frac{1}{4}v_0 = 0 \end{cases} \rightarrow \begin{cases} \frac{1}{6}v_2 + \frac{1}{4}v_0 = -\frac{1}{3} \\ \frac{3}{4}v_2 - \frac{1}{4}v_0 = 0 \end{cases}$$

By solving the equations, we have

$$\begin{cases} v_2 = -\frac{4}{11}V \\ v_0 = -\frac{12}{11}V \end{cases}$$

Finish.

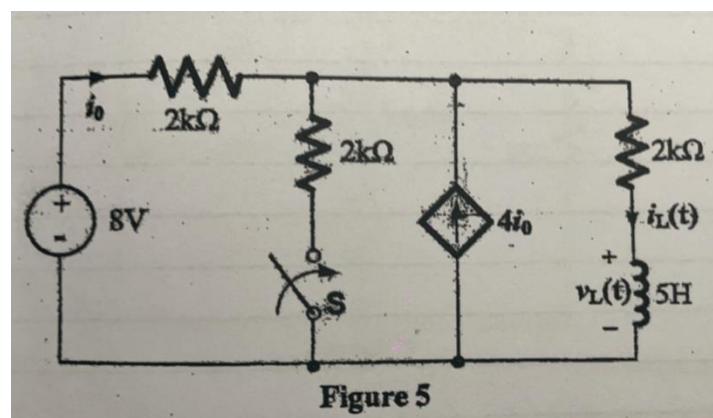Question 5 (12 Marks): The switch in the circuit in Figure 5 has been opened for a long time. At $t = 0$ the switch is closed. Find $v_L(t)$ for $t \geq 0^+$.



【考点 Point】

自然响应 Natural Responses in an RC circuit.


Answer: $v_L(t) = -\frac{70}{9}e^{-\frac{1400}{3}t}(t \geq 0^+)$.

【解析 Analysis】

本题考察电感自然响应的电路分析。分别对 $t < 0$ 和 $t \geq 0$ 的电路进行求解，还是老三步：初态、时间常数以及写表达式。初态可以直接根据 $t < 0$ 的电路写出，时间常数是求解戴维南电阻+电感，表达式就是带个自然常数。在这个思路下，可以求得我们需要的电感的电压随时间变化的函数。

Solution:

When $t < 0$,

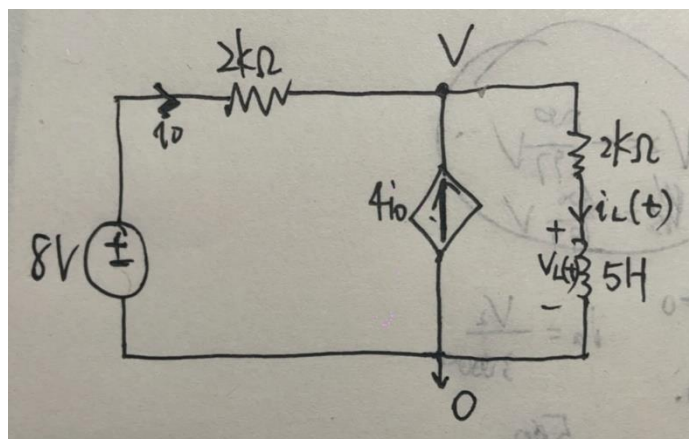

$$i_L(0) = 5i_0$$

$$\frac{v-8}{2000} - 4i_0 + \frac{v}{2000} = 0$$


$$i_0 = \frac{8-v}{2000}$$

$$\frac{6v-40}{2000} = 0$$

$$v = \frac{20}{3}V$$

$$i_L(0) = \frac{v}{2000} = \frac{1}{300}A$$


Then we find the Thevenin equivalent circuit at $t > 0$.

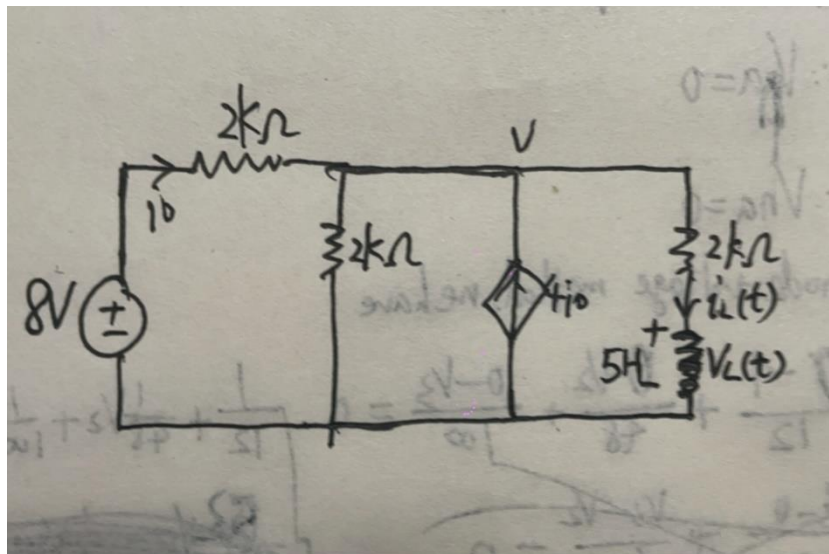

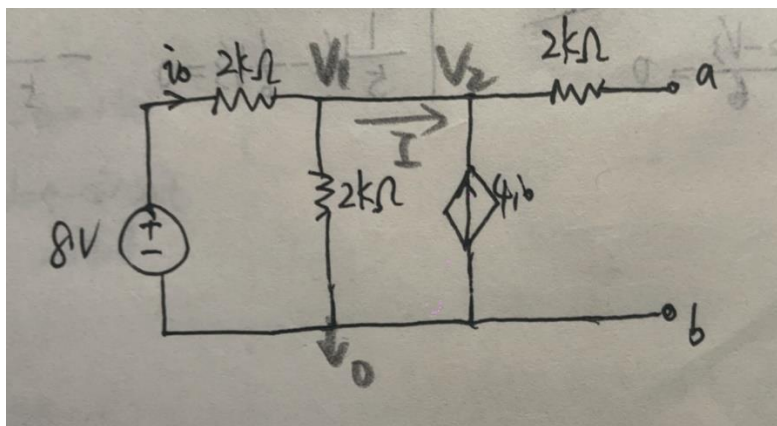Part 1: 求解戴维南电压 V_{Th}

这里只提供节点电压法，网孔电流不赘述了~

We set the reference point and the node point as the picture below.



By node-voltage method, we have the equations

$$\begin{cases} \frac{v_1}{2000} + I + \frac{v_1 - 8}{2000} = 0 \\ -I - 4i_0 = 0 \end{cases}$$

By solving the equations, we have

$$\frac{v_1}{2000} + \frac{v_1 - 8}{2000} - 4i_0 = 0$$

$$\frac{v_1}{1000} - \frac{1}{250} - 4i_o = 0$$

Since $i_o = \frac{8-v_1}{2000}$, then

$$\frac{v_1}{1000} - \frac{1}{250} - 4\left(\frac{8-v_1}{2000}\right) = 0$$

$$\frac{3v_1}{1000} - \frac{1}{50} = 0$$

$$v_1 = \frac{20}{3}V$$


$$v_a = v_1 = \frac{20}{3}V, v_b = 0V$$

Then $v_{TH} = v_a - v_b = \frac{20}{3}V$

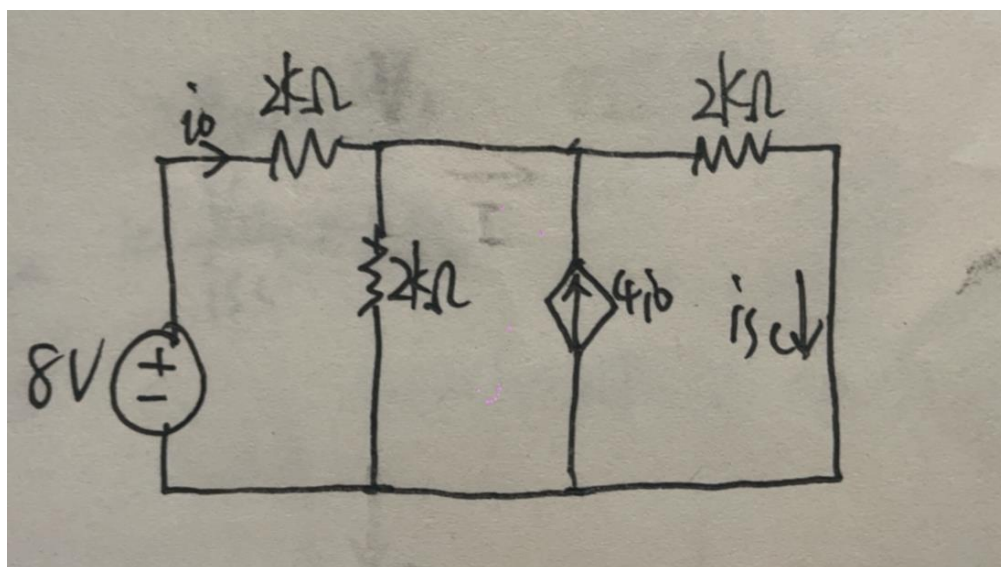Part 2: 求解戴维南电阻 R_{Th}


使用短路电流法求解。

By the method of short-circuit current, we have the circuit:



(这里只给了节点电压法，网孔电流就不再赘述了~)

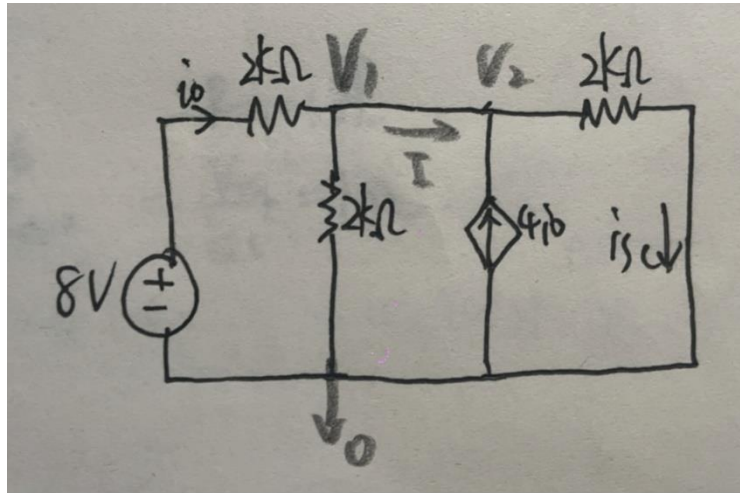By node-voltage method, we set the reference point and the node point as the picture below:



We have the equations:

$$\begin{cases} \frac{v_1}{2000} + I + \frac{v_1 - 8}{2000} = 0 \\ -I - 4i_0 + i_{sc} = 0 \end{cases}$$

That is,

$$\frac{v_1}{2000} + \frac{v_1 - 8}{2000} - 4i_0 + i_{sc} = 0$$

Since $i_0 = \frac{8 - v_1}{2000}$, then

$$\frac{v_1}{2000} + \frac{v_1 - 8}{2000} - 4\left(\frac{8 - v_1}{2000}\right) + i_{sc} = 0$$

$$\frac{3v_1}{1000} - \frac{1}{50} + i_{sc} = 0$$

Since $v_a = v_b = 0$, then $i_{sc} = \frac{v_2}{2000} A = \frac{v_1}{2000} A$

By solving the equations, we have

$$\frac{3v_1}{1000} - \frac{1}{50} + \frac{v_1}{2000} = 0$$

$$\frac{7v_1}{2000} - \frac{1}{50} = 0$$

Then, we have $v_1 = \frac{40}{7} V$

$$i_{sc} = \frac{v_1}{2000} = \frac{1}{350} A$$

Then $R_{TH} = \frac{V_{th}}{I_{sc}} = \frac{\frac{20}{3}V}{\frac{1}{350}A} = \frac{7000}{3} \Omega$

Then, the time constant of the capacitance is:

$$\tau = \frac{L}{R_{TH}} = \frac{3}{1400} s$$

Then, the expression of $i_L(t)$ at $t \geq 0^+$ is:


$$i_L(t) = \frac{1}{300} e^{-\frac{1400}{3}t} (t \geq 0)$$

Then, the expression of $v_L(t)$ is:

$$v_L(t) = L \frac{di_L(t)}{dt} = -\frac{70}{9} e^{-\frac{1400}{3}t} (t \geq 0^+)$$

Finish.

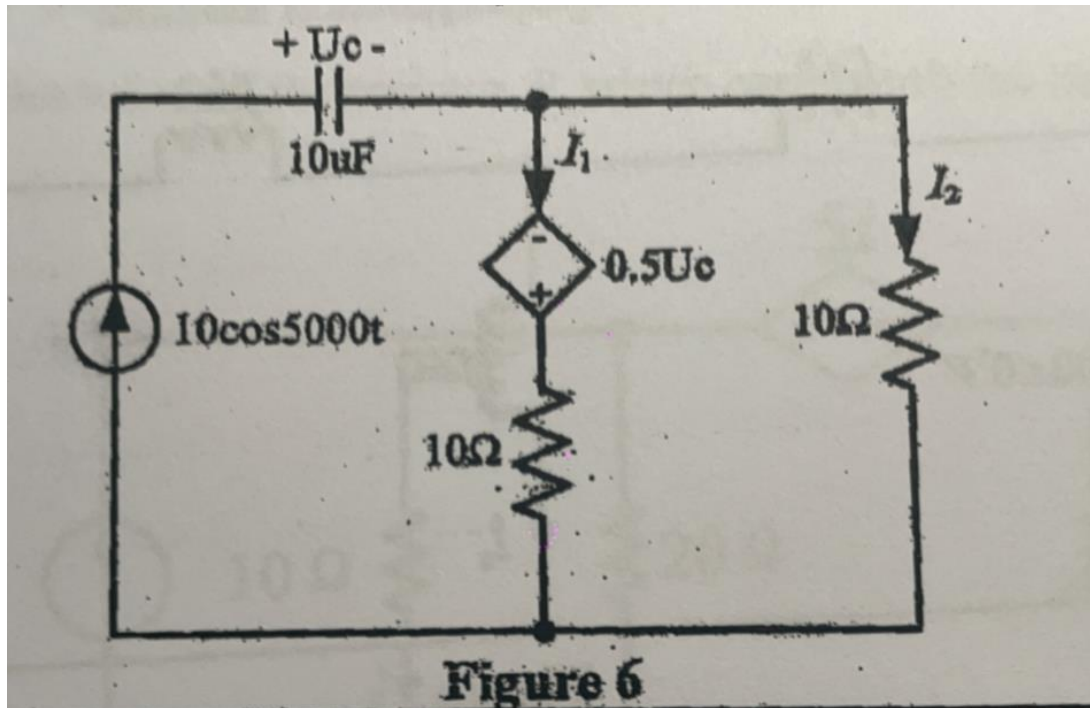Question 6 (13 Marks): Determine the currents I_1 and I_2 in Figure 6 with node voltage analysis method. The currents can be given by phasor form.



【考点 Point】

正弦稳态分析 The analysis of steady sinusoidal circuit

Answer:

$$i_1 = (5 - 5j)A = 5\sqrt{2}\angle -45^\circ A = 5\sqrt{2}\cos(5000t - 45^\circ)A.$$


$$i_2 = (5 + 5j)A = 5\sqrt{2}\angle 45^\circ A = 5\sqrt{2}\cos(5000t + 45^\circ)A$$

【解析 Analysis】

正弦稳态电路分析。和正常电路没啥区别，就多个复数计算。然后按题目要求节点电压法解就 ok 了。

Solution:

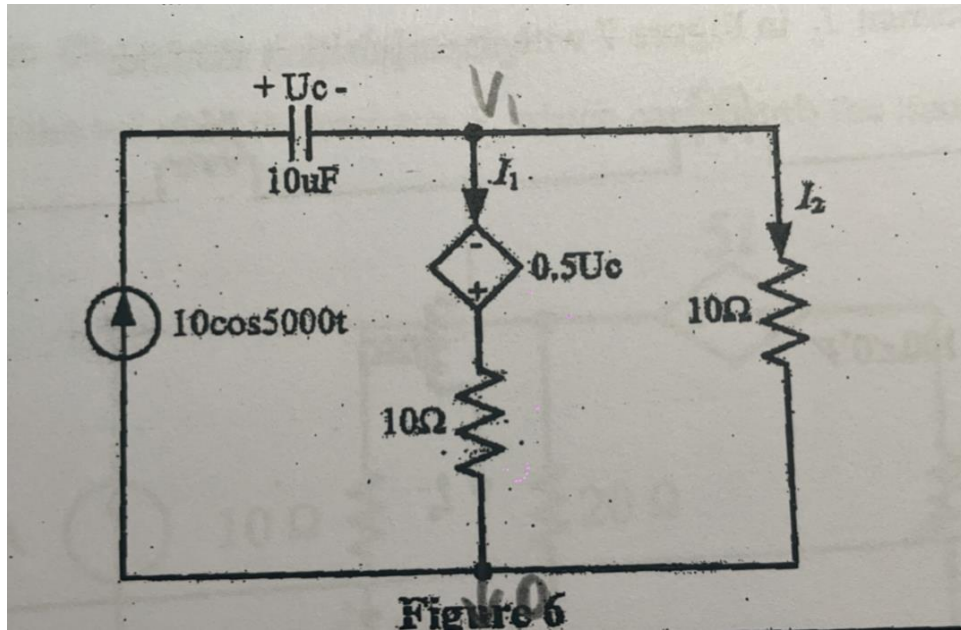We set the reference point and the node point as the picture below.



By node-voltage method, we have the equations

$$\frac{v_1 + 0.5U_c}{10} - 10\angle 0^\circ + \frac{v_1}{10} = 0$$

The resistor of the capacitor is:

$$Z_c = \frac{1}{j\omega C} = \frac{1}{j5000 \times 10 \times 10^{-6}} = -j20\Omega$$

Then, we have $U_c = 10\angle 0^\circ A \times (-j20\Omega) = -200jV$

That is,

$$\begin{aligned} \frac{v_1 - 100jV}{10} - 10\angle 0^\circ + \frac{v_1}{10} &= 0 \\ -10j - 10 + \frac{v_1}{5} &= 0 \end{aligned}$$

Then, we have $v_1 = 50 + 50j$.


Then,

$$\begin{aligned} i_1 &= \frac{v_1 + 0.5U_c}{10} = (5 - 5j)A = 5\sqrt{2}\angle -45^\circ A = 5\sqrt{2}\cos(5000t - 45^\circ)A. \\ i_2 &= \frac{v_1}{10} = (5 + 5j)A = 5\sqrt{2}\angle 45^\circ A = 5\sqrt{2}\cos(5000t + 45^\circ)A \end{aligned}$$

Finish.

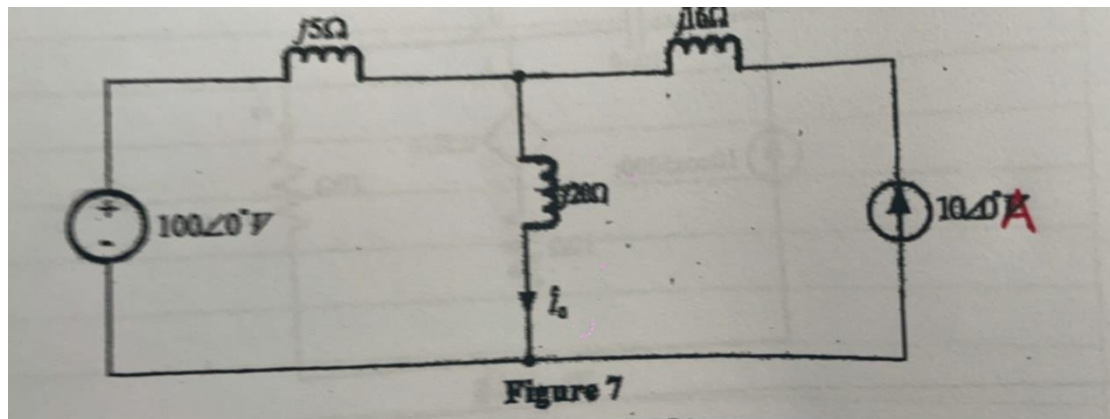Question 7 (13 Marks)——For Classes 1-16 Only:

Determine the phasor current I_0 in Figure 7 with superposition method.



【考点 Point】

叠加法 Superposition Method

Answer: $2 - 4jA$ / $2\sqrt{5}\angle -63.43^\circ A$ / $2\sqrt{5}\cos(\omega t - 63.43^\circ)(A)$.


【解析 Analysis】

叠加法来个简单复习：每次拆掉一个独立源（电压表短路、电流表断路）。

然后分别对每个电路的 I_0 进行求解，再把所有的分 I_0 加起来，得到答案。

Solution:

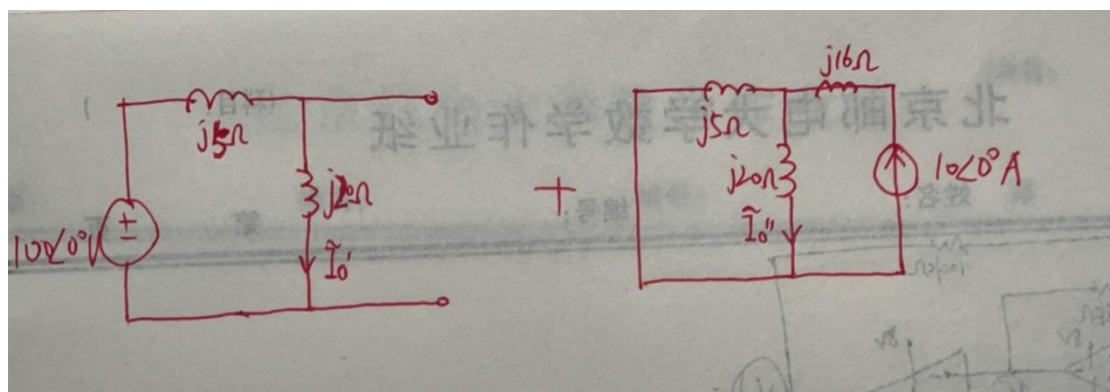By superposition method, since there are two independent sources, so we have two circuits to find the I_0 .



$$I'_0 = \frac{100\angle 0^\circ}{j5 + j20} + A = j(-4)A$$

$$I''_0 + \frac{j20\Omega}{j5\Omega} I''_0 = 10\angle 0^\circ = 0$$

$$I''_0 = 2\angle 0^\circ A$$

Then,

$$I_0 = I'_0 + I''_0 = 2 - 4jA$$


$$I_0 = 2\sqrt{5}\angle -63.43^\circ A$$

$$I_0 = 2\sqrt{5}\cos(\omega t - 63.43^\circ)(A)$$

Finish.

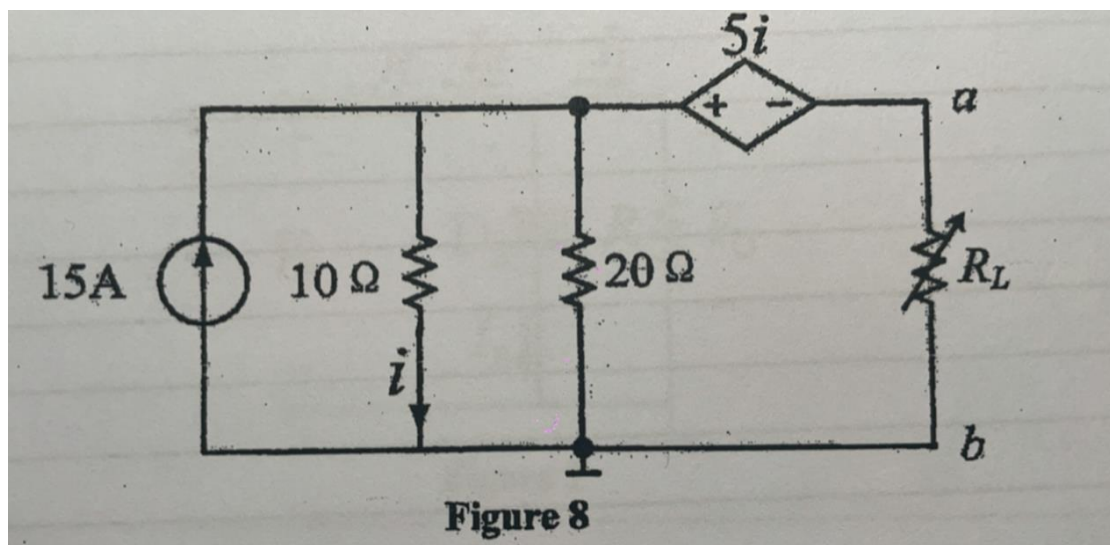Question 8 (13 Marks)——For Classes 1-16 Only:

In the circuit in Figure 8, find the value of the resistor R_L which can absorb the maximum power? And what is the maximum power?



【考点 Point】

最大功率传输 Maximum Power transformation

戴维南等效电路求解 Find the Thevenin Equivalent Circuit

Answer: $\frac{10}{3} \Omega$, $187.5W$.

【解析 Analysis】

电路达到最大功率是当外阻等于内阻的时候。我们需要先求出戴维南等效电路，之后当 $R_L = \text{戴维南电阻}$ 可以得到功率最大值 (理论解释部分请看教材或各任课教师 ppt)。在本道题的戴维南电路求解，仍然给出节点/网孔双解法 (求解戴维南电压)，因本题存在受控源，不能使用除源法，且因为独立源存在，我们只能用开路电压短路电流的方法来求解戴维南电阻。

所以说白，解对戴维南等效电路，是解对本题的关键！


Solution:

First, we find the Thevenin Equivalent circuit.

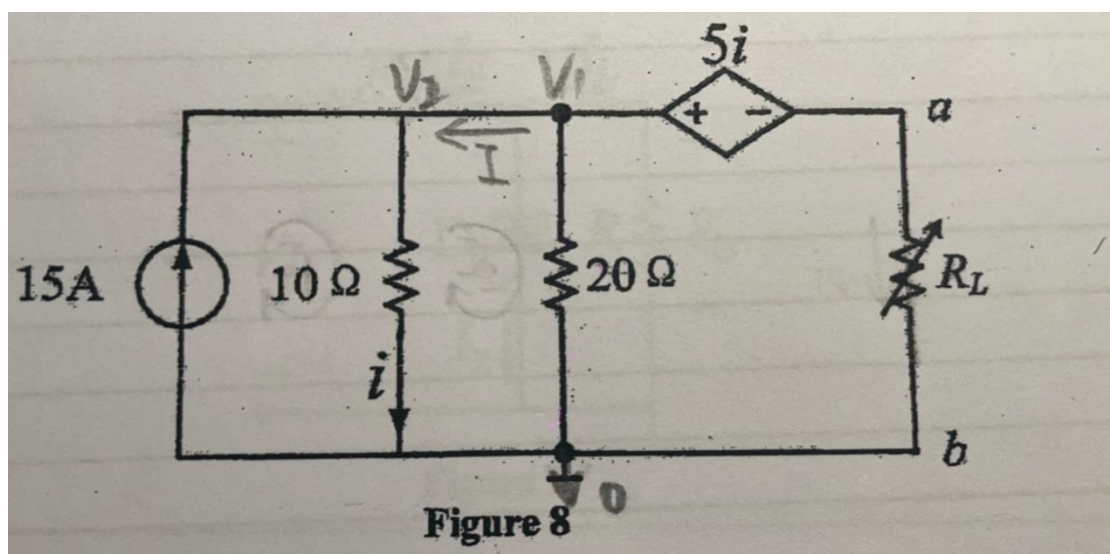Part 1: 求解戴维南电压 V_{Th}

Method 1: 节点电压法

We set the reference point and the node point as the picture below.



By node-voltage method, we have the equations

$$\begin{cases} \frac{v_1}{20} + I = 0 \\ \frac{v_2}{10} - I - 15 = 0 \end{cases}$$

Since $v_1 = v_2$, $i = \frac{v_2}{10}$, we have

$$\frac{v_1}{20} + \frac{v_1}{10} - 15 = 0$$

By solving the equations, we have


$$\begin{cases} v_1 = 100V \\ i = \frac{v_2}{10} = \frac{v_1}{10} = 10A \end{cases}$$

Since $v_b = 0V$, $v_a = v_1 - 5i = 50V$, then

$$v_{TH} = v_a - v_b = 50V - 0V = 50V$$

Method 2: 网孔电流法

We set the meshes as the picture below.

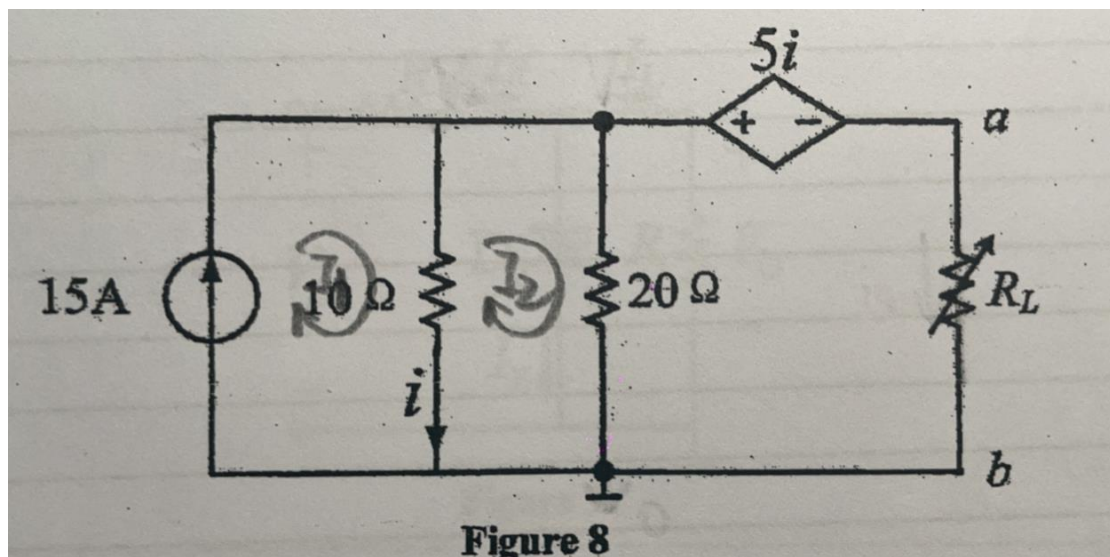

By mesh-current method, we have the equations

$$\begin{cases} V_{15A} - 10(I_1 - I_2) = 0 \\ -10(I_2 - I_1) - 20I_2 = 0 \\ I_1 = 15A \end{cases}$$

By solving the equations, we have

$$\begin{cases} I_1 = 15A \\ I_2 = 5A \end{cases}$$

$$i = I_1 - I_2 = 10A, v_a = v_1 - 5i = 50V.$$

Since $v_b = 0V$ then,


$$v_{ab} = v_1 - 5i - 0 = 50V$$

Next, we find the Thevenin equivalent resistor.

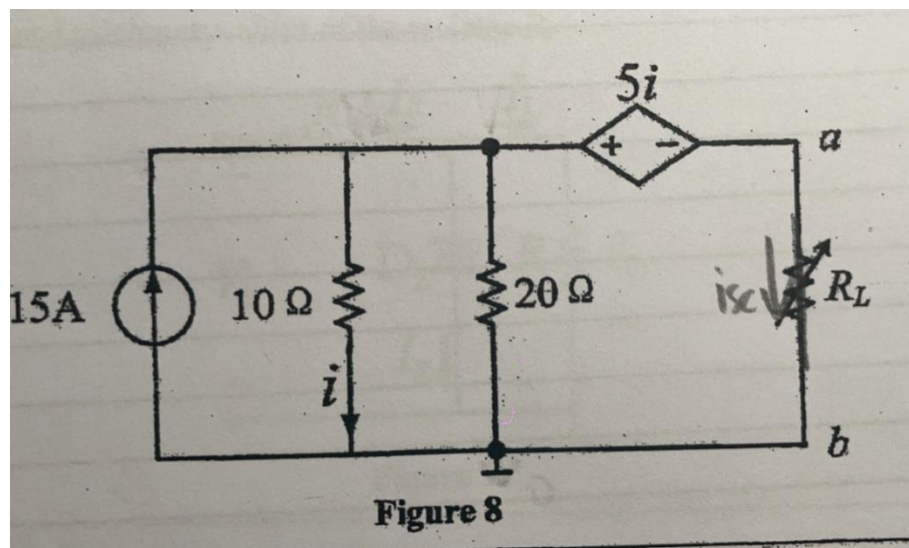Part 2: 求解戴维南电阻 R_{Th}


使用短路电流法求解。

By the method of short-circuit current, we have the circuit:



(这里只给了节点电压法，网孔电流就不再赘述了~)

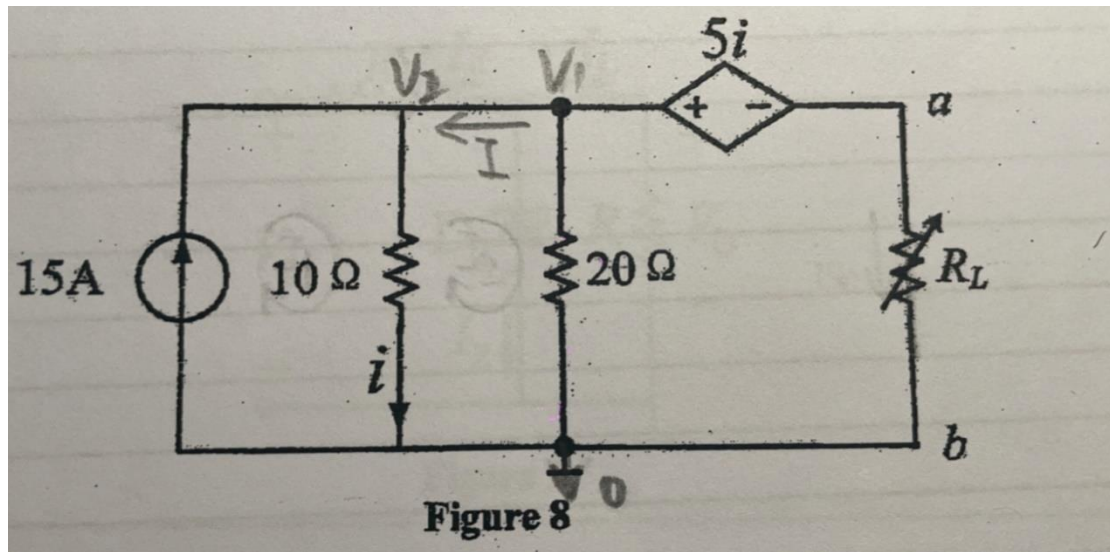By node-voltage method, we set the reference point and the node point as the picture below:



And we have the equations:

$$\begin{cases} \frac{v_1}{20} + I + i_{sc} = 0 \\ \frac{v_2}{10} - I - 15 = 0 \end{cases}$$

Since $v_1 = v_2$, $i = \frac{v_2}{10}$, we have


$$\frac{v_1}{20} + \frac{v_1}{10} - 15 + i_{sc} = 0$$

Since $v_a = v_b = 0V$, then $v_1 = 5i = \frac{v_1}{2}$

Then, $v_1 = 0V$, $i = 0A$.

$$i_{sc} = 15A$$

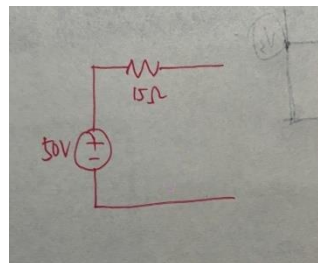Then $R_{TH} = \frac{V_{th}}{i_{sc}} = \frac{50V}{15A} = \frac{10}{3}\Omega$



We find the Thevenin equivalent circuit.


When $R_L = R_{TH} = \frac{10}{3}\Omega$, the resistor will absorb the maximum power, and the

power is $P_{max} = \frac{(V_{Th})^2}{4R_L} = 187.5W$ Finish.

EEF 部分

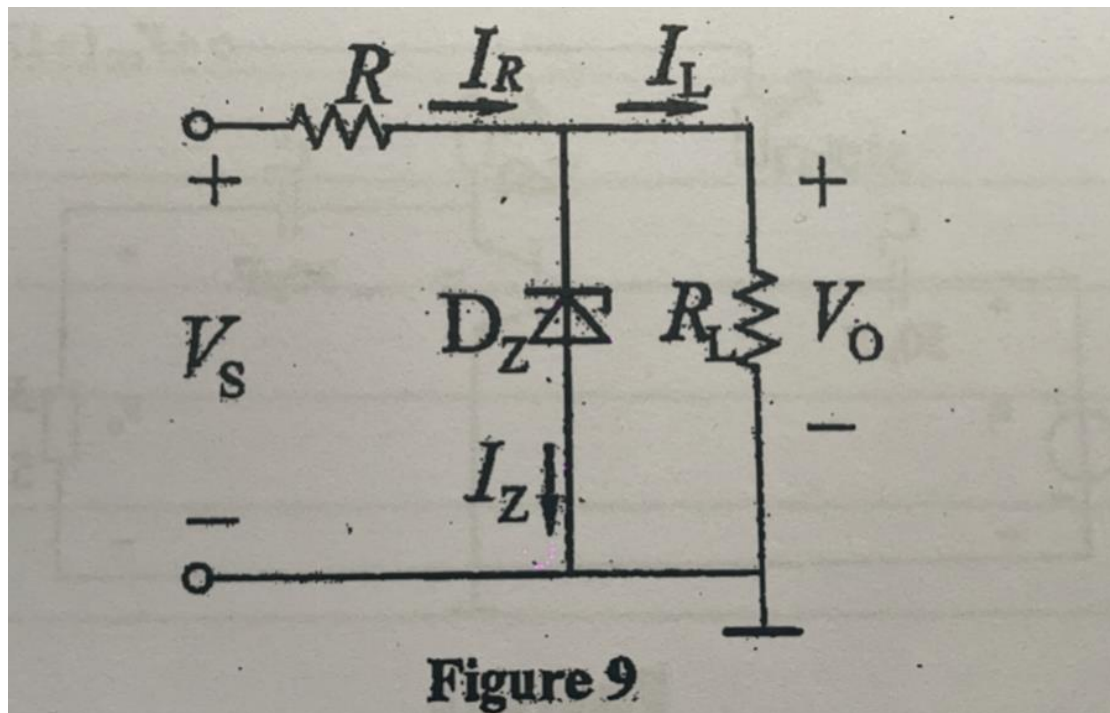Question 9 (10 Marks)——For Classes 17-22 Only:

In the circuit shown in Figure 9, $V_s = 11V$, $R_L = 800\Omega$. For the Zener diode D_Z , the regulation voltage $V_Z = 8V$, the maximum regulation current $I_{Zmax} = 25mA$, and the minimum regulation current $I_{Zmin} = 5mA$. Determine the maximum and minimum values of the resistor R .



【考点 Point】

二极管求限制电阻的范围 Find the range of a restrict resistor in a circuit with Semiconductor.

Answer: *Max*: 200Ω , *Min*: 85.71Ω .

【解析 Analysis】

模电二极管稳压电路考点。先求负载电阻上的电流，然后求限流电阻上的电压，根据限流电阻上最大和最小电流的取值，分别求得电阻的最小值和最大值。

Solution:

$$V_0 = V_Z = 8V$$

The current on the load resistor R_L is: $I_L = \frac{V_0}{R_L} = \frac{8V}{800\Omega} = 10mA$

The voltage of the resistor R is $V_R = V_S - V_0 = 3V$.

The maximum of the current passing the resistor R is:

$$I_{Rmax} = I_L + I_{Zmax} = 10mA + 25mA = 35mA$$

The minimum of the current passing the resistor R is:

$$I_{Rmin} = I_L + I_{Zmin} = 10mA + 5mA = 15mA$$

The maximum of the resistor R is:

$$R_{max} = \frac{V_R}{I_{Rmin}} = \frac{3V}{15mA} = 200\Omega$$

The minimum of the resistor R is:

$$R_{min} = \frac{V_R}{I_{Rmax}} = \frac{3V}{35mA} = 85.71\Omega$$


Finish.

Question 10 (16 Marks)——For Classes 17-22 Only:

The common-emitter BJT circuit is shown in Figure 10.

(1) Assume $\beta = 120$ and $V_{BEQ} = 0.8V$, analyze the Q-point, including I_{BQ} , V_{CEQ} , I_{CQ} ;

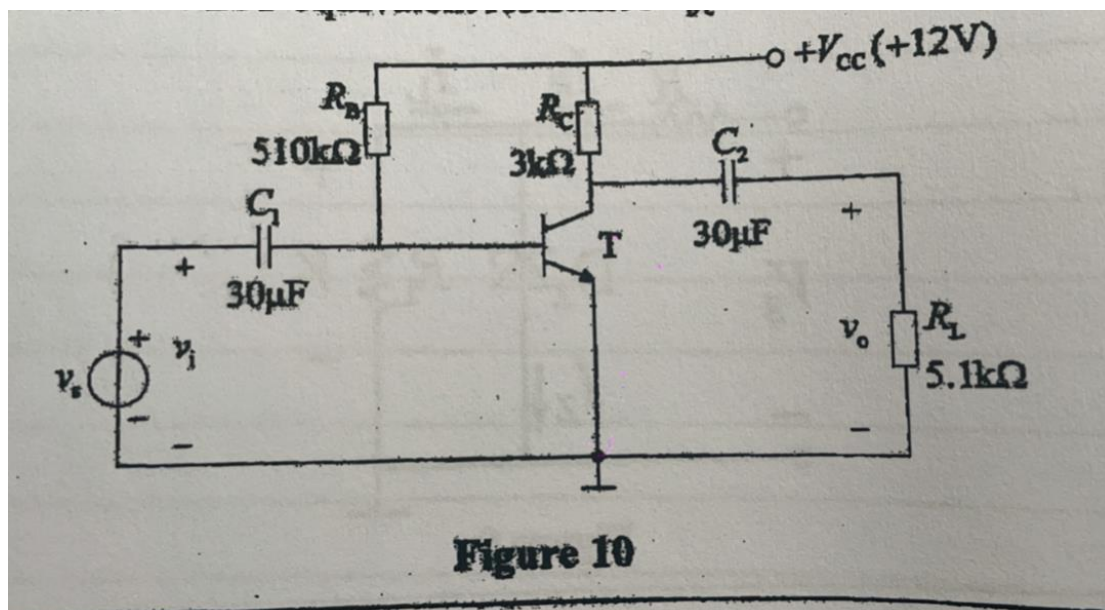(2) Assume $r_{bb'} = 0$ and $r_{ce} = \infty$, draw its small-signal hybrid- π equivalent circuit and calculate the BJT equivalent resistance $r_{b'e}$ and voltage gain A_v . ($V_T = 26mV$) 原题目有误!!



【考点 Point】

三极管（双极型晶体管）电路 BJT circuit

静态工作点分析 Analysis of quiet point Q

混合派模型电路 hybrid- π model circuit


交流动态分析 Dynamic analysis

Answer:

$$(1) I_{BQ} = 22.0\mu\text{A}, I_{CQ} = 2.64\text{mA}, V_{CEQ} = 4.08\text{V}$$

$$(2) r_{bre} \approx 1.18(\text{k}\Omega), A_v \approx -192.2$$

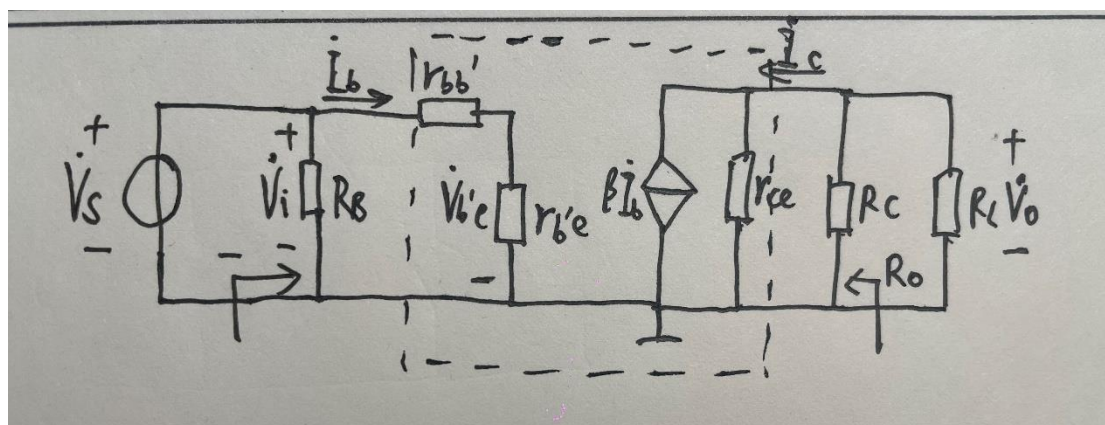Small-signal hybrid- π equivalent circuit:



【解析 Analysis】

模电三极管混合派模型考点。第一问考察静态工作点得情况，根据已知条件和相关公式即可求解这三个量。第二问为交流电路小信号的动态分析。并画出混合派模型的电路图。根据公式可求相关交流分析量。混合派模型电路图只需根据记忆画出即可。

Solution:

(1)


$$I_{BQ} = \frac{V_{CC} - V_{BEQ}}{R_B} = \frac{12V - 0.8V}{510k\Omega} = 22.0\mu A$$

$$I_{CQ} = \beta I_{BQ} = 2.64mA$$

$$V_{CEQ} = V_{CC} - I_{CQ}R_C = 12V - 2.64mA \times 3k\Omega = 4.08V$$

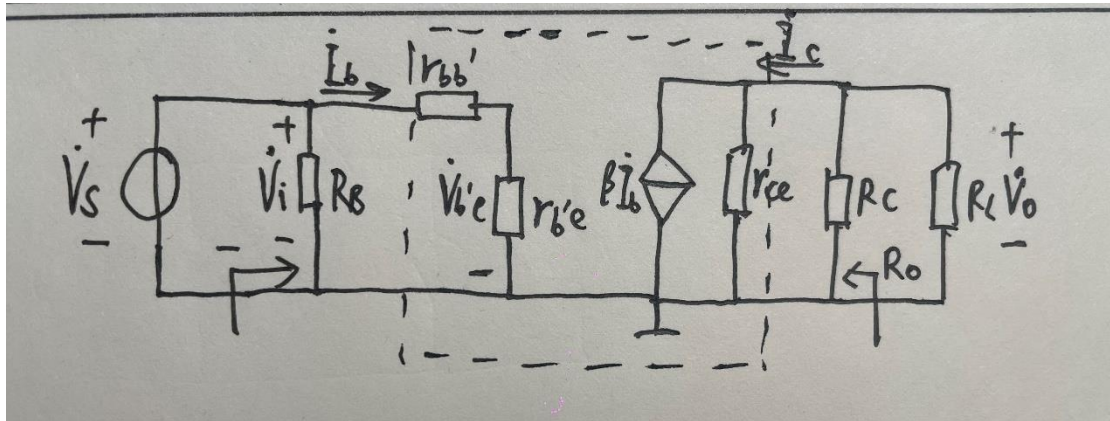(2)

The small-signal hybrid- π equivalent circuit is:



Then, the BJT equivalent resistance r_{be} is:

$$r_{be} = \frac{V_T}{I_{BQ}} = \frac{26mV}{22.0 \times 10^{-3}mA} \approx 1.18(k\Omega)$$

Next, we find the voltage gain.

$$r_{be} = r_{bb'} + r_{b'e} = r_{bb'} + \frac{V_T}{I_{BQ}} = 0 + \frac{V_T}{I_{BQ}} \approx 1.18(k\Omega)$$

Total resistor load is:

$$R'_L = r_{ce} || R_c || R_L = 1.89(k\Omega)$$

The voltage gain A_v is:

$$A_v = \frac{V_o}{V_i} = -\frac{\beta R'_L}{r_{be}} \approx -192.2$$

Finish.

考点分析

具体考点：

- 1、 网孔电流法
- 2、 节点电压法
- 3、 戴维南等效电路
- 4、 运算放大器
- 5、 自然响应
- 6、 正弦稳态电路
- 7、 叠加法+正弦稳态
- 8、 最大功率传输
- 9、 二极管 稳压电路 求限流电阻范围
- 10、 三极管 静态工作点分析+动态交流小信号相关物理量计算