

Chapter 7

Power Amplifiers

7.1 Introduction

-- Definitions and Amplifier Types

In small-signal amplifiers, the main factors are:

- *Amplification*
- *Linearity*
- *Gain*

Since large-signal, or power, amplifiers handle relatively large voltage signals and current levels, the main factors are:

- *Efficiency*
- *Maximum power capability*
- *Impedance matching to the output device*

7.1 Introduction



-- Power Amplifier Index

- *The power is sufficiently **large**.*
- *The efficiency is very **high**.*
- *Output signal is **not distorted**.*
- *The power amplifier has **powerful load capacity**.*
- ***Safety** precautions should be done very well.*

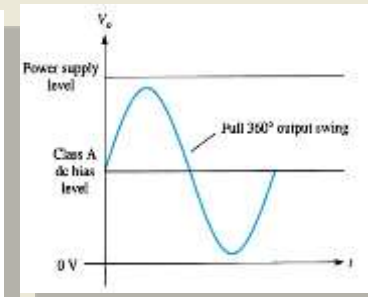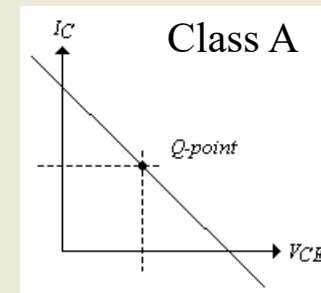7.1 Introduction -- Power Amplifier Types



Class A

The amplifier conducts through the full 360° of the input. The Q-point is set near the middle of the load line.




Class B

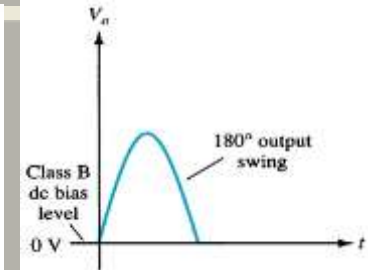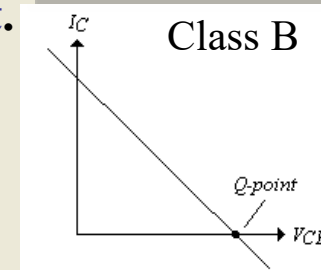The amplifier conducts through 180° of the input. The Q-point is set at the cutoff point.




Class AB

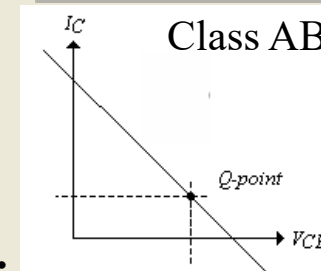This is a compromise between the class A and B amplifiers. The amplifier conducts somewhere between 180° and 360° . The Q-point is located between the mid-point and cutoff.



Class C

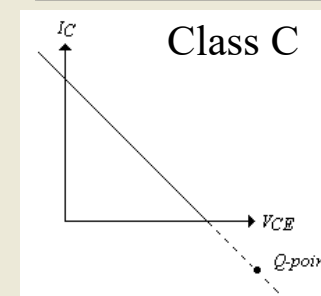The amplifier conducts less than 180° of the input. The Q-point is located below the cutoff level.




Class D

This is an amplifier that is biased especially for digital signals.

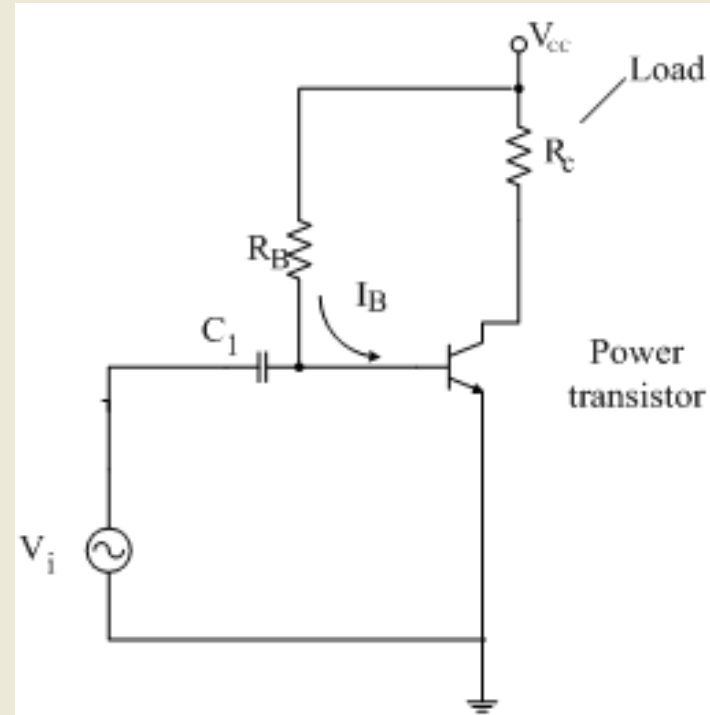7.2 Class A Amplifier

- The transistor used is a high-power transistor.
- It will handle higher voltages.
- The analysis is similar to the small-signal amplifier.



DC Operation: Class A Amplifier

The DC bias is set by V_{CC} and R_B , the base current is

$$I_B = \frac{V_{CC} - 0.7V}{R_B}$$

The collector current is

$$I_C = \beta I_B$$


The collector-emitter voltage is

$$V_{CE} = V_{CC} - I_C R_C$$

AC Operation: Class A Amplifier

A small input signal causes the output voltage to swing to a maximum of V_{cc} and a minimum of 0V.

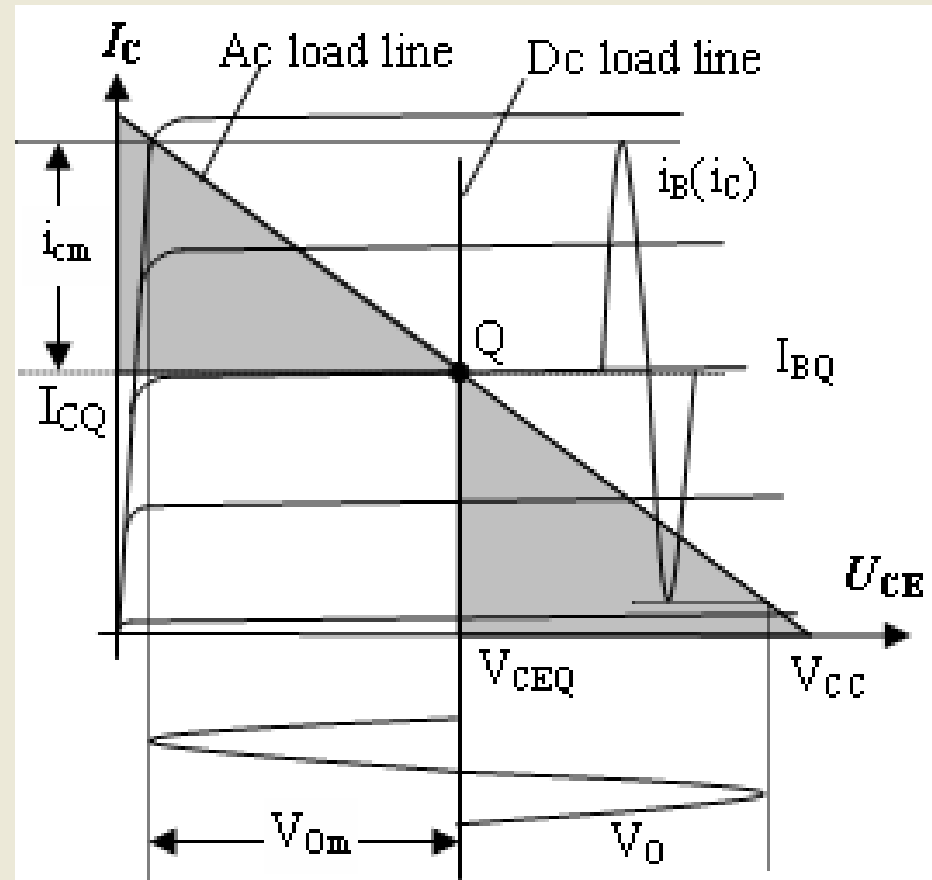The current can also swing from 0mA to I_{CSAT} (V_{cc}/R_C).



Class A Amplifier

Input Power

The power into the amplifier is from the DC supply. Without input signal, the DC current drawn is the collector bias current I_{CQ} .

$$P_i(dc) = V_{CC}I_{CQ}$$

Output Power

$$(rms\ mode) \quad P_o(ac) = V_{CE}(rms)I_C(rms), P_o(ac) = I_C^2(rms)R_C, P_o(ac) = \frac{V_{CE}^2(rms)}{R_C}$$

$$(p\ mode) \quad P_o(ac) = \frac{V_{CE}(p)I_C(p)}{2}, P_o(ac) = \frac{I_C^2(p)}{2}R_C, P_o(ac) = \frac{V_{CE}^2(p)}{2R_C}$$

$$(p-p\ mode) \quad P_o(ac) = \frac{V_{CE}(p-p)I_C(p-p)}{8}, P_o(ac) = \frac{I_C^2(p-p)}{8}R_C, P_o(ac) = \frac{V_{CE}^2(p-p)}{8R_C}$$

Efficiency

$$\eta\% = \frac{P_o(ac)}{P_i(dc)} \times 100\%$$

Class A Amplifier

Maximum Efficiency


$$P_o(ac) = \frac{V_{CC} (V_{CC} / R_C)}{8} = \frac{V_{CC}^2}{8R_C}$$

(*p-p mode*: maximum p-p current is V_{CC}/R_C)

$$P_i(dc) = V_{CC} \frac{(V_{CC} / R_C)}{2} = \frac{V_{CC}^2}{2R_C}$$

(dc bias current I_{CQ} equals to one-half maximum current value V_{CC}/R_C)

$$\eta\% = \frac{\max P_o(ac)}{\max P_i(dc)} = \frac{V_{CC}^2 / 8R_C}{V_{CC}^2 / 2R_C} 100\% = 25\%$$

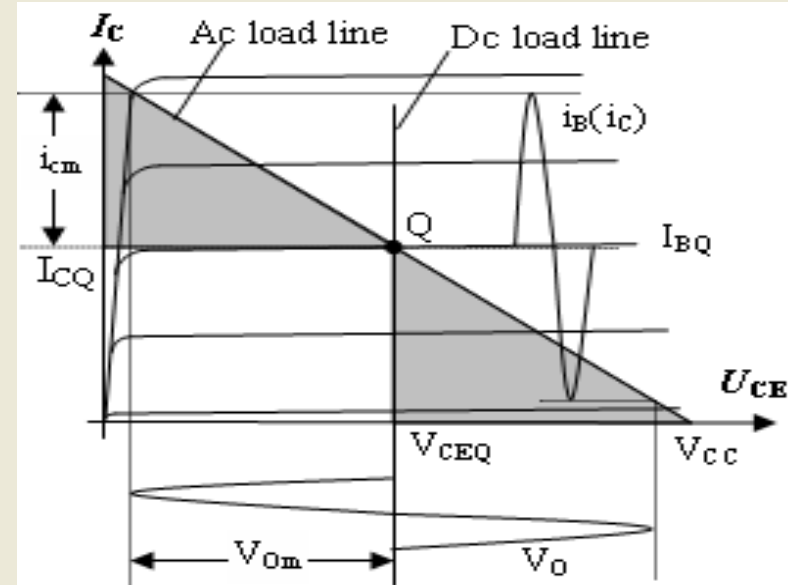

Example 7.1

Calculate the input power, output power and efficiency of Fig. 7.1 for an input of the base signal is 10mA peak.


Solution:

First, we must determine the Q-point:

$$I_{BQ} = \frac{V_{CC} - 0.7V}{R_B} = \frac{20 - 0.7V}{1k\Omega} = 19.3mA$$

$$I_{CQ} = \beta I_B = 25(19.3mA) = 0.48A$$

$$V_{CEQ} = V_{CC} - I_C R_C = 20V - (0.48A)(20\Omega) = 10.4V$$

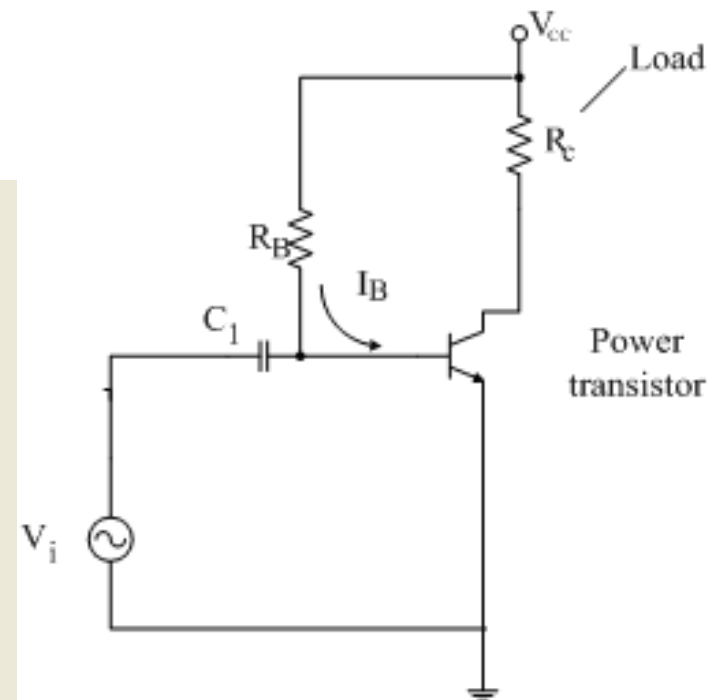

Example 7.1

When the input ac base current increases from its dc bias level, the collector current rises by

$$I_C(p) = \beta I_B(p) = 25(10mA) = 250mA(peak) ,$$

Then the ac power is

$$P_o(ac) = \frac{I_C^2(p)}{2} R_C = \frac{(250 \times 10^{-3})^2}{2} (20\Omega) = 0.625W , \quad (p \text{ mode})$$

The dc power is

$$P_i(dc) = V_{CC} I_{CQ} = (20V)(0.48A) = 9.6W ,$$

The amplifier's power efficiency is

$$\eta\% = \frac{P_o(ac)}{P_i(dc)} \times 100\% = \frac{0.625W}{9.6W} = 6.5\%$$


7.3 Class B Amplifier

In class B, the dc bias leaves the transistor biased just off. The AC signal turns the transistor on. This is essentially no bias.

The transistor only conducts when it is turned on by one-half of the AC cycle.

In order to get a full AC cycle out of a class B amplifier, you need two transistors:

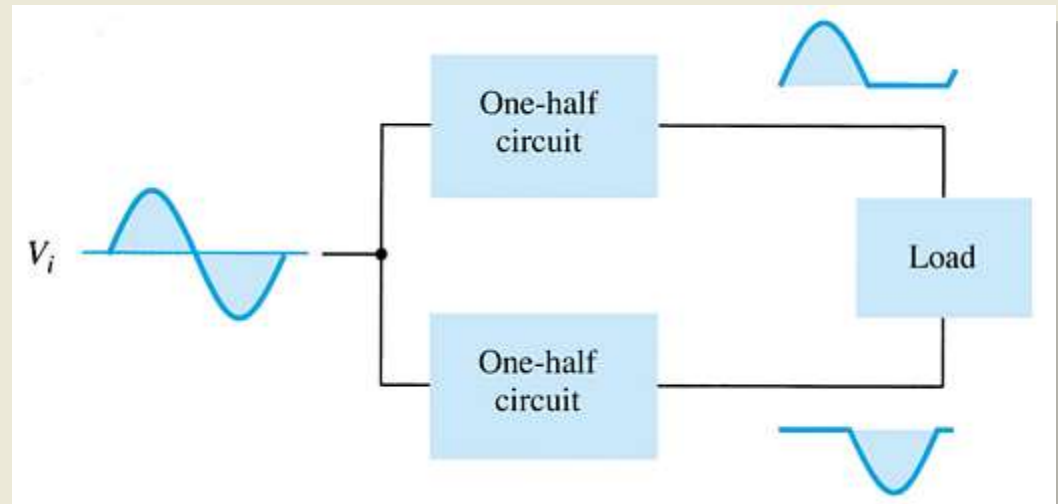- *One transistor provides the negative half of the AC cycle;*
- *One transistor provides the positive half of the AC cycle;*
- ***Push-Pull Circuits.***



Class B Amplifier: Input Power

- I_{dc} is the *average or dc current* drawn from the power supplies.
- I_{dc} has the form of a full-wave rectified signal or half-wave rectified signal, can be expressed as

$$I_{dc} = \frac{1}{\pi} \int_0^{\pi} I(p) \sin t dt = \frac{2}{\pi} I(p)$$

- $I(p)$ is the peak value of the output current waveform. The input power can be expressed as

$$P_i(dc) = V_{cc} \left(\frac{2}{\pi} I(p) \right)$$

Class B Amplifier: Output Power

- The output power can be calculated as:

$$P_o(ac) = \frac{V_L^2(p-p)}{8R_L} = \frac{V_L^2(p)}{2R_L}$$

$$\eta\% = \frac{P_o(ac)}{P_i(dc)} \times 100\% = \frac{V_L^2(p)/2R_L}{V_{cc}[(2/\pi)I(p)]} = \frac{\pi}{4} \frac{V_L}{V_{cc}} \times 100\%$$

For maximum output power, $V_L(p) = V_{cc}$

$$\eta\% = \frac{\pi}{4} \frac{V_{cc}}{V_{cc}} \times 100\% = 78.54\%$$

The maximum efficiency of Class B is 78.54%.

Example 7.2

For a Class B amplifier providing a 10V peak signal to a 8Ω load and a supply of $V_{CC}=20V$, determine the input power, output power, and circuit efficiency.

Solution:

A 10V peak signal across a 8Ω load provides a peak load current of

$$I(p) = \frac{V_L(p)}{R_L} = \frac{10V}{8\Omega} = 1.25A$$

The dc value of the current drawn from the power supply is then

$$I_{dc} = \frac{2}{\pi} I(p) = \frac{2}{\pi} \times 1.25A = 0.796A$$

The input power delivered by the supply voltage is

$$P_i(dc) = V_{CC} I_{dc} = (20V)(0.796A) = 15.92W$$

The output power delivered to the load is

$$P_o(ac) = \frac{V_L^2(p)}{2R_L} = \frac{(10V)^2}{2(8\Omega)} = 6.25W$$

For a resulting efficiency of

$$\eta\% = \frac{P_o(ac)}{P_i(dc)} \times 100\% = \frac{6.25W}{15.92W} \times 100\% = 39.3\%$$

Class B: Power Dissipated by Transistors

$$P_{2Q}(ac) = P_i(dc) - P_o(ac), P_Q(ac) = P_{2Q}(ac) / 2$$

The maximum power dissipated by the transistors does not occur at the maximum power input or output condition.

$$\begin{aligned} P_{2Q}(ac) &= P_i(dc) - P_o(ac) \\ &= V_{CC} \frac{2}{\pi} I(p) - \frac{V_L^2(p)}{2R_L}, I(p) = \frac{V_L(p)}{R_L} \\ &= V_{CC} \frac{2}{\pi} \frac{V_L(p)}{R_L} - \frac{V_L^2(p)}{2R_L} \end{aligned}$$

To get the maximum value, we can take the derivative of above equation:

$$\frac{\partial P_{2Q}(ac)}{\partial V_L(p)} = \frac{2}{\pi} \frac{V_{CC}}{R_L} - \frac{V_L(p)}{R_L} = 0$$

Class B: Maximum Dissipated Power

The voltage for the maximum power dissipated by transistors will be:


$$V_L(p) = \frac{2}{\pi} V_{CC}$$



$$P_{2Q}(ac) = P_i(dc) - P_o(ac)$$

$$= V_{CC} \frac{2}{\pi} I(p) - \frac{V_L^2(p)}{2R_L}, I(p) = \frac{V_L(p)}{R_L}$$
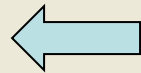
$$\max P_{2Q} = \frac{2V_{CC}^2}{\pi^2 R_L}$$




$$= V_{CC} \frac{2}{\pi} \frac{V_L(p)}{R_L} - \frac{V_L^2(p)}{2R_L}$$

$$\eta\% = \frac{P_o(ac)}{P_i(dc)} \times 100\% = \frac{V_L^2(p)/2R_L}{V_{CC} [(2/\pi)I(p)]} = \frac{\pi}{4} \frac{V_L}{V_{CC}} \times 100\%$$

$$\eta\% = \frac{P_o(ac)}{P_i(dc)} \times 100\% = \frac{\pi}{4} \frac{V_L}{V_{CC}} \times 100\% = \frac{\pi}{4} \frac{2}{\pi} \times 100\% = 50\%$$

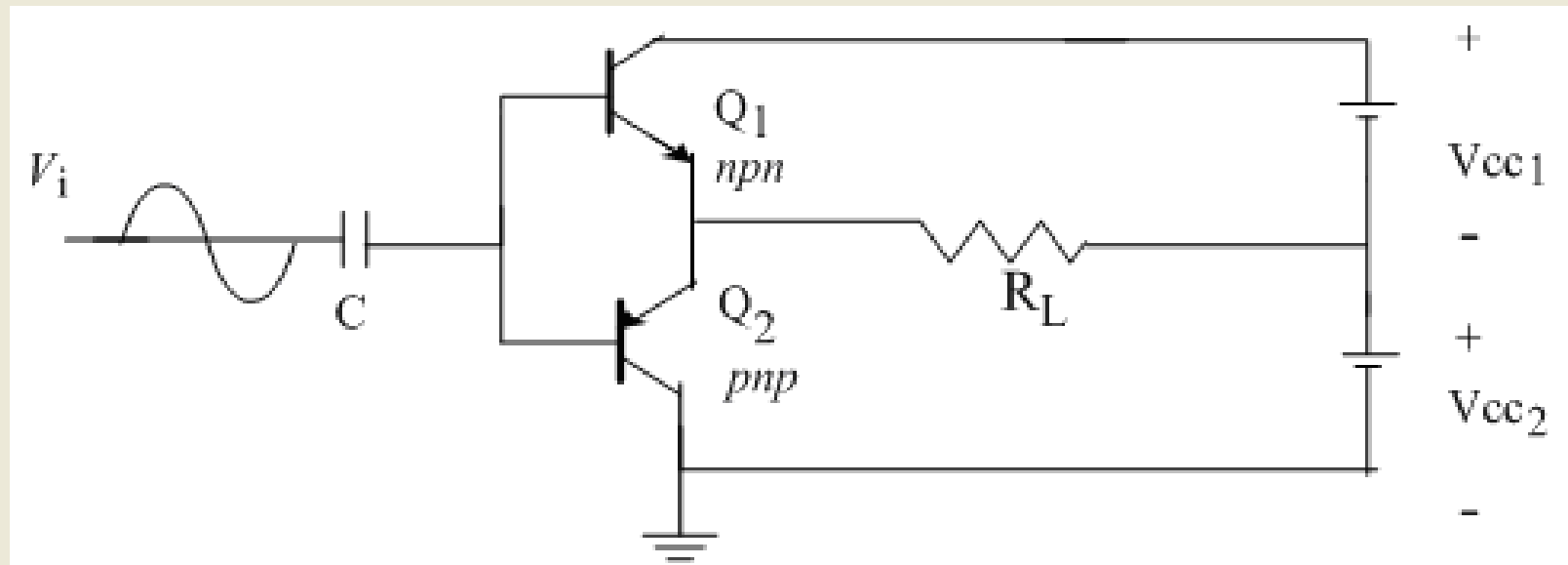
7.4 Push-Pull Class B Amplifier Circuit

Complementary BJT circuit (npn and pnp transistors)




7.4 Push-Pull Class B Amplifier Circuit

The positive half cycle:

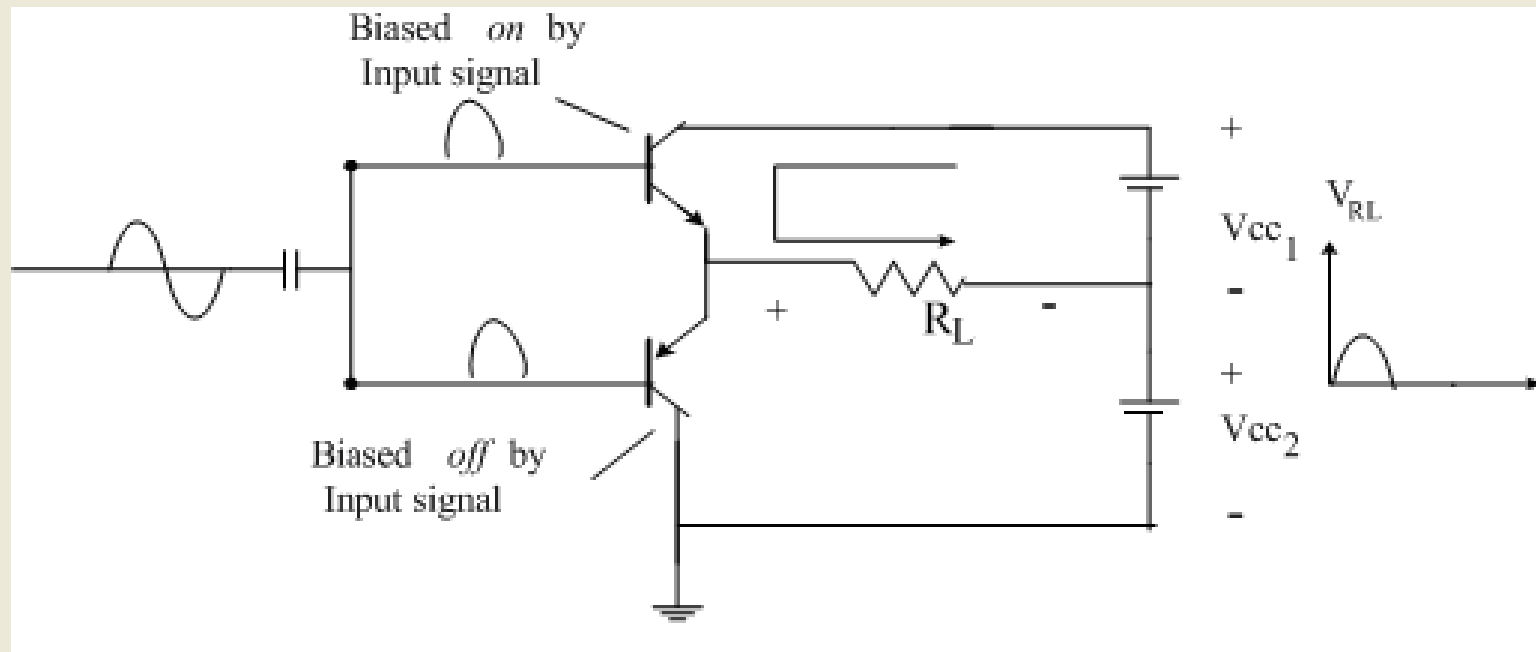

7.4 Push-Pull Class B Amplifier Circuit

The negative half cycle:

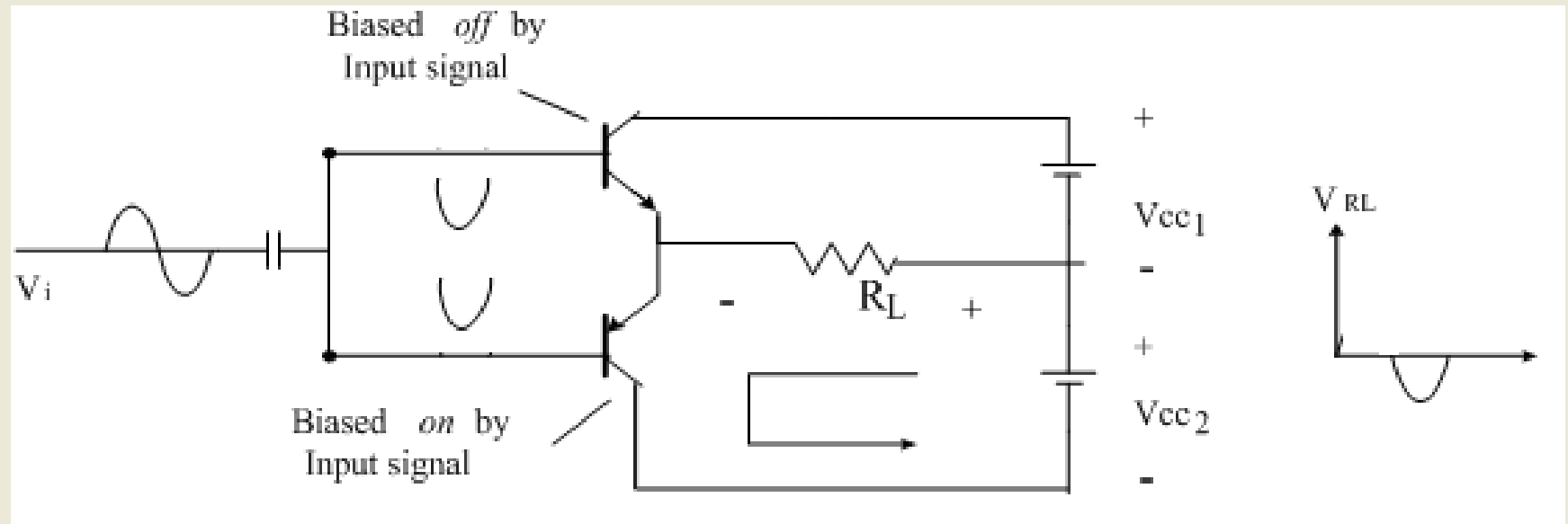


7.4 Push-Pull Class B Amplifier Circuit

There are two disadvantages:

- One is the need for two separated voltage supplies.
- The other is the crossover distortion.

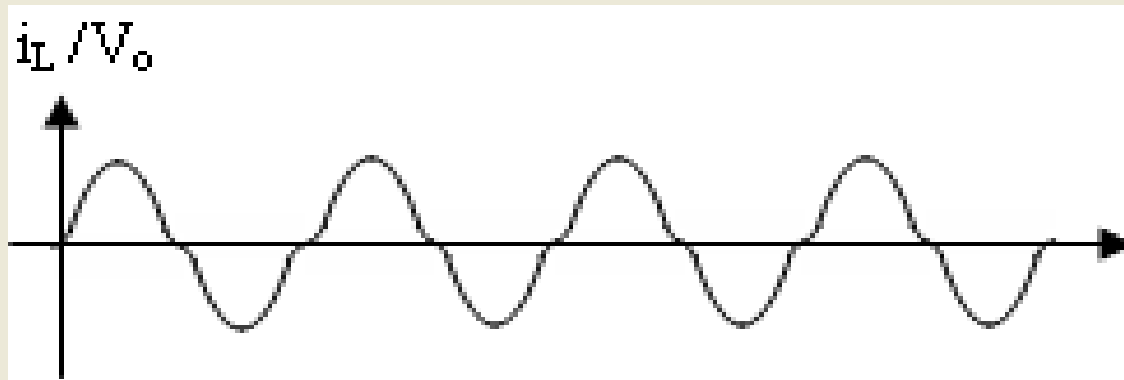Crossover Distortion: During the signal crossover from positive to negative (or vice versa), there is nonlinearity in the output.



Reason:


The amplifier does not provide exact switching of one transistor off and the other on at the zero voltage condition.

Solution:

Biasing the transistors in class AB improves this operation by biasing both transistors to be on for more than half a cycle.

Example 7.4

For the Fig.7.6, calculate the input power, output power, power dissipated by each output transistor and circuit efficiency for an input of 12V rms.

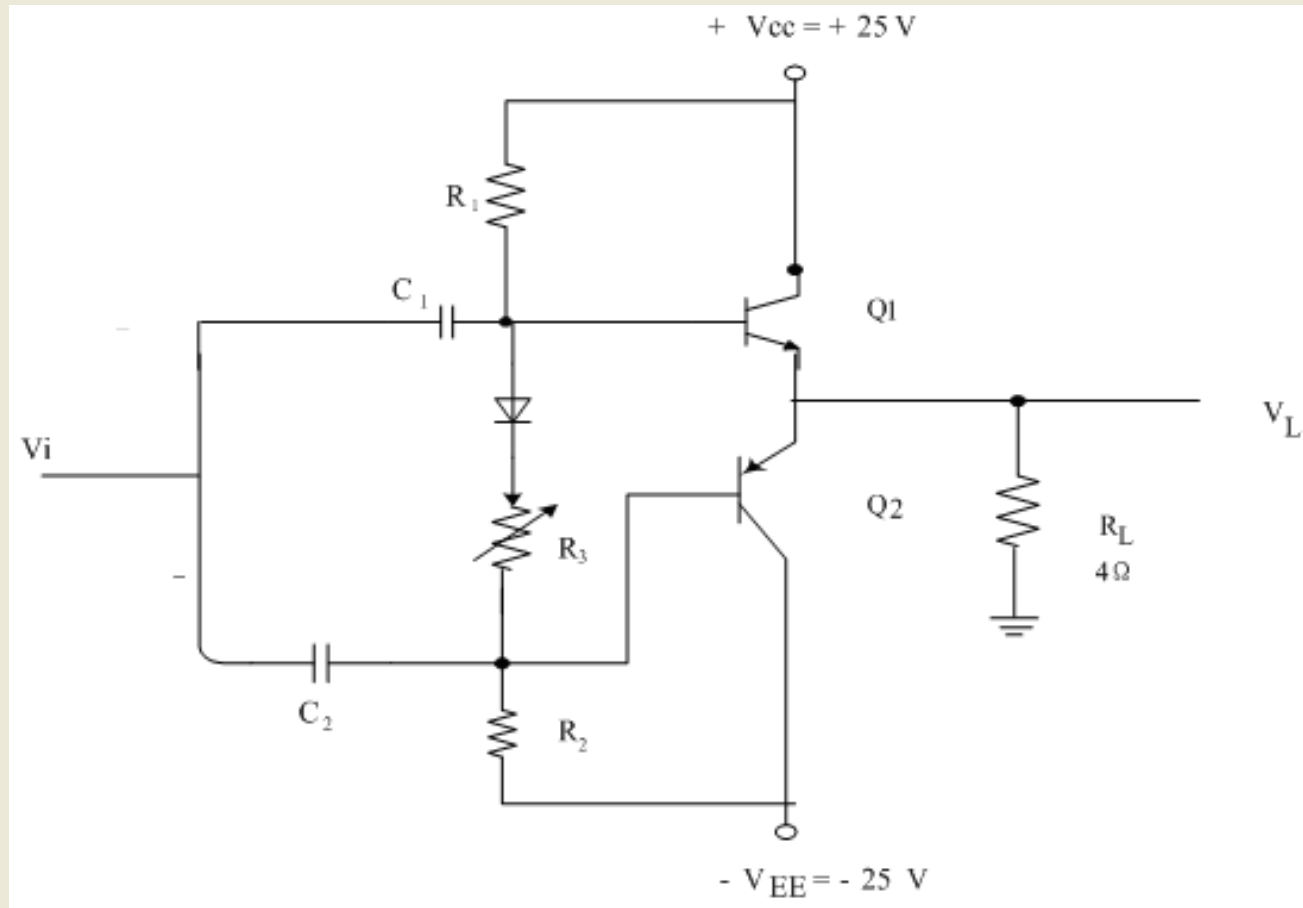

Example 7.4

Solution:

Ideally, the power amplifier has a voltage gain of unity, the peak input and output voltage is

$$V_L(p) = V_i(p) = \sqrt{2}V_i = \sqrt{2}(12V) \approx 17V$$

The output across the load is

$$P_o(ac) = \frac{V_L^2}{2R_L} = \frac{(17V)^2}{2(4\Omega)} = 36.125W$$

The peak load current is

$$I_L(p) = \frac{V_L(p)}{R_L} = \frac{17V}{4\Omega} = 4.25A$$

Example 7.4

The dc current from the supplies is

$$I_{dc} = \frac{2}{\pi} I_L(p) = \frac{2}{\pi} (4.25A) = 2.71A$$

The power supplies to the circuit is

$$P_i(dc) = V_{CC} I_{dc} = (25V)(2.71A) = 67.75W$$

The power dissipated by each output transistor is

$$P_Q = \frac{P_{2Q}}{2} = \frac{P_i - P_o}{2} = \frac{67.75 - 36.125}{2} W = 15.8W$$

The circuit efficiency is

$$\eta\% = \frac{P_o(ac)}{P_i(dc)} \times 100\% = \frac{36.125W}{67.75W} \times 100\% = 53.3\%$$

7.5 Summary

1. Amplifier classes:

Class A : the output signal varies for a full 360° of the cycle.

Class B: the output varying over one-half the input signal cycle or 180° of signal.

Class AB: the output signal swing occurs between 180° and 360°

Class C: the output conducts for less than 180°

Class D: has operation using pulse/digital signal

2. Amplifier efficiency:

Class A: maximum efficiency of 25%(without transformer) and 50%(transformer)

Class B: maximum efficiency of 78.5%

3. Power considerations:

Input power: provided by the dc power supply

Output power: delivered to the load

Dissipated power: the difference between input and output powers.