


# **Chapter 8**

## **Operational Amplifiers and Comparators**


# 8.1 Construction and Basic Features of Operational Amplifiers
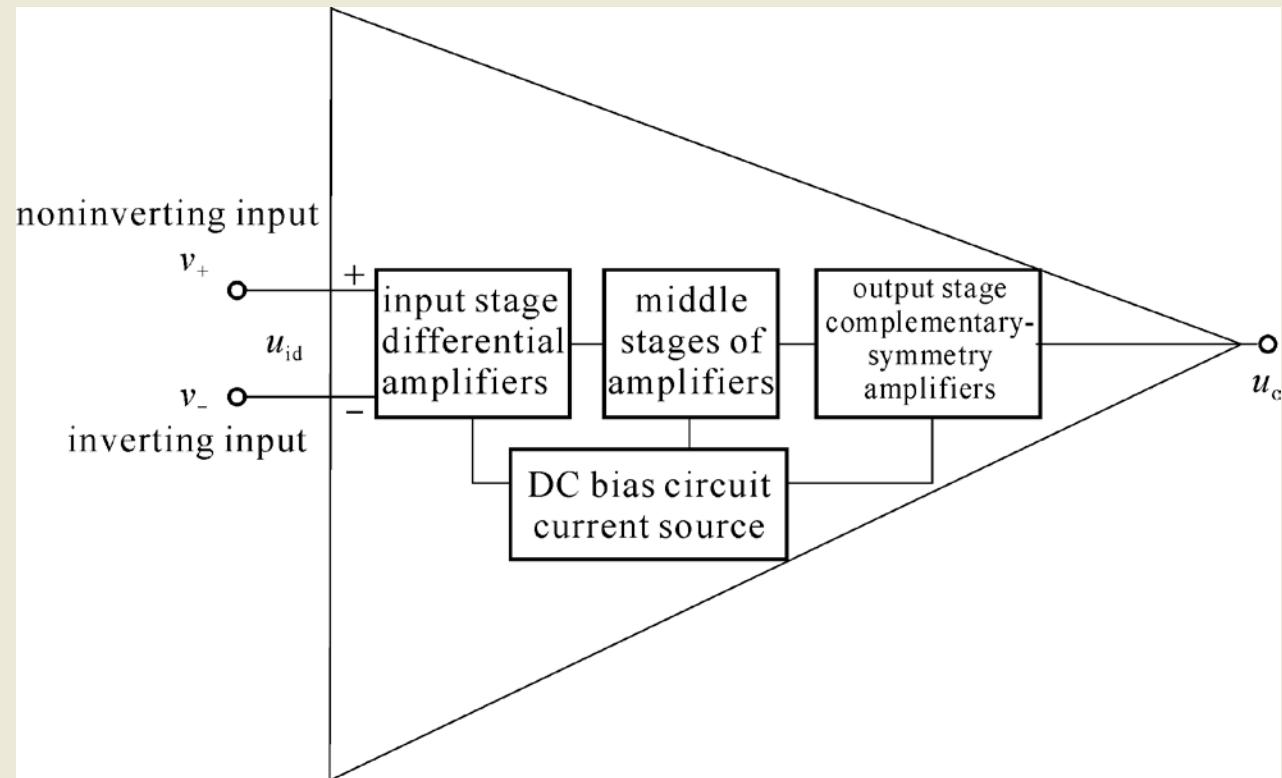
## Construction of the op-amp:


- *Input stage*
- *Middle stage*
- *Output stage*
- *DC bias*



## Symbol of the op-amp:

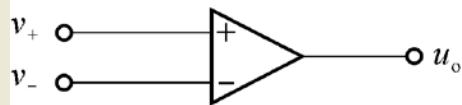

(a) the international symbol

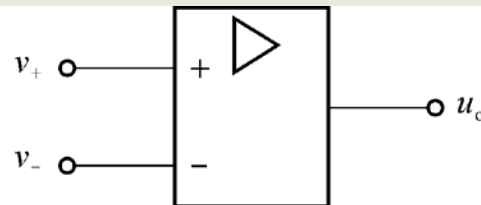

(b) the Chinese domestic symbol


*Note that the Op-amp has two inputs and one output.*

## 8.2 Characteristics and Analyses on Ideal Operational Amplifiers

### Characteristics of ideal op-amps:

- Infinite gain for the differential signal:  $A_{ud} = \infty, A_{uc}=0$
- Infinite Common Mode Rejection Ratio:  $K_{CMRR} = \infty$
- Infinite input resistance:  $R_i = \infty$
- Zero output resistance:  $R_o = 0$
- Infinite bandwidth

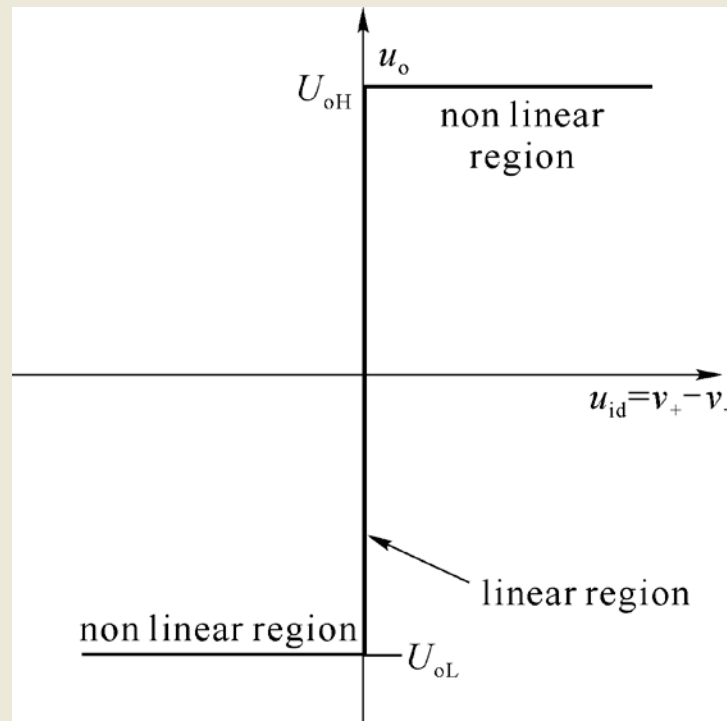
### Transfer characteristics of ideal op-amps:



In the linear region, “*virtue short*” and “*virtue open*” are features for ideal op-amps


$$u_{id} = \frac{u_o}{A_{ud}} \Rightarrow \text{virtual short: } u_{id}=0, \text{ or } u_+ = u_-$$
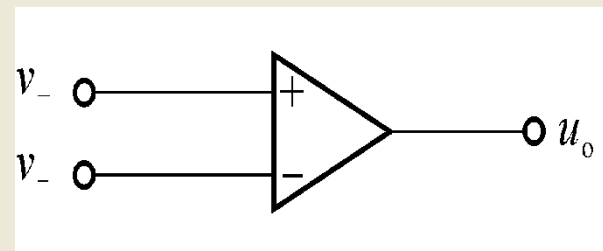
$$i_{id} = \frac{u_{id}}{R_i} \Rightarrow \text{virtual open: } i_{id}=0$$



## 8.3.1 Multiplication with a Constant

### (1) Inverting amplifiers

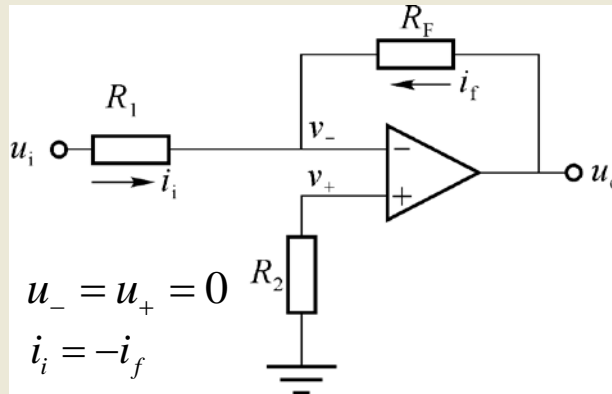

- The input signal is applied to the **inverting (-) input**.
- The **non-inverting input (+)** is grounded.
- The resistor  $R_F$  is the **feedback resistor**.

The *non-inverting input* pin is at ground. The *inverting input* pin is also at 0V for an AC signal due to **virtual short** concept. The *inverting input* is at **virtual ground**.

$$\frac{u_i}{R_1} = -\frac{u_o}{R_f} \quad u_o = -\frac{R_f}{R_1} u_i$$

$$A_{uf} = -\frac{R_f}{R_1}$$

$$R_{if} = R_1$$

$$R_{of} = 0$$


### (2) Non-inverting amplifiers

$$u_+ = u_i \quad u_- = \frac{R_1}{R_1 + R_f} u_o$$


$$u_+ = u_-$$

$$u_i = \frac{R_1}{R_1 + R_f} u_o$$
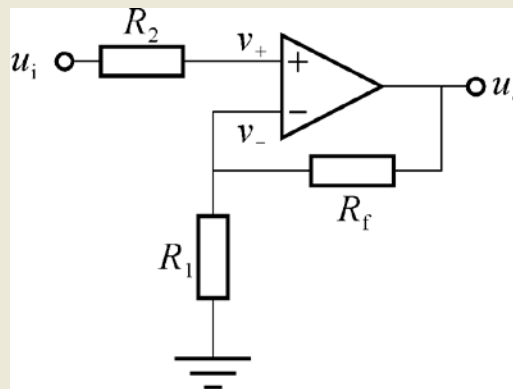
$$u_o = \left(1 + \frac{R_f}{R_1}\right) u_i \quad A_{uf} = 1 + \frac{R_f}{R_1}$$



(a) Noninverting amplifier

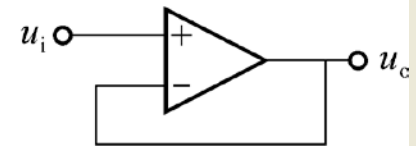


$$\text{If } R_f = 0, \quad u_o = u_i$$

(b) voltage follower

**For symmetric requirements:**  $(R_2 = R_1 \parallel R_f)$

## 8.3.2 Summing Amplifiers

### (1) Inverting Summing amplifiers

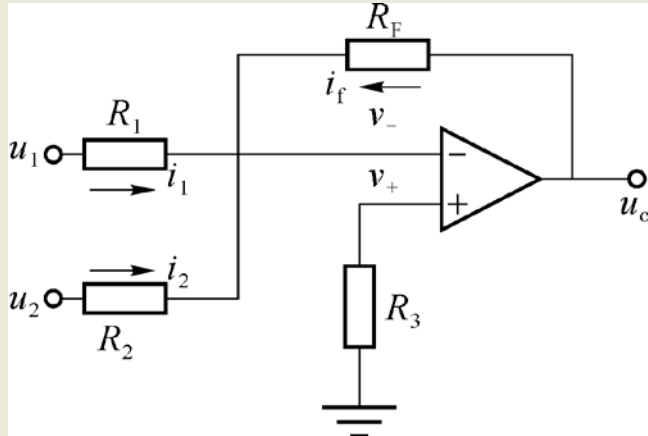

$$u_- = u_+ = 0$$


$$i_1 + i_2 = -i_f$$

$$\frac{u_1}{R_1} + \frac{u_2}{R_2} = -\frac{u_o}{R_f}$$

$$u_o = -\left(\frac{R_f}{R_1}u_1 + \frac{R_f}{R_2}u_2\right)$$

$$(R_3 = R_1 \parallel R_2 \parallel R_f)$$

### (2) Non-inverting Summing

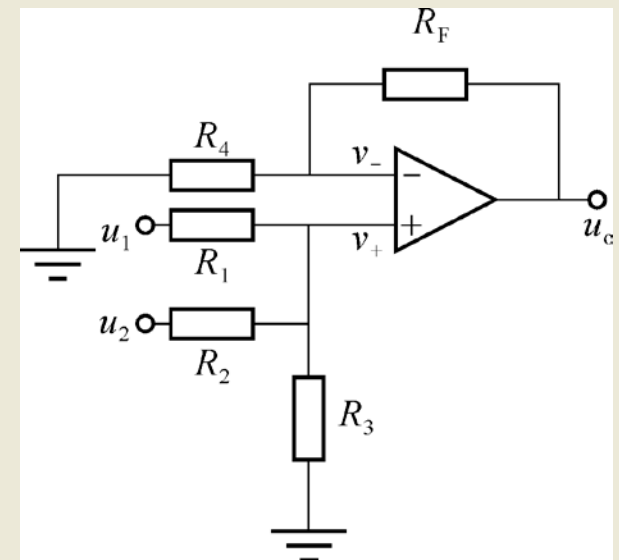

$$u_+ = u_-$$


$$u_+ = \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3}u_1 + \frac{R_1 \parallel R_3}{R_2 + R_1 \parallel R_3}u_2$$

$$u_- = \frac{R_4}{R_4 + R_f}u_o$$

$$\frac{R_4}{R_4 + R_f}u_o = \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3}u_1 + \frac{R_1 \parallel R_3}{R_2 + R_1 \parallel R_3}u_2$$

$$u_o = \left(1 + \frac{R_f}{R_4}\right) \left( \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3}u_1 + \frac{R_1 \parallel R_3}{R_2 + R_1 \parallel R_3}u_2 \right)$$

## 8.3.3 Subtraction Amplifiers

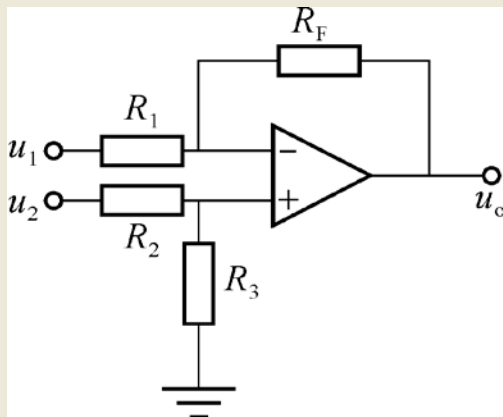


$$u_1 = 0 \quad u_{o2} = \left(1 + \frac{R_f}{R_1}\right) \left(\frac{R_3}{R_2 + R_3}\right) u_2$$

$$u_2 = 0 \quad u_{o1} = -\frac{R_f}{R_1} u_1$$

$$u_o = \left(1 + \frac{R_f}{R_1}\right) \left(\frac{R_3}{R_2 + R_3}\right) u_2 - \frac{R_f}{R_1} u_1$$

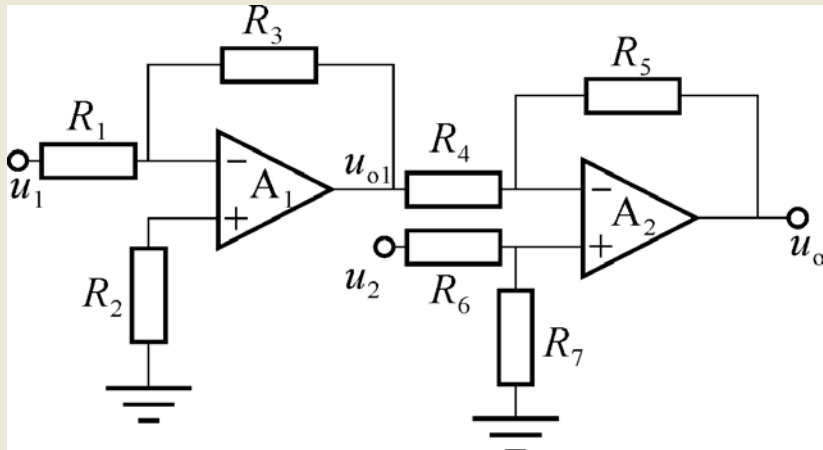**Example 8.1** ( $R_4 = R_5 = R_6 = R_7$ )



$$u_{o1} = -\frac{R_3}{R_1} u_1$$


$$u_o = \frac{R_4 + R_5}{R_4} \cdot \frac{R_7}{R_6 + R_7} u_2 - \frac{R_5}{R_4} u_{o1} = u_2 - u_{o1}$$

$$u_o = u_2 + \frac{R_3}{R_1} u_1$$

$$(R_2 = R_1 \parallel R_3)$$

## 8.3.4 Integrators

### (1) Inverting Integrators

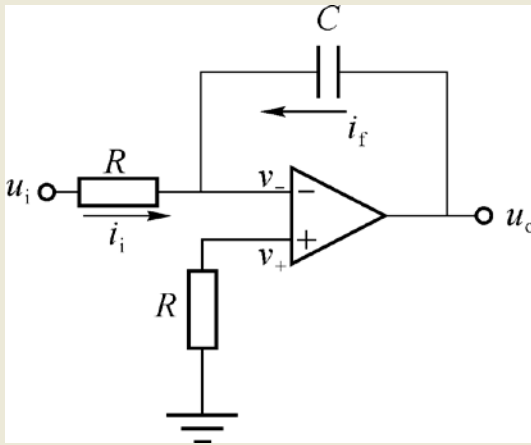


$$u_- = u_+ = 0$$

$$i_i = -i_f$$

$$\frac{u_i}{R} = -C \frac{du_o(t)}{dt}$$

$$u_o(t) = -\frac{1}{RC} \int_{t_0}^t u_i(t) dt + u_o(t_0)$$

### (2) Non-inverting Integrators

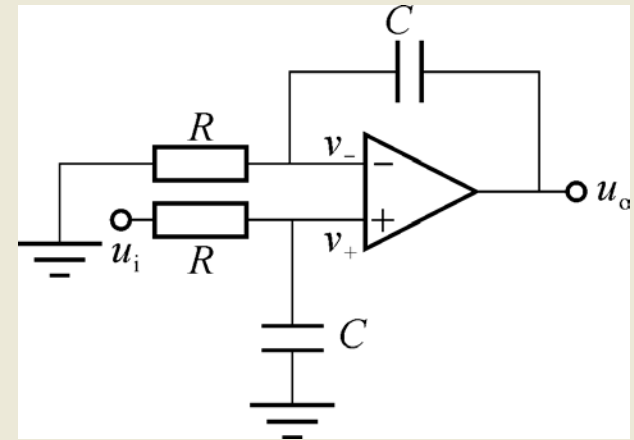

$$u_+(j\omega) = \frac{1}{j\omega C} \frac{1}{R + \frac{1}{j\omega C}} u_i(j\omega)$$


$$u_-(j\omega) = \frac{R}{R + \frac{1}{j\omega C}} u_o(j\omega)$$

$$u_+ = u_- \quad u_o(j\omega) = \frac{1}{j\omega CR} u_i(j\omega)$$

$$u_o(t) = \frac{1}{CR} \int_{t_0}^t u_i(t) dt + u_o(t_0)$$

## 8.3.5 Differentiators

### (1) Inverting Differentiators

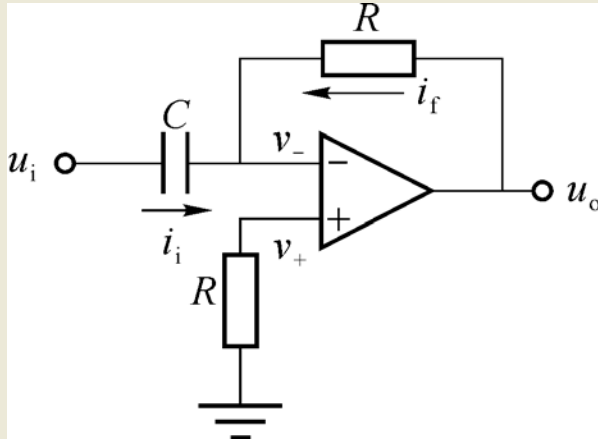


$$u_- = u_+ = 0$$

$$i_f = -i_i$$

$$\frac{u_o}{R} = -C \frac{du_i(t)}{dt}$$

$$u_o(t) = -RC \frac{du_i(t)}{dt}$$

### (2) Non-inverting Differentiators

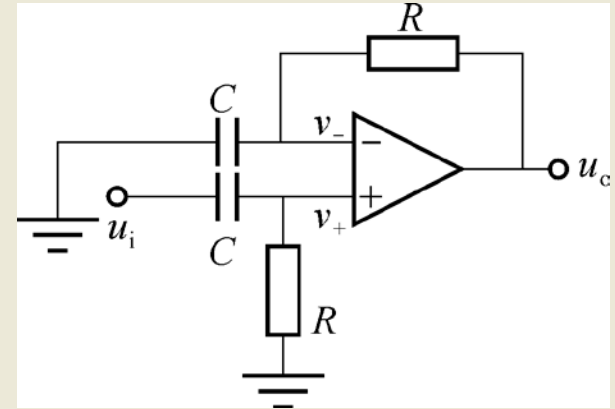

$$u_-(j\omega) = \frac{1}{R + \frac{1}{j\omega C}} u_o(j\omega)$$

$$u_+(j\omega) = \frac{R}{R + \frac{1}{j\omega C}} u_i(j\omega)$$


$$u_+ = u_- \quad u_o(j\omega) = j\omega CR \cdot u_i(j\omega)$$

$$u_o(t) = RC \frac{du_i(t)}{dt}$$



## Example 8.2:

Sketch the output waveform

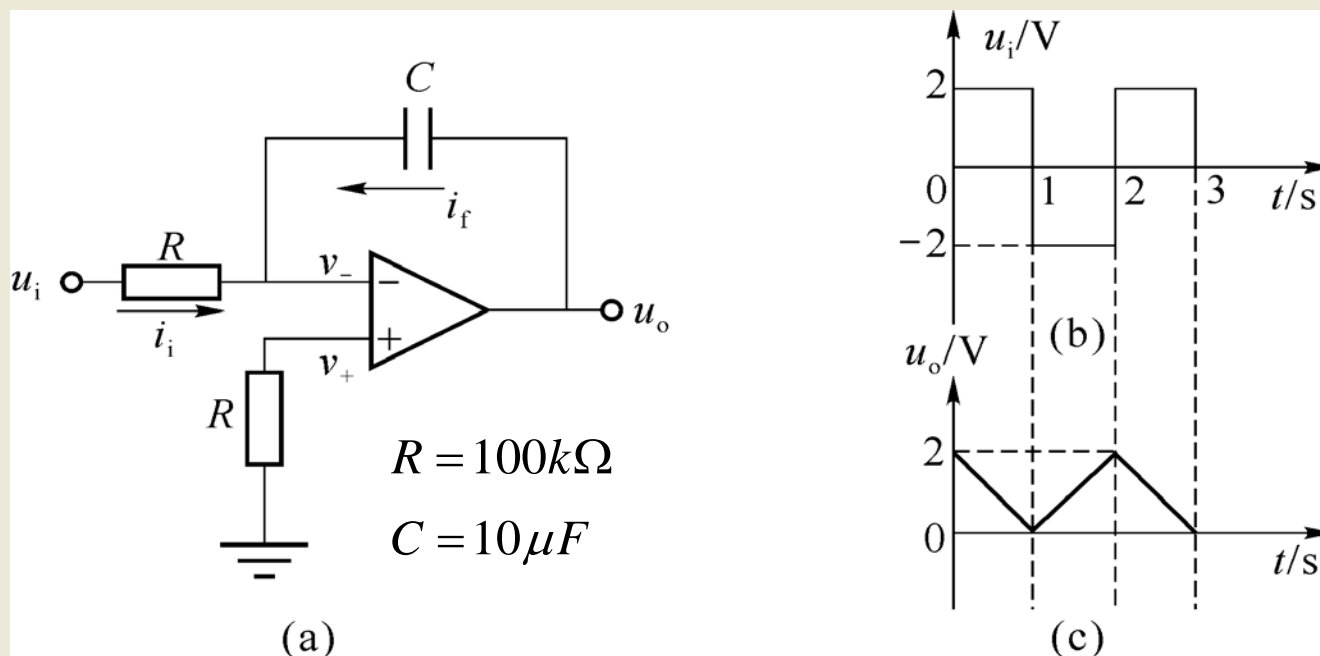


$$u_o(t) = -\frac{1}{RC} \int_{t_0}^t u_i(t) dt + u_o(t_0)$$

In the time duration of  $0 \sim 1s$      $u_i = 2V$      $u_o(0) = 2V$      $u_o(t) = -2t + 2$      $u_o(1) = 0V$

In the time duration of  $1 \sim 2s$      $u_i = -2V$      $u_o(1) = 0V$      $u_o(t) = 2t$      $u_o(2) = 2V$

## 8.4 Comparators
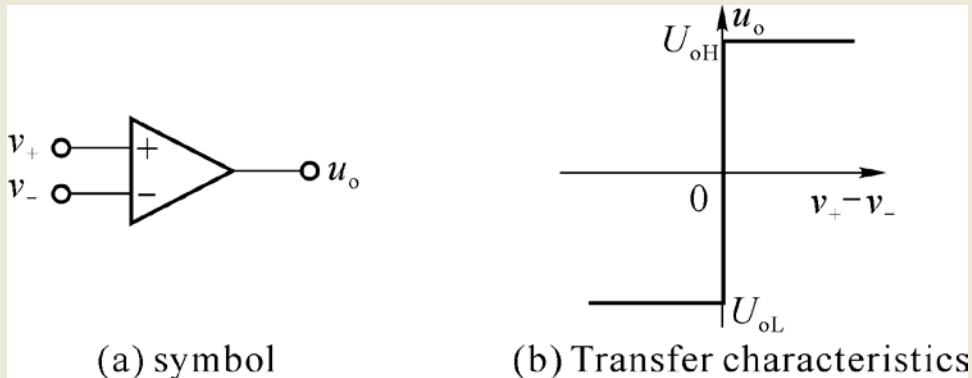
### Symbol and voltage transfer characteristics of comparators



*The operation is a basic comparator.  
The output swings between its maximum and minimum voltage, depending upon whether one input is **greater or less than the other**.*





### 8.4.1 Basic Comparators with a single threshold

For **non-inverting input comparator**:

- $u_o = U_{oH}$ , if  $u_i > V_{th}$
- $u_o = U_{oL}$ , if  $u_i < V_{th}$


For **inverting input comparator**:

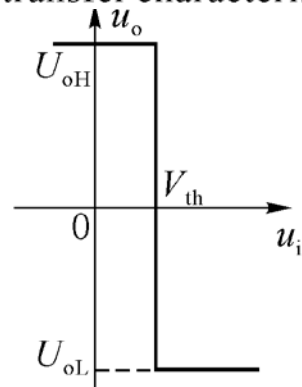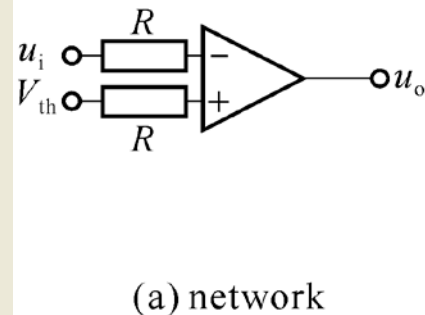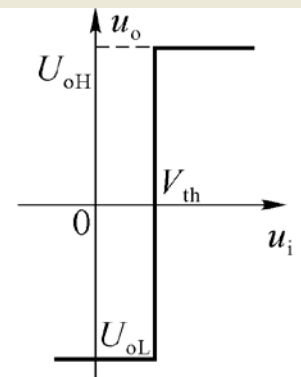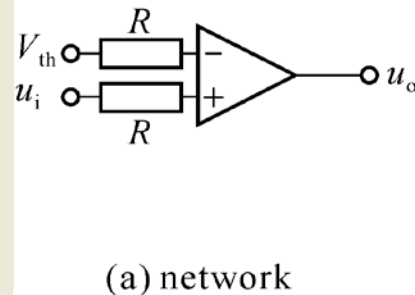- $u_o = U_{oH}$ , if  $u_i < V_{th}$
- $u_o = U_{oL}$ , if  $u_i > V_{th}$




# Examples of Comparators

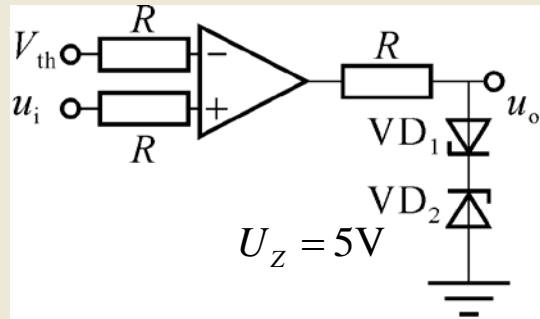
**Example 8.3:** Sketch the transfer characteristics and the waveform of the output.




(a)

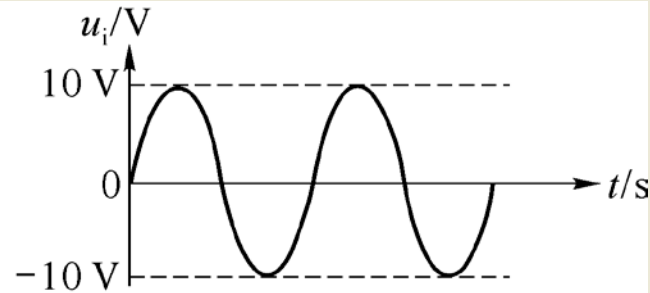

(b)

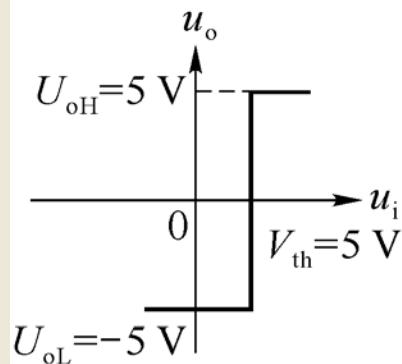

(a)

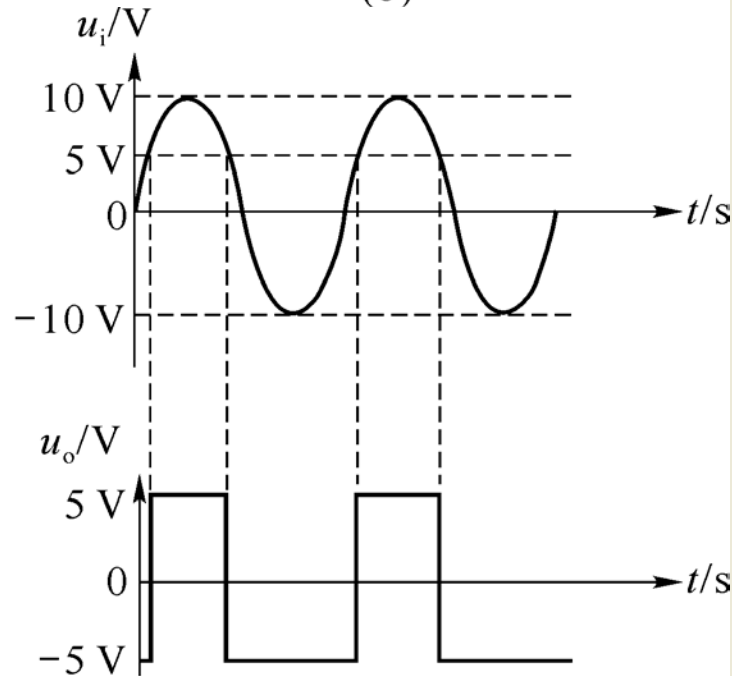

(b)

# Summary

- **Characteristics of op-amps and comparators**
  - *Ideal assumptions*
  - *Virtual short and Virtual open*
- **Application of op-amps in the linear region**
  - *Inverting vs. non-inverting*
  - *Summing*
  - *Subtraction*
  - *Integrator*
  - *Differentiator*
- **Comparator: application of op-amps in the nonlinear region**
  - *Basic comparator with single threshold*