

Chapter 5:

Frequency Response

5.1 The basis of Frequency Response

- Analyses limited to particular frequencies.
- Need to investigate the frequency effects:
 - *Larger capacitive elements of the network at low frequency.*
 - *Smaller capacitive elements of the active device at high frequency.*
- The concept of the decibel (dB).
- Similar features for both BJT and FET.

5.1 The basis of Frequency Response

The **Frequency Response** of an amplifier refers to the frequency range in which the amplifier will operate with negligible effects from capacitors and capacitance in devices.

This range of frequencies were usually called **mid-range**.

- *At frequencies above and below the mid-range, Capacitance and Inductance will affect the gain of the amplifier.*
 - At low frequencies, coupling and bypass capacitors lower the gain.
 - At high frequencies, stray capacitances associated with the active device lower the gain.
- *Also, cascading amplifiers limits the gain at high and low frequencies.*

Bandwidth and Cutoff Frequencies

The mid-range frequency of an amplifier is called the **bandwidth** of the amplifier.


The bandwidth is defined by the **lower** and **upper** cutoff frequencies.

Cutoff - Frequency at which the gain has dropped by:

0.5 power

-3dB

0.707 voltage

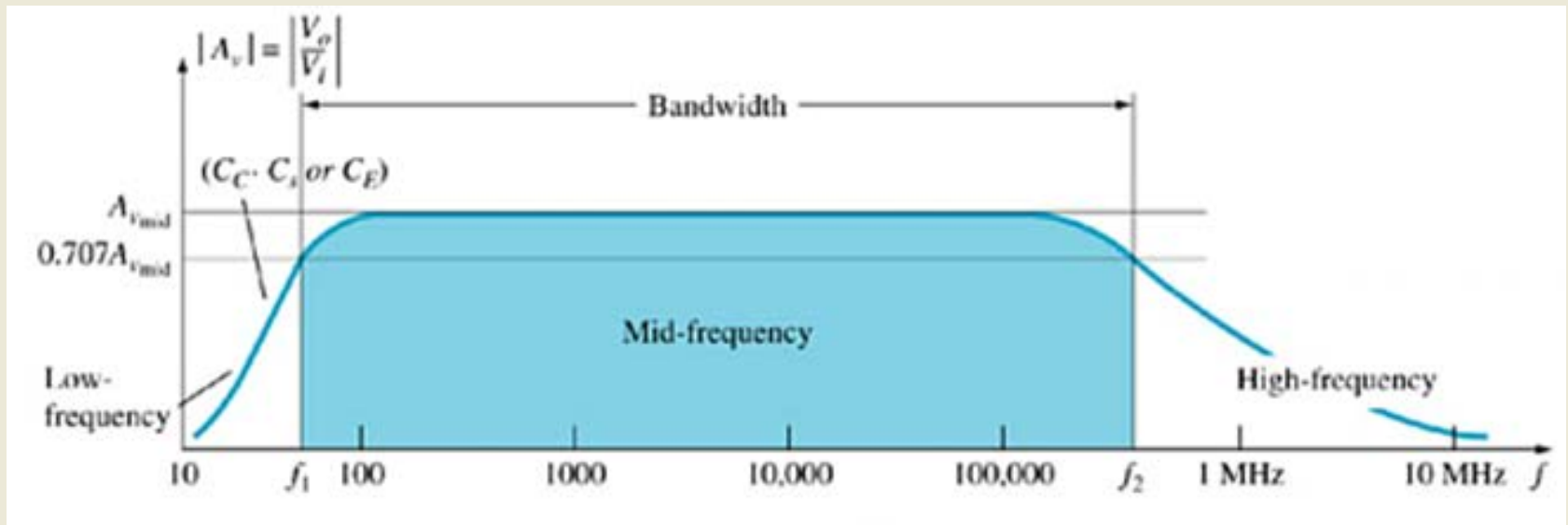

Bandwidth and Cutoff Frequencies

Mid-frequency:

$$P_{omid} = \frac{|V_o^2|}{R_o} = \frac{|A_{vmid} V_i|^2}{R_o}$$

Half-power frequency
 f_H, f_L

$$P_{oHPF} = 0.5 P_{omid}$$

$$P_{oHPF} = 0.5 \frac{|A_{vmid} V_i|^2}{R_o} = \frac{|0.707 A_{vmid} V_i|^2}{R_o}$$

Bandwidth (BW) = $f_H - f_L$

Decibel definition:


$$\frac{A_v}{A_{vmid}} \Big|_{dB} = 20 \log_{10} \frac{A_v}{A_{vmid}}$$

(1) Low-Pass Circuit

(a) If the input signal is at low frequency, the reactance X_C of capacitor is very large. *The output signal equals to the input signal approximately.*

(b) If the frequency is very high, the reactance of capacitor will be shorted, *the output is zero.*

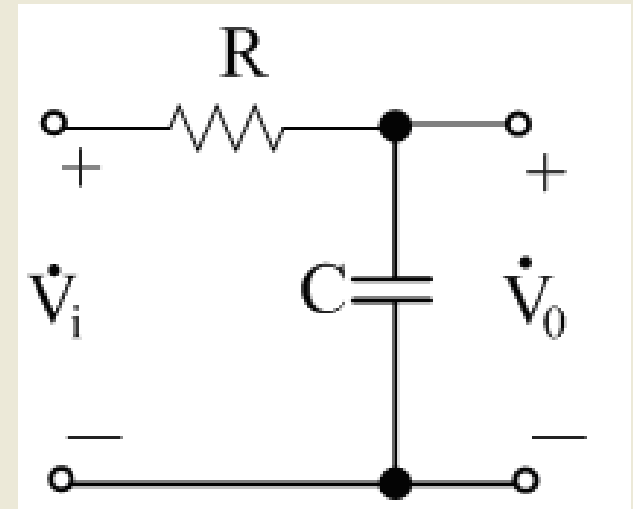(c) So, it's *Low-Pass*, but with *high frequency cutoff* point.



$$X_C = \frac{1}{2\pi fC}$$

(1) Low-Pass Circuit

For the case when: $X_C=R$


The output is 3dB drop (0.707) of the input at the frequency for $X_C=R$.

The high frequency cutoff point is determined from:

$$f_H = \frac{1}{2\pi RC}$$

The gain of any frequency can be:
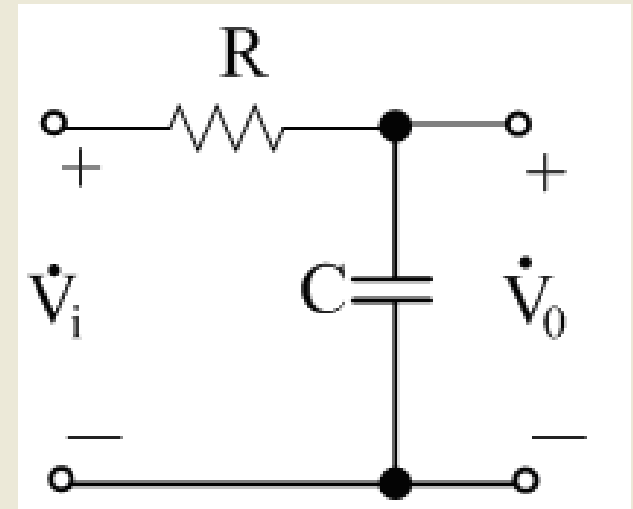
$$A_v = \frac{V_o}{V_i} = \frac{1}{1 + j(f / f_H)}$$




(1) Low-Pass Circuit

In the magnitude and phase form:

$$|A_v| = \left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{1 + (f / f_H)^2}}, \varphi = -\arctan(f / f_H)$$

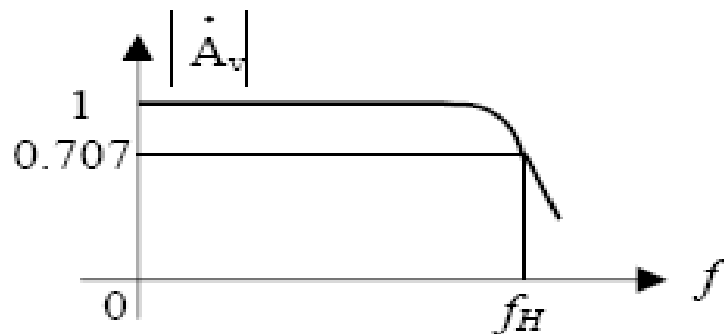
The frequency response of low-pass circuit:



(a) Magnitude response

(2) High-Pass Circuit

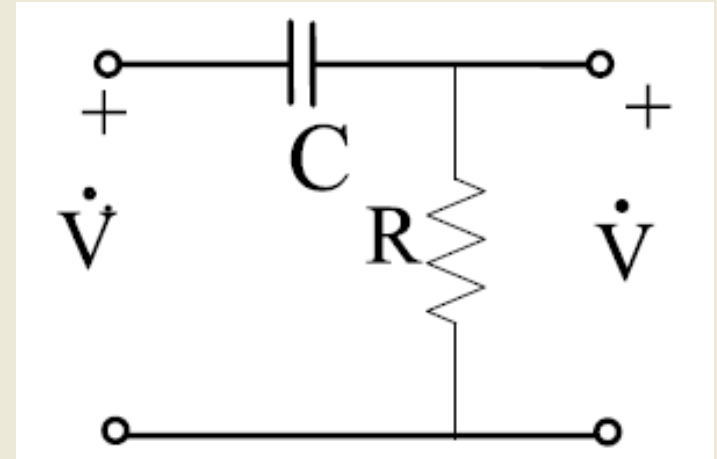- (a) At low frequency, the reactance X_C is very large. *The output is zero.*
- (b) At high frequency, the reactance will be shorted, *the output equals to the input.*
- (c) So, it's *High-Pass*, but with *low frequency cutoff* point.



$$X_C = \frac{1}{2\pi fC}$$

(2) High-Pass Circuit

For the case where $X_C=R$


The output is 3dB drop of the input at the frequency for $X_C=R$.

The low frequency cutoff point is determined from:

$$f_L = \frac{1}{2\pi RC}$$

The gain of any frequency can be:
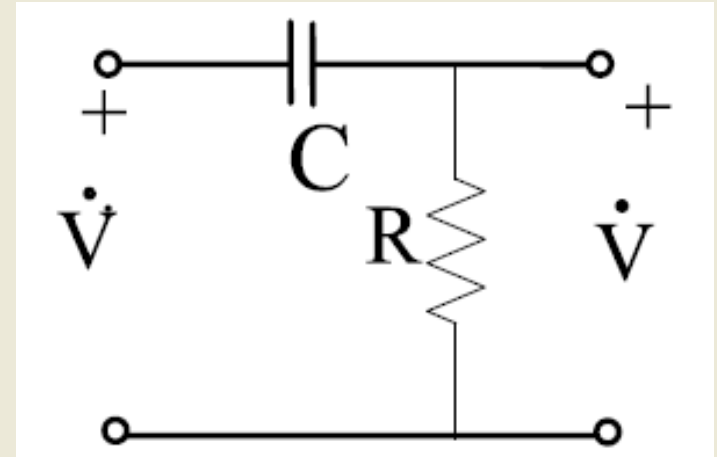
$$A_v = \frac{V_o}{V_i} = \frac{1}{1 - j(f_L / f)}$$




(2) High-Pass Circuit

In the magnitude and phase form:

$$|A_v| = \left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{1 + (f_L / f)^2}}, \varphi = \arctan(f_L / f)$$

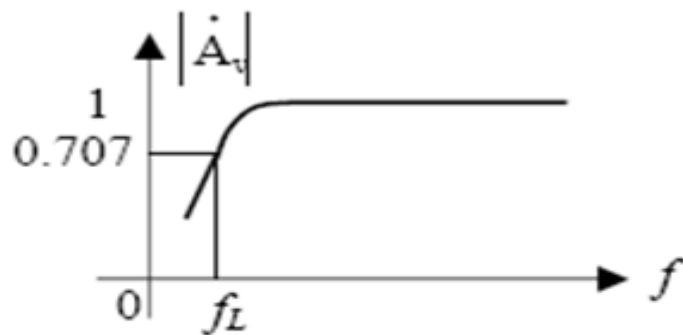The frequency response of high-pass circuit:



(a) amplitude response

(3) Bode Plot

- If the frequency response is plotted by logarithmic scale, the plot is called the Bode Plot.

In the logarithmic form, the gain of low-pass circuit in dB is

$$A_{v(dB)} = 20 \log_{10} \frac{1}{\sqrt{1 + (f / f_H)^2}} = -20 \log_{10} \sqrt{1 + (f / f_H)^2}$$
$$A_{v(dB)} = -20 \log_{10} \sqrt{1 + (f / f_H)^2} = -10 \log_{10} \left[1 + (f / f_H)^2 \right]$$

For the frequencies where $f \gg f_H$, the equation above can be approximated by

$$A_{v(dB)} = -10 \log_{10} (f / f_H)^2 = -20 \log_{10} \frac{f}{f_H} \Big|_{f \gg f_H}$$


(3) Bode Plot

- A straight line is drawn for the condition 0dB for $f \ll f_H$
- But the straight line are only accurate for $f \ll f_H$,
when $f = f_H$ there is **actually a 3dB drop** from the mid-range level.

$$\text{At } f = f_H : \frac{f}{f_H} = 1, -20\log_{10} 1 = 0dB$$

$$\text{At } f = 2f_H : \frac{f}{f_H} = 2, -20\log_{10} 2 = -6dB$$
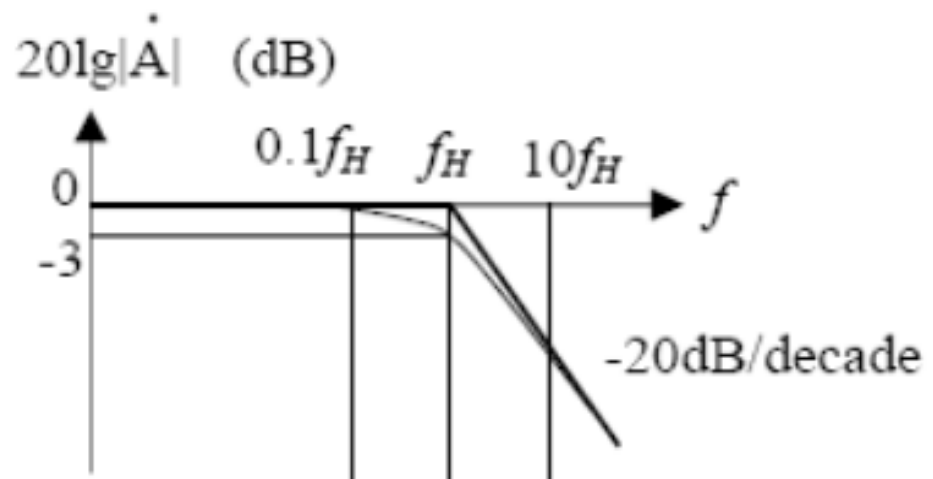
$$\text{At } f = 10f_H : \frac{f}{f_H} = 10, -20\log_{10} 10 = -20dB$$



(3) Bode Plot

In the logarithmic form, the gain of high-pass circuit in dB is

$$A_{v(dB)} = 20 \log_{10} \frac{1}{\sqrt{1 + (f_L / f)^2}} = -20 \log_{10} \sqrt{1 + (f_L / f)^2}$$

For the frequencies where $f \ll f_L$, the equation above can be approximated by

$$A_{v(dB)} = -10 \log_{10} (f_L / f)^2 = -20 \log_{10} \frac{f_L}{f} \Big|_{f \ll f_L}$$


$$\text{At } f = \frac{1}{2} f_L : \frac{f_L}{f} = 2, -20 \log_{10} 2 = -6 \text{ dB}$$

$$\text{At } f = \frac{1}{10} f_L : \frac{f_L}{f} = 10, -20 \log_{10} 10 = -20 \text{ dB}$$

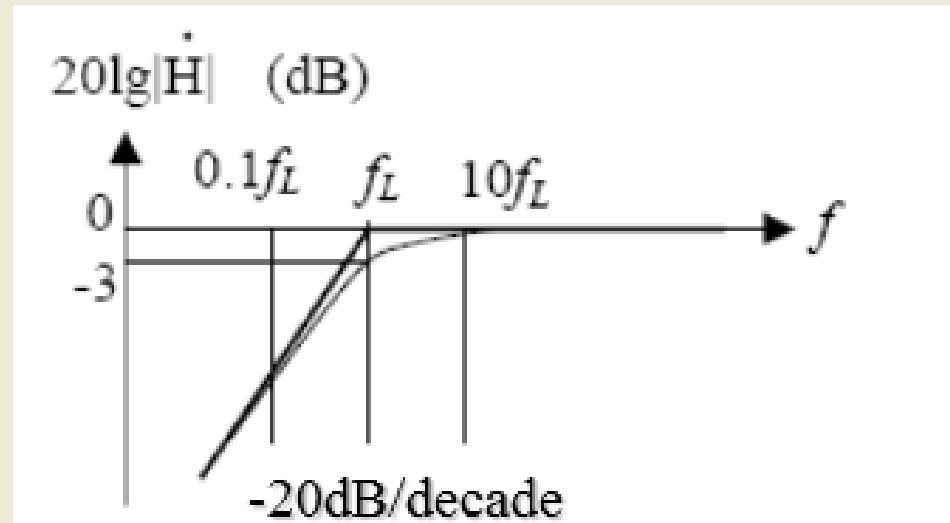(3) Bode Plot


- A straight line is drawn for the condition 0dB for $f \ll f_L$
- But the straight line are only accurate for $f \ll f_L$,

when $f = f_L$ there is **actually a 3dB drop** from the mid-range level.



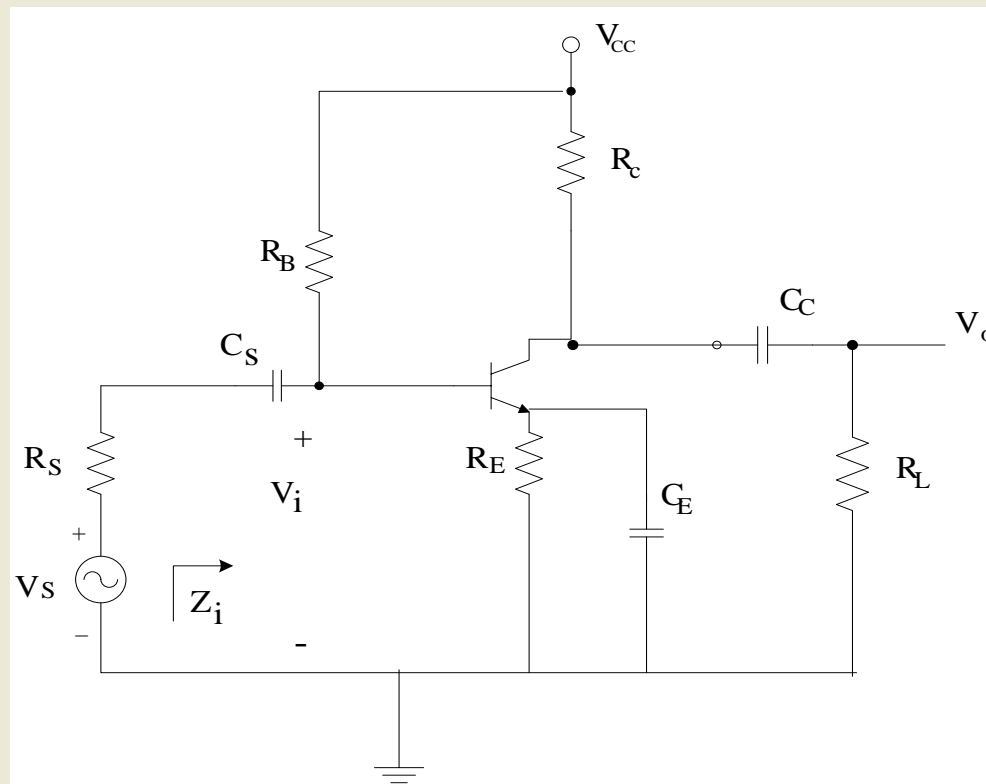5.2 Low-Frequency Response for BJT


- Find the appropriate equivalent resistance for the high-pass circuit.
- The drop in gain at the low frequency is due to the increasing reactance of C_S , C_E and C_C .
- Consider the large capacitor independently.



5.3 High-Frequency Response for BJT

Equivalent model for high frequency response

---- hybrid π model

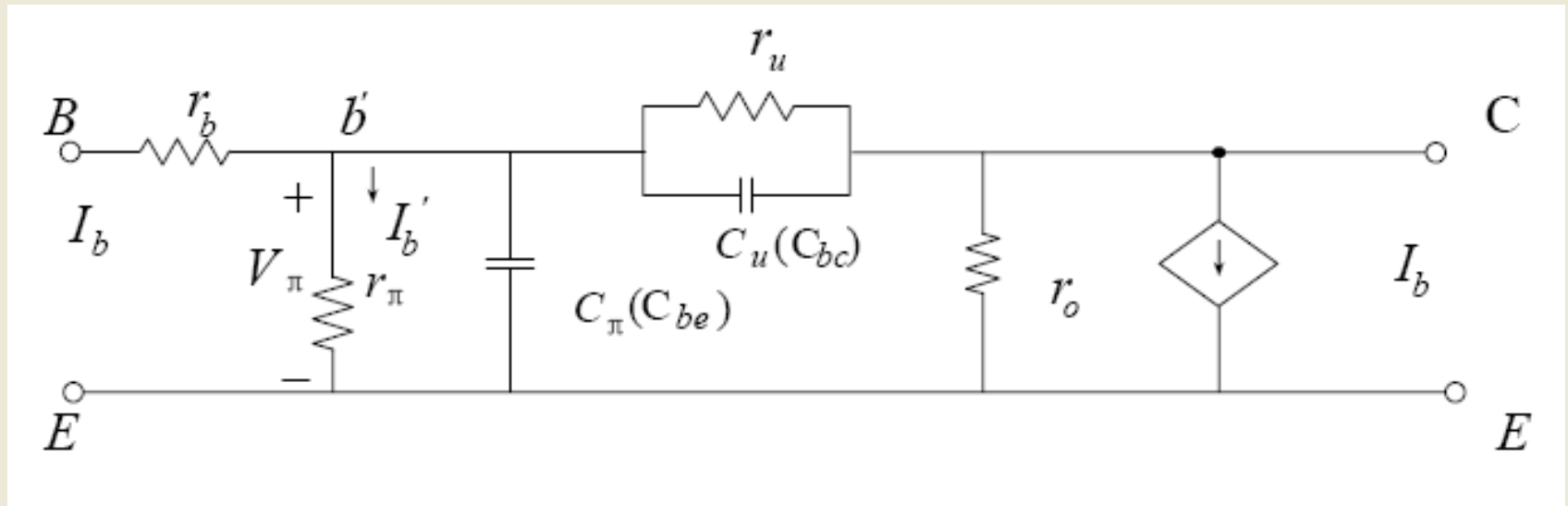

r_b : Base contact, bulk, and spreading resistance.


r_π , r_u , r_o : resistance between terminals

C_{bc} C_{be} : the inter-electrode capacitances.


r_π : Base-to-Emitter resistance, is βr_e .

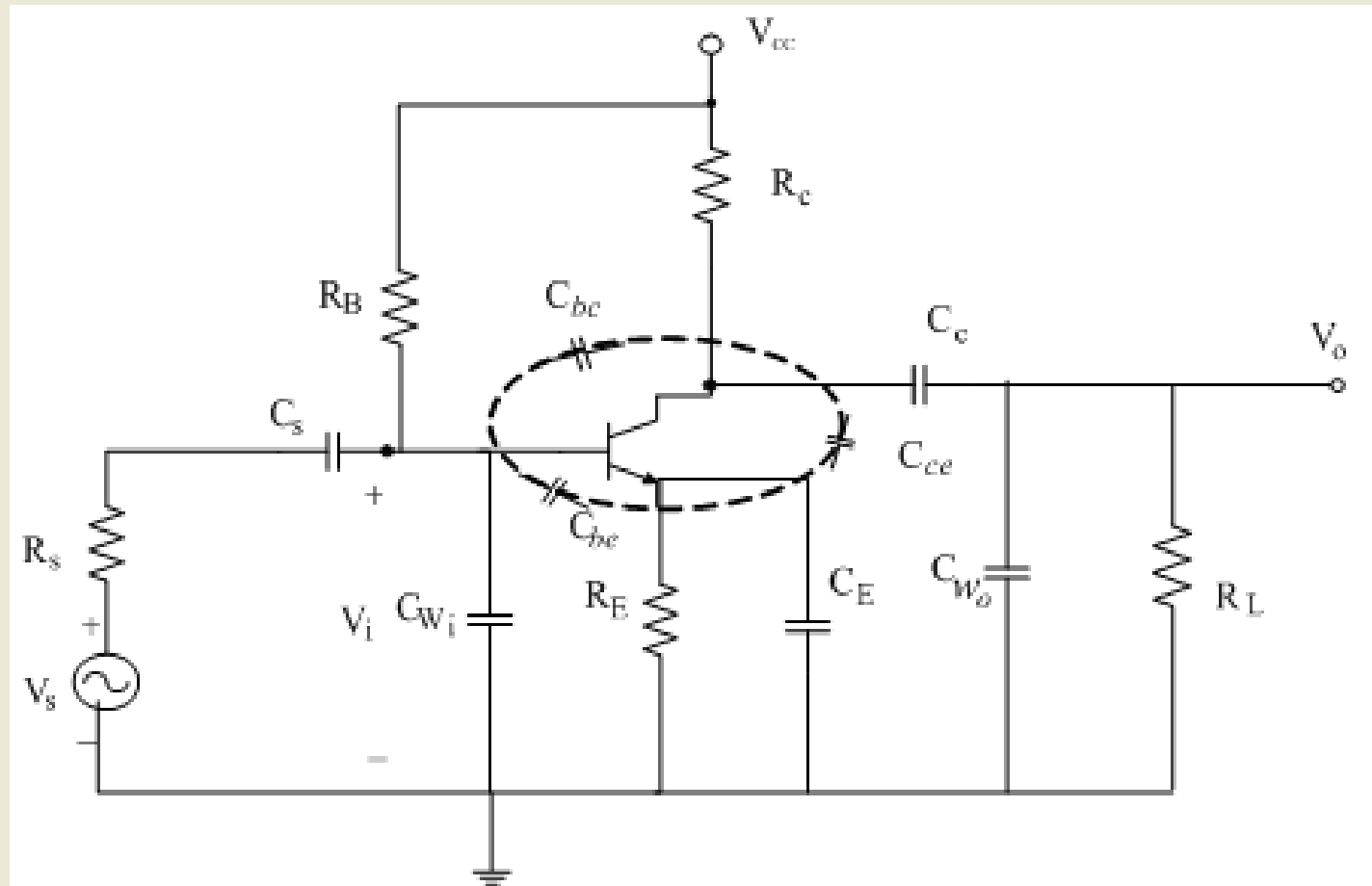5.3 High-Frequency Response for BJT

The capacitor for high frequency response:



Full Frequency Response for BJT

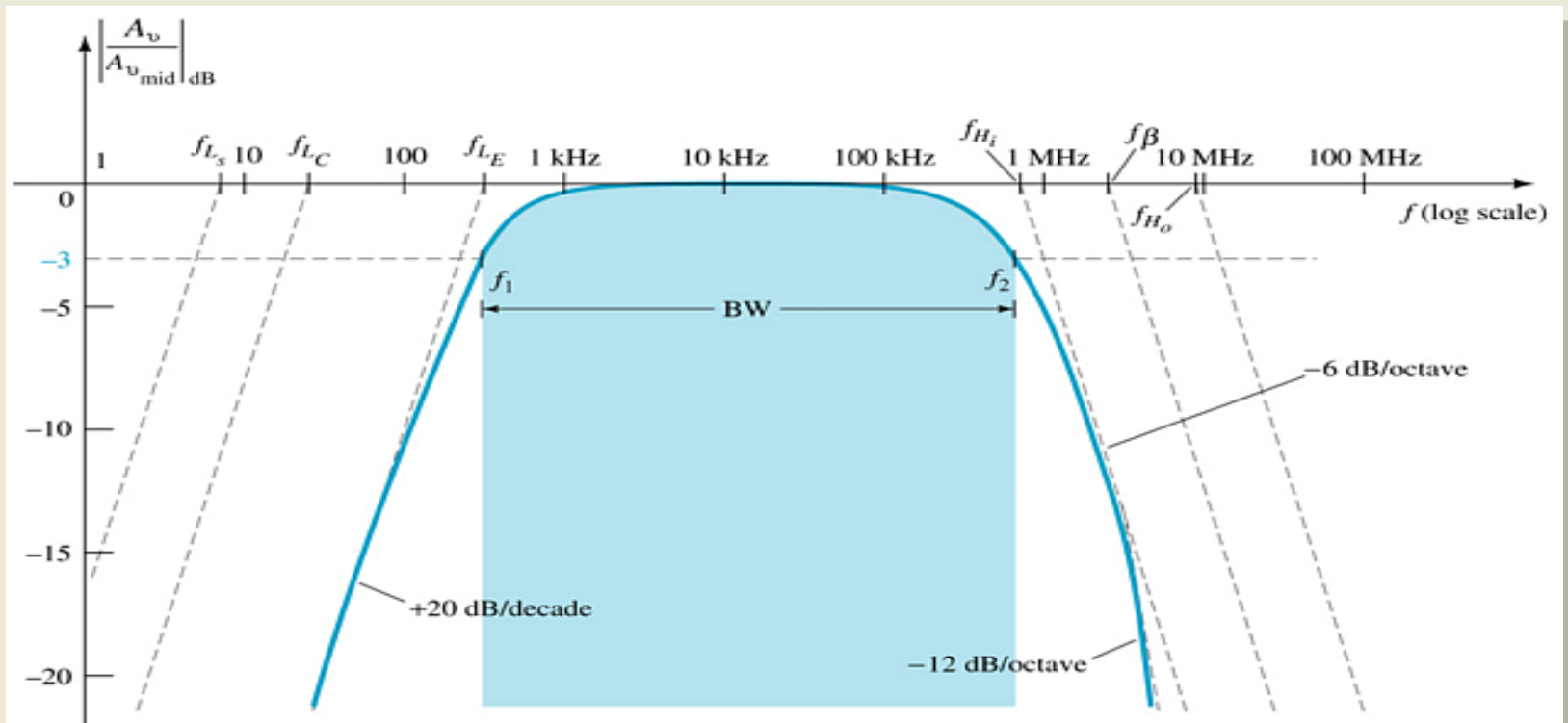

Middle-frequency region: resistance features by short and open equivalents of capacitances

Low-frequency region: coupling and bypass capacitors determine lower cutoff frequency

High-frequency region: network capacitance (parasitic and introduced) determine the upper cutoff frequency

Summary

The bandwidth of an amplifiers is determined by:

- Larger capacitive elements
- Smaller parasitic capacitors

Bode plot is required to present frequency response, and determine

- Cutoff frequencies
- Bandwidth

Capacitances that affect the low-frequency response are:

- Coupling capacitances: C_S , C_C
- Bypass capacitance: C_E

Capacitances that affect the high-frequency response are:

- Junction and parasitic capacitances: C_{be} , C_{bc} , C_{ce}
- Wiring capacitances: C_{wi} , C_{wo}